

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

الكلول المختارة لطلاب الهندسة والعمارة

تحليل دوائر (1)

اعداد

د/ محمد يوسف برعاوي

رحمه الله

وسامه محمد الفياض

الاستاذ المساعد بقسم الهندسة الكهربائية والالكترونيات

بجامعة ام القرى

الحمد لله وحده والصلوة والسلام على من لا نبي بعده سيدنا

محمد وعلى آله وصحبه وسلّم تبعهم بإحسان ،

وبعد ، فهذه مجرّدة من المسائل المحلولة في مادة تحليل دوائر (أ)

لطلبة الهندسة والعمارة بإختبار بعض الدكتور / محمد يوسف برناريا رحمه

الله عليه درّس هذه المادة في الفصل الأول للعام ١٤٠٨ هـ ، وهو مأخوذة

من كتاب :

Basic Electrical Engineering

A. Fitzgerald, D. Higginbotham & A. Grabel

للمؤلفين :

الطبعة الخامسة ١٩٨٢م

ومرضاً على الألب ينقطع عمله رحمه الله فقد رجوت الدكتور / سفيان

أنه يأذن لي فيما أخرج هذا البعض لإبناؤنا الطلاب من نسخة الخاصة

ناستجاب شكراً وزودني برك ما خرجت للطلابي حين درّسهم

هذه المادة في الفصل الأول للعام ١٤١٠ هـ. ثم زدت الآء بعضاً آخر هو

حصيلة ما أعطيتهم إياه آنذاك لتخرج هذه المجرّدة في أفراس الأء

فذا وقد تمت بتوجيه وزير ستر والسيدان ما فيك من الرفقة

لتسود وتمت المراجعة غير ، واكتفيت عند ذكر المسألة بذكر رقم

والصفحة التي ردت في الكتاب المذكور بحالهِ والمقرّرة لمادة تحليل

دوائر (أ) لطلاب الهندسة والعمارة الإسلامية بجامعة أم القرى ،

والله أسأل أنه لو فقه وينفع بهذا العمل لكل من طالعه وأنه

يرحم كاتبه الأول برحمته التي وسعت كل شيء إنه كيع قريب مجيب.

سليم بن محمد
١٤٤٠/٤/١٤ هـ

الفهرس

الصفحة

1	# الباب الأول وسجل المسائل التالية:
1	١٥٦٣٦١
2	٤٤
3	٤٥
4	٤٩
5	٤٤
6	٤١٢
7	٤١٦
8	٤١٧
9	٤١٦١٨
10	٤٤٤
11	٤٤٤٤٤٣
12	٤٤٦٤٥٥
13	٤٤٨
14	٤٣٠٤٤٩
15	٤٢٢
15	حلول استقامات على الباب الأول
17	# الباب الثاني وسجل المسائل التالية:
17	٤٥٤١
19	٤١٢٤٤٤
20	٤١٤

السؤال

- 21 _____ ٤٥٠٤١٧
- 22 _____ ٤٥١
- 23 _____ ٤٥٠٤٤٤
- 24 _____ ٤٥٨
- 25 _____ ٤٣.
- 27 _____ ٤٣٤٦٣١
- 28 _____ ٤٣٥
- 29 _____ ٤٣٨
- 31 _____ ٤٣٩
- 32 _____ ٤٤٠
- 33 _____ ٤٤٤
- 34 _____ ٤٤٥
- 36 _____ ٤٤٦
- 37 _____ ٤٤٨٤٤٧
- 38 _____ ٤٥٠٤٤٩
- 39 _____ ٤٥١
- 39 _____ حلول امتحانات على الباب الثاني
- 43 # الملحق ب المرشد للباب الثالث وسؤال المسائل التالية: ٤٣
- 43 _____ ٤٤٤١
- 44 _____ ٣
- 45 # الباب الثالث وسؤال المسائل التالية: ٤٥
- 45 _____ ٤٤٦٣٦١
- 46 _____ ٤٦٦٥

47	٤١٣
48	٤١٤
49	٤١٧
50	٤١٩
51	٤٢٤
52	٤٢٧
53	٤٢٨
54	٤٢٩
55	٤٣١
56	٤٣٣
57	٤٣٩
58	٤٤٠
59	٤٤٧
61	٤٤٨
62	٤٤٩
63	٤٥٠
64	٤٥١
65	٤٥٣
66	٤٥٥
67	٤٥٩
68	حلول انتخابات على الباب الثالث
73	# الباب الرابع وسؤال المسائل التالية:
73	٤١
74	٤٤

الصفحة

75 ————— ٤١. ٤٨

76 ————— ٤١٣

77 ————— ٤١٧


78 ————— ٤١٩

79 ————— ٤٢١

80 ————— حلول امتحانات على الباب الرابع

1-1
28

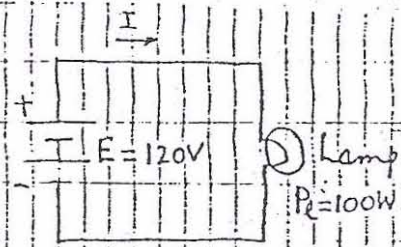a) $I = \frac{P}{E} = \frac{100}{120} = 0.833 \text{ A}$



b) $Q = It = 0.833 (60 \times 60) = 3,000 \text{ C}$


c) $W = P_L t = 100 (365 \times 10) = 365,000 \text{ Wh} = 365 \text{ kWh}$

$\therefore \text{Cost} = W \times \text{cost of energy} = 365 \times 6 = 2190 \text{ cents} = 21.9 \text{ dollars}$

1-2
28

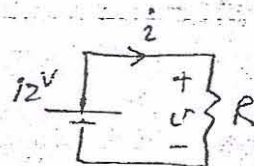a) $120 = P = iV = 12i$

$\therefore i = 10 \text{ Amp, the load current}$



b) $60 \text{ Ah} = iT = 10AT$




$\therefore T = 6 \text{ hours, the duration of supply}$

c) $q = iT = 10 \text{ A} \times 6 \text{ h} = 60 \text{ Ah} = 60 \frac{\text{C}}{\text{s}} \times 3600 \text{ s} = 216000 \text{ C}$

$\therefore q, \text{ the total charge} = 216 \text{ KC}$

d) $R = \frac{V}{i} = \frac{12 \text{ V}}{10 \text{ A}} = 1.2 \Omega, \text{ the load resistance.}$

1-3
28

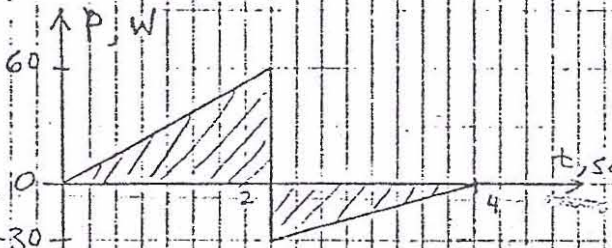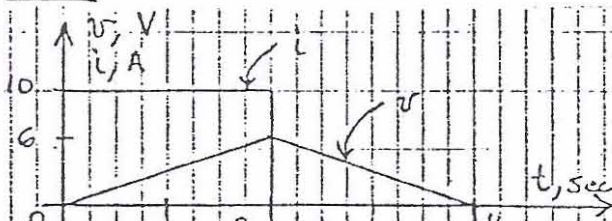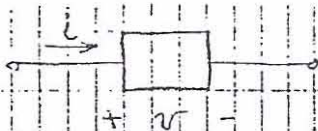

a) $P = i v$

b) Average power is $\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} P dt$; $t_1 = 0 \text{ sec}$; $t_2 = 4 \text{ sec}$
 $= (\text{area under curve divided by the time})$

$\therefore P = \frac{1}{4-0} \left(\frac{1}{2} \times 2 \times 60 - \frac{1}{2} \times 2 \times 30 \right) = \frac{30}{4} = 7.5 \text{ W}$

$\frac{1-4}{29}$ a) In $t \in [0, 10]$ ns;

$$v(t) = -5t + 5, \text{ Volts } \neq$$

$$i(t) = 2t, \text{ mA}$$

$$\therefore p(t) = 2t(5 - 5t) =$$

$$= 10t - t^2, \text{ mW}$$

This is a parabolic shape with maxima of 25 mW at $t = 5$ ns

Note: $p(0) = p(10) = 0$

In $t \in [10, 50] \cup [60, 100]$ ns;

$$v(t) * i(t) = 0 \quad \therefore p(t) = 0$$


In $t \in [50, 60]$ ns; the shape of $p(t)$ is just similar to that in $t \in [0, 10]$ ns

The sketch is therefore as shown above.

b) $P_{av} = \frac{1}{100} * 2 * \frac{2}{3} * 10 * 25 = 3.3 \text{ mW}$, average power during a period

c) $V_{av} = \frac{1}{100} * \frac{60+40}{2} * 5 = 2.5 \text{ Volts}$, average voltage during a period.
 $i_{av} = \frac{1}{100} * \frac{60+40}{2} * 20 = 10 \text{ mA}$, average current during a period.

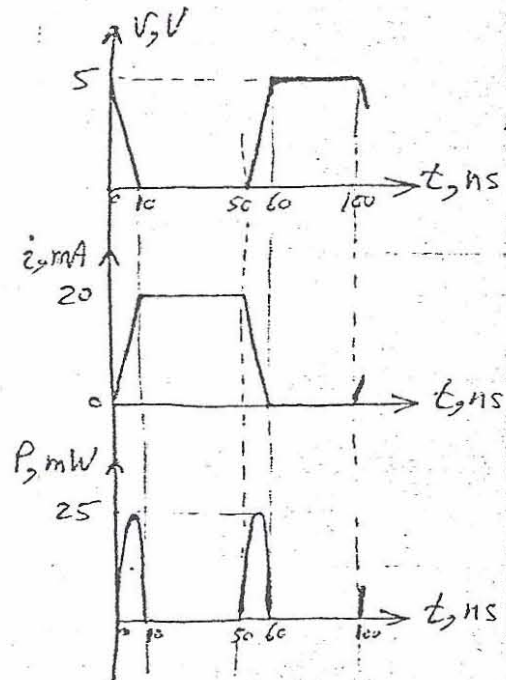
d) $V_{av} * i_{av} = 2.5 * 10 = 25 \text{ mW} > 3.3 \text{ mW} = P_{av}$. The reason is due v in $t \in [10, 50]$ ns being zero hence no power is dissipated its average gives false




$$\frac{1-5}{29}$$

$$v(t) = 20 \cos t, V, \quad i(t) = 5 \cos t, A$$

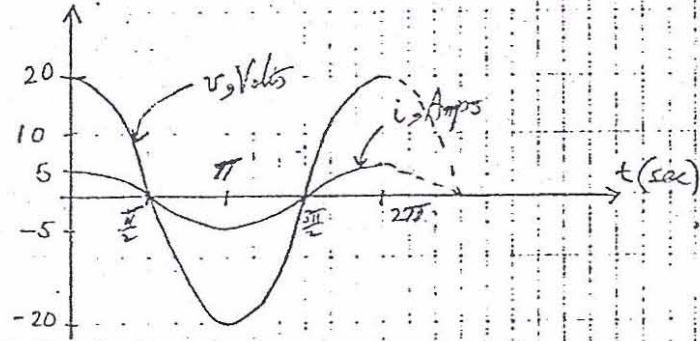Notice that the voltage across a resistor is in phase with the current through it.


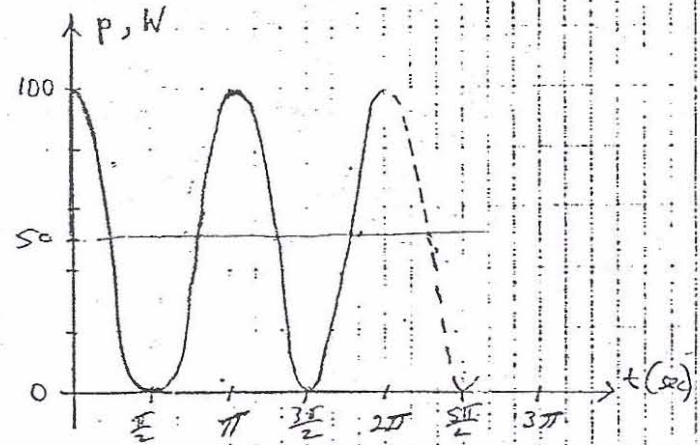
$$\begin{aligned} \text{(a) } p &= vi \\ &= (20 \cos t)(5 \cos t) \\ &= 100 \cos^2 t \\ &= \frac{100}{2} (1 + \cos 2t) \\ &= 50 (1 + \cos 2t) \text{ W} \end{aligned}$$




$$\text{(b) } P_{av} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p \, dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \frac{100}{2} (1 + \cos 2t) \, dt = \frac{50}{2\pi} \left[t + \frac{\sin 2t}{2} \right]_0^{2\pi} = \frac{50}{2\pi} \times 2\pi = 50 \text{ W}$$

$$\therefore \boxed{P_{av} = 50 \text{ W}}$$

1-9
30

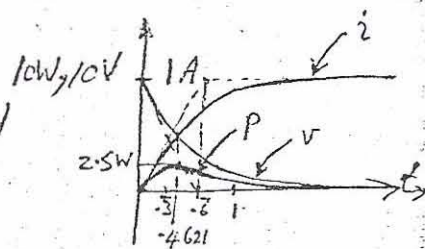a) $v(t) = 10e^{-1.5t}$ V as shown
 $i(t) = 1 - e^{-1.5t}$ A as shown
 $\therefore P(t) = v(t) \cdot i(t) = 10e^{-1.5t} \cdot (1 - e^{-1.5t})$ W



$P(t)$ is max. at $t = t_1$

$\therefore P'(t) = 10(-1.5e^{-1.5t} + 3e^{-3t}) = 0$

$\therefore e^{1.5t_1} = 2 \quad \therefore t_1 = \frac{\ln 2}{1.5} = 0.4621$ sec

$\therefore P(t_1) = P_{\max} = 10 \times \frac{1}{2} \cdot (1 - \frac{1}{2}) = 5 \times \frac{1}{2} = 2.5$ W

\therefore Max. power occurs at $t = 0.4621$ sec with value of 2.5 W

Note that $P(0) = P(\infty) = 0$ W & $P(t)$ is as shown.

$W \{ \text{in } t \in [0, \frac{2}{3}] \} = \int_0^{\frac{2}{3}} P(t) dt = 10 \int_0^{\frac{2}{3}} (e^{-1.5t} - e^{-3t}) dt = 10 \left[\frac{e^{-1.5t}}{-1.5} - \frac{e^{-3t}}{-3} \right]_0^{\frac{2}{3}}$

$= -\frac{10}{3} \left[2(e^{-1} - 1) - (e^{-2} - 1) \right] = -\frac{10}{3} \left(\frac{2}{e} - 2 + \frac{1}{e} + 1 \right) = \frac{10(e - 2\sqrt{e} + 1)}{3e}$

$\therefore W \{ \text{in } t \in [0, \frac{2}{3}] \text{ sec} \} = \frac{10(e - 2\sqrt{e} + 1)}{3e} = 0.5161$ J

$W \{ \text{in } t \in [0, 1] \text{ sec} \} = \int_0^1 P(t) dt = -\frac{10}{3} \left[2(e^{-1.5} - 1) - (e^{-3} - 1) \right] = 2.0118$ J

b) $v(t) = 20e^{-t}$ V as shown

$i(t) = te^{-t}$ A as shown

max i is at t_1 : $e^{-t_1}(1 - t_1) = 0 \Rightarrow t_1 = 1$ sec.

$i_{\max} = i(t_1) = 1e^{-1} = 0.36788$ Amp

$i(0) = i(\infty) = 0$

$\therefore P(t) = 20te^{-2t}$ W


$P(t)$ is max at $t = t_2$: $e^{-2t_2}(1 - 2t_2) = 0 \Rightarrow t_2 = 0.5$ sec & $P(t_2) = 20 \times 0.5 \times e^{-1} = 3.678$

\therefore Max. power occurs at $t = 0.5$ sec with value of 3.6788 W.

Note that $P(0) = P(\infty) = 0$ W giving the shape of $P(t)$ shown above.

$W \{ \text{in } t \in [0, \frac{2}{3}] \text{ sec} \} = \int_0^{\frac{2}{3}} 20te^{-2t} dt = -10te^{-2t} - 5e^{-2t} \Big|_0^{\frac{2}{3}} = 5e^{-\frac{4}{3}}(1 + \frac{2}{3})$
 $= 5e^{-\frac{4}{3}}(1 + \frac{2}{3}) = 5 - \frac{25}{3}e^{-\frac{4}{3}} = 0.72152$ J

$W \{ \text{in } t \in [0, 1] \text{ sec} \} = 5e^{-2}(1 + 2t) \Big|_0^1 = 5 - 15e^{-2} = 2.96997$ J

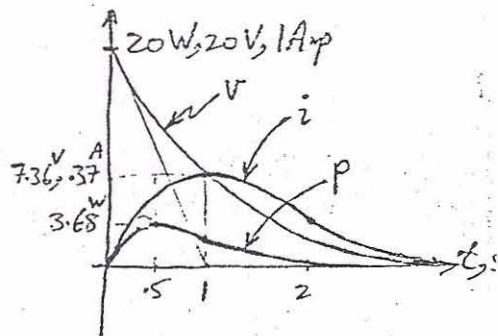


$\frac{1-12}{30}$

$$R_T = R_0 (1 + 5.42 \times 10^{-2} T - 4.17 \times 10^{-6} T^2) \Omega$$

$R_0 = \text{resistance at } T = 0^\circ\text{C}$

(a) $R_0 = 25 \Omega$, $0^\circ\text{C} \leq T \leq 600^\circ\text{C}$

$T (^\circ\text{C})$	$R_T (\Omega)$
0	25
100	159.5
200	291.8
300	422.1
400	550.3
500	676.4
600	800.5

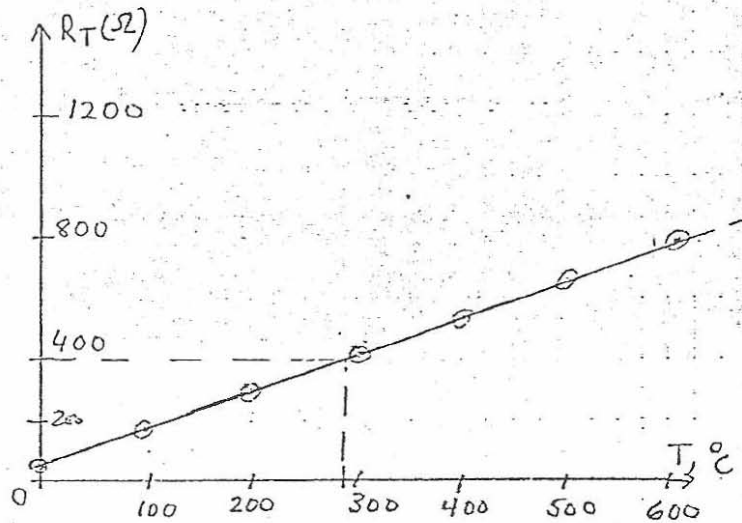

(b) $V = -6\text{V}$, $I = 15\text{mA}$

$$R_T = \frac{V}{I} = \frac{6}{15 \times 10^{-3}} = 400 \Omega$$

From the R_T curve ; for $R_T = 400 \Omega \rightarrow T \approx 285^\circ\text{C}$

~~Temperature~~ ~~is not~~ ~~the~~ ~~correct~~ ~~answer~~; solve for T the above quadratic

$$\therefore 400 = 25 (1 + 5.42 \times 10^{-2} T - 4.17 \times 10^{-6} T^2)$$


$$4.17 \times 10^{-6} T^2 - 5.42 \times 10^{-2} T + 15 = 0$$

$$\frac{5.42 \times 10^{-2} \pm \sqrt{(5.42 \times 10^{-2})^2 - 4 \times 4.17 \times 10^{-6} \times 15}}{2 \times 4.17 \times 10^{-6}} = 12,714.7^\circ\text{C} \text{ OR } 282.9^\circ\text{C}$$

(out of range $[0, 600]^\circ\text{C}$) OR (within range)

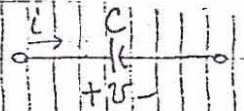1-13
30

$C = 100 \mu\text{F}$, $v = 120\sqrt{2} \sin 377t \text{ V}$



(a) $i = C \frac{dv}{dt} = 100 \times 10^{-6} \frac{d}{dt} (120\sqrt{2} \sin 377t) = 10^{-4} (120\sqrt{2} (377 \cos 377t))$


$i = 6.398 \cos 377t \text{ A}$

(b) Notice that in a Capacitor, the current leads the voltage by 90° .

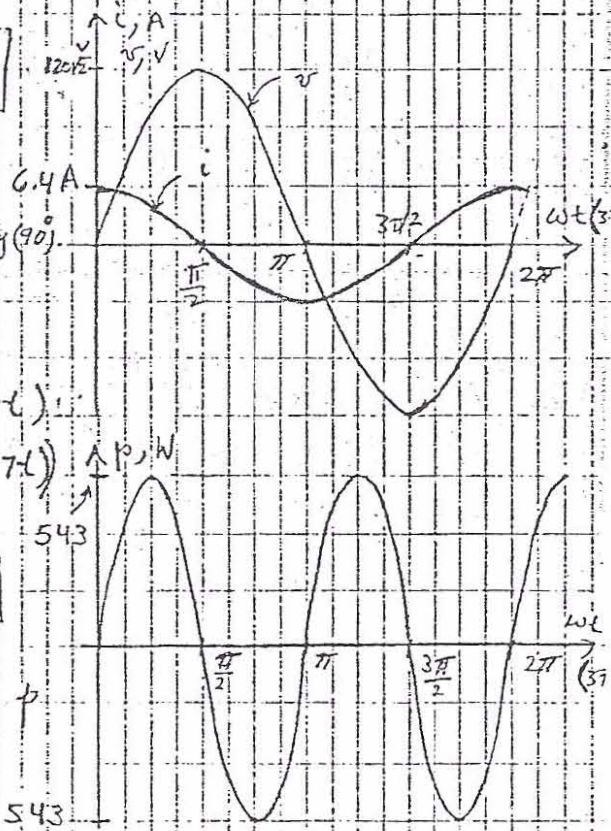(c) $p = v i = (120\sqrt{2})(6.398) (\sin 377t \cos 377t)$
 $= 1086 (\frac{1}{2} \sin(2 \times 377t))$

$p = 543 \sin 754t \text{ W}$

Notice that the frequency of p is twice that of v and i .




1-15
31

$C = 50 \text{ pF}$
 $v(t) = \begin{cases} 10^8 \text{ V} & 0 \leq t < 50 \text{ ns} \\ 7.5 - 5 \times 10^7 t \text{ V} & 50 \leq t \leq 150 \text{ ns} \\ 0 \text{ V} & t > 150 \text{ ns} \end{cases}$


(a) $i = C \frac{dv}{dt} = 50 \times 10^{-12} \times \begin{cases} 10^8 & 0 \leq t < 50 \text{ ns} \\ -5 \times 10^7 & 50 \leq t \leq 150 \text{ ns} \\ 0 & t > 150 \text{ ns} \end{cases} = \begin{cases} 5 \text{ mA} & 0 \leq t < 50 \text{ ns} \\ -2.5 \text{ mA} & 50 \leq t \leq 150 \text{ ns} \\ 0 \text{ mA} & t > 150 \text{ ns} \end{cases}$

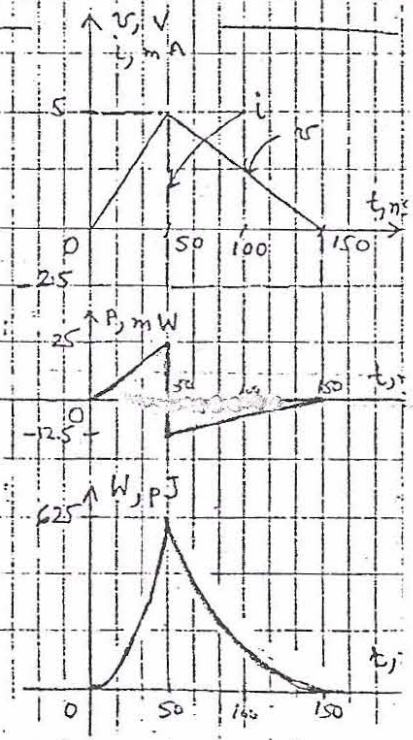(b) $p(t) = v i = \begin{cases} 5 \times 10^5 t \text{ W} & 0 \leq t < 50 \text{ ns} \\ -18.75 \times 10^{-3} + 12.5 \times 10^{-4} t \text{ W} & 50 \leq t \leq 150 \text{ ns} \\ 0 \text{ Watt} & t > 150 \text{ ns} \end{cases}$

$W = \frac{C v^2}{2} = 25 \times 10^{-12} \times \begin{cases} 10^{16} t^2 \text{ Joul} & 0 \leq t < 50 \text{ ns} \\ (7.5 - 5 \times 10^7 t)^2 \text{ Joul} & 50 \leq t \leq 150 \text{ ns} \\ 0 \text{ Joul} & t > 150 \text{ ns} \end{cases}$



1-16
31

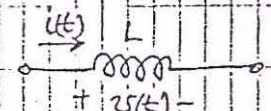
$$i(t) = 0.1414 \sin 377t, \text{ A}, \quad L = 10 \text{ mH}$$


(a) $v(t) = L \frac{di}{dt} = 10^{-2} \frac{d}{dt} (0.1414 \sin 377t) = 0.5331 \cos 377t \text{ V}$

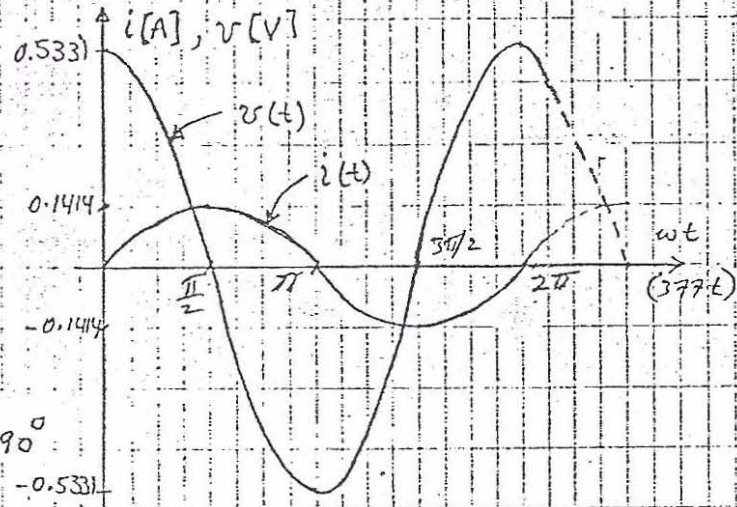(b) Waveforms;


Note that in Inductance,

the voltage leads the current by $\frac{\pi}{2} = 90^\circ$



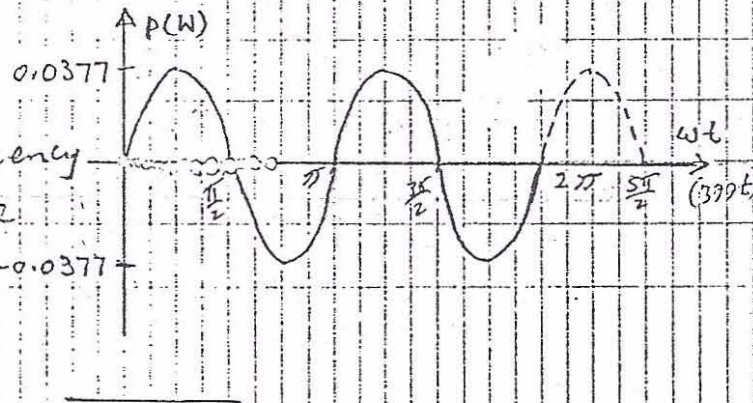
(c) $p = v \cdot i = (0.5331 \cos 377t)(0.1414 \sin 377t)$
 $= 0.0754 \sin 377t \cos 377t$
 $= 0.0754 \left(\frac{1}{2} \sin 2 \times 377t \right), \text{ W}$

$\therefore p = 0.0377 \sin 754t, \text{ Watt}$



Note that the frequency of the power is twice that of current or voltage.

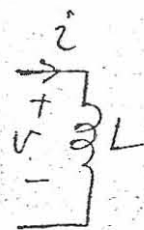$\frac{1-17}{31}$ a) $v = L di/dt$
 $\therefore i(t) = 1 - e^{-10^6 t}$, mA
 $\& L = 10 \text{ mH}$
 $\therefore v = 10 \text{ m} \times 10^6 \times e^{-10^6 t}$, mV
 $= 10 e^{-10^6 t}$, V




$\therefore v(t) = 10 e^{-10^6 t}$, V

b) Sketches are as shown

c) $P(t) = i(t) \cdot v(t) =$
 $= 10 e^{-10^6 t} \cdot (1 - e^{-10^6 t})$, mW

$\&$ Sketch of $p(t)$ is shown.

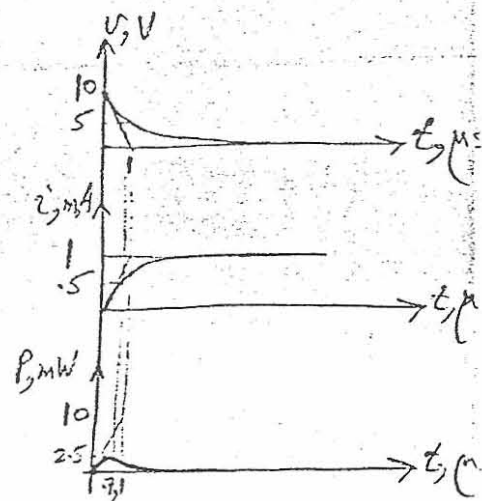

Note that $P(0) = P(\infty) = 0$
and that max. power is at $t = t_1$ where $P'(t_1) = 0$


$\therefore 10 [e^{-10^6 t_1} (-10^6) - e^{-2 \times 10^6 t_1} * (-2 \times 10^6)] = 0 \quad \therefore 10 e^{-10^6 t_1} = 2 \times 10 e^{-2 \times 10^6 t_1}$

$\therefore 1 = 2 e^{-10^6 t_1} \quad \therefore t_1 = 10^{-6} \ln 2 \text{ sec} = 0.693 \mu\text{sec}$

$\therefore P(t)$ is max at $t = 0.693 \mu\text{s}$ and $P(t_1) = P_{\text{max}} = \frac{10}{2} (1 - \frac{1}{2}) = 2.5 \text{ mW}$

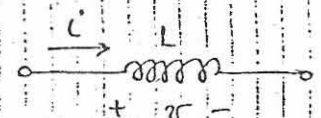1-18
31

$$L = 5.00 \mu\text{H} = 5 \times 10^{-4} \text{H}$$



$$i(t) = \begin{cases} 10^4 t, \text{ A} & 0 \leq t \leq 2 \mu\text{s} \\ 2.5 \times 10^2 - 2.5 \times 10^3 t, \text{ A} & 2 < t \leq 10 \mu\text{s} \\ 0, \text{ A} & t > 10 \mu\text{s} \end{cases}$$

$$\text{(a) } v = L \frac{di}{dt} = 5 \times 10^{-4} \times \begin{cases} 10^4 & 0 \leq t \leq 2 \mu\text{s} \\ -2.5 \times 10^3 & 2 < t \leq 10 \mu\text{s} \\ 0 & t > 10 \mu\text{s} \end{cases} = \begin{cases} 5 \text{ V} & 0 \leq t \leq 2 \mu\text{s} \\ -1.25 \text{ V} & 2 < t \leq 10 \mu\text{s} \\ 0 \text{ V} & t > 10 \mu\text{s} \end{cases}$$


$$\text{(b) Energy, } W = \frac{1}{2} L i^2$$

$$\therefore W = \frac{5 \times 10^{-4}}{2} \times \begin{cases} 10^8 t^2, \text{ J} & 0 \leq t \leq 2 \mu\text{s} \\ (2.5 \times 10^2 - 2.5 \times 10^3 t)^2, \text{ J} & 2 < t \leq 10 \mu\text{s} \\ 0, \text{ J} & t > 10 \mu\text{s} \end{cases}$$

$$\text{a) } t = 0, W = 0 \text{ J}$$

$$\text{a) } t = 2 \mu\text{s}, W = 0.1 \mu\text{J}$$

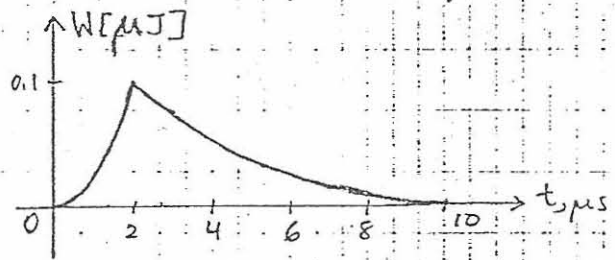
$$\text{a) } t \geq 10 \mu\text{s}, W = 0 \text{ J}$$



1-21
31

$$V_1 = 45 \text{ V}, V_2 = 15 \text{ V}$$

(a) Same current I flows in the ckt.

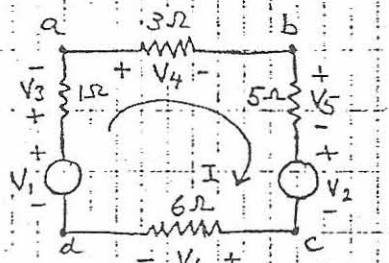

$$\text{KVL} \rightarrow V_1 - V_3 - V_4 - V_5 - V_2 - V_6 = 0$$

$$\text{Ohm's law} \rightarrow V_3 = 1I, V_4 = 3I, V_5 = 5I, V_6 = 6I$$

$$\therefore 45 - I - 3I - 5I - 15 - 6I = 0 \Rightarrow \boxed{I = \frac{30}{15} = 2 \text{ A}}$$

$$\text{(b) } V_{ac} = V_4 + V_5 + V_2 = 2 \times 3 + 2 \times 5 + 15 = 31 \text{ V}$$

$$\text{(c) } P_1 = V_1 I = 45 \times 2 = 90 \text{ W}$$

$$\text{(d) } P_{bc} = I^2 R + V_2 I = 5(2)^2 + 15(2) = 50 \text{ W}$$

Notice source V_2 absorbs power \Rightarrow charges battery V_2 .


$$\frac{1-22}{32}$$

$$V_{ac} = 12V = V_2 + 8i \quad (1)$$

$$V_{bd} = 21V = V_2 + 11i \quad (2)$$

$$(2) - (1) \Rightarrow$$
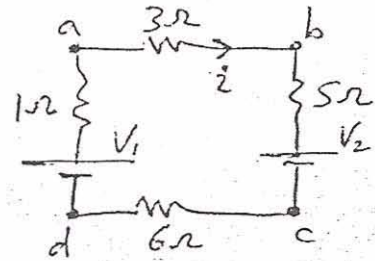
$$21 - 12 = 3i \quad \therefore i = \frac{21 - 12}{3} = 3A$$



into (1):

$$\therefore 12 = V_2 + 8 \times 3 \Rightarrow V_2 = 12 - 24 = -12 \text{ Volts}$$

$$\text{but } i = \frac{V_1 - V_2}{1 + 3 + 5 + 6} = \frac{V_1 + 12}{15} = 3A$$


$$\therefore V_1 = 3 \times 15 - 12 = 45 - 12 = 33 \text{ Volts}$$

$$\therefore V_1 = 33V \quad \text{and} \quad \underline{V_2 = -12V}$$

1-23
32

$I_A = 3 \text{ A}, I_B = 5 \text{ A}$

(a) KCL @ upper Node

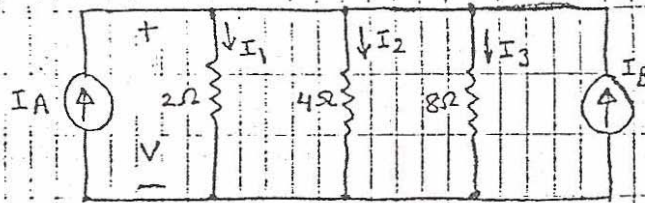

$I_A - I_1 - I_2 - I_3 + I_B = 0$

from Ohm's law

$I_1 = \frac{V}{2}, I_2 = \frac{V}{4}, I_3 = \frac{V}{8}$

$\therefore 3 - \frac{V}{2} - \frac{V}{4} - \frac{V}{8} + 5 = 0$

$\Rightarrow V = \frac{64}{7} = 9.14 \text{ V}$

(b) $\therefore I_1 = \frac{9.14}{2} = 4.57 \text{ A}, I_2 = \frac{9.14}{4} = 2.285 \text{ A}, I_3 = \frac{9.14}{8} = 1.142 \text{ A}$

(c) $P_B = I_B V = 5 \times 9.14 = 45.7 \text{ W}$

1-24
33

$i_1 = 2 \text{ A}, i_3(t) = 10e^{-t} \text{ A}$


$i_4(t) = 5\cos 2t \text{ A}$

$v_1, v_2, v_3, v_4, i_2, i_5 = ?$

$v_1 = i_1 R_1 = 2 \times 5 = 10 \text{ V}$

$v_3 = L \frac{di_3}{dt} = 2 \frac{d}{dt} (10e^{-t}) = -20e^{-t} \text{ V}$

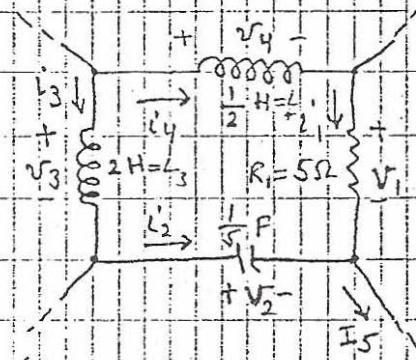$v_4 = L \frac{di_4}{dt} = \frac{1}{2} \frac{d}{dt} (5\cos 2t) = -5 \sin 2t \text{ V}$



\therefore KVL $\rightarrow v_3 - v_4 - v_1 + v_2 = 0$

$\therefore v_2 = 10 + 20e^{-t} - 5 \sin 2t \text{ V}$


$\therefore i_2 = \frac{1}{5} \frac{dv_2}{dt} = \frac{1}{5} \frac{d}{dt} (10 + 20e^{-t} - 5 \sin 2t) = -4e^{-t} - 2 \cos 2t \text{ A}$

KCL $\rightarrow i_5 = i_1 + i_2 = 2 - 4e^{-t} - 2 \cos 2t \text{ A}$

1-25
33

$$i_L = 2e^{-2t} \text{ A}$$

$$i_A, v_{ab} = ?$$

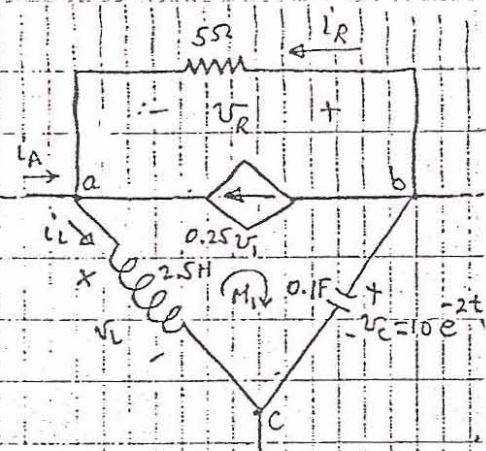

$$v_L = 2.5 \frac{d}{dt} (2e^{-2t}) = -10e^{-2t} \text{ V}$$

KVL around Mesh $M_1 \rightarrow v_L - v_{ab} - v_C = 0$

$$-v_{ab} = v_R = v_C - v_L = 10e^{-2t} + 10e^{-2t} = 20e^{-2t} \text{ V}$$

$$\therefore v_{ab} = -20e^{-2t} \text{ V}$$

$$i_R = \frac{v_R}{5} = 4e^{-2t} \text{ A}$$

KCL @ Node a: $i_A = i_L - 0.25v_C - i_R$

1st Assume $v_C = v_L$

$$\therefore i_A = 2e^{-2t} - 0.25(-10e^{-2t}) - 4e^{-2t} = 0.5e^{-2t} \text{ A}$$

2nd Assume $v_C = v_C$

$$\therefore i_A = 2e^{-2t} - 0.25(10e^{-2t}) - 4e^{-2t} = -4.5e^{-2t} \text{ A}$$


1-26
34

$$v_0(t) = ?$$

KCL @ Node a

$$i_C = i_R - i_L = 12e^{-5t} - 10e^{-5t}$$

$$\therefore i_C = 2e^{-5t} \text{ A}$$

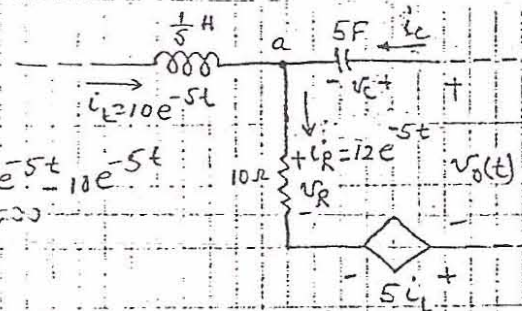

KVL $\rightarrow v_0 = v_C + v_R - 5i_L = v_C + 10(12e^{-5t}) - 5(10e^{-5t})$

$$v_C = \frac{1}{C} \int i_C dt = \frac{1}{5} \int 2e^{-5t} dt = \frac{-2}{25} e^{-5t} + K = -0.08e^{-5t} + K$$

$$\therefore v_0 = K - 0.08e^{-5t} + 120e^{-5t} - 50e^{-5t} = 69.92e^{-5t} + K \text{ V}$$

(K could be found from capacitor initial charge)

$$\frac{1-28}{34} \quad i_c = C \frac{dV_c}{dt} = 1 \times 0 = 0 \text{ A}$$

$$\therefore i_L = 20 \sin 2t - i_c = 20 \sin 2t, \text{ A}$$

$$\therefore V_L = L \frac{di_L}{dt} =$$

$$= 0.1 \times 20 \times 2 \cos 2t$$

$$= 4 \cos 2t, \text{ V}$$

$$\text{f} \quad i_R = i_L - 20 = 20 \sin 2t - 20 = 20 (\sin 2t - 1), \text{ A}$$

$$\therefore V_R = R \cdot i_R = 0.2 \times 20 (\sin 2t - 1) = 4 (\sin 2t - 1), \text{ V}$$

$$\therefore V(t) = 4 - V_L - V_R = 4 - 4 \cos 2t - 4 (\sin 2t - 1) = 4 (2 - \sin 2t - \cos 2t)$$

$$\text{f} \quad P_R = \frac{1}{T} \int_0^T i_R^2 \cdot R \, dt = \frac{\omega}{2\pi} \int_0^{2\pi/\omega} i_R^2 \cdot R \, dt \quad (\text{with } \omega = 2) =$$


$$= \frac{2}{2\pi} \int_0^\pi 20^2 (\sin 2t - 1)^2 \times 0.2 \, dt = \frac{80}{\pi} \int_0^\pi (\sin^2 2t - 2 \sin 2t + 1) \, dt =$$

$$= \frac{80}{\pi} \int_0^\pi \left(\frac{1 - \cos 4t}{2} - 2 \sin 2t + 1 \right) \, dt = \frac{80}{\pi} \left[\frac{3t}{2} - \frac{\sin 4t}{8} + \cos 2t \right]_0^\pi =$$

$$= \frac{80}{\pi} \left[\frac{3\pi}{2} - 0 - 0 + 0 + 1 - 0 \right] = 120 \text{ W}$$

OR $P_R = \text{power due to } 20 \sin 2t, \text{ A} + \text{power due to } -20 \text{ A} =$
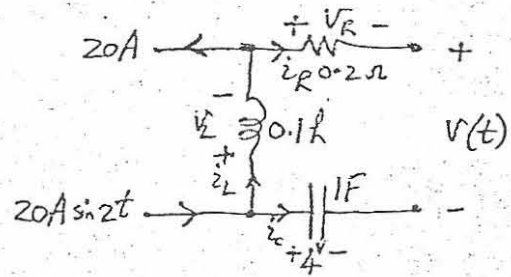
$$= \left(\frac{20}{\sqrt{2}} \right)^2 \times 0.2 + (-20)^2 \times 0.2 = \left(\frac{400}{2} + 400 \right) \times 0.2 = 600 \times 0.2 = 120 \text{ W} \quad (\therefore \text{OK})$$



1-29
35

$$v(t) = 5e^{-t} \text{ V}, i(t) = ?$$

$$i_2 = 2 \frac{d}{dt}(5e^{-t}) = -10e^{-t} \text{ A}$$

$$i_R = \frac{v}{V_3} = 15e^{-t} \text{ A}$$

KCL @ Node B: $i_L = i_R + i_2 = 15e^{-t} - 10e^{-t} = 5e^{-t} \text{ A}$

KVL around Mesh M_1 : $\therefore v_C = v_L + v$


$$v_L = 0.5 \frac{di_L}{dt} = 0.5(-5e^{-t}) = -2.5e^{-t} \text{ V}$$

$$\therefore v_C = -2.5e^{-t} + 5e^{-t} = 2.5e^{-t} \text{ V}$$

$$\therefore i_{C1} = 4 \frac{dv_C}{dt} = 4 \frac{d}{dt}(2.5e^{-t}) = -10e^{-t} \text{ A}$$

KCL @ Node A: $i(t) = i_{C1} + i_L = -10e^{-t} + 5e^{-t}$

$$\therefore i(t) = -5e^{-t} \text{ A}$$

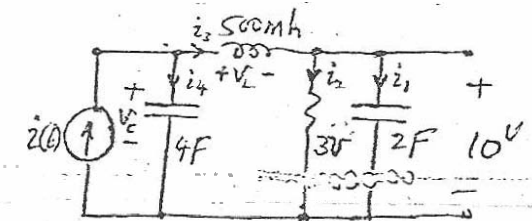

1-30
35

Assuming orientations shown:

$$\therefore i_1 = C \frac{d}{dt}(10V) = 2 * 0 = 0 \text{ A}$$

$$\therefore i_2 = 3V * 10V = 30$$

$$\therefore \text{KCL: } i_3 = i_1 + i_2 = 30 \text{ A}$$

$$\therefore v_L = L \frac{di_3}{dt} = .5 * \frac{d30}{dt} = 0 \text{ Volts}$$


$$\therefore \text{KVL: } v_C = v_L + 10V = 0 + 10 = 10V$$

$$\therefore i_4 = C \frac{dv_C}{dt} = 4 \frac{d10V}{dt} = 4 * 0 = 0 \text{ A}$$

$$\therefore i(t) = i_3 + i_4 = 30 + 0 = 30 \text{ A, the source current.}$$

$v = 10 \cos 2t$ V, Find i, p & sketch v, i & p .

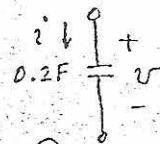
(a) $i = C \frac{dv}{dt} = 0.2 (-20 \sin 2t) = -4 \sin 2t$ A




(b) sketches of v & i

(c) $p = vi = (10 \cos 2t)(-4 \sin 2t)$

$\therefore p = -20 \sin 4t$

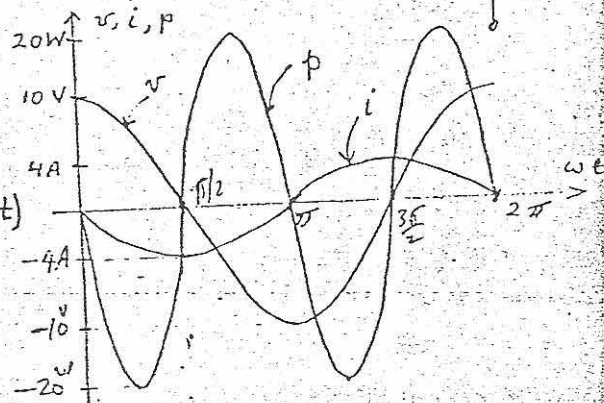

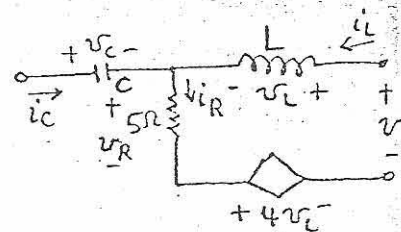$i_L = 5 \sin 2t$ A, $v_C = 10e^{-5t}$ V, find $v(t)$



$v(t) = v_L + v_R + 4v_C$ [KVL]

$v_L = L \frac{di_L}{dt} = 10L \cos 2t$ V

$i_R = i_L + i_C$ (KCL)

$i_C = C \frac{dv_C}{dt} = -50C e^{-5t}$ A


$\therefore i_R = 5 \sin 2t - 50C e^{-5t}$ A

$v_R = 5i_R = 25(\sin 2t - 10C e^{-5t})$ V

$\therefore v(t) = 10L \cos 2t + 25(\sin 2t - 10C e^{-5t}) + 40L \cos 2t$
 $= 25[2L \cos 2t + \sin 2t - 10C e^{-5t}]$ V

1-33
35

$V_0 = 5V, I_5 = ?$

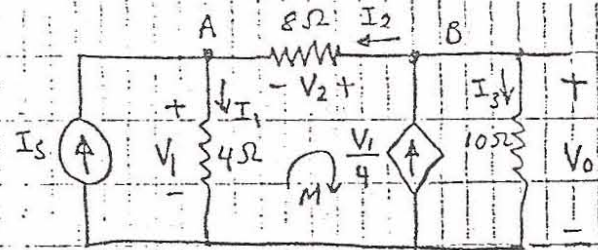

$I_3 = \frac{V_0}{10} = 0.5A$

KCL @ Node B $I_2 = \frac{V_1}{4} - I_3 = 0.25V_1 - 0.5$

KVL around Mesh M $V_1 = V_0 - V_2 = 5 - 8(0.25V_1 - 0.5)$ Ohm's law

$\therefore V_1 = \frac{9}{3} = 3V$

$\therefore I_2 = 0.25 \times 3 - 0.5 = 0.25A$

$\therefore I_1 = \frac{V_1}{4} = \frac{3}{4} = 0.75A$

KCL @ Node A

$I_5 = I_1 - I_2 = 0.75 - 0.25 = 0.5A$


$P_{4\Omega} = I_{4\Omega}^2 \times 4 = \left(\frac{3}{4}\right)^2 \times 4 = \frac{9}{4} = 2.25 \text{ Watt}$

$i_1 = 5A, i_3 = 10 \sin 3t A, i_4 = 2e^{-5t} A$
 $v_1, v_2, v_3, v_4, i_2, i_5 = ?$

$v_1 = 2i_1 = 10V$

$v_3 = 3 \frac{di_3}{dt} = 3(30 \cos 3t) = 90 \cos 3t V$

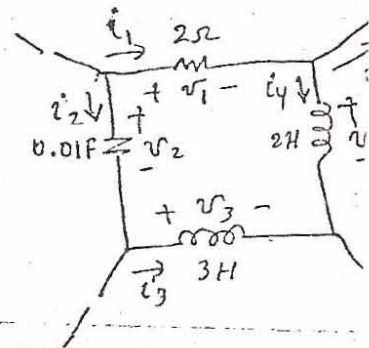$v_4 = 2 \frac{di_4}{dt} = 2(-10e^{-5t}) = -20e^{-5t} V$



KVL $v_2 = v_1 + v_4 - v_3 = 10 - 20e^{-5t} - 90 \cos 3t, V$

$i_2 = C \frac{dv_2}{dt} = 0.01 (+100e^{-5t} + 270 \sin 3t) = e^{-5t} + 2.7 \sin 3t$

KCL $\therefore i_5 = i_1 - i_4 = 5 - 2e^{-5t}, A$

2-1
78


$I_{M0} = 1 \text{ mA}, R_M = 25 \Omega$

(a) for ammeter, $R_S = ?$ if $I_D = 5 \text{ A}$

$R_S = \frac{R_M I_{M0}}{I_D - I_{M0}} = \frac{25 \times 10^{-3}}{5 - 10^{-3}} \approx 0.005 \Omega$

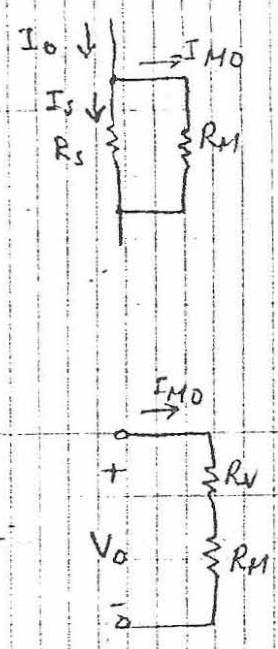
(b) for Voltmeter, $R_V = ?$ if $V_0 = 50 \text{ V}$

$R_V = \frac{V_0}{I_{M0}} - R_M = \frac{50}{10^{-3}} - 25 = 50,000 - 25 \approx 50 \text{ k}\Omega$



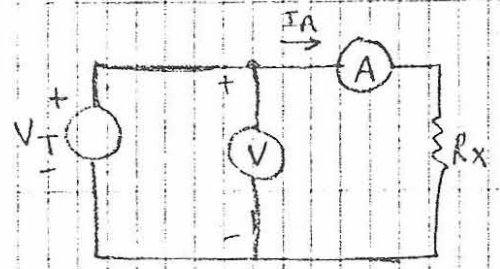2-5
79

$R_V = \text{Voltmeter Resistance} = 10 \text{ k}\Omega$
 $R_A = \text{Ammeter } \quad \quad \quad = 1 \Omega$
 $V_T = 10 \text{ V}, R_X = 2000 \Omega = 2 \text{ k}\Omega$




(a) Fig(a): $V = V_T = 10 \text{ V}$

KVL $\rightarrow V = I_A R_A + I_A R_X$

$\therefore I_A = \frac{V_T}{R_A + R_X} = \frac{10}{2001} = 4.9975 \text{ mA}$

Fig(b)

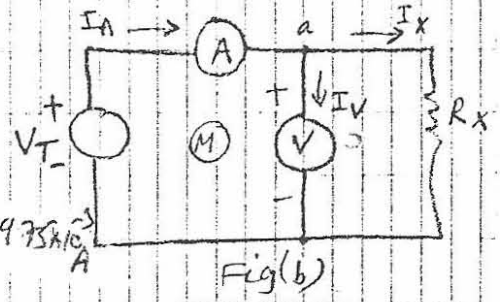


KCL (a) $\rightarrow I_A = I_V + I_X$
 $I_X R_X = V = I_V R_V \quad \therefore \frac{I_X}{I_V} = \frac{R_V}{R_X} = \frac{10}{2} = 5 \quad \text{--- (1)}$
 $\therefore I_V = \frac{I_A}{6} \quad \text{--- (2)}$

KVL for Mesh M $\rightarrow V_T = I_A R_A + I_V R_V$
 $\therefore I_A = \frac{10}{1667.667} = 0.0059964 \text{ A} = 5.9964 \text{ mA}$
 $V = I_V R_V = \frac{I_A}{6} (10^4) = 9.994 \text{ V}$

$$\frac{2-12}{81}$$

$V = ?$ by direct application:

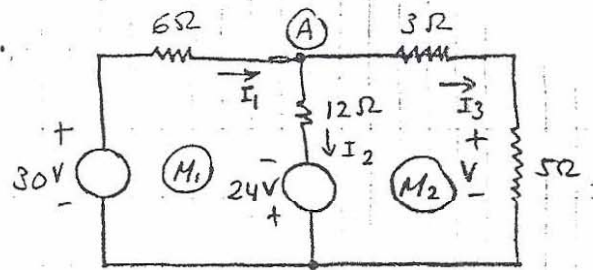

KCL at node A

$$I_1 = I_2 + I_3 \quad (1)$$

KVL for Mesh M_1 $30 + 24 = 6I_1 + 12I_2 \Rightarrow I_1 = 9 - 2I_2 \quad (2)$

from (1) & (2) $I_2 + I_3 = 9 - 2I_2 \Rightarrow I_2 = 3 - \frac{I_3}{3} \quad (3)$

KVL for Mesh M_2 $12I_2 = 3I_3 + 5I_3 + 24 \quad (4)$

using (3) in (4) $\rightarrow \boxed{I_3 = 1A} \quad \& \quad \boxed{V = 5I_3 = 5V}$

$$\frac{2-13}{81}$$

$$V = 8 * (I - 5) \quad (1)$$

$$V' = V + 28I \quad (2)$$

$$V' = 4 * (10 - I) \quad (3)$$

(2) into (3)


$$\therefore V + 28I = 40 - 4I$$

$$\therefore V = 40 - 32I$$

into (1)

$$\therefore 40 - 32I = 8I - 40$$
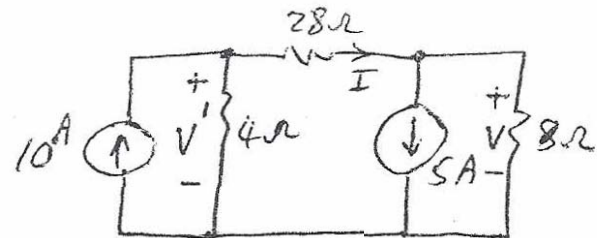
$$\therefore 40I = 80 \quad \therefore \underline{I = 2 \text{ Amp.}}$$




$\frac{2-14}{81}$

$$\textcircled{a} I_1 = \frac{0.3 \text{ V}}{(1+0.5) \text{ k}\Omega} = 0.2 \text{ mA}$$

$$\therefore V_1 = (0.2 \text{ mA})(1 \text{ k}\Omega) = 0.2 \text{ V}$$
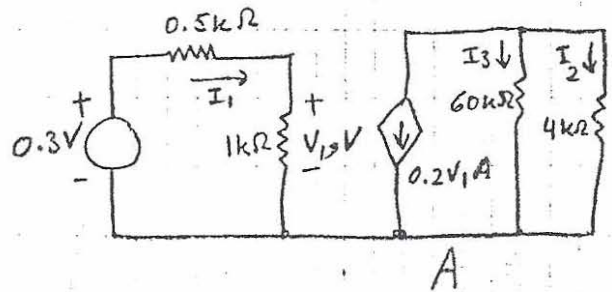
$$\therefore 0.2 V_1 = 0.04 \text{ A} = 400 \text{ mA}$$



$$4I_2 = 60I_3 \quad \therefore \quad I_3 = \frac{I_2}{15}$$

$$\textcircled{a} \text{ node A} \quad I_3 = -(0.2V_1 + I_2)$$

$$\textcircled{1} \quad I_2 + I_3 \text{ in mA}$$

$$\textcircled{2}$$


$$\text{from } \textcircled{1} \text{ and } \textcircled{2} \quad \frac{I_2}{15} = -400 - I_2 \quad \Rightarrow \quad \boxed{I_2 = \frac{-6000}{16} = -375 \text{ mA}}$$

$$\textcircled{b} P_{in} = 0.3I_1 = 0.06 \text{ mW} = 60 \mu\text{W}$$


$$\textcircled{c} P_{out} = I_2^2 (4\text{k}) = (-37.5 \times 10^{-3})^2 (4 \times 10^3) = 5.625 \text{ W}$$

It is an amplifier

2-17
82

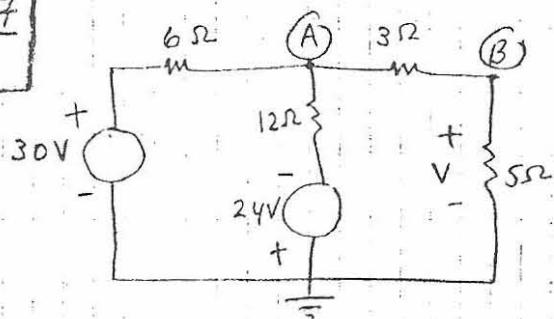

Convert
Redraw

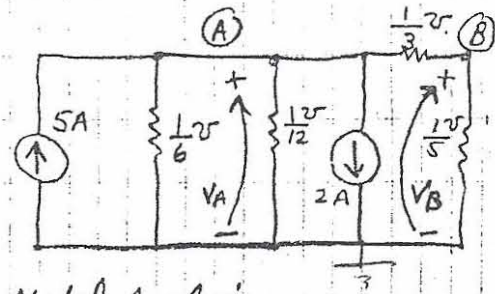

V = ? using Nodal Analysis

① (A) $(\frac{1}{6} + \frac{1}{12} + \frac{1}{3})V_A - \frac{1}{3}V_B = 5 - 2$

$\Rightarrow 7V_A - 4V_B = 36$ (1)

② (B) $-\frac{1}{3}V_A + (\frac{1}{3} + \frac{1}{5})V_B = 0$


$\Rightarrow V_A = \frac{8}{5}V_B$ (2)

② in ① $\Rightarrow 7(\frac{8}{5}V_B) - 4V_B = 36$

$V = V_B = \frac{180}{36} = 5V$

2-20
82

Converting and Redrawing, we obtain

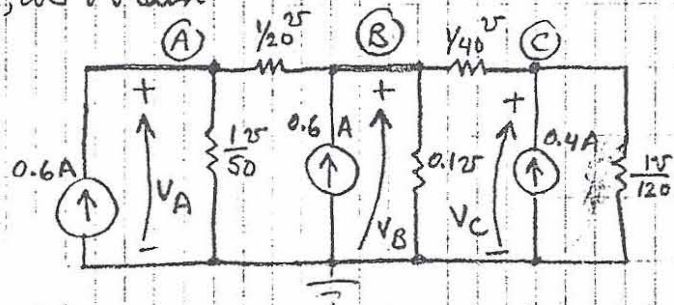

① To find V_B :

① (A) $(\frac{1}{50} + \frac{1}{20})V_A - \frac{V_B}{20} - 0.6V_C = 0.6$

$\Rightarrow 0.07V_A - 0.05V_B - 0.6V_C = 0.6$ (1)

② (B) $-\frac{V_A}{20} + (\frac{1}{20} + 0.1 + \frac{1}{40})V_B - \frac{V_C}{40} = 0.6$

$\Rightarrow -0.05V_A + (0.175)V_B - 0.025V_C = 0.6$ (2)

③ (C) $-0.6V_A - \frac{V_B}{40} + (\frac{1}{40} + \frac{1}{120})V_C = 0.4$

$\Rightarrow -0.6V_A - 0.025V_B + 0.0333V_C = 0.4$ (3)

$$V_B = \begin{vmatrix} 0.07 & 0.6 & 0 \\ -0.05 & 0.6 & -0.025 \\ 0 & 0.4 & 0.0333 \end{vmatrix} = \begin{vmatrix} 0.07 & -0.05 & 0 \\ -0.05 & 0.175 & -0.025 \\ 0 & -0.025 & 0.0333 \end{vmatrix}$$

$= 11.0222 \text{ Volts}$

② To find I_3 :


KVL: $V_B = 10I_3 + 6$

$\therefore I_3 = \frac{11.0222 - 6}{10} = 0.50222 \text{ A}$

2-21
82

$V_B = ?$

Convert & Redraw

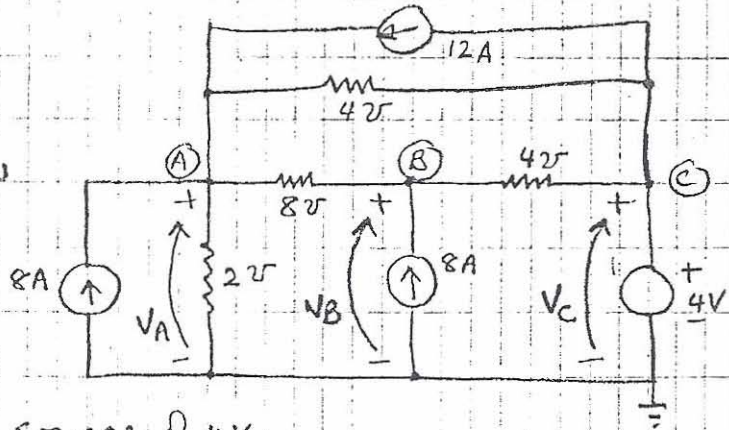

Notice that voltage source of 4V has no series resistance \Rightarrow can't be converted to current source.

However, $V_C = 4V$ (known) \Rightarrow need only 2 eqs. for V_A & V_B .

a) node (A)

$$(2 + 8 + 4) V_A - 8 V_B - 4 V_C = 8 + 12$$

OR

$$7 V_A - 4 V_B = 18 \quad (1)$$

a) node (B)

$$-8 V_A + (8 + 4) V_B - 4 V_C = 8$$

OR


$$-2 V_A + 3 V_B = 6 \quad (2)$$

from (2) $V_A = \frac{3}{2} V_B - 3 \quad (3)$

(3) in (1) $7\left(\frac{3}{2} V_B - 3\right) - 4 V_B = 18 \Rightarrow V_B = 6V$

2-24
83

Find I using mesh analysis.

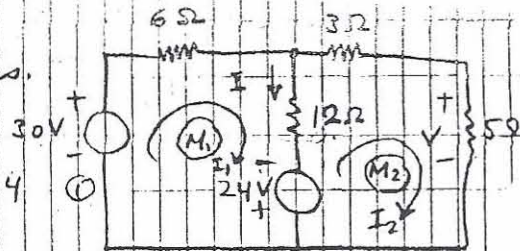

M_1 $(6+12)I_1 - 12I_2 = 30 + 24 = 54$ ①

M_2 $-12I_1 + (12+3+5)I_2 = -24$
OR $-3I_1 + 5I_2 = -6$ ②

① $\rightarrow I_1 = 3 + \frac{2}{3}I_2$

Substitute in ② $\rightarrow -3(3 + \frac{2}{3}I_2) + 5I_2 = -6$


Solving for $I_2 \Rightarrow I_2 = 1A$

$\therefore I_1 = 3 + \frac{2}{3} = 3.667A$

$\therefore I = I_1 - I_2 = 2.667A$

2-25
83

Convert and redraw:

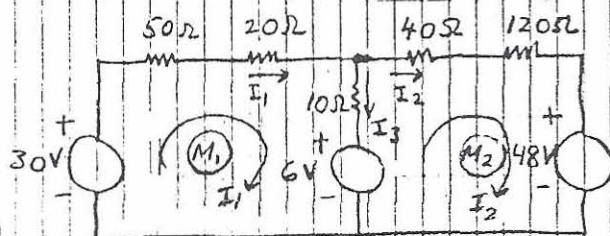

M_1 $(50+20+10)I_1 - 10I_2 = 30 - 6$
 $\therefore 80I_1 - 10I_2 = 24$ ①

M_2 $-10I_1 + (10+40+120)I_2 = 6 - 48 = -42$ ②

from ① $I_2 = 8I_1 - 2.4$

Substitute in ② $\therefore -10I_1 + 170(8I_1 - 2.4) = -42$

$\Rightarrow I_1 = 0.27A$ and $I_2 = -0.231A$

$\therefore I_1 = 0.27A$, $I_2 = -0.231A$


$\therefore I_3 = I_1 - I_2 = 0.502A$

2-28
84

Convert the current source with parallel conductance only and redraw the ckt.

Notice that the 8A-current source has no parallel conductance, so we can't convert it.

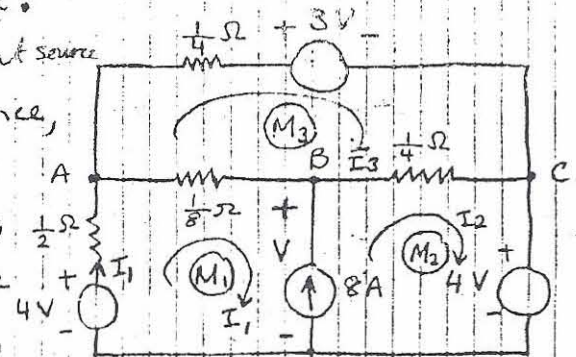However, a voltage exists across this current source say V as shown. This voltage is considered as a source in the Mesh Analysis.



$$(M_1) \quad \left(\frac{1}{2} + \frac{1}{8}\right) I_1 - \frac{1}{8} I_3 = 4 - V \Rightarrow 5I_1 - I_3 = 32 - 8V \quad (1)$$

$$(M_2) \quad \frac{1}{4} I_2 - \frac{1}{4} I_3 = V - 4 \Rightarrow -2I_2 + 2I_3 = 32 - 8V \quad (2)$$

from (1) & (2): $5I_1 - I_3 = -2I_2 + 2I_3 \Rightarrow 5I_1 + 2I_2 - 3I_3 = 0 \quad (3)$

$$(M_3) \quad -\frac{1}{8} I_1 - \frac{1}{4} I_2 + \left(\frac{1}{8} + \frac{1}{4} + \frac{1}{4}\right) I_3 = -3 \Rightarrow -I_1 - 2I_2 + 5I_3 = -24 \quad (4)$$


But $8 = I_2 - I_1 \Rightarrow -I_1 + I_2 + 0I_3 = 8 \quad (5)$

Solve eqs. (3), (4) & (5) simultaneously:

$$I_1 = \frac{\begin{vmatrix} 0 & 2 & -3 \\ -24 & -2 & 5 \\ 8 & 1 & 0 \end{vmatrix}}{\begin{vmatrix} 5 & 2 & -3 \\ -1 & -2 & 5 \\ -1 & 1 & 0 \end{vmatrix}} = \frac{(0)(0-5) - (-24)(0+3) + (8)(10-6)}{5(0-5) - (-1)(0+3) + (-1)(10-6)} = \frac{72+32}{-25+3-4} = \frac{104}{-26} = -4 \text{ A}$$

$\therefore I_1 = -4 \text{ A}$ is the current in the $\frac{1}{2} \Omega$ resistor.

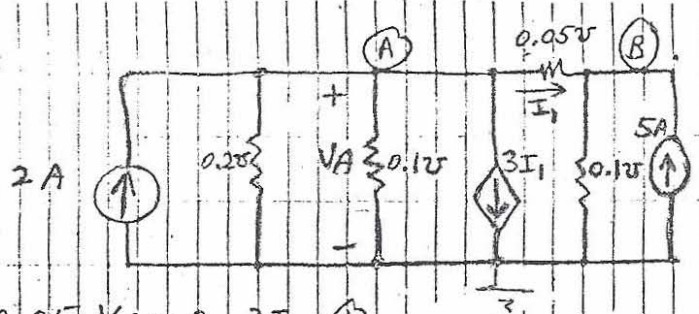$\frac{2-30}{84}$ Convert all voltage sources and redraw.



Node (A)

$$(0.2 + 0.1 + 0.05)V_A - 0.05V_B = 2 - 3I_1 \quad (1)$$

Node (B)

$$-0.05V_A + (0.05 + 0.1)V_B = 5 \quad (2)$$

Constraint

$$I_1 = 0.05(V_A - V_B) \quad (3)$$

substitute (3) in (1) \Rightarrow


$$V_B = -10 + 2.5V_A \quad (4)$$

substitute (4) in (2) \Rightarrow

$$V_A = 20V, \text{ the voltage across } 5A$$

from (4) $V_B = 40V$, from (3) $I_1 = -1A$

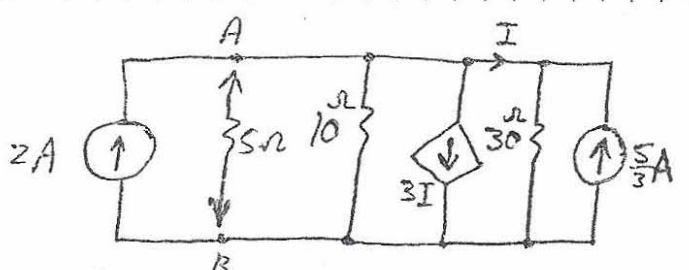
$\frac{2-30}{84}$ Remove the 5Ω and convert to current sources



$$\therefore V_{AB} = (2 + \frac{5}{3} - 3I) \cdot (10 || 30) = \frac{11 - 9I}{3} \cdot \frac{300}{40} = 27.5 - 22.5I \quad (1)$$

Constraint Eq:
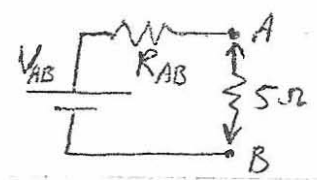
$$I = \frac{V_{AB}}{30} - \frac{5}{3} = \frac{V_{AB} - 50}{30} \quad (2)$$



$$(2) \text{ into } (1) \Rightarrow V_{AB} = 27.5 - 22.5 \left(\frac{V_{AB} - 50}{30} \right) \therefore V_{AB} \left(1 + \frac{22.5}{30} \right) = 27.5 + \frac{22.5 \times 5}{3}$$

$$\therefore V_{AB} \left(1 + \frac{3}{4} \right) = 27.5 + 37.5 = 65$$

$$\therefore V_{AB} = 65 \times \frac{4}{7} = \frac{260}{7} \text{ Volts} = 37.143 \text{ Volts}$$

To find I_{AB} short AB, \therefore from (2) $I = \frac{0 - 50}{30} = -\frac{5}{3} A$

$$\therefore I_{AB} = 2 + \frac{5}{3} - 3I - 0 \cdot (10 || 30) = \frac{6 + 5 - 3 \times (-5)}{3} = \frac{26}{3} A = 8.6 A$$

$$\therefore R_{AB} = V_{AB} / I_{AB} = \frac{260}{7} \times \frac{3}{26} = \frac{30}{7} \Omega = 4.2857 \Omega$$

$$\therefore V_{5\Omega} = V_{AB} \times \left(\frac{5}{5 + R_{AB}} \right) = \frac{260}{7} \times \left(\frac{5 \times 7}{5 \times 7 + 30} \right) = \frac{260 \times 5 \times 7}{7 \times 65} = 20 \text{ Volts}$$

For max. power replace 5Ω by $\frac{30}{7} \Omega$, hence getting max. power of $\left(\frac{13}{3} \right)^2 \cdot \frac{30}{7} = \frac{1690}{21} W = 80.476W$

2-30
84

Solution by Thevenin Theorem:

Take away the 5Ω resistor & denote the terminals by AB.

V_{AB} when the 5Ω is out = E_{th}






R_{AB} = " " " " = $R_{th} = \frac{E_{th}}{I_{th}}$

where I_{th} is the short circuit

current through AB.

Using simplification:

$I_2 = -I_1 + \frac{5}{3} A$

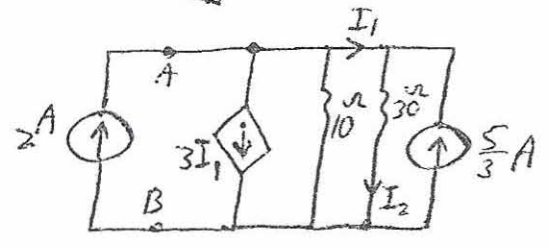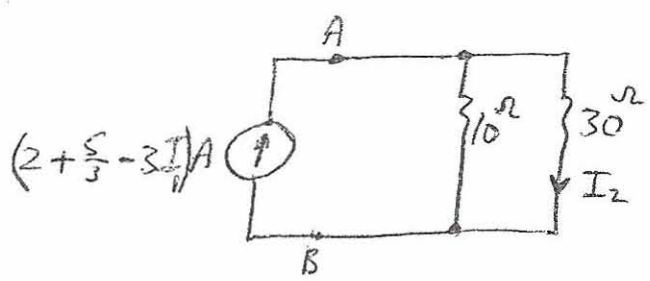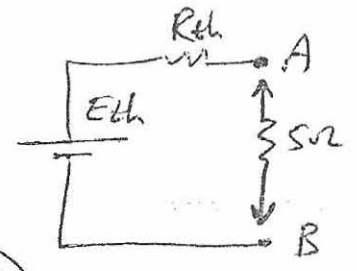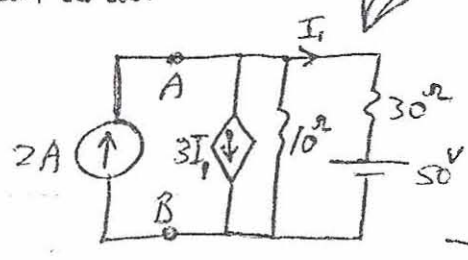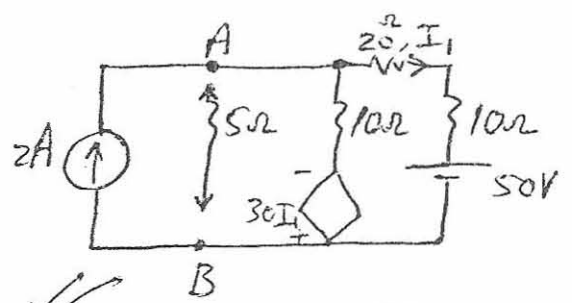

$\therefore I_2 = (2 + \frac{5}{3} - 3I_1) \times \frac{10}{10+30} = I_1 + \frac{5}{3}$

$\therefore \frac{11}{3} - 3I_1 = 4I_1 + \frac{20}{3} \Rightarrow 7I_1 = \frac{11-20}{3} = \frac{-9}{3} = -3$

$\therefore I_1 = \frac{-3}{7} A = -0.4286 A$

$\therefore I_2 = \frac{-3}{7} + \frac{5}{3} = \frac{-9+35}{21} = \frac{26}{21} = 1.2381 A$

$\therefore V_{AB} = E_{th} = 30 I_2 = \frac{260}{7} = 37.1429 V$

Now recalculate with AB shorted together, hence $I_2 = 0$ & $I_1 = -\frac{5}{3} A$


$\therefore I_{th} = 2 + \frac{5}{3} - 3I_1 = \frac{11}{3} + 5 = \frac{11+15}{3} = \frac{26}{3} = 8.6 A$

$\therefore R_{th} = E_{th} / I_{th} = (260/7) / (\frac{26}{3}) = \frac{260 \times 3}{7 \times 26} = \frac{30}{7} = 4.2857 \Omega$

$\therefore i_{sr} = E_{th} / (R_{th} + 5) = \frac{260/7}{30/7 + 5} = \frac{260}{65} = 4 A$ & $V_{sr} = 20 V$

\therefore max. power is when 5Ω is replaced by $\frac{30}{7} \Omega$ hence giving $(\frac{26}{6})^2 \times \frac{30}{7} = 80.4762 W$

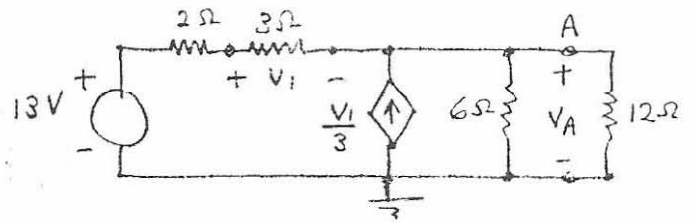2-31
85 Constant voltage source to current source.




Node (B)

$$\left(\frac{1}{2} + \frac{1}{3}\right) V_B - \frac{1}{3} V_A = \frac{13}{2} \quad (1)$$

Node (A)
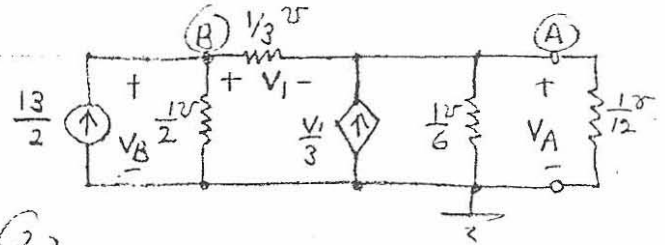
$$-\frac{1}{3} V_B + \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{12}\right) V_A = \frac{V_1}{3} \quad (2)$$



Constraint Eq. $V_1 = V_B - V_A \quad (3)$

$$(3) \text{ in } (2) \quad -\frac{1}{3} V_B + \frac{7}{12} V_A = \frac{V_B - V_A}{3} \Rightarrow V_B = \frac{11}{8} V_A \quad (4)$$


$$(4) \text{ in } (1) \quad \frac{5}{6} \times \frac{11}{8} V_A - \frac{1}{3} V_A = \frac{13}{2} \Rightarrow \boxed{V_A = 8 \text{ V}}$$

Voltage across 12Ω

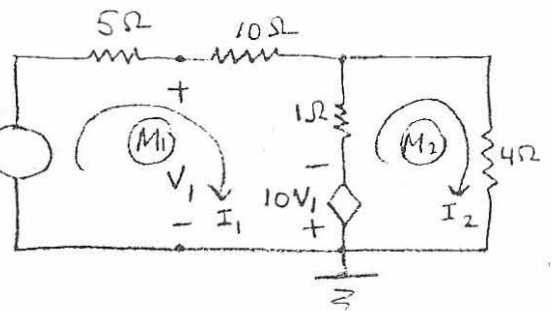2-34
86 (a) Power dissipated, $P_d = I_2^2 (4) \text{ W}$

$$(M_1) \quad (5 + 10 + 1) I_1 - (1) I_2 = 31 + 10V_1 \quad (1)$$

$$(M_2) \quad -(1) I_1 + (1 + 4) I_2 = -10V_1 \quad (2)$$



Constraint Eq.: $V_1 = 31 - 5I_1 \quad (3)$

$$(3) \text{ in } (1) \quad \rightarrow 16I_1 - I_2 = 31 + 10(31 - 5I_1) \Rightarrow I_2 = 66I_1 - 341 \quad (4)$$

$$(4) \text{ \& } (3) \text{ in } (2) \quad \rightarrow -I_1 + 5(66I_1 - 341) = -10(31 - 5I_1) \Rightarrow \boxed{I_1 = 5 \text{ A}} \quad (5)$$

from (4) $\boxed{I_2 = -11 \text{ A}}$ $\therefore P_d = (-11)^2 (4) = 484.0 \text{ W}$


(b) Power supplied, $P_{in} = 31 I_1 = 155 \text{ W}$

$$\frac{2-35}{86}$$

(a)

(M₁) $(10^3 + 10^3) I_1 - 10^3 I_0 = 10^{-3}$ (1)

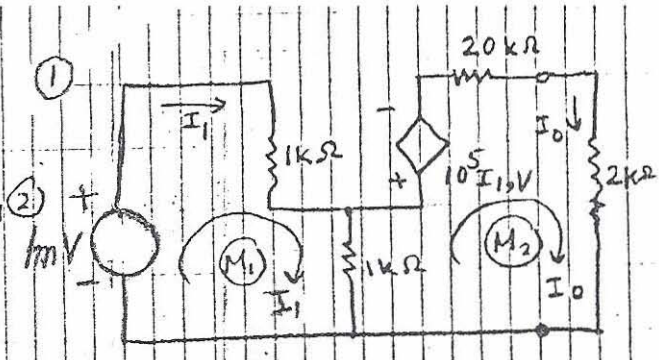(M₂) $-10^3 I_1 + (1 + 20 + 2) 10^3 I_0 = -10 I_1$ (2)



(2) $\Rightarrow 99 I_1 + 23 I_0 = 0 \Rightarrow I_0 = -\frac{99}{23} I_1$

into (1) $\Rightarrow (2 + \frac{99}{23}) \times 10^3 I_1 = 10^{-3} \Rightarrow I_1 = 0.159 \mu A$

$I_0 = -0.683 \mu A$

(b) Power input by the source, $P_{in} = 10^{-3} I_1 = 0.159 \times 10^{-9} W$

(c) Power output, $P_{out} = I^2 (2 \times 10^3) = (-0.683 \times 10^{-6})^2 \times 2 \times 10^3$
 $P_{out} = 0.932 \times 10^{-9} W$


(d) Power in the dependent source, $= (10^5 I_1) I_0$ into it

$\therefore P_d = (10^5 \times 0.159 \times 10^{-6}) (-0.683 \times 10^{-6}) = -10.83 \times 10^{-9} W$
 \therefore power source is $-10.83 nW$

OR power out of dependent source is $10.83 nW$
 \therefore Dependent supplies power of $10.83 n$

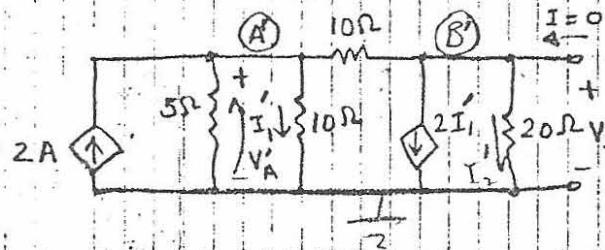2-38
88

1st suppress the current source to see the effect of the independent voltage source.
Converting the voltage source, redraw the ckt.



Node (A)

$$\left(\frac{1}{5} + \frac{1}{10} + \frac{1}{10}\right) V_A' - \frac{1}{10} V_B' = 2 \quad (1)$$

Node (B)

$$-\frac{1}{10} V_A' + \left(\frac{1}{10} + \frac{1}{20}\right) V_B' = -2 I_1' \quad (2)$$

Constraint

$$I_1' = \frac{V_A'}{10} \quad (3)$$

$$(3) \text{ in } (2) \rightarrow -0.1 V_A' + 0.15 V_B' = -0.2 V_A'$$

$$\Rightarrow V_A' = -1.5 V_B' \quad (4)$$

$$(4) \text{ in } (1) \rightarrow -0.4 \times 1.5 V_B' - 0.1 V_B' = 2 \Rightarrow V_B' = -2.857 V = V_2$$


$$\therefore V_A' = 4.286 V$$

$$(3) \rightarrow$$

$$\therefore I_1' = 0.4286 A$$

$$4 I_2' = \frac{V_2}{20} = -0.14286 A$$

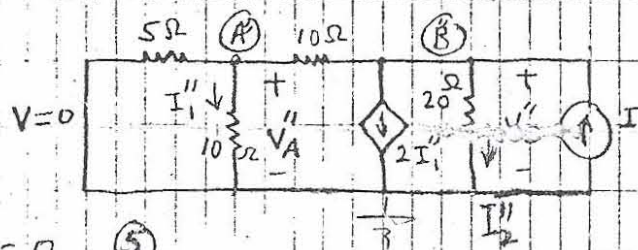2nd suppress the voltage source to see the effect of the current source.
Redraw the ckt.



Node (A)

$$\left(\frac{1}{5} + \frac{1}{10} + \frac{1}{10}\right) V_A'' - \frac{1}{10} V_B'' = 0 \quad (5)$$

Node (B)

$$-\frac{1}{10} V_A'' + \left(\frac{1}{10} + \frac{1}{20}\right) V_B'' = I - 2 I_1'' \quad (6)$$

Constraint

$$I_1'' = \frac{V_A''}{10} \quad (7)$$

$$(7) \text{ in } (6) \rightarrow -0.1 V_A'' + 0.15 V_B'' = I - 0.2 V_A'' \Rightarrow V_A'' = 10 I - 1.5 V_B''$$

$$(8) \text{ in } (5) \rightarrow 0.4(10I - 1.5V_B'') - 0.1V_B'' = 0 \Rightarrow V_B'' = 5.714I \quad V = V_2''$$

$$\therefore I_2'' = \frac{V_2''}{20} = 0.2857I \quad \text{A} \quad \text{and } I_2 = I_2' + I_2'' \rightarrow (9)$$


$$\text{Since } V_2 = I_2(20) = 0 \text{ For } V_2 = 0 \Rightarrow I_2 = 0$$

$$\therefore \text{ from } (9) \rightarrow -0.14285 + 0.2857I = 0$$

$$\boxed{I = 0.5 \text{ A}}$$

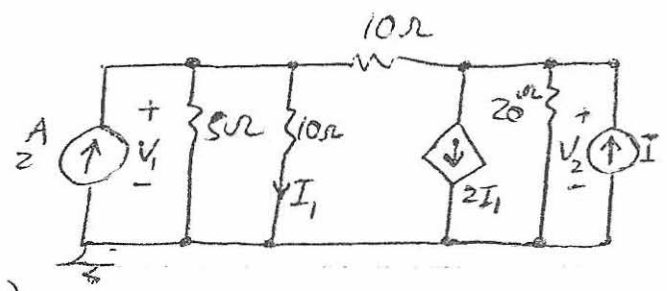2-38
88

Solution by Nodal analysis:
convert the 10V source;
denote the terminal voltage
of the new source by V_1 .



$$\therefore V_1 \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{10} \right) - V_2 \left(\frac{1}{10} \right) = 2 \quad (1)$$

$$\text{and } V_1 \left(-\frac{1}{10} \right) + V_2 \left(\frac{1}{10} + \frac{1}{20} \right) = I - 2I_1 \quad (2)$$

$$\text{with constraint Eq: } I_1 = V_1/10 \quad (3)$$

$$\therefore V_2 = 0$$


$$\therefore \text{ from } (1) : \frac{4}{10}V_1 = 2 \quad \therefore V_1 = \frac{20}{4} = 5V \quad \text{into } (3)$$

$$\therefore I_1 = 5/10 = 0.5 \text{ Amp} \quad \text{into } (2)$$

$$\therefore 5 \left(-\frac{1}{10} \right) = I - 1 \quad \therefore I = 1 - \frac{1}{2} = 0.5 \text{ Amp}$$
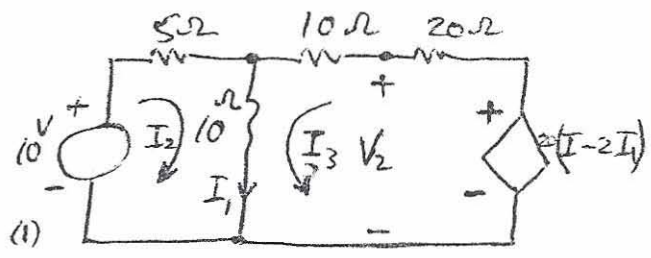
#

Solution by Mesh analysis:
convert the combined current
sources into voltage one.



$$\therefore (10+10+20)I_3 + 10I_2 = 20(I-2I_1) \quad (1)$$

$$\text{and } 10I_3 + (5+10)I_2 = 10 \quad (2)$$

$$\text{with constraint equation: } I_1 = I_2 + I_3 \quad (3)$$

$$\therefore V_2 = 0$$

$$\therefore 10I_3 + 10(I_2 + I_3) = 0 \Rightarrow I_2 + 2I_3 = 0 \Rightarrow I_2 = -2I_3 \quad (4)$$

$$(4) \text{ into } (2) \Rightarrow 10I_3 + 15(-2I_3) = 10 \Rightarrow -20I_3 = 10 \therefore I_3 = -0.5A$$

$$\text{into } (4) \Rightarrow I_2 = 1 \text{ Amp}$$

$$\text{into } (3) \Rightarrow I_1 = 0.5 \text{ Amp}$$

$$\text{into } (1) \Rightarrow 40(-0.5) + 10(1) = 20(I-1) \Rightarrow -10 = 20I - 20$$

$$\therefore I = (20-10)/20 = 0.5 \text{ Amp}$$


#

Solution by simplification:

$$\therefore V_2 = 0 \quad \therefore I_2 = \frac{10}{5+10/10} = \frac{10}{5+5} = 1 \text{ Amp} \quad \therefore I_1 = 0.5A = I_3 = 2I_1 - I \therefore I = 0.5A$$

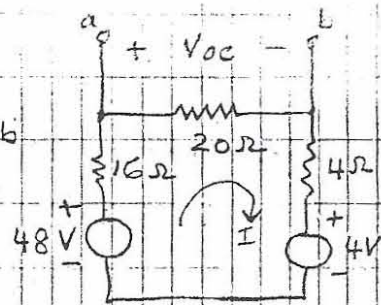2-39
88

Convert the current source,
and open the chkt @ the terminals ab




(a) $I = \frac{48-4}{16+20+4} = \frac{44}{40} = 1.1 \text{ A}$

$\therefore V_{oc} = 20 \cdot I = 22 \text{ V}$

Now, short circuit the terminals ab.


Since voltage across 20Ω resistor = 0,
in I in the resistor = 0.

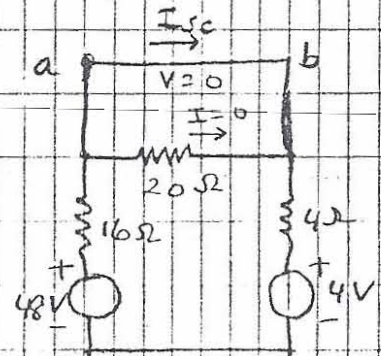$\therefore I_{sc}$ exists in the outer loop only.



From KVL, $I_{sc} = \frac{48-4}{16+4} = \frac{44}{20} = 2.2 \text{ A}$

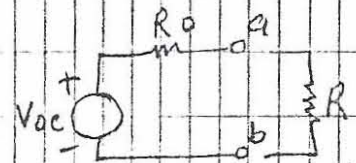$\therefore R_o = \frac{V_{oc}}{I_{oc}} = \frac{22}{2.2} = 10 \Omega$



(b) For max Power delivery to Resistance, R , between ab:

$\therefore R$ must equal $R_o = 10 \Omega$.

(c) $P_{R_{max}} = \left(\frac{V_{oc}}{R_o + R_o} \right)^2 R_o = \left(\frac{22}{20} \right)^2 \times 10 =$

$= (1.1)^2 \times 10 = 1.21 \times 10 = 12.1 \text{ W}$

$\frac{2-40}{88}$

1st convert the current source, and open ckt between c.d.

$$(M_1) \quad (3+4+2)I_1 - 4I_2 = 144 \quad (1)$$

$$(M_2) \quad -4I_1 + (4+4+8)I_2 = 0 \quad (2)$$

from (2) $I_1 = 4I_2 \quad (3)$

$$(3) \text{ in } (1) \quad 9(4I_2) - 4I_2 = 144 \Rightarrow I_2 = 4.5 \text{ A} \Rightarrow I_1 = 18 \text{ A}$$

KVL $\rightarrow \quad V_{oc} = 8I_2 + 2I_1 = 36 + 36 = 72 \text{ V}$


2nd Short circuit terminals c.d:

$$(M_I) \quad (3+4+2)I_I - 4I_{II} - 2I_{III} = 144 \quad (4)$$

$$(M_{II}) \quad -4I_I + (4+4+8)I_{II} - 8I_{III} = 0 \quad (5)$$



$$(M_{III}) \quad -2I_I - 8I_{II} + (2+8)I_{III} = 0 \quad (6)$$

$$I_{sc} = I_{III} = \begin{vmatrix} 9 & -4 & 144 \\ -1 & 4 & 0 \\ -1 & -4 & 0 \end{vmatrix} = \frac{144(4+4)}{9(20-8) - (-1)(-20-8) + (-1)(8+8)} = \frac{1152}{64} = 18 \text{ A}$$
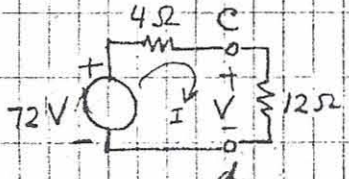
$$\therefore I_{sc} = 18 \text{ A} \Rightarrow R_0 = \frac{V_{oc}}{I_{sc}} = \frac{72}{18} = 4 \Omega$$

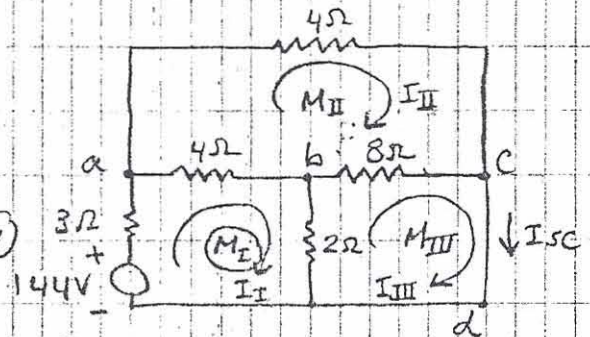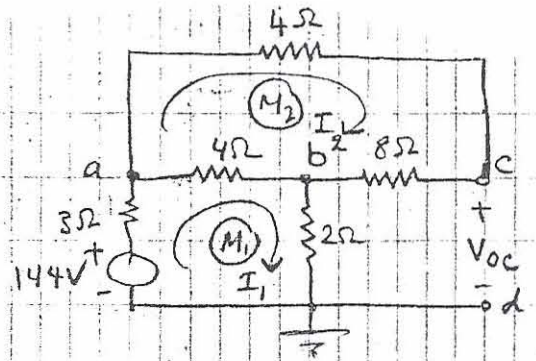
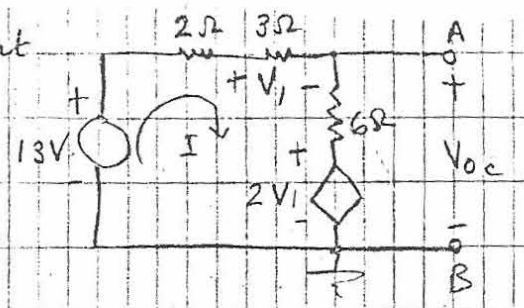
$$I = \frac{72}{4+12} = 4.5 \text{ A}$$

$V = 12 \times 4.5 = 54 \text{ V}$, the voltage across 12Ω resistor.



2-42
89

1st Convert the controlled current source & open ckt @ AB.



KVL → $(2+3+6)I = 13 - 2V_1$ (1)

Constraint $V_1 = 3I$ (2)

(2) in (1) $11I = 13 - 2 \times 3I \Rightarrow I = \frac{13}{17} = 0.765A$

$V_{oc} = 6I + 2V_1 = (6+6)I = 12 \times 0.765 = 9.176V$


2nd short ckt. AB.

KCL:

$I_{sc} = I_1 + I_2$ (3)

KVL (Right-hand side Loop)

$2V_1 = 6I_2$ (4)

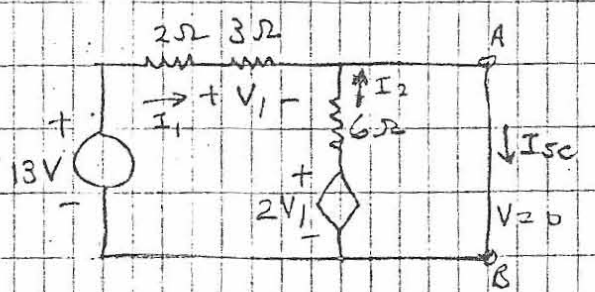


Constraint $V_1 = 3I_1$ (5)

KVL (outer loop) $(2+3)I_1 = 13 \Rightarrow I_1 = \frac{13}{5} = 2.6A$ (6)

(5) → $V_1 = 3 \times 2.6 = 7.8V$

(4) → $I_2 = \frac{V_1}{3} = \frac{7.8}{3} = 2.6A$

(3) → $I_{sc} = 2.6 + 2.6 = 5.2A$

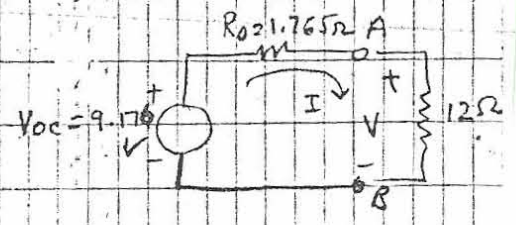

$R_0 = \frac{V_{oc}}{I_{sc}} = \frac{9.176}{5.2} = 1.765\Omega$



(6) $V = 12I = 12 \times \frac{9.176}{12+1.765} = 8.1V$, the voltage across 12Ω resistor.

2-45
89

Assume the notations shown:

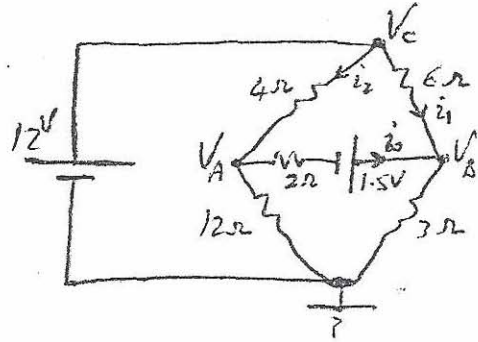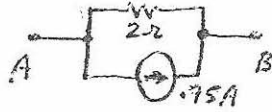a) Nodal Analysis:

∴ Converting the voltage source between AB to current source, we'll get



∴ The equations are:

$$V_c = 12 \text{ Volts} \quad (1)$$

$$\left(\frac{1}{4} + \frac{1}{2} + \frac{1}{12}\right)V_A - \frac{1}{2}V_B - \frac{1}{4}V_c = -0.75 \quad (2)$$

$$-\frac{1}{2}V_A + \left(\frac{1}{6} + \frac{1}{2} + \frac{1}{3}\right)V_B - \frac{1}{6}V_c = -0.75 \quad (3)$$

$$(1) \text{ into } (2): \frac{10V_A}{12} - \frac{6V_B}{12} - \frac{36}{12} = -\frac{9}{12} \Rightarrow 10V_A - 6V_B = 27$$

$$(1) \text{ into } (3): -\frac{6V_A}{12} + \frac{12V_B}{12} - \frac{24}{12} = \frac{9}{12} \Rightarrow -2V_A + 4V_B = 11$$

$$\therefore V_A = \frac{27 \times 4 + 6 \times 11}{10 \times 4 - 6 \times 2} = \frac{108 + 66}{40 - 12} = \frac{174}{28} \text{ V} \quad \& \quad V_B = \frac{10 \times 11 + 2 \times 27}{10 \times 4 - 6 \times 2} = \frac{110 + 54}{28} = \frac{164}{28}$$

$$\therefore i_0 = \frac{V_A - V_B + 1.5}{2} = \frac{174 - 164 + 42}{56} = \frac{52}{56} = \frac{13}{14} \text{ Amp} = 0.92857 \text{ A}$$

b) Mesh Analysis:

∴ Sources are already converted.

∴ Equations are:

$$\text{loop 1: } 12V - 6\Omega - 3\Omega: \quad (6+3)i_1 + 0i_2 + 3i_0 = 12$$

$$\text{loop 2: } 12V - 4\Omega - 12\Omega: \quad 0i_1 + (4+12)i_2 - 12i_0 = 12$$


$$\text{loop 3: } 1.5V - 3\Omega - 12\Omega - 2\Omega: \quad 3i_1 - 12i_2 + (3+12+2)i_0 = 1.5$$

$$\therefore i_0 = \frac{\begin{vmatrix} 9 & 0 & 12 \\ 0 & 16 & 12 \\ 3 & -12 & 1.5 \end{vmatrix}}{\begin{vmatrix} 9 & 0 & 3 \\ 0 & 16 & -12 \\ 3 & -12 & 17 \end{vmatrix}} = \frac{9 \times 16 \times 1.5 + 0 + 0 - 12 \times 16 \times 3 - 0 + 9 \times 12 \times 12}{9 \times 16 \times 17 + 0 + 0 - 3 \times 16 \times 3 - 0 - 9 \times 12 \times 12} = \frac{936}{1008} = \frac{13}{14} \text{ A} = 0.92857 \text{ A}$$

c) Superposition Method

$$\therefore i_c = i_c|_{12V} + i_c|_{1.5V}$$

$i_c|_{12V}$: circuit is as shown

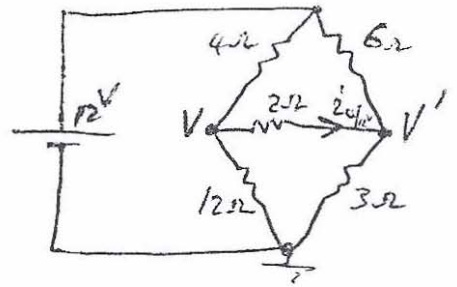

$$\therefore i_c|_{12V} = \frac{12-V}{4} - \frac{V}{12} = 3 - \frac{V}{3} \quad (4)$$

$$\& V - 2i_c = V' \& \frac{12-V'}{6} - \frac{V'}{3} = -i_c|_{12V} \quad (6)$$

$$(4) \Rightarrow V = 9 - 3i_c|_{12V} \quad (7)$$

$$\& (6) \Rightarrow 2 - \frac{V'}{2} = -i_c|_{12V} \Rightarrow V' = 4 + 2i_c|_{12V} \quad (8)$$


(7) & (8) into (5):

$$\therefore 9 - 3i_c|_{12V} - 2i_c|_{12V} = 4 + 2i_c|_{12V} \Rightarrow \therefore i_c|_{12V} = \frac{9-4}{3+2+2} = \frac{5}{7} \text{ Amp}$$

$i_c|_{1.5V}$: circuit is as shown

$$\therefore i_c|_{1.5V} = \frac{1.5}{2 + 6 \parallel 3 + 4 \parallel 12}$$
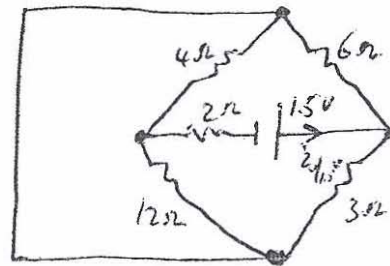
$$= \frac{1.5}{2 + \frac{6 \times 3}{6+3} + \frac{4 \times 12}{4+12}} = \frac{1.5}{2+2+3} = \frac{1.5}{7} \text{ A}$$



$$\therefore i_c = \frac{1.5}{7} + \frac{5}{7} = \frac{6.5}{7} = \frac{13}{14} \text{ Amp} = 0.92857 \text{ A}$$


d) Thevenin Theorem:

Take the branch between AB away.

$$\therefore E_{th} = V_{AB} =$$

$$= \frac{12}{4+12} \times 12 - \frac{12}{6+3} \times 3$$
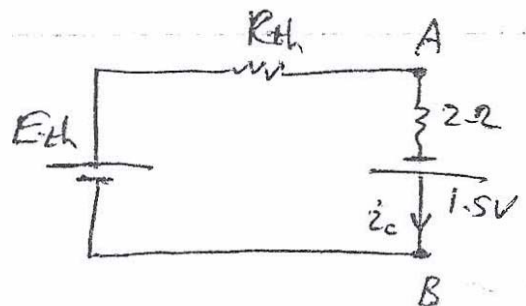
$$= \frac{144}{16} - \frac{36}{9} = 9 - 4 = 5 \text{ V}$$



$$\& R_{th} = 4 \parallel 12 + 6 \parallel 3 = 3 + 2 = 5 \Omega$$

$$\therefore i_c = \frac{E_{th} + 1.5}{R_{th} + 2} = \frac{5 + 1.5}{5 + 2} = \frac{6.5}{7} = \frac{13}{14} \text{ Amp} = 0.92857 \text{ A}$$

$$\frac{2-46}{89}$$

(a) 1st open ckt AB

$$(M_1) (10+30)I_1 - 30I_2 = 0.55 \quad (1)$$

$$(M_2) -30I_1 + (30+2+6)I_2 - (2+6)I_3 = 0 \quad (2)$$

$$(M_3) -(2+6)I_2 + (2+40+12+6)I_3 = 3V_1 \quad (3)$$


Constraint $V_1 = 6(I_2 - I_3) \quad (4)$

$$(4) \text{ in } (3) \quad I_3 = \frac{I_2}{3} \quad (5)$$

$$(5) \text{ in } (2) \quad I_1 = \frac{106}{90} I_2 \quad (6)$$

$$(6) \text{ in } (1) \quad I_2 = 32.143 \text{ mA}$$

from (5) $I_3 = 10.714 \text{ mA}$

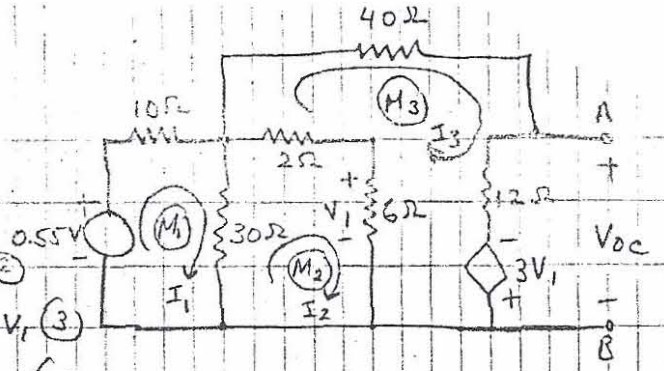

$$V_{oc} = 12I_3 - 3V_1 = 12 \times 10.714 \times 10^{-3} - 3 \times 6 \times 10^{-3} (32.143 - 10.714)$$

$$V_{oc} = -0.257 \text{ V}$$

2nd short ckt AB \Rightarrow Points A & B are at the same potential

$$\Rightarrow 40\Omega \text{ \& \; } 30\Omega \text{ in parallel, } R = \frac{30 \times 40}{30+40} = 17.143\Omega$$

$$(M_1) (10+17.143)I_I - 17.143I_{II} = 0.55 \quad (7)$$

$$(M_2) -17.143I_I + (17.143+2+6)I_{II} = 0 \quad (8)$$

$$(M_3) I_{sc} = \frac{-3V_1}{12} \quad (9)$$

Constraint $V_1 = 6I_{II} \quad (10)$



$$(10) \text{ in } (9) \quad I_{sc} = -1.5I_{II} \quad (11)$$

from (8) $I_I = 1.467I_{II} \quad (12)$

$$(12) \text{ in } (7) \quad I_{II} = 24.265 \text{ mA}$$

from (11) $I_{sc} = -36.397 \text{ mA}$
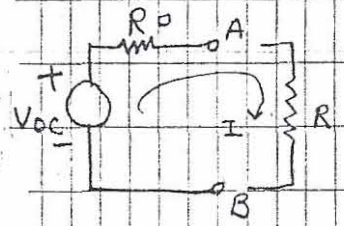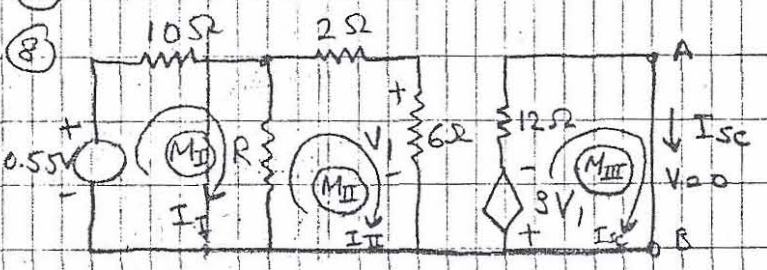
$$\therefore R_0 = \frac{V_{oc}}{I_{sc}} = \frac{-0.257}{-36.397 \times 10^{-3}} = 7.065 \Omega$$



(b) For max. power delivery, $R = R_0 = 7.065 \Omega$

$$P_{max} = I^2 R_0 = \left(\frac{V_{oc}}{2R_0} \right)^2 R_0 = \frac{(-0.257)^2}{4 \times 7.065} = 2.340 \text{ mW}$$

2-47
89

Convert Δ_{ACD} into Y and redraw.

$$R_1 = \frac{6 \times 18}{6 + 6 + 18} = \frac{108}{30} = 3.6 \Omega$$

$$R_2 = \frac{6 \times 6}{30} = 1.2 \Omega$$



$$R_3 = \frac{18 \times 6}{30} = 3.6 \Omega$$

$$R_{EDB} = 3.6 + 18 = 21.6 \Omega$$

$$R_{ECB} = 1.2 + 6 = 7.2 \Omega$$

$$R_{EB} = R_{ECB} \parallel R_{EDB} = \frac{7.2 \times 21.6}{7.2 + 21.6} = 5.4 \Omega$$
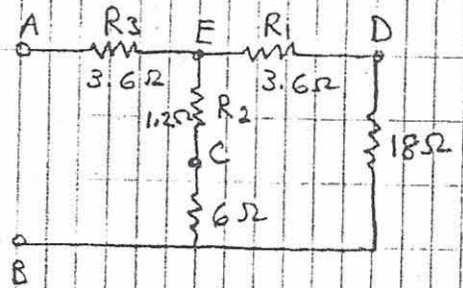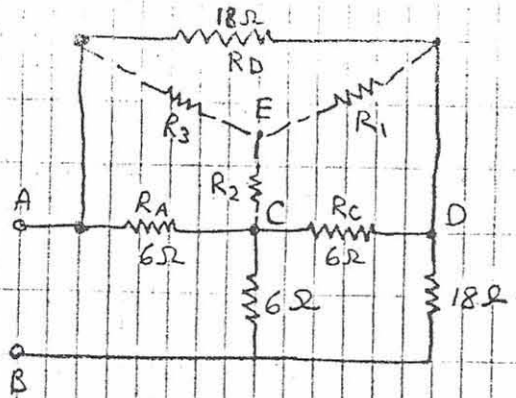
$$R_{AB} = R_3 + R_{EB} = 3.6 + 5.4 = 9.0 \Omega$$



2-48
89



Convert current sources

$$(M_1) \quad (70 + 10)I_1 - 10I_2 = 30 - 6 \quad (1)$$

$$(M_2) \quad -10I_1 + (10 + 160)I_2 = 6 - 48 \quad (2)$$

from (2) $I_1 = 17I_2 + 4.2 \quad (3)$


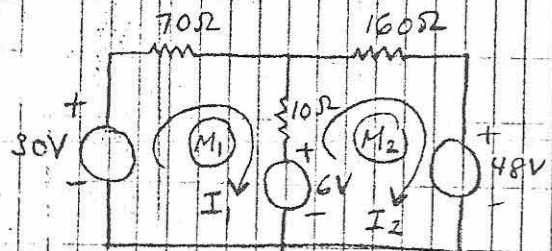
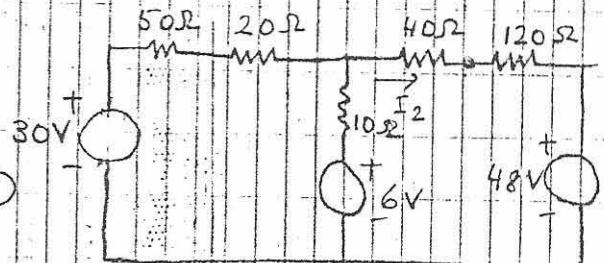
$$(3) \text{ in } (1) \quad I_2 = -0.231 \text{ A}$$



OR, you can convert the two voltage sources to current ones, then reduce them to a single current source, then convert to voltage source then solve for I_2 .

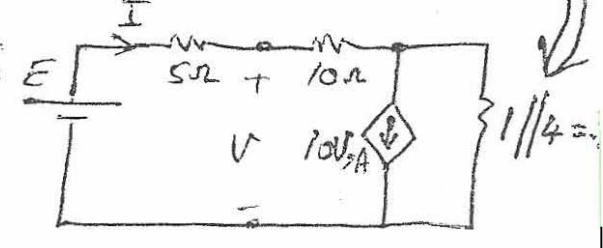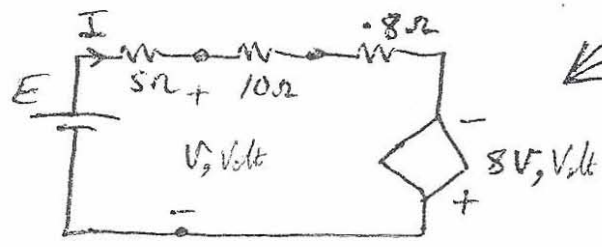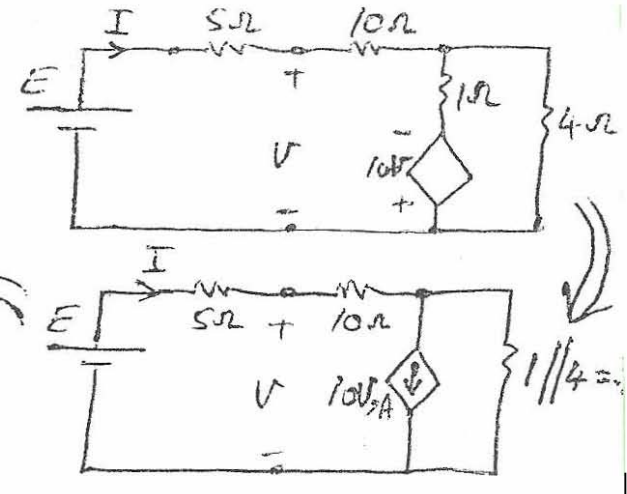2-49
89

Assume a supply current, I .
Using circuit simplification
as shown:



$\therefore V = E - 5I$ (1)

$\therefore I = \frac{E + 8V}{5 + 10 + 8} = \frac{E + 8V}{15.8}$ (2)


(1) into (2) $\therefore 15.8I = E + 8(E - 5I) = 9E - 40I$

$\therefore 15.8I + 40I = 9E \quad \therefore I = \frac{9E}{55.8}$



\therefore The equivalent resistor, R , will take same current I

$\therefore IR = E \quad \therefore R = \frac{E}{I} = \frac{55.8}{9} = 6.2 \Omega$, resistance seen by E .

2-50
89

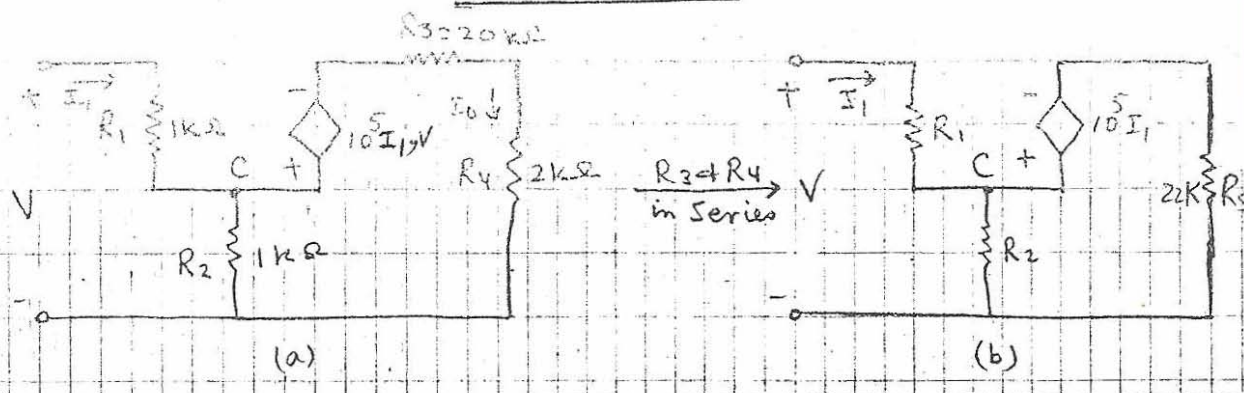


Convert controlled voltage source

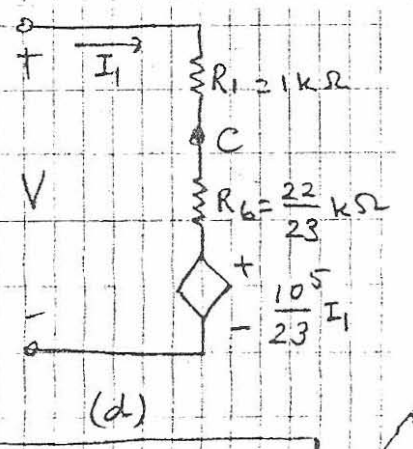
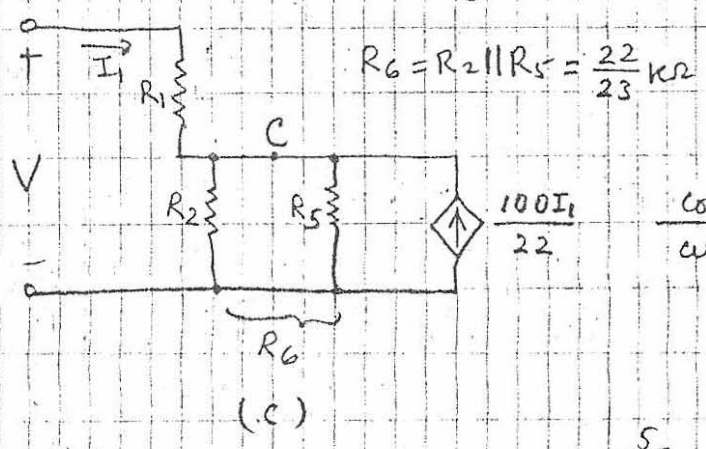


From Fig (d) : $V = (R_1 + R_6) I_1 + \frac{105 I_1}{23} \Rightarrow R_{in} = \frac{V}{I_1} = 6.304 k\Omega$

2-51
90

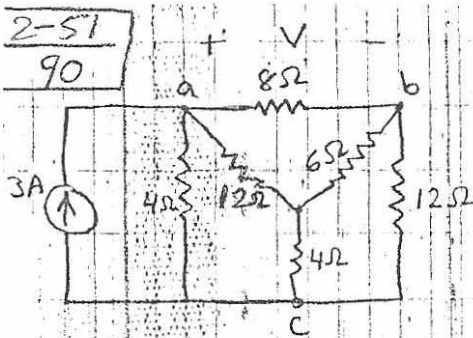

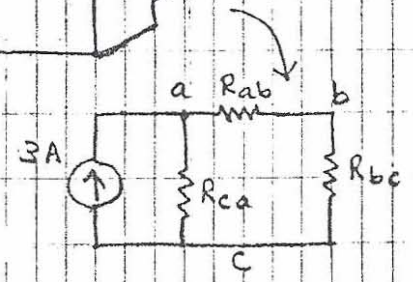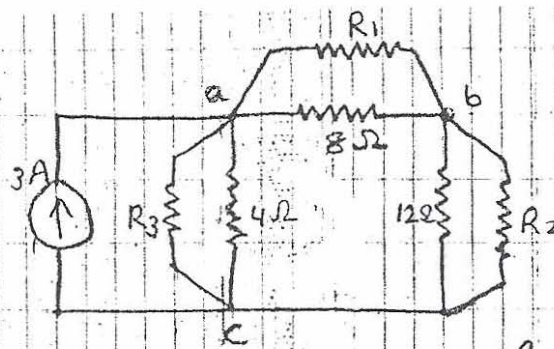convert
 $Y_{abk} \rightarrow \Delta_{abc}$




$$R_1 = \frac{(6 \times 12) + (12 \times 4) + (4 \times 6)}{4} = \frac{144}{4} = 36 \Omega$$

$$R_2 = \frac{144}{12} = 12 \Omega, \quad R_3 = \frac{144}{6} = 24 \Omega$$

$$R_{ab} = \frac{8 \times 36}{8 + 36} = 6.54 \Omega, \quad R_{bc} = \frac{12 \times 12}{12 + 12} = 6 \Omega, \quad R_{ca} = \frac{4 \times 24}{4 + 24} = 3.429 \Omega$$

Convert current source: $\therefore V = \frac{3 R_{ca}}{R_{ca} + R_{ab} + R_{bc}} \times R_{ab}$
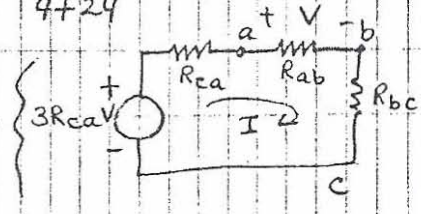
$$\therefore V = \frac{3 \times 3.429 \times 6.54}{15.974} = 4.215 \text{ V}$$




To find V_A by Node Voltage Method:

$$\left(\frac{1}{28} + \frac{1}{14} + \frac{1}{5}\right) V_A - \frac{1}{5} V_B = 28 \quad (1)$$

$$-\frac{1}{5} V_A + \left(\frac{1}{5} + \frac{1}{20} + \frac{1}{10}\right) V_B = 1.4 I_1 \quad (2)$$

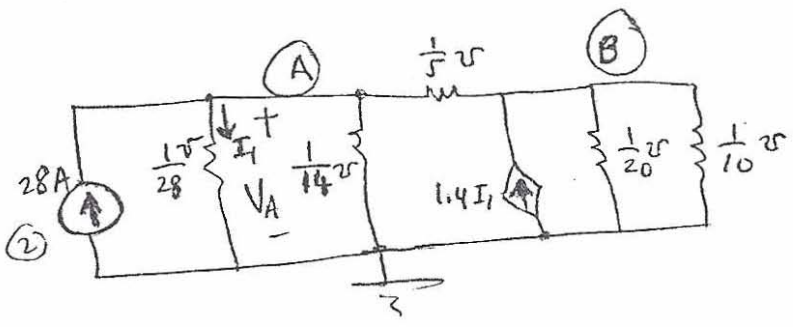Constraint Eq. $\therefore I_1 = \frac{V_A}{28} \quad (3)$



$$(3) \text{ in } (2) \rightarrow \left(\frac{1.4}{28} + \frac{1}{5}\right) V_A = 0.35 V_B \Rightarrow V_B = 0.7143 V_A \quad (4)$$


$$(4) \text{ in } (1) \rightarrow (0.307 - 0.2 \times 0.7143) V_A = 28$$

$$\therefore V_A = 170.435 \text{ Volts.}$$

To find I_1 & I_2 by Mesh Analysis:

$$(M_1) \quad (25+10+5)I_1 - 5I_2 = 75-30 \quad (1)$$
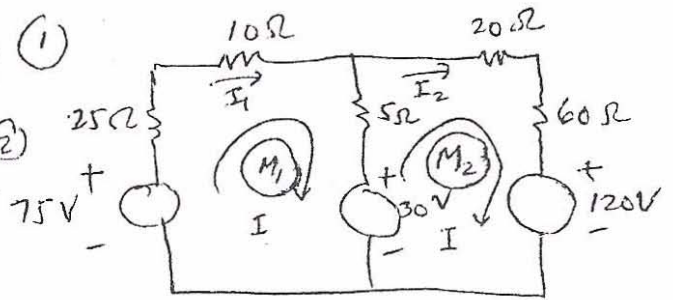
$$(M_2) \quad -5I_1 + (5+20+60)I_2 = 30-120 \quad (2)$$



from (1) $I_2 = 8I_1 - 9$


in (2) $-I_1 + 17(8I_1 - 9) = -18 \Rightarrow I_1 = \frac{153-18}{136-1} = 1 \text{ A}$

in (1) $\Rightarrow I_2 = 8 - 9 = -1 \text{ A}$

(a) To find Thevenin Equivalent at ab:


$$I = \frac{24-4}{8+10+2} = 1 \text{ A}$$

$$V_{oc} = 10I = 10 \text{ V}$$

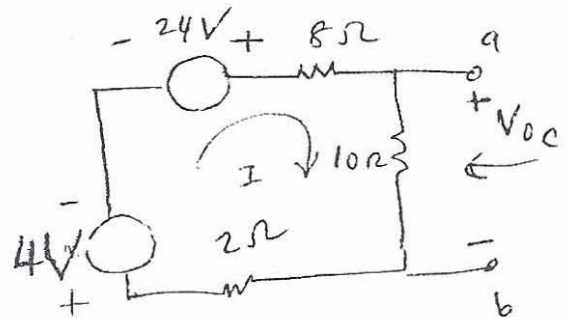


$$I_{sc} = \frac{24-4}{8+2} = 2 \text{ A}$$
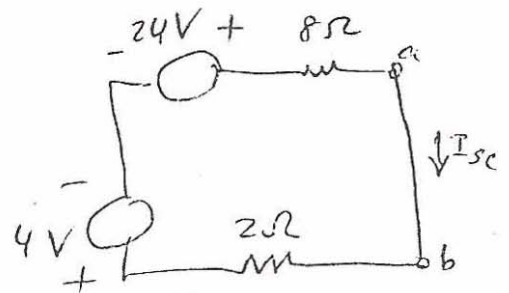
$$\therefore R_0 = \frac{V_{oc}}{I_{sc}} = 5 \Omega$$



(b) For R to receive the greatest power, it has to equal to R_0

$$\Rightarrow R = R_0 = 5 \Omega$$

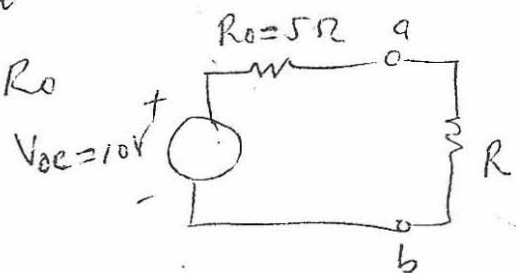

$$(c) P_{max} = I^2 R_0 = \left(\frac{10}{2R_0}\right)^2 R_0 = 5 \text{ W}$$

(a) Thevenin Equivalent at ab:

Open ckt @ ab — A.

convert current source to voltage.

KVL

$$I(2+4+6) = 130 - 10 - 228$$

$$\therefore I = \frac{-108}{12} = -9 \text{ A}$$

$$\therefore V_{oc} = 6I + 228 = 174 \text{ V}$$

Now, find I_{sc} using Mesh analysis.

$$(M_1) (2+4+6)I_1 - 6I_2 = 130 - 228 - 10 \quad (1)$$

$$(M_2) -6I_1 + 6I_2 = 228 \Rightarrow I_1 = I_2 - 38 \quad (2)$$

in (1)

$$12(I_2 - 38) - 6I_2 = -108 \Rightarrow I_{sc} = I_2 = 58 \text{ A}$$




$$R_0 = \frac{V_{oc}}{I_{sc}} = \frac{174}{58.0} = 3 \Omega.$$

(b) R of max. power transfer:

For Max. Power, $R = R_0 = 3 \Omega$

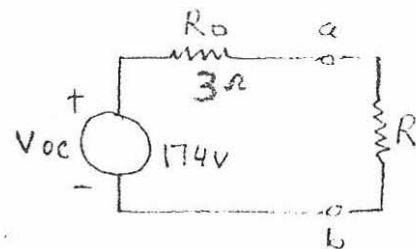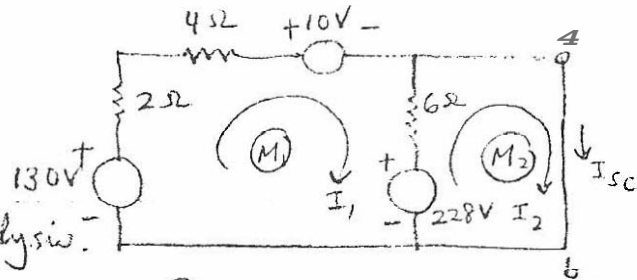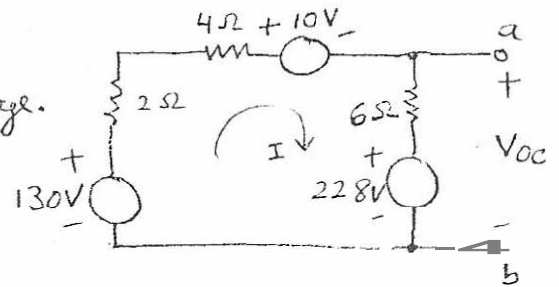
(c) Maximum output power:

$$P_{max} = \left(\frac{V_{oc}}{2R_0}\right)^2 (R_0) = \frac{(174)^2}{4 \times 3.0} = 2.523 \text{ kW}$$



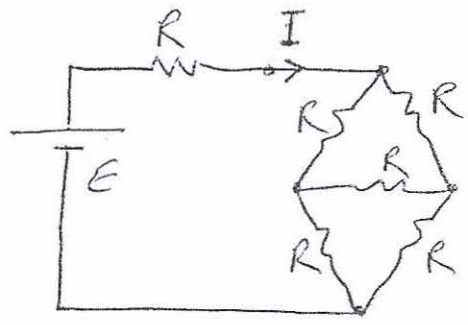
#


To find I of the network shown by simplification we change one of the Δ 's (upper or lower) to Y . All values of resistors in Y are equal
 $= \frac{R \cdot R}{R+R+R} = \frac{R}{3}$


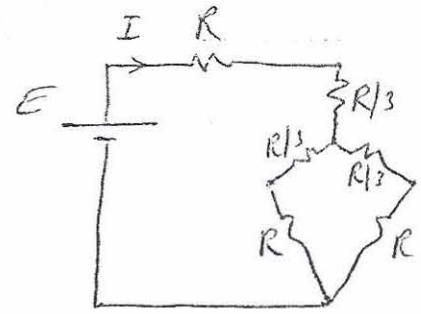
$$\begin{aligned} \therefore I &= \frac{E}{R + \frac{R}{3} + \left(\frac{R}{3} + \frac{R}{3}\right) \parallel \left(\frac{R}{3} + \frac{R}{3}\right)} \\ &= \frac{E}{\frac{4R}{3} + \frac{1}{2} \times \frac{4R}{3}} \\ &= \frac{3E}{4R+2R} = \frac{3E}{6R} = \frac{E}{2R} \end{aligned}$$



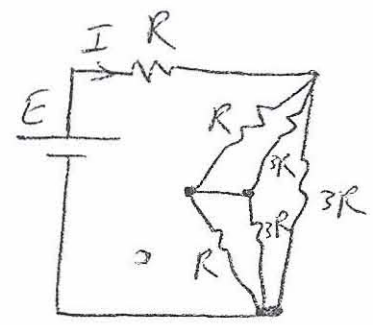OR Change one of the Y 's (right or left) to Δ . All values of resistors in Δ are equal $= \frac{R \cdot R + R \cdot R + R \cdot R}{R}$
 $= \frac{3R^2}{R} = 3R$



$$\begin{aligned} \therefore I &= \frac{E}{R + \left[\left(R \parallel 3R \right) + \left(R \parallel 3R \right) \right] \parallel 3R} \\ &= \frac{E}{R + \left[\frac{R \cdot 3R}{R+3R} \times 2 \right] \parallel 3R} = \frac{E}{R + \left(\frac{6R^2}{4R} \right) \parallel 3R} \\ &= \frac{E}{R + 1.5R \parallel 3R} = \frac{E}{R + \frac{1.5R \times 3R}{1.5R+3R}} = \frac{E}{R + \frac{4.5R}{4.5R}} = \frac{E}{2R} \end{aligned}$$

B1
908

(a) $2.24 \angle 26.4^\circ = 2.24 (\cos 26.4^\circ + j \sin 26.4^\circ) = 2.01 + j1.00$
 $10 e^{j30^\circ} = 10 (\cos 30^\circ + j \sin 30^\circ) = 8.66 + j5.00$
 $15 \angle -72^\circ = 15 (\cos 72^\circ - j \sin 72^\circ) = 4.64 - j14.27$
 $20 e^{-j126.9^\circ} = 20 (\cos 126.9^\circ - j \sin 126.9^\circ) = -(12 + j16)$
 $0.3 \angle 140^\circ = 0.3 (\cos 140^\circ + j \sin 140^\circ) = -0.230 + j0.193$

(b) $3 - j4 = \sqrt{(3)^2 + (4)^2} \angle \tan^{-1} \frac{-4}{3} = 5 \angle -53.1^\circ = 5 e^{-j53.1^\circ}$
 $-15 + j5 = 15.81 \angle 180^\circ - 18.43^\circ = 15.81 \angle 161.57^\circ = 15.81 e^{j161.57^\circ}$
 $10 + j20 = 22.36 \angle 63.43^\circ = 22.36 e^{j63.43^\circ}$
 $-10 - j24 = 26 \angle 180^\circ + 67.38^\circ = 26 \angle 247.38^\circ = 26 e^{j247.38^\circ}$
 $0.25 + j0.433 = 0.5 \angle 60^\circ = 0.5 e^{j60^\circ}$

B-2
908

$A = 8 - j6 = 10 \angle -36.9^\circ = 10 e^{-j36.9^\circ}$
 $B = 20 + j10 = 22.36 \angle 26.57^\circ = 22.36 e^{j26.57^\circ}$
 $C = 0.866 - j0.5 = 1 \angle -30^\circ = 1 e^{-j30^\circ}$

(a) $A - B + C = (8 - j6) - (20 + j10) + (0.866 - j0.5) = -11.134 - j16.5$

(b) $BC - A = (22.36 \angle 26.57^\circ)(1 \angle -30^\circ) - A = 22.36 \angle -3.44^\circ - A$
 $= (22.32 - j1.34) - (8 - j6) = 14.32 + j4.66$

(c) $(ABC)^2 = [(10 e^{-j36.9^\circ})(22.36 e^{j26.57^\circ})(1 e^{-j30^\circ})]^2$
 $= (223.6 \angle -40.31^\circ)^2 = 49997.8 \angle -80.61^\circ$

(d) $AC/B - BC/A = \frac{(10 \angle -36.9^\circ)(1 \angle -30^\circ)}{22.36 \angle 26.57^\circ} - \frac{(22.36 \angle 26.57^\circ)(1 \angle -30^\circ)}{10 \angle -36.9^\circ}$
 $= 0.45 \angle -93.44^\circ - 2.236 \angle 33.43^\circ$
 $= [-0.45 (\cos 86.56^\circ + j \sin 86.56^\circ)] - [1.87 + j1.23]$
 $= (-0.03 - 1.87) - j(0.45 + 1.23) = -(1.9 + j1.68)$

43

43

B3
908

$$A = 10 e^{-j45^\circ} = 7.07 - j7.07 = 10 \angle -45^\circ$$

$$B = -4 + j2 = 4.47 \angle 180 - 26.57^\circ = 4.47 \angle 153.43^\circ = 4.47 e^{j153.43^\circ}$$

$$C = 12 \angle 30^\circ = 12 e^{j30^\circ} = 10.39 + j6$$

$$\begin{aligned} \text{(a)} \quad AB - C/B &= (10 \angle -45^\circ \times 4.47 \angle 153.43^\circ) - \frac{12 \angle 30^\circ}{4.47 \angle 153.43^\circ} = \\ &= 44.7 \angle 108.43^\circ - 2.68 \angle -123.43^\circ \\ &= 44.7 (-\cos 71.57^\circ + j \sin 71.57^\circ) - 2.68 (-\cos 56.57^\circ - j \sin 56.57^\circ) \\ &= -12.66 + j44.67 \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad C + A/(B-C) &= (10.39 + j6) + \frac{10 \angle -45^\circ}{-14.39 - j4} \\ &= (10.39 + j6) - \frac{10 \angle -45^\circ}{14.94 \angle 155.3^\circ} = (10.39 + j6) - 0.67 e^{-j60.5^\circ} \\ &= 10.06 + j6.58 \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad BC &= 53.67 \angle 183.43^\circ = 53.64 (-\cos 3.43^\circ - j \sin 3.43^\circ) \\ &= -53.57 - j3.22 \end{aligned}$$

$$AB = 44.7 \angle 108.43^\circ = -14.14 + j42.43$$

$$\begin{aligned} A + BC &= (7.07 - j7.07) + (-53.57 - j3.22) = -46.50 - j10.29 \\ &= 47.62 \angle 112.47^\circ \end{aligned}$$

$$\begin{aligned} C - AB &= (10.39 + j6) - (-14.14 + j42.43) = 24.53 - j36.43 \\ &= 43.92 \angle -56.04^\circ \end{aligned}$$

$$\therefore \frac{A + BC}{C - AB} = \frac{47.62 \angle 112.47^\circ}{43.92 \angle -56.04^\circ} = 1.08 \angle 68.51^\circ = 1.08 \angle 248.51^\circ$$

$$\begin{aligned} \text{(d)} \quad A - B &= 11.07 - j9.07 = 14.31 \angle -39.33^\circ \\ \therefore \sqrt{C(A-B)} &= \sqrt{171.75 \angle -9.33^\circ} = 13.11 \angle -4.66^\circ \end{aligned}$$


3-1
145

$$s = -1/\text{sec}$$

(a) $Z_L = sL = -2 \Omega$

(b) $Y_L = \frac{1}{Z_L} = \frac{1}{sL} = \frac{1}{-2} = -0.5 \text{ S}$

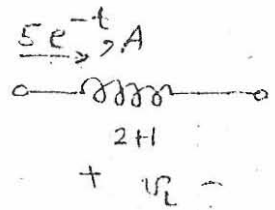(c) $v_L = L \frac{di}{dt} = -10e^{-t} \text{ V}$




3-3
145


$$v = 10e^{-2t} \text{ V}, V = 10 \text{ volt}$$

$$\therefore s = -2/\text{sec}$$
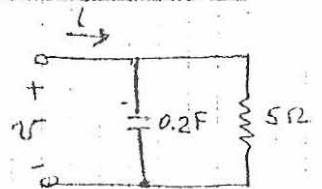
$$G = \frac{1}{R} = 0.2 \text{ S}, Y_C = sC = -0.4 \text{ S}$$



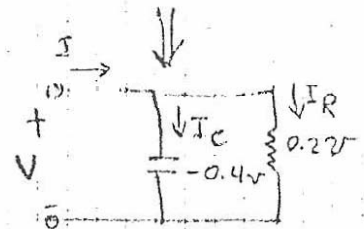(a) $I_R = GV = 0.2 \times 10 = 2 \text{ A} \Rightarrow i_R = 2e^{-2t} \text{ A}$
 $I_C = Y_C V = -0.4 \times 10 = -4 \text{ A} \Rightarrow i_C = -4e^{-2t} \text{ A}$



(b) $I = I_R + I_C = -2 \Rightarrow i = -2e^{-2t} \text{ A}$

(c) $s = Y_C + G = 0.2 - 0.4 = -0.2 \text{ S}$

3-4
145

$$i = 3e^{-20t} \text{ A}, I = 3 \text{ A}, s = -20/\text{s}$$


$$Z_L = sL = -2 \Omega$$

(a) $V_R = IR = 30 \text{ V}, v_R = 30e^{-20t} \text{ V}$

$V_L = Z_L I = -6 \text{ V}, v_L = -6e^{-20t} \text{ V}$

(b) $V = V_R + V_L = 30 - 6 = 24 \text{ V}, v = 24e^{-20t} \text{ V}$

(c) $Z = R + sL = 10 - 2 = 8 \Omega$

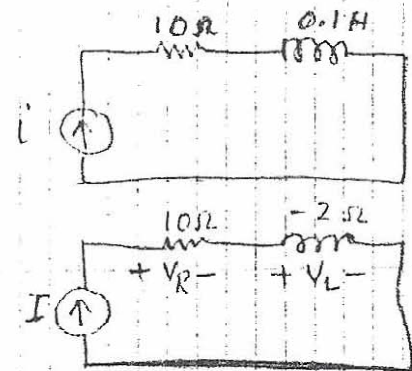


3-5
145

$i = I e^{st}$ A
 $z_c = \frac{1}{sC} \Omega$, $z_L = sL \Omega$

(a) ∴ Network is as shown in Fig. (a).

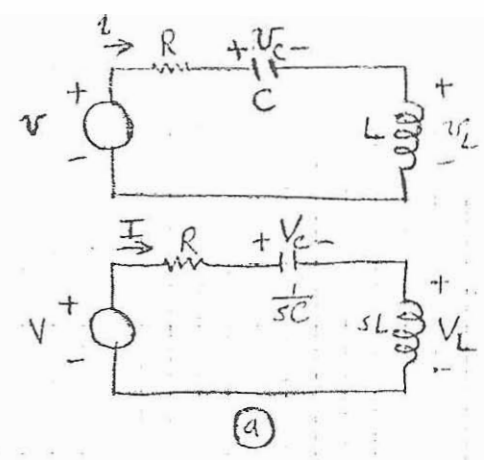(b) KVL $\rightarrow V = (R + \frac{1}{sC} + sL) I$

$\therefore v(t) = V e^{st} = (R + sL + \frac{1}{sC}) I e^{st}$, V



3-6
146

$R = 2 \Omega =$ Transformed impedance
 $C = .5 F \therefore \frac{1}{sC} = \frac{1}{.5s} = \frac{2}{s} \Omega$
 $L = 3 H \therefore sL = 3s \Omega$

∴ Network becomes as shown:

$\therefore i_L(t) = 12 e^{-t/2}$, Ap

$\therefore s = -\frac{1}{2}$ rad/sec

$\therefore I_L = 12$ Ap

$\therefore V = 12 * 3s = 36 * -\frac{1}{2} = -18$ Volts


$\therefore v(t) = -18 e^{-t/2}$, volts

$\therefore I_C = \frac{V}{\frac{2}{s}} = \frac{-18}{2(-\frac{1}{2})} = \frac{-18 * (-\frac{1}{2})}{2} = \frac{9}{2}$ Ap

$\therefore I_R = \frac{V}{R} = \frac{-18}{2} = -9$ Ap

$\therefore I = I_R + I_C + I_L = -9 + \frac{9}{2} + 12 = \frac{-18 + 9 + 24}{2} = \frac{15}{2} = 7.5$ A

$\therefore i(t) = 7.5 e^{-t/2}$, Ap.

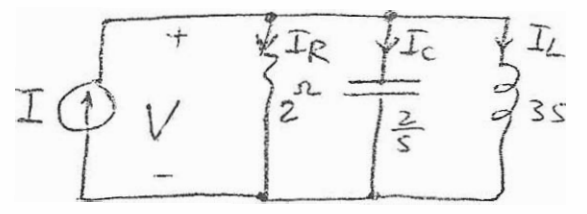


3-7
146

$$R = 4\Omega, C = 1F, L = 2H, i_R = 3e^{-t} A$$

$$s = -1/\text{Sec}$$
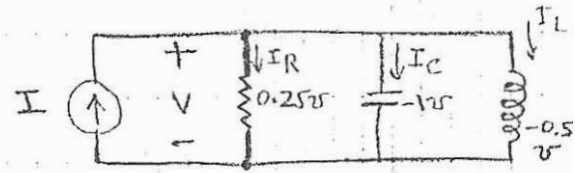
$$Y_C = sC = -1s, Y_L = \frac{1}{sL} = -0.5s$$



$$V = R I_R = 4 \times 3 = 12V$$

$$I_C = Y_C V = -12 A, I_L = Y_L V = -6A$$

$$\text{KCL} \rightarrow I = I_R + I_C + I_L = 3 - 12 - 6 = -15A \Rightarrow \boxed{i = -15e^{-t} A}$$

3-10
146


$$i(t) = 12e^{-3t} A \rightarrow s = -3/\text{sec} \Delta I = 12A$$

$$G = 6s, Y_C = sC = -1s, Y_L = \frac{1}{sL} = -2s$$

$$\text{KCL} \rightarrow I = 12 = V(G + Y_C + Y_L) = 3 \times V$$

$$\therefore V = 4 \text{ volts}$$
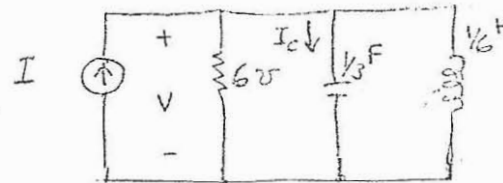
$$\therefore I_C = Y_C V = -4 A \Rightarrow \underline{i_C(t) = -4e^{-3t} A}$$



3-13
147

$$i(t) = 10^{-3} \cos(3.14 \times 10^5 t - 30^\circ) = 10^{-3} \cos(3.14 \times 10^5 t - \frac{\pi}{6}), A$$

(a) $\omega = 2\pi f = 3.14 \times 10^5 \Rightarrow f = 50 \text{ kHz}$

(b) $i \rightarrow I_{\max}$ when $3.14 \times 10^5 t_1 - \frac{\pi}{6} = 0 \Rightarrow \boxed{t_1 = 1.67 \mu\text{sec}}$

(c) $i \rightarrow I_{\min}$ when $3.14 \times 10^5 t_2 - \frac{\pi}{6} = \pi \Rightarrow \boxed{t_2 = 11.67 \mu\text{sec}}$

(d) Time between max. & min = $\frac{T}{2} = t_2 - t_1 = 10.0 \mu\text{sec}$

\therefore Time between two consecutive maxima = T

$$\therefore \boxed{T = 2 \times 10 = 20 \mu\text{sec}}$$

3-14
147

$$f = 60 \text{ Hz}, V_m = 169 \text{ V}, v = 102 \text{ V at } t = 0$$

$$\omega = 2\pi f = 376.99 \text{ rad/sec.}$$

(a) Assume, $v = V_m \cos(\omega t + \theta) = 169 \cos(376.99t + \theta)$

(i) $t = 0, v = 102 = 169 \cos \theta \Rightarrow \theta = 52.88^\circ = 0.92 \text{ rad.}$

$$\therefore v = 169 \cos(376.99t + 52.88^\circ) \text{ V}$$

(b) $v \rightarrow 0 \Rightarrow 376.99t_1 + 0.92 = \frac{\pi}{2} \Rightarrow t_1 = 1.72 \times 10^{-3} \text{ sec}$

(c) Notice the period $T = \frac{1}{f} = \frac{1}{60} \text{ sec} = 1.6 \times 10^{-2} \text{ sec} = 16.6 \text{ msec}$

(i) $t_2 = \frac{1}{30} \text{ sec} = 2T$ from the time origin, the voltage


will have the same value as it has at the origin, i.e.,
at $t = 0 \Rightarrow v(2T) = v(0) = 102 \text{ V.}$

3-17
147

$$R = \frac{1}{6} \Omega = \text{impedance}$$

$$C = \frac{1}{3} F \quad \& \quad L = \frac{1}{6} H$$

$$i(t) = 12 \cos(3t + 45^\circ), A$$

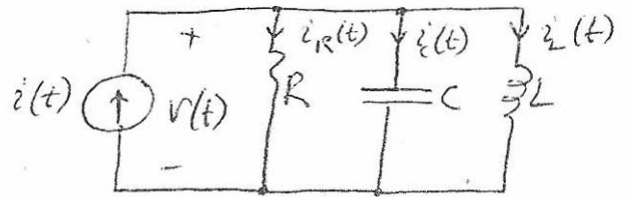


$$\therefore \omega = j\omega = j3 \text{ rad/sec}$$

$$\& \quad I = 12 A \angle 45^\circ$$

$$\text{impedance of } C = \frac{1}{\frac{1}{3} \times j3} = \frac{1}{j} = -j \Omega$$

$$\therefore \quad \text{impedance of } L = \frac{1}{6} \times j3 = j \cdot 5 \Omega$$

Transformed network is as shown.

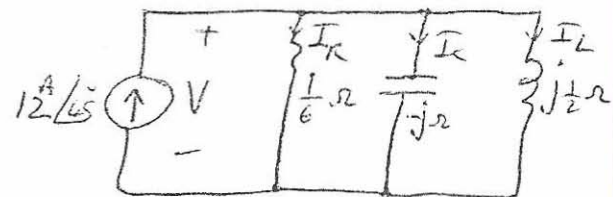

$$\begin{aligned} \therefore I_C &= 12 \angle 45^\circ * \frac{(\frac{1}{6} \parallel j\frac{1}{2})}{(\frac{1}{6} \parallel j\frac{1}{2}) + (-j)} = 12 \angle 45^\circ * \frac{\frac{j/12}{1/6 + j/12}}{\frac{j/12}{1/6 + j/12} - j} \\ &= 12 \angle 45^\circ * \frac{j/12}{j/12 - j(\frac{1}{6} + j/2)} = 12 \angle 45^\circ * \frac{j}{j - 2j + 6} = \frac{12 \angle 45^\circ \times \angle 90^\circ}{6 - j} \\ &= \frac{12 \angle 135^\circ}{\sqrt{37} \angle -9.46^\circ} = 1.9728 \angle 144.46^\circ, \text{ Amp} \end{aligned}$$

$$\therefore i_C(t) = 1.9728 \cos(3t + 144.46^\circ), \text{ Amp}$$

OR: Total impedance = $\frac{1}{6} \parallel -j \parallel j \cdot 5 = \frac{1}{\left[\frac{1}{1/6} + \frac{1}{-j} + \frac{1}{j \cdot 5}\right]} = \frac{1}{\left[6 + j - j2\right]} = \frac{1}{6 - j} = Z, \Omega$

$$\therefore V = I Z = 12 \angle 45^\circ * \frac{1}{6 - j} = \frac{12 \angle 45^\circ}{\sqrt{37} \angle -9.46^\circ} = 1.9728 \angle 54.46^\circ, V$$


$$\therefore I_C = \frac{V}{-j} = \frac{1.9728 \angle 54.46^\circ}{1 \angle -90^\circ} = 1.9728 \angle 144.46^\circ, \text{ Amp}$$

$$\therefore i_C(t) = 1.9728 \cos(3t + 144.46^\circ), \text{ Amp}$$

3-18
147

$R = 6\Omega, C = \frac{1}{6}F, L = \frac{1}{3}H; v_L(t) = ?$

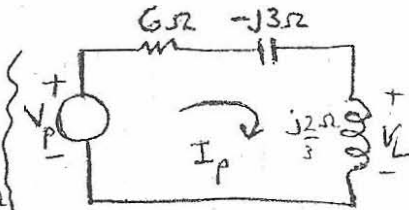
(a) $v(t) = 10 \cos(2t - 30^\circ) \equiv 10e^{-j30^\circ} \text{ V}$ $\phi s = j\omega = j2$
 $Z_C = \frac{1}{j\omega C} = \frac{-j}{2/6} = -j3\Omega$ $\phi Z_L = j\omega L = j2/3 = j\frac{2}{3}\Omega$



$$I_P = \frac{V_P}{Z} = \frac{10 \angle -30^\circ}{6 - j3 + j\frac{2}{3}} = \frac{10 \angle -30^\circ}{6 - j2.333} = \frac{10 \angle -30^\circ}{6.4377 \angle -21.25^\circ} = 1.553 \angle -8.75^\circ \text{ A}$$

$$V_{L_P} = I_P Z_L = (1.553 \angle -8.75^\circ)(0.667 \angle 90^\circ) = 1.0356 \angle 81.25^\circ \text{ V}$$

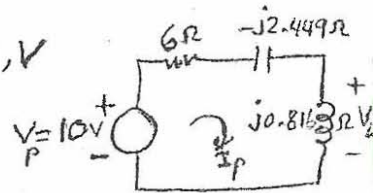$\therefore V_{L_P} \equiv v_L(t) = 1.0356 \cos(2t + 81.25^\circ) \text{ V}$



(b) $v(t) = 10 \cos \sqrt{6}t \equiv 10e^{j0} \text{ Volt} = V_P \phi s = j\sqrt{6}$

$$I_P = \frac{V_P}{Z} = \frac{10 \angle 0^\circ}{6 + j(0.816 - 2.449)} = \frac{10}{6.218 \angle -15.23^\circ} = 1.61 \angle 15.23^\circ \text{ A}$$

$$V_{L_P} = I_P Z_L = (1.61 \angle 15.23^\circ)(0.816 \angle 90^\circ) = 1.313 \angle 105.23^\circ \text{ V}$$

$\therefore V_{L_P} \equiv v_L(t) = 1.313 \cos(\sqrt{6}t + 105.23^\circ) \text{ Volt}$

3-19
147

$i = 10^{-2} \cos 5 \times 10^3 t \text{ A} \Rightarrow I = \frac{10^{-2}}{\sqrt{2}} \angle 0^\circ \text{ A}$

$\omega = 5 \times 10^3 \text{ rad/sec}$

(a) $Z_L = j\omega L = j5 \times 10^3 \times 10 \times 10^{-3} = j50 \Omega$

$Z = 50 + j50 = 70.71 \angle 45^\circ \Omega$


(b) $V = ZI = 70.71 \angle 45^\circ \times \frac{10^{-2}}{\sqrt{2}} = 0.5 \angle 45^\circ \text{ V}$

$\therefore v(t) = 0.7071 \cos(5 \times 10^3 t + 45^\circ) \text{ V}$

(c) $V_R = IR = 50 \times \frac{10^{-2}}{\sqrt{2}} \angle 0^\circ = 0.3536 \text{ V}$

$V_L = IZ_L = (50 \angle 90^\circ) \left(\frac{10^{-2}}{\sqrt{2}} \right) = 0.3536 \angle 90^\circ \text{ V}$


$V = V_R + V_L$

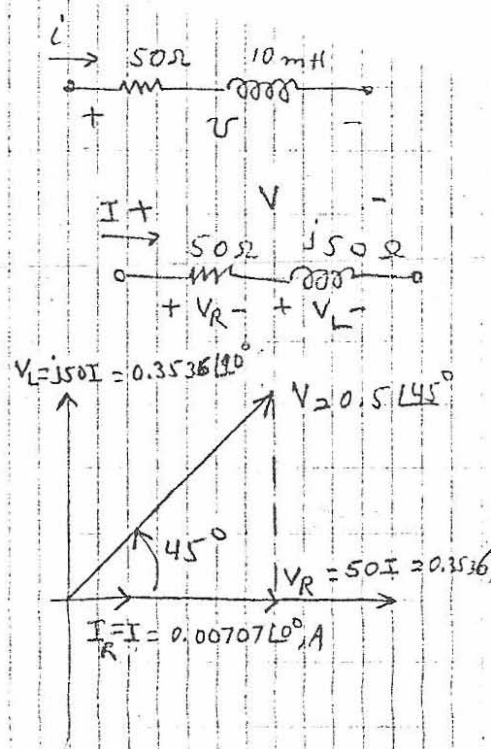

3-21
148

$$v = V_m \quad 0 \leq t \leq \frac{T}{4}$$

$$v = 0 \quad \frac{T}{4} < t \leq T$$

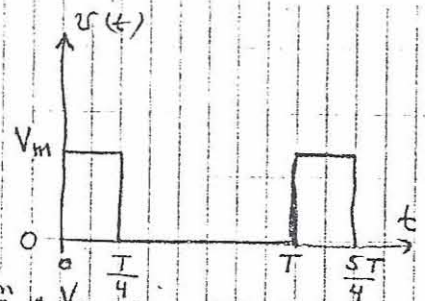


$$V_{rms} = \sqrt{\frac{1}{T} \int_0^{T/4} V_m^2 dt} = V_m \sqrt{\frac{1}{T} [t]_0^{T/4}} = \frac{V_m}{2} \sqrt{\frac{T}{4}} = \frac{V_m}{2} \sqrt{\frac{T}{4}}$$

$$V_{av} = \frac{1}{T} \int_0^{T/4} V_m dt = \frac{V_m}{T} [t]_0^{T/4} = \frac{V_m}{4} \sqrt{\frac{T}{4}}$$

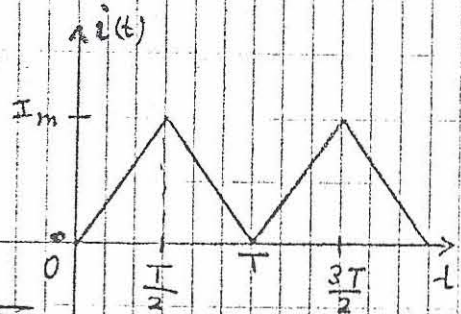3-24
148

$$i(t) = \frac{I_m}{T/2} t \quad 0 \leq t \leq \frac{T}{2}$$

$$i(t) = -\frac{I_m}{T/2} t + 2I_m \quad \frac{T}{2} < t \leq T$$



$$I_{rms} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} \left(\frac{I_m}{T/2} t \right)^2 dt + \int_{T/2}^T \left(-\frac{I_m}{T/2} t + 2I_m \right)^2 dt \right]}$$

$$= \sqrt{\frac{1}{T} \left\{ \left(\frac{I_m^2}{T^2/4} \right) \left[\frac{t^3}{3} \right]_0^{T/2} + \left(\frac{I_m^2}{T^2/4} \right) \left[\frac{t^3}{3} \right]_{T/2}^T - \left(\frac{4I_m^2}{T/2} \right) \left[\frac{t^2}{2} \right]_{T/2}^T + (4I_m^2) \left[t \right]_{T/2}^T \right\}}$$

$$= 2I_m \sqrt{\frac{1}{T} \left\{ \frac{1}{T^2} \left[\frac{T^3/8}{3} \right] + \frac{1}{T^2} \left[\frac{T^3 - T^3/8}{3} \right] - \frac{2}{T} \left[\frac{T^2 - T^2/4}{2} \right] + \left[T - \frac{T}{2} \right] \right\}}$$

$$= 2I_m \sqrt{\frac{1}{12}} \Rightarrow I_{rms} = \frac{I_m}{\sqrt{3}}$$

$$I_{av} = \frac{1}{T} \left\{ \int_0^{T/2} \left(\frac{I_m t}{T/2} \right) dt + \int_{T/2}^T \left(-\frac{I_m t}{T/2} + 2I_m \right) dt \right\}$$


$$= \frac{2I_m}{T} \left\{ \frac{1}{T} \left[\frac{t^2}{2} \right]_0^{T/2} - \frac{1}{T} \left[\frac{t^2}{2} \right]_{T/2}^T + \left[t \right]_{T/2}^T \right\} = 2I_m \left\{ \frac{1}{4} \right\}$$

$$\therefore I_{av} = \frac{I_m}{2}$$

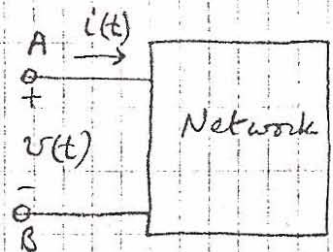3-25
148

$$v(t) = 100\sqrt{2} \cos 10^3 t, \text{ V}$$

$$i(t) = 10\sqrt{2} \cos(10^3 t + 60^\circ), \text{ A}$$



(a) $V = 100 \angle 0^\circ, \text{ V}$ & $I = 10 \angle 60^\circ, \text{ A}$

$\therefore P = VI \cos \theta = 100 \times 10 \cos 60 = 500 \text{ W}$

$\nabla Q = VI \sin \theta = 100 \times 10 \sin 60 = 866 \text{ var}$

$\nabla VA = 100 \times 10 = 1000 \text{ VA} = 1 \text{ KVA}$

(b) $Z = \frac{V}{I} = \frac{100 \angle 0}{10 \angle 60} = 10 \angle -60 = 5 - j8.66, \Omega$

(c) X is -ve \Rightarrow Capacitive $\therefore -jX_c = -j8.66 \Omega$

$\therefore X_c = \frac{1}{\omega C} = 8.66, \omega = 10^3 \text{ rad/s}$

$\therefore C = \frac{1}{8.66 \times 10^3} = 115.47 \mu\text{F}$

3-27
149

$$v(t) = 220\sqrt{2} \cos(377t - 15^\circ) \text{ V}; i(t) = 10 \cos(377t - 60^\circ) \text{ A}$$

$\therefore V = 220 \angle -15^\circ \text{ V}$ & $I = \frac{10}{\sqrt{2}} \angle -60^\circ \text{ A}$ & $\omega = 377 \text{ rad/s}$

(a) $P = VI \cos(-15^\circ - (-60^\circ)) = \frac{220 \times 10}{\sqrt{2}} \cos(45^\circ) = 1100 \text{ W} = 1.1 \text{ KW}$

$Q = VI \sin 45^\circ = 1100 \text{ var} = 1.1 \text{ KVar}$

$VA = VI = \frac{220 \times 10}{\sqrt{2}} = 1555.6 \text{ VA} = 1.5 \text{ KVA}$

(b) $Z = R + jX = \frac{V}{I} = \frac{220 \angle -15^\circ}{(10/\sqrt{2}) \angle -60^\circ} = 31.1 \angle 45^\circ = 22 + j22 \Omega$

(c) Since X is +ve \Rightarrow It is inductive ckt. $\therefore jX_L = j22$

$\therefore X = X_L = \omega L = 377L = 22 \Rightarrow L = 58.4 \text{ mH}$

$$\frac{3-28}{149} \quad v(t) = 4 \cos 3t + 3 \sin 3t, V$$

$$i(t) = 3 \cos 3t - 4 \sin 3t, A$$


$$\therefore \sin 3t = \cos(3t - 90^\circ)$$

$$\therefore v(t) = 4 \cos 3t + 3 \cos(3t - 90^\circ) = (4 + 3 \angle -90^\circ) \cos 3t, V$$

$$\therefore V_{rms} = \frac{4 + 3 \angle -90^\circ}{\sqrt{2}} = \frac{4 - j3}{\sqrt{2}} = \frac{5 \angle -36.87^\circ}{\sqrt{2}} = 3.5355 \angle -36.87^\circ, V$$

$$i(t) = 3 \cos 3t - 4 \cos(3t - 90^\circ) = (3 - 4 \angle -90^\circ) \cos 3t, A$$
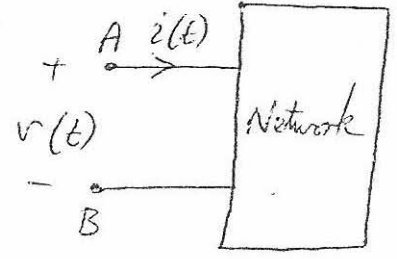
$$\therefore I_{rms} = \frac{3 - 4 \angle -90^\circ}{\sqrt{2}} = \frac{3 + j4}{\sqrt{2}} = \frac{5 \angle 53.13^\circ}{\sqrt{2}} = 3.5355 \angle 53.13^\circ, A$$



$$a) \therefore P_{avr} = I_{rms} \cdot V_{rms} \cdot \cos \angle_{I_{rms}}^{V_{rms}} = 3.5355 * 3.5355 * \cos(-36.87^\circ - 53.13^\circ) = 12.5 \cos(-90^\circ) = 0 \text{ Watt.}$$

$$Q = I_{rms} \cdot V_{rms} \cdot \sin \angle_{I_{rms}}^{V_{rms}} = 12.5 \sin(-90^\circ) = -12.5 \text{ Vars} = 12.5 \text{ Cap. Vars}$$

$$S = I_{rms} \cdot V_{rms} = 12.5 \text{ VA.}$$

$$b) Z_{AB} = \frac{V_{rms}}{I_{rms}} = \frac{3.5355 \angle -36.87^\circ}{3.5355 \angle 53.13^\circ} = 1 \angle -90^\circ, \quad \omega = -j\omega = R - jX_c$$

$\therefore R = 0 \Omega$, the equivalent resistance between AB


$X_c = 1 \Omega$, " " capacitive reactance between AB.

$$c) \therefore \omega = 3 \text{ rad/sec} \quad \text{and} \quad X_{c\omega} = \frac{1}{\omega C}$$

$$\therefore C = \frac{1}{\omega X_c} = \frac{1}{3 * 1} = \frac{1}{3} \text{ F, the capacitance realizing } X_c \text{ at } 3 \text{ rad/sec.}$$

$$\# \quad I_{avr} = \frac{1}{4a} \left[I * a + \frac{I * 2a}{2} + 0 \right] = \frac{2Ia}{4a} = I/2$$
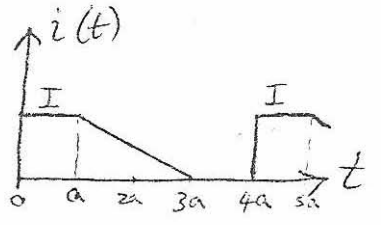
$$I_{rms} = \sqrt{\frac{1}{4a} \left[I^2 a + \frac{I^2 * 2a}{3} + 0 \right]} = \sqrt{\frac{3I^2 a + 2I^2 a}{12a}} = \sqrt{\frac{5}{12}} \cdot I = 0.6455 I$$



3-29
149

$$v = 16\sqrt{2} \cos t \text{ V}$$

$$\omega = 1 \text{ rad/sec}$$


$$\textcircled{a} \textcircled{M_1} (3-j)I_1 - 2I_2 = 16\sqrt{2} \textcircled{1}$$

$$\textcircled{M_2} -2I_1 + (5-j)I_2 = 0 \textcircled{2}$$

$$\textcircled{2} \rightarrow I_1 = (2.5 - j0.5)I_2 \textcircled{3}$$

$$\textcircled{3} \text{ in } \textcircled{1} \rightarrow [(3-j)(2.5 - j0.5) - 2]I_2 = 16$$
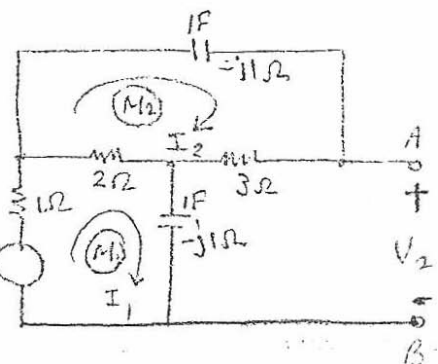
$$v = 16\sqrt{2} \angle 0^\circ \text{ V}$$



$$\therefore I_2 = \frac{16}{5-j4} = \frac{16}{6.4 \angle -38.7^\circ} = 2.5 \angle 38.7^\circ = 1.95 + j1.56 \text{ A}$$

$$I_1 = (2.5 \angle -11.3^\circ)(2.5 \angle 38.7^\circ) = 6.37 \angle 27.3^\circ = 5.66 + j2.93 \text{ A}$$


$$V_2 = 3I_2 - jI_1 = 8.78 - j0.98 = 8.83 \angle -6.34^\circ \text{ V}$$

$$v_2 = 8.83\sqrt{2} \cos(t - 6.34^\circ) \text{ V} = 12.5 \cos(t - 6.34^\circ) \text{ V}$$

$\frac{3-30}{150}$

$$V_2 = (4-j1)(2 \angle -30^\circ) = 8.94 \angle -56.57^\circ \text{ V}$$

$$= 4.93 - j7.46 \text{ V}$$

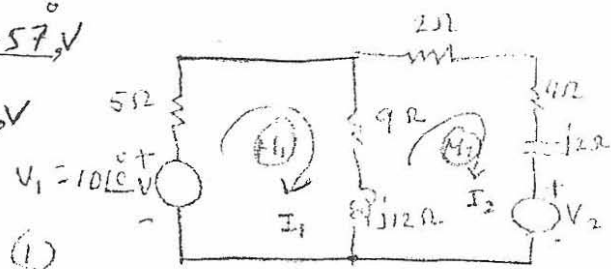

$$(M_1) (14+j12)I_1 - (4+j12)I_2 = 10 \angle 0^\circ \quad (1)$$

$$(M_2) -(4+j12)I_1 + (15+j10)I_2 = -8.94 \angle -56.57^\circ \quad (2)$$

$$(1) \rightarrow I_1 = \frac{10 + (4+j12)I_2}{14+j12} \quad (3)$$

$$(3) \text{ in } (2): \frac{-(4+j12) \times 10}{14+j12} + \left[\frac{-(4+j12)(9+j12)}{14+j12} + (15+j10) \right] I_2 =$$

$$= -8.94 \angle -56.57^\circ$$


$$\Rightarrow I_2 = 0.196 + j0.948 = 0.968 \angle 78.3^\circ \text{ A}$$

$$(3) \rightarrow I_1 = 0.400 + j0.434 = 0.590 \angle 47.3^\circ \text{ A}$$

$\frac{3-31}{150}$

$$Y_1 = \frac{1}{9+j12} = 0.07 \angle -53.1^\circ \text{ S}$$
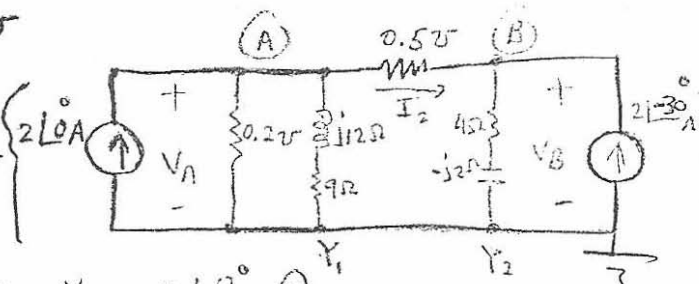
$$Y_2 = \frac{j}{4-j2} = 0.22 \angle +26.57^\circ \text{ S}$$



$$(A) (0.2 + 0.07 \angle -53.1^\circ + 0.5) V_A - 0.5 V_B = 2 \angle 0^\circ \quad (1)$$

$$(B) -0.5 V_A + (0.5 + 0.22 \angle +26.57^\circ) V_B = 2 \angle -30^\circ \quad (2)$$

$$(1) \rightarrow V_A = \frac{2 + 0.5 V_B}{0.74 \angle -4.12^\circ} \quad (3)$$

$$(3) \text{ in } (2): -0.5 \left(\frac{2 + 0.5 V_B}{0.74 \angle -4.12^\circ} \right) + (0.7 + j0.1) V_B = 2 \angle -30^\circ$$


$$\Rightarrow V_B = 7.61 - j4.07 = 8.63 \angle -28.12^\circ \text{ Volts}$$

$$\therefore V_A = 8.00 - j2.17 = 8.29 \angle -15.18^\circ \text{ Volts}$$

$$\therefore I_2 = \frac{V_A - V_B}{2} = 0.196 + j0.948 = 0.968 \angle 78.32^\circ \text{ Amp}$$

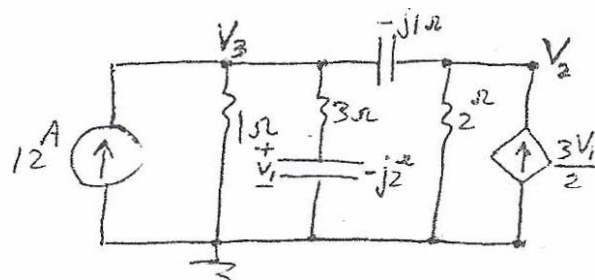3-33
150

Convert to phasor voltages and impedances using current sources as shown.



$$\therefore \left(\frac{1}{1} + \frac{1}{3-j2} + \frac{1}{-j}\right)V_3 - \frac{1}{-j}V_2 = 12 \quad (1)$$

$$\text{K} \quad -\frac{1}{-j}V_3 + \left(\frac{1}{-j} + \frac{1}{2}\right)V_2 = \frac{3V_1}{2} \quad (2)$$

Constraint Eq. $V_1 = \frac{V_3}{3-j2} * (-j2) \quad (3)$

$$(3) \text{ into } (2) \Rightarrow \frac{V_3}{j} + \left(\frac{j-2}{2j}\right)V_2 = \frac{3}{2} \left(\frac{-j2}{3-j2}\right)V_3$$

$$\therefore V_2 = V_3 \left[\frac{-j3}{3-j2} - \frac{1}{j} \right] \left(\frac{j-2}{2j} \right) = \frac{-j3 + j(3-j2)}{3-j2} \cdot \frac{2j}{j-2} \cdot V_3 = \frac{4jV_3}{-4+j7} \quad (4)$$

$$(4) \text{ into } (1) \Rightarrow \left[\frac{3-j2+1+j(3-j2)}{3-j2} - j \cdot \frac{4j}{-4+j7} \right] V_3 = 12$$

$$\therefore \left(\frac{6+j}{3-j2} + \frac{4}{-4+j7} \right) V_3 = 12 \Rightarrow \frac{(6+j)(-4+j7) + 4(3-j2)}{(3-j2)(-4+j7)} \cdot V_3 = 12$$

$$\therefore \frac{-31+38j+12-j8}{(3-j2)(-4+j7)} \cdot V_3 = 12 \Rightarrow V_3 = \frac{12 * (3-j2) * (-4+j7)}{-19+j30}$$

$$\text{into } (4) \Rightarrow V_2 = \frac{4j}{(-4+j7)} \cdot \frac{12 * (3-j2)(-4+j7)}{-19+j30} = \frac{48j(3-j2)}{-19+j30}$$


$$= \frac{48(2+j3)(-19-j30)}{(-19)^2 - (j30)^2} = \frac{48(52-j117)}{361+900} = \frac{48 * 13(4-j9)}{1261}$$

$$\therefore V_2 = \frac{48}{97} \cdot \sqrt{97} \angle -\tan^{-1}\left(\frac{9}{4}\right) = \frac{48}{\sqrt{97}} \angle -\tan^{-1}(2.25) = 4.8737 \angle -66.04^\circ, V$$

$$\therefore v_2(t) = 4.8737\sqrt{2} \cos(2t - 66.04^\circ) = 6.8924 \cos(2t - 66.04^\circ), V$$

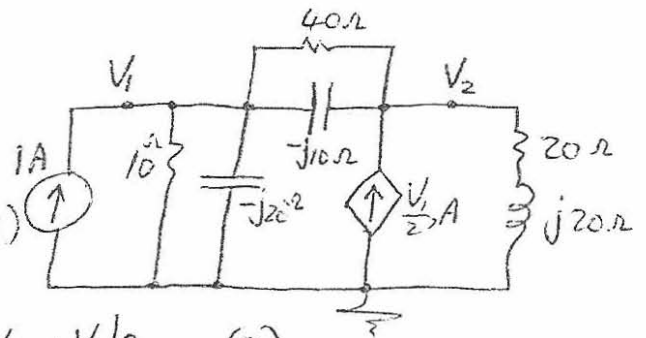3-39
153

Solution by Nodal Analysis:
Sources are already converted.



$$\therefore \left(\frac{1}{10} + \frac{1}{-j20} + \frac{1}{40} + \frac{1}{-j10}\right)V_1 - \left(\frac{1}{40} + \frac{1}{-j10}\right)V_2 = 1 \quad (1)$$

$$\text{KCL at } V_2: -\left(\frac{1}{40} + \frac{1}{j10}\right)V_1 + \left(\frac{1}{40} + \frac{1}{j10} + \frac{1}{20 + j20}\right)V_2 = +V_1/2 \quad (2)$$

$$(2) \Rightarrow \left(-\frac{1}{2} - \frac{1}{40} - \frac{j}{10}\right)V_1 + \left(\frac{1}{40} + \frac{j}{10} + \frac{20 - j20}{20^2 + 20^2}\right)V_2 = 0$$

$$\therefore \frac{21 + j4}{40} V_1 = \frac{20 + j80 + 20 - j20}{800} V_2 = \frac{40 + j60}{800} V_2 = \frac{2 + j3}{40} V_2$$

$$\therefore V_1 = \left(\frac{2 + j3}{21 + j4}\right)V_2 = \left(\frac{3.6056 \angle +56.31^\circ}{21.3776 \angle +10.78^\circ}\right)V_2 = \left(0.16866 \angle +45.53^\circ\right)V_2 \quad (3)$$

$$(3) \text{ into } (1) \Rightarrow \left[\left(\frac{j4 - 2 + j - 4}{j40}\right)(0.16866 \angle 45.53^\circ) - \frac{j - 4}{j40}\right]V_2 = 1$$

$$\therefore \left[(j5 - 6)(0.16866 \angle 45.53^\circ) - j + 4\right]V_2 = j40$$

$$\therefore \left(7.8102 \angle 140.19^\circ\right)(0.16866 \angle 45.53^\circ) + 4 - j)V_2 = j40$$

$$\therefore \left(1.3173 \angle 185.72^\circ + 4 - j\right)V_2 = j40$$

$$\therefore \left(-1.3107 - j.1313 + 4 - j\right)V_2 = j40$$

$$\therefore \left(2.6893 - j1.1313\right)V_2 = j40$$

$$\therefore V_2 = \frac{j40}{2.6893 - j1.1313} = \frac{40 \angle 90^\circ}{2.9175 \angle -22.81^\circ} = 13.7102 \angle 112.81^\circ \text{ V}$$


$$\therefore V_2 = 13.7102 \angle 112.81^\circ \text{ V}$$

3-40
153

Solution by Mesh Analysis:

Convert to voltage sources;
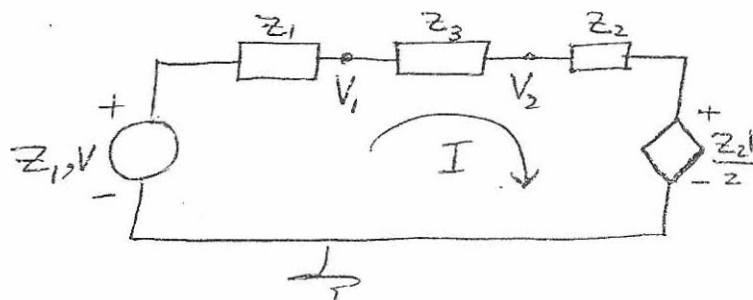
$$\begin{aligned} \therefore Z_1 &= 10 \parallel (-j20) \\ &= \frac{10(-j20)}{10-j20} \\ &= \frac{-j200}{10-j20} \\ &= \frac{200 \angle -90^\circ}{22.3607 \angle -63.43^\circ} \\ &= 8.9443 \angle -26.57^\circ, \Omega \\ &= 8 - j4, \Omega \end{aligned}$$



$$\# Z_3 = 40 \parallel (-j10) = \frac{40(-j10)}{40-j10} = \frac{-j400}{40-j10} = \frac{400 \angle -90^\circ}{41.2311 \angle -14.04^\circ} = 9.7014 \angle -75.96^\circ = 2.3529 - j9.4118$$

$$\# Z_2 = 20 + j20 = 28.2843 \angle 45^\circ, \Omega$$

$$\therefore I = \frac{Z_1 - (Z_2 V_1 / 2)}{Z_1 + Z_2 + Z_3} = \frac{Z_1 - V_1}{Z_1} \quad (1)$$

$$\therefore V_1 \left(\frac{Z_2 / 2}{Z_1 + Z_2 + Z_3} - \frac{1}{Z_1} \right) = \frac{Z_1}{Z_1 + Z_2 + Z_3} - 1 = \frac{-Z_2 - Z_3}{Z_1 + Z_2 + Z_3}$$

$$\therefore V_1 \# \left(\frac{Z_2 Z_1 - 2Z_1 - 2Z_2 - 2Z_3}{2Z_1(Z_1 + Z_2 + Z_3)} \right) = \frac{-Z_2 - Z_3}{Z_1 + Z_2 + Z_3}$$

$$\therefore V_1 = \frac{2Z_1(Z_2 + Z_3)}{2(Z_1 + Z_2 + Z_3) - Z_2 Z_1} \quad (2)$$

$$\therefore V_2 = V_1 - Z_3 I = (\text{from (1)}) V_1 - Z_3 \left(\frac{Z_1 - V_1}{Z_1} \right) = V_1 \left(1 + \frac{Z_3}{Z_1} \right) - Z_3$$

using (2)

$$\therefore V_2 = \frac{2Z_1(Z_2 + Z_3)}{2(Z_1 + Z_2 + Z_3) - Z_2 Z_1} \cdot \frac{Z_1 + Z_3}{Z_1} - Z_3 = \frac{2(Z_1 + Z_3)(Z_2 + Z_3)}{2(Z_1 + Z_2 + Z_3) - Z_2 Z_1} - Z_3$$

$$= \frac{2(8 - j4 + 2.3529 - j9.4118)(20 + j20 + 2.3529 - j9.4118)}{2(8 - j4 + 20 + j20 + 2.3529 - j9.4118) - 8.9443 \angle -26.57^\circ \times 28.2843 \angle 45^\circ}$$

$$= \frac{2(10.3529 - j13.4118)(22.3529 + j10.5882)}{2(30.3529 + j6.5882) - 252.98 \angle 18.43^\circ} - Z_3$$

$$= \frac{2 \times 16.9428 \angle -52.33^\circ \times 24.7339 \angle 25.35^\circ}{60.7058 + j13.1764 - 240 - j80} - Z_3 = \frac{838.12 \angle -26.99^\circ}{-179.29 - j66.824}$$


$$= \frac{838.12 \angle -26.99^\circ}{191.34 \angle -159.56^\circ} - Z_3 = 4.3802 \angle 132.57^\circ - Z_3 = -2.9633 + j3.2258$$

$$= -2.9633 + j3.2258 - 2.3529 + j9.4118 = -5.3162 + j12.6376$$

$$= 13.7102 \angle 112.81^\circ$$

$$\therefore V_2 = 13.7102 \angle 112.81^\circ, V$$
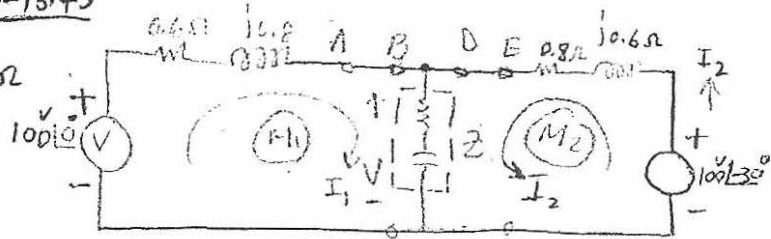
$$\frac{3-45}{155} z = \frac{10(8-j6)}{10+(8-j6)} = 5.27 \angle -18.43^\circ = 5-j1.67 \Omega$$



$$(M_1) \{0.6 + j0.8\} I_1 + (5 - j1.67) I_2 = 100 \angle 0^\circ \quad (1)$$

$$(M_2) + (5 - j1.67) I_1 + [(5 - j1.67) + (0.8 + j0.6)] I_2 = +100 \angle -30^\circ \quad (2)$$

$$(1) \rightarrow I_1 = 17.65 \angle 8.80^\circ - 0.93 \angle -9.64^\circ I_2 \quad (3)$$

$$(3) \text{ in } (2) \quad + (5 - j1.67)(17.65 \angle 8.80^\circ) + [(5 - j1.67)(-0.93 \angle -9.64^\circ) + (5.8 - j1.07)] I_2 = +100 \angle -30^\circ$$

$$\therefore I_2 = -18.06 \angle 41.52^\circ = -13.52 - j11.97 \text{ A}$$

into (3):

$$\therefore I_1 = 33.75 \angle 20.1^\circ = 31.70 + j11.57 \text{ A}$$

$$\therefore V = (I_1 + I_2) z = 95.85 \angle -19.70^\circ = 90.24 - j32.31 \text{ Volts}$$

$$(a) P_a = I_{AB} \cdot V_{BC} \cdot \cos \angle_{I_{AB}}^{V_{BC}}$$

$$\therefore P_a = V I_1 \cos \angle_{V}^{I_1} = 95.85 * 33.75 * \cos(20.1^\circ - (-19.7^\circ)) = 2487 \text{ W} = 2.487 \text{ kW}$$

$$(b) P_b = I_{DE} \cdot V_{EF} \cdot \cos \angle_{I_{DE}}^{V_{EF}}$$

$$\therefore P_b = V I_2 \cos \angle_{V}^{-I_2} = 95.85 * 18.06 * \cos(41.52^\circ + 19.7^\circ) = 833.4 \text{ W}$$

$$(c) P_{100 \angle 0^\circ} = I_1 * 100 * \cos(0 - (20.1^\circ)) = 33.75 * 100 * \cos 20.1^\circ = 3170.4 \text{ W} = 3.17 \text{ kW}$$

$$P_{100 \angle -30^\circ} = I_2 * 100 * \cos(-30^\circ - (180^\circ + 41.52^\circ)) = 18.06 * 100 * \cos 251.52^\circ = -572.4 \text{ W}$$


i.e. it absorbs 572.4 W.

$$\frac{3-47}{155}$$

$$v = 16\sqrt{2} \cos t \text{ V} \Rightarrow \omega = 1 \text{ rad/s}$$

$$(M_1) (3-j) I_1 - 2 I_2 = 16 \angle 0^\circ \quad (1)$$
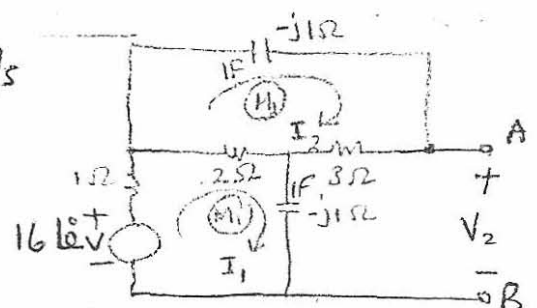
$$(M_2) -2 I_1 + (5-j) I_2 = 0 \quad (2)$$



$$(2) \rightarrow I_1 = (2.5 - j0.5) I_2 = 2.55 \angle -11.31^\circ I_2 \quad (3)$$

$$\textcircled{3} \text{ in } \textcircled{1} \quad [(3-j)(2.55 \angle -11.31^\circ) - 2] I_2 = 16$$

$$\therefore I_2 = 2.5 \angle 38.7^\circ = 1.95 + j 1.56 \text{ A}$$

$$\therefore I_1 = 6.37 \angle 27.3^\circ = 5.66 + j 2.93 \text{ A}$$

$$\therefore V_{oc} = V_2 = 3I_2 + (-j1)I_1 = 8.83 \angle -6.34^\circ = 8.78 - j 0.98, \text{ Volts}$$

To determine Z_0 , suppress the voltage source and use $\Delta \rightarrow Y$ transformation.

$$\Sigma Z = 2 + 3 - j = 5 - j = 5.1 \angle -11.31^\circ \Omega$$

$$Z_1 = \frac{3(-j)}{\Sigma Z} = 0.59 \angle -78.69^\circ = 0.12 - j 0.58 \Omega$$

$$Z_2 = \frac{2 \times 3}{\Sigma Z} = 1.18 \angle 11.31^\circ = 1.15 + j 0.23 \Omega$$

$$Z_3 = \frac{2(-j)}{\Sigma Z} = 0.39 \angle -78.69^\circ = 0.077 - j 0.385 \Omega$$

$$Z_0 = Z_1 + [(Z_2 - j) \parallel (Z_3 + 1)] = Z_1 + \frac{(1.15 - j 0.77)(1.077 - j 0.385)}{1.15 - j 0.77 + 1.077 - j 0.385}$$


$$= -0.12 - j 0.58 + (0.57 - j 0.28)$$

$$\therefore Z_0 = 0.683 - j 0.854 = 1.09 \angle -51.34^\circ \Omega$$

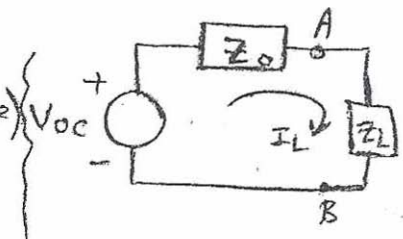(b) For Max. Power output,

$$Z_L = (Z_0)^* = 0.683 + j 0.854 \Omega \text{ (inductive)}$$

$$= 1.09 \angle 51.34^\circ = R_L + j X_L$$



$$\textcircled{c} \quad I_L \Big|_{P_{max}} = \frac{V_{oc}}{Z_0 + Z_0^*} = \frac{8.83 \angle -6.34^\circ}{0.683 + 0.683} = 6.47 \angle -6.34^\circ, \text{ Amp}$$




$$\therefore P_{max} = |I_L|^2 R_L = (6.47)^2 (0.683) = 28.6 \text{ W.}$$

$\frac{3-48}{156}$

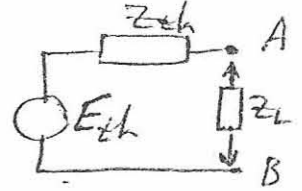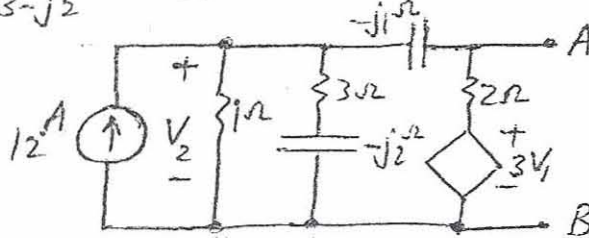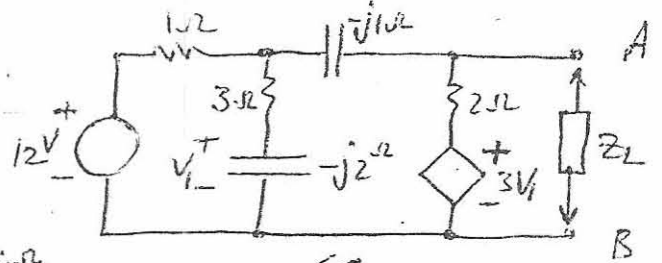
a) Converting to phasor voltages and impedances the circuit becomes as shown opposite.

Using simplification:

$$\therefore V_1 = V_2 \cdot \frac{-j2}{3-j2} \quad (1)$$


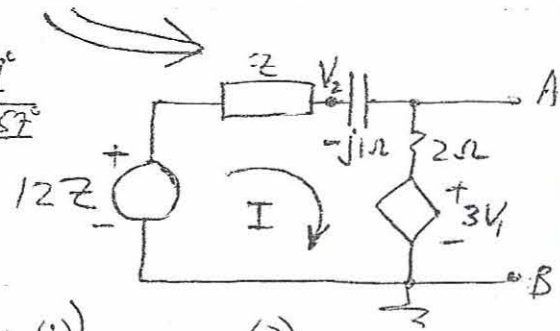
$$\begin{aligned} Z &= 1 \parallel (3-j2) \\ &= \frac{1 \cdot (3-j2)}{1+3-j2} = \frac{3-j2}{4-j2} = \frac{3.6056 \angle -33.69^\circ}{4.4721 \angle -26.57^\circ} \\ &= 0.8062 \angle -7.13^\circ = 0.8 - j0.1 \Omega \quad (2) \end{aligned}$$



$$\therefore I = \frac{12Z - V_2}{Z} = \frac{V_2 - 3V_1}{2-j1} \quad (\text{using (1)})$$

$$= \frac{V_2 - 3V_2(-j2/(3-j2))}{2-j1} = \frac{V_2}{(3-j2)(2-j)} [3-j2 + j6] = V_2 \left(\frac{3+j4}{4-j7} \right)$$

$$\begin{aligned} \therefore 12 &= \frac{V_2}{Z} + V_2 \left(\frac{3+j4}{4-j7} \right) \therefore V_2 = \frac{12}{\frac{1}{Z} + \frac{3+j4}{4-j7}} = \frac{12Z(4-j7)}{4-j7 + (3+j4)Z} \\ &= \frac{12 \times 0.8062 \angle -7.13^\circ \times 8.0623 \angle -60.26^\circ}{4-j7 + 5.0 \angle 53.13^\circ \times 0.8062 \angle -7.13^\circ} = \frac{78 \angle -67.38^\circ}{4-j7 + 4.0311 \angle 46.01^\circ} \end{aligned}$$

$$\therefore V_2 = \frac{78 \angle -67.38^\circ}{4-j7 + 2.8 + j2.9} = \frac{78 \angle -67.38^\circ}{6.8 - j4.1} = \frac{78 \angle -67.38^\circ}{7.9404 \angle -31.09^\circ} = 9.8232 \angle -36.29^\circ$$

$$\therefore V_{AB} = V_2 + jI = (\text{using (3)}) V_2 + j \left(12 - \frac{V_2}{Z} \right) = +j12 + V_2 \left(1 - \frac{j}{Z} \right) = +j12 + V_2 \left(1 - \frac{j}{0.8-j0.1} \right)$$

$$= +j12 + V_2 (1 - 1.2403 \angle 97.13^\circ) = +j12 + V_2 (1 + 0.1538 - j1.2308) =$$

$$= +j12 + V_2 (1.1538 - j1.2308) = +j12 + 9.8232 \angle -36.29^\circ \times 1.6871 \angle -46.85^\circ$$

$$= +j12 + 16.5722 \angle -83.14^\circ = +j12 + 1.9794 - j16.4536 = 1.9794 - j4.45$$

$$\therefore E_{Th} = V_{AB} = 4.8737 \angle -66.04^\circ, V \quad \left\{ = 4.8737 \angle -66.04^\circ \right.$$

$$\neq \frac{E_{Th}}{Z_{Th}} = I_{AB} = \frac{3V_1}{2} + \frac{12Z}{Z-j1} = \frac{3}{2} V_2 \left(\frac{-j2}{3-j2} \right) + \frac{12Z}{Z-j1} = \left(\frac{-j3}{3-j2} \right) \left(\frac{-j}{Z-j1} \right) 12Z + \frac{12Z}{Z-j1}$$

$$= \frac{12Z}{(Z-j1)(3-j2)} [3-j2-3] = \frac{12 \times 0.8062 \angle -7.13^\circ \times 2 \angle -90^\circ}{(0.8-j0.1-j) \times 3.6056 \angle -33.69^\circ} =$$

$$= \frac{19.3494 \angle -97.13^\circ}{(-0.8 - j1.1) \times 3.6056 \angle -33.69^\circ} = \frac{5.3666 \angle -63.43^\circ}{1.3601 \angle 53.97^\circ} = 3.9456 \angle -9.46^\circ, A$$

$$\therefore Z_{th} = \frac{E_{th}}{I_{AB}} = \frac{4.8737 \angle -66.04^\circ}{3.9456 \angle -9.46^\circ} = 1.2352 \angle -56.58^\circ, \Omega = .6804 - j1.0309, \Omega$$

b) \therefore Maximum power in Z_L is obtained when $Z_L = \bar{Z}_{th} = -.6804 + j1.0309, \Omega$

c) Value of max. power = $\left(\frac{E_{th}}{Z_{th} + \bar{Z}_{th}}\right)^2 \times R_L = \left(\frac{4.8737}{2 \times .6804}\right)^2 \times .6804 = 8.72 \text{ Watts}$


3-49
156

a) $I_1 = \frac{10 \angle 0^\circ}{5 + (9 + j12)} A$

KVL $\rightarrow V_{oc} = (9 + j12)I_1 - (4 - j2)I$


$$\therefore V_{oc} = \frac{(10)(9 + j12)}{14 + j12} - (2 \angle 30^\circ)(4.471 \angle -26.57^\circ)$$
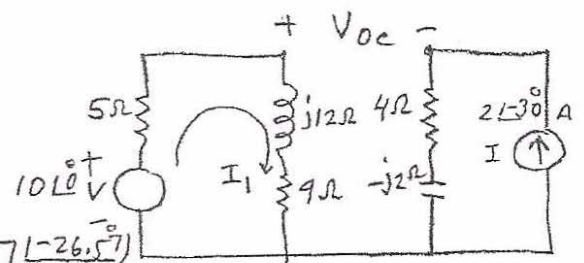
$$= (7.94 + j1.76) - (4.93 - j7.46) = 3.01 + j9.23 = 9.71 \angle 71.92^\circ V$$



To determine Z_0 , suppress the sources

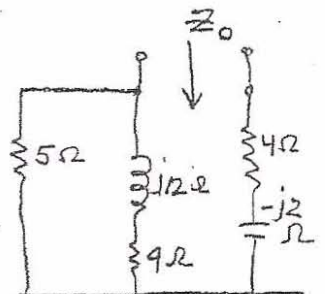
$$Z_1 = 5 \parallel (9 + j12) = \frac{5(9 + j12)}{5 + (9 + j12)} = 3.97 + j0.88 \Omega$$



$$Z_0 = Z_1 + (4 - j2) = 7.97 - j1.12 = 8.05 \angle -8.0^\circ \Omega$$

b) $I_2 = \frac{V_{oc}}{Z_0 + 2} = \frac{9.71 \angle 71.92^\circ}{10.031 \angle -6.4^\circ}$

$$I_2 = 0.97 \angle 78.3^\circ A$$

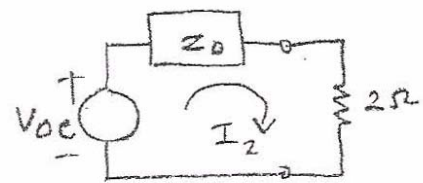


$\frac{3-50}{156}$

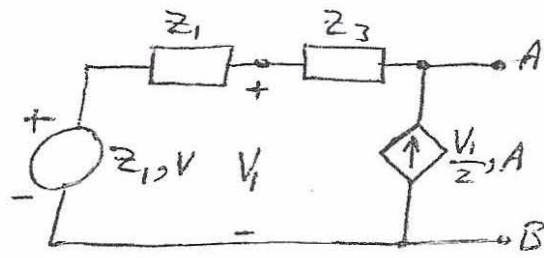a) Take away the load at AB and convert current source to voltage, then circuit is as shown here.

$$z_1 \left(\text{as in } \frac{3-40}{153} \right) = 8.9443 \angle -26.57^\circ = 8 - j4, \Omega$$

$$z_3 = 9.7014 \angle -75.96^\circ = 2.3529 - j9.4118, \Omega$$



$$\therefore V_1 = z_1 + z_1 \left(\frac{V_1}{z_2} \right) \Rightarrow V_1 = \frac{z_1}{1 - z_1/z_2} = \frac{z_1 z_2}{z_2 - z_1}$$

$$\begin{aligned} \therefore V_{AB} &= V_1 + \left(\frac{V_1}{z_2} \right) z_3 = V_1 \left(1 + \frac{z_3}{z_2} \right) = \frac{z_1 z_2}{z_2 - z_1} \cdot \frac{z_2 + z_3}{z_2} = \left(\frac{z_2 + z_3}{z_2 - z_1} \right) \cdot z_1 \\ &= \frac{2 + 2.3529 - j9.4118}{2 - 8 + j4} \cdot z_1 = \frac{4.3529 - j9.4118}{-6 + j4} \cdot z_1 = \frac{10.3696 \angle -65.18^\circ}{7.2111 \angle 146.31^\circ} \\ &= (1.4380 \angle -211.49^\circ) 8.9443 \angle -26.57^\circ = 12.8620 \angle 121.95^\circ, V \end{aligned}$$


$$\begin{aligned} \# \quad I_{AB} &= \frac{V_1}{z_2} + \frac{z_1}{z_1 + z_3} = \frac{1}{z_2} \left(z_1 \cdot \frac{z_3}{z_1 + z_3} \right) + \frac{z_1}{z_1 + z_3} = \frac{z_1 (z_2 + z_3)}{2(z_1 + z_3)} \\ &= \frac{z_1 (2 + 2.3529 - j9.4118)}{2(8 - j4 + 2.3529 - j9.4118)} = \frac{z_1 (4.3529 - j9.4118)}{2(10.3529 - j13.4118)} \\ &= \frac{8.9443 \angle -26.57^\circ \times 10.3696 \angle -65.18^\circ}{2 \times 16.9428 \angle -52.33^\circ} = 2.7371 \angle -39.41^\circ, A \end{aligned}$$

$$\therefore z_{AB} = \frac{V_{AB}}{I_{AB}} = \frac{12.8620 \angle 121.95^\circ}{2.7371 \angle -39.41^\circ} = 4.6991 \angle 161.36^\circ, \Omega$$

$$= -4.4525 + j1.5023, \Omega$$

\therefore Thevenin Equivalent at AB is as shown.
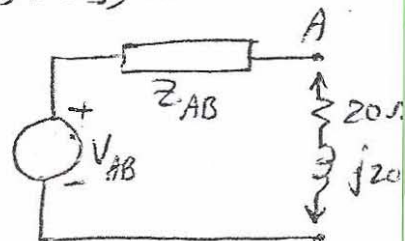
$$\begin{aligned} \text{b) } \therefore V_2 &= V_{AB} \cdot \frac{20 + j20}{z_{AB} + 20 + j20} = \frac{12.8620 \angle 121.95^\circ \times 20\sqrt{2} \angle 45^\circ}{-4.4525 + j1.5023 + 20 + j20} \\ &= \frac{363.791 \angle 166.95^\circ}{15.5475 + j21.5023} = \frac{363.791 \angle 166.95^\circ}{26.5344 \angle 54.13^\circ} = 13.7102 V \angle 112.81^\circ \end{aligned}$$



Since z_{AB} has a negative real part due to nature of controlled sources then the power becomes infinite when load at $AB = -z_{AB} = 4.4525 - j1.5023$

$$\frac{3-51}{156} \quad (a) \quad z_1 = (10) \parallel (8-j6)$$


$$= \frac{(10)(8-j6)}{10+8-j6}$$

$$= 5.27 \angle -18.43^\circ = 5.0 - j1.67 \Omega$$

$$I_2 = \frac{100 \angle -30^\circ}{(0.8+j0.6)+z_1} = \frac{100 \angle -30^\circ}{5.90 \angle -10.42^\circ} = 16.96 \angle -19.58^\circ \text{ A}$$

$$\therefore V_{oc} = I_2 z_1 = 16.96 \angle -19.58^\circ \times 5.27 \angle -18.43^\circ = 89.37 \angle -38.01^\circ$$

$$= 70.41 - j55.04 \text{ V}$$

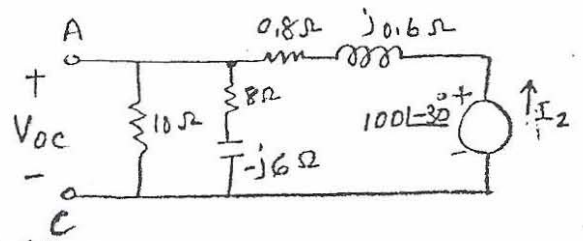


To determine \hat{z}_0 , suppress the source

$$z_0 = z_1 \parallel (0.8+j0.6) = \frac{(5.27 \angle -18.43^\circ)(1.36.9^\circ)}{(5.0-j1.67)+(0.8+j0.6)}$$

$$= \frac{5.27 \angle -18.43^\circ}{5.90 \angle -10.42^\circ} = 0.89 \angle 28.86^\circ = 0.78 + j0.43 \Omega$$

$$(b) \quad I = \frac{(100 \angle 0^\circ) - (89.37 \angle -38.01^\circ)}{(0.6+j0.8) + (0.78+j0.43)}$$
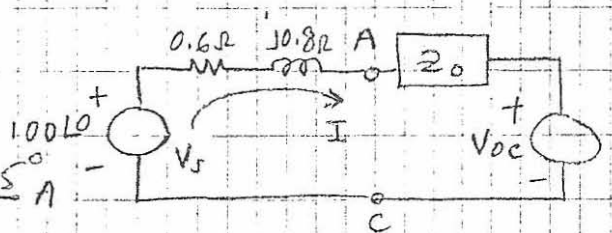
$$= \frac{62.49 \angle 61.74^\circ}{1.85 \angle 41.68^\circ} = 33.75 \angle 20.05^\circ \text{ A}$$




$$\therefore P_s = |I| |V_s| \cos(\angle V_s - \angle I) = 33.75 \times 100 \cos(0 - 20.05^\circ) = 3170.4 \text{ W}$$

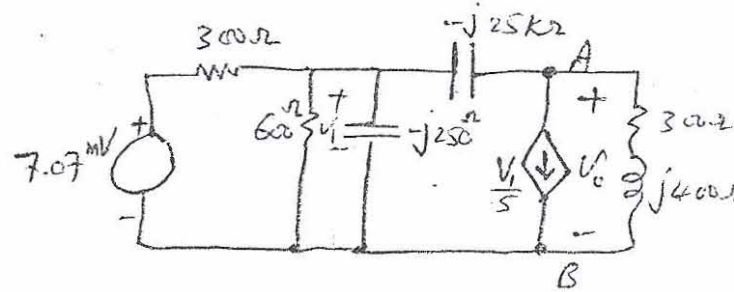3-53
156




Solution by Thevenin at AB:

Remove $300 + j400 \Omega$
and find E_{th} & Z_{th}




$\therefore E_{th} = V_{AB}$

Using simplification:

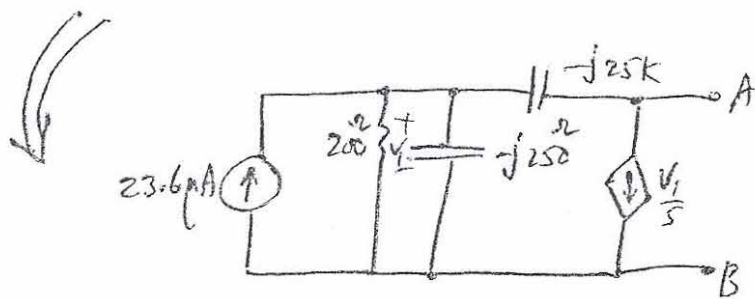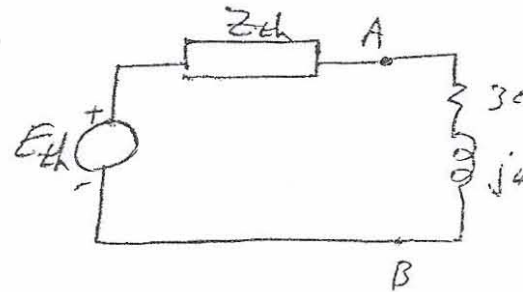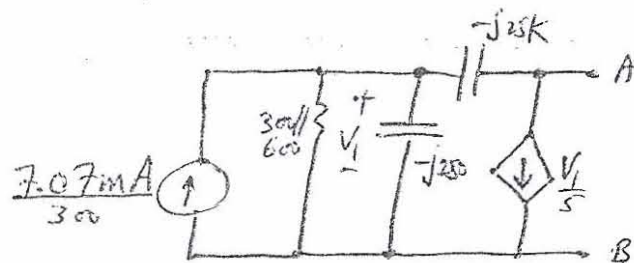

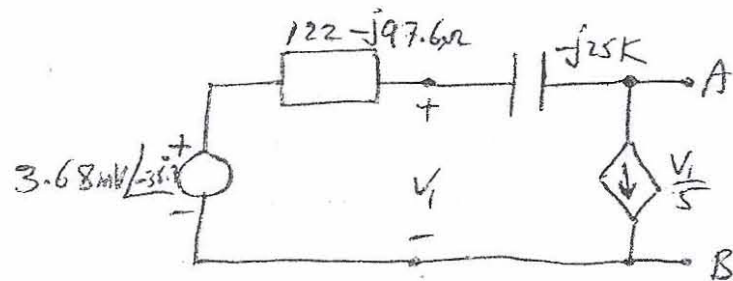Let $Z = 200 \parallel -j25K$
 $= 122 - j97.6$
 $= 156 \angle -38.7^\circ$



$\therefore \frac{V_1}{5} = \frac{3.68 \angle -38.7^\circ \text{ mV} - V_1}{122 - j97.6} \quad \therefore V_1 = \frac{3.68 \text{ m} \angle -38.7^\circ}{\frac{122 - j97.6}{5} + 1} = .115 \text{ mV} \angle -1.1^\circ$

$\therefore V_{AB} = V_1 - \frac{V_1}{5} (-j25K) = V_1 (1 + j5K) = .115 \text{ mV} \angle -1.1^\circ * 5K \angle 90^\circ = E_{th} = .575 \text{ V} \angle 88.9^\circ$

$\therefore Z_{th} = \frac{E_{th}}{I_{sc}} \Rightarrow I_{sc} = \frac{3.68 \text{ mV} \angle -38.7^\circ}{122 - j97.6 - j25K} \left(1 - \frac{1}{5} (-j25K)\right) = 733 \mu\text{A} \angle 141.0^\circ$

$\therefore Z_{th} = \frac{.575 \angle 88.9^\circ}{733 \mu \angle 141.0^\circ} = 784 \Omega \angle -52.1^\circ = 482 - j619 \Omega$

$\therefore V_o = \frac{E_{th} (300 + j400)}{Z_{th} + 300 + j400} = \frac{.575 \angle 88.9^\circ * 500 \angle 53.1^\circ}{782 - j219} = 0.354 \text{ V} \angle 157.1^\circ$

OK
65


3-55
156

$$V_2 = 200 \angle 0^\circ \text{ V}$$

$$\theta_2 = \cos^{-1} 0.707 = 45^\circ$$

lagging pf $\Rightarrow I_2$ lags V_2

$$\therefore \angle_{I_2} = -45^\circ$$

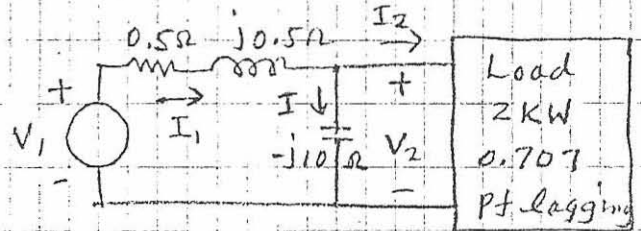

$$P_{\text{Load}} = 2000 = |V_2| |I_2| \cos \theta_2 = 200 \times 0.707 I_2$$

(a) $\therefore |I_2| = 14.14 \text{ A} \Rightarrow I_2 = 14.14 \angle -45^\circ \text{ A} = 10 - j10 \text{ A}$

(b) $I = \frac{V_2}{-j10} = \frac{200}{10 \angle -90^\circ} = j20 \text{ A} = 20 \angle 90^\circ \text{ A}$

KCL $\rightarrow I_1 = I_2 + I = (10 - j10) + (j20) = 14.14 \angle 45^\circ \text{ A} = 10 + j10 \text{ A}$

KVL $\rightarrow V_1 = (0.5 + j0.5) I_1 + V_2 = (10 \angle 90^\circ) + 200 \angle 0^\circ = 200.25 \angle 2.86^\circ$

(c) $P = |V_1| |I_1| \cos \angle_{V_1} = 200.25 \times 14.14 \cos(2.86 - 45)$
 $= 200.25 \times 14.14 \times 0.742 = 2100.0 \text{ W} = 2.1 \text{ kW}$

$Q = |V_1| |I_1| \sin \angle_{V_1} = 200.25 \times 14.14 \sin(-42.14) = -1900.0 \text{ vars}$
 (Capacitive)

$VA = |V_1| |I_1| = 200.25 \times 14.14 = 2831.96 \text{ VA}$

3-59
158

$$I_L = \frac{10 \text{ K}}{440 \times 0.8} \angle^{-\cos^{-1} 0.8} =$$

$$= 28.409 \text{ A} \angle^{-36.87^\circ} =$$


$$= 22.727 - j17.045, \text{ A}$$

$$\therefore E_2 = (0.6 + j0.7) I_L + 440 =$$

$$= 0.92195 \angle^{49.40^\circ} \times 28.409 \angle^{-36.87^\circ} + 440 =$$

$$= 26.192 \angle^{12.53^\circ} + 440 = 25.568 + j5.6818 + 440 =$$
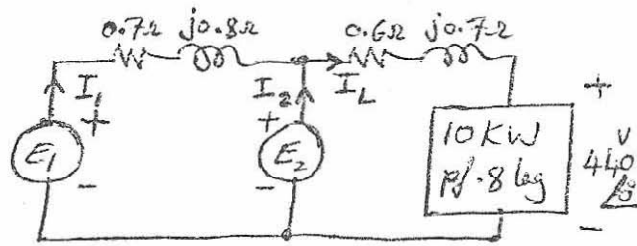
$$= 465.57 + j5.6818 = 465.60 \angle^{0.70^\circ}, \text{ V}$$



$$\therefore I_2 = \frac{5 \text{ K}}{465.60 \times 0.6} \angle^{-\cos^{-1} 0.6 + 0.70^\circ} = 17.898 \text{ A} \angle^{-53.13^\circ + 0.70^\circ}$$

$$= 17.898 \text{ A} \angle^{-52.43^\circ} = 10.913 - j14.186, \text{ A}$$

$$\therefore I_1 = I_L - I_2 = 22.727 - j17.045 - 10.913 + j14.186 =$$

$$= 11.814 - j2.8592, \text{ A} = 12.156 \angle^{-13.60^\circ}, \text{ A}$$

$$\therefore E_1 = (0.7 + j0.8) * I_1 + E_2 = 1.0630 \angle^{48.81^\circ} * 12.156 \angle^{-13.60^\circ} + E_2 =$$

$$= 12.922 \angle^{35.21^\circ} + E_2 = 10.558 + j7.4502 + 465.57 + j5.6818 =$$

$$= 476.13 + j13.132, \text{ V} = 476.31 \angle^{1.58^\circ}, \text{ V}$$

a) Hence, the terminal voltage of generator 1 is 476.31 Volts,

& that of generator 2 is 465.60 Volts.


$$b) S_1 = 12.156 * 476.31 = 5789.8 \text{ VA} = 5.7898 \text{ KVA}$$

$$\text{pf at } E_1 = \cos \angle_{I_1}^{E_1} = \cos(1.58^\circ + 13.60^\circ) = \cos 15.18^\circ = 0.96509 \text{ lag}$$

$$\# \text{ Line losses} = |I_1|^2 * 0.7 + |I_2|^2 * 0.6 = 12.156^2 * 0.7 + 17.898^2 * 0.6 =$$

$$= 103.43 + 192.20 = 295.63 \text{ Watts.}$$

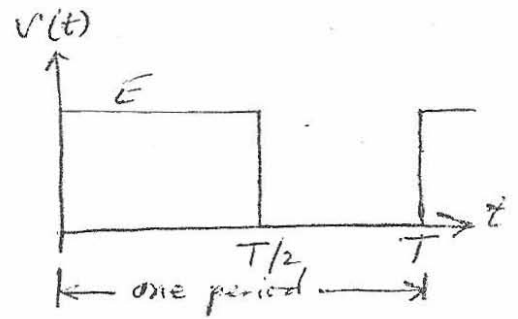To find Fourier Series of the waveform shown, assuming periodic.



$$\therefore A_v = \frac{E \cdot T/2}{T} = \frac{E}{2}$$

$$\text{Fundamental frequency} = \frac{2\pi}{T} \text{ rad/sec} = \omega$$

$$\therefore V_s(t) = \frac{E}{2} + \sum_{n=1}^{\infty} a_n \sin n\omega t + b_n \cos n\omega t$$

$$\begin{aligned} \therefore a_n &= \frac{2}{T} \int_0^T V_s(t) \sin n\omega t dt = \frac{2}{T} \int_0^{T/2} E \sin n\omega t dt = \frac{2E}{T} \cdot \left. \frac{-\cos n\omega t}{n\omega} \right|_0^{T/2} \\ &= \frac{2E}{n\omega T} [1 - \cos(n\omega T/2)] = \frac{2E}{n2\pi} (1 - \cos(n2\pi/2)) = \frac{E}{n\pi} (1 - \cos n\pi) \\ &= \frac{2E}{n\pi} \text{ for odd } n \text{ \& zero for even } n \end{aligned}$$

$$\begin{aligned} \& b_n = \frac{2}{T} \int_0^T V_s(t) \cos n\omega t dt = \frac{2}{T} \int_0^{T/2} E \cos n\omega t dt = \frac{2E}{T} \cdot \left. \frac{\sin n\omega t}{n\omega} \right|_0^{T/2} \\ &= \frac{2E}{n\omega T} (\sin(n\omega T/2) - 0) = \frac{2E}{n2\pi} (\sin(n2\pi/2) - 0) = \frac{E}{n\pi} (\sin n\pi - 0) = 0 \end{aligned}$$


$$\therefore V_s(t) = \frac{E}{2} + \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} \frac{2E}{n\pi} \sin n\omega t = \frac{E}{2} + \frac{2E}{\pi} \sum_{\substack{n=1 \\ \text{odd}}}^{\infty} \frac{1}{n} \sin\left(\frac{2n\pi t}{T}\right)$$

$$\therefore V_s(t) = \frac{E}{2} + \frac{2E}{\pi} \left(\sin\left(\frac{2\pi t}{T}\right) + \frac{1}{3} \sin\left(\frac{6\pi t}{T}\right) + \frac{1}{5} \sin\left(\frac{10\pi t}{T}\right) + \dots + \frac{1}{n} \sin\left(\frac{2n\pi t}{T}\right) \right)_{\text{odd}}$$

To find the current $i(t)$ for the circuit shown given that:

$$V(t) = 12 + 3 \cos t - 2 \sin t + 1.5 \cos 2t - \sin 3t, \text{ V}$$

we apply the superposition principle.

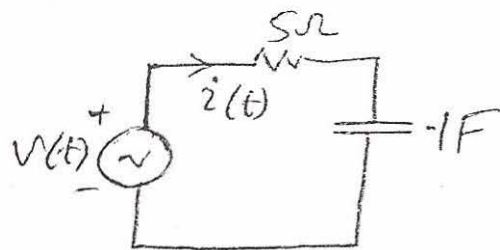


$$\therefore i(t) = i(t) \Big|_{\text{due } 12\text{V}} + i(t) \Big|_{\text{due } 3 \cos t, \text{V}} + i(t) \Big|_{\text{due } -2 \sin t, \text{V}} + i(t) \Big|_{\text{due } 1.5 \cos 2t, \text{V}} + i(t) \Big|_{\text{due } -\sin 3t, \text{V}}$$

$i(t) \Big|_{12\text{V}} = 0$ Amp since the 1F capacitor looks like open circuit for dc.

$$i(t) \Big|_{V \cos \omega t} = \frac{V / \left(\frac{1}{\omega C} \right)}{\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}} \cos \omega t = \frac{\omega C V}{\sqrt{1 + (\omega C R)^2}} \cos(\omega t + \phi)$$
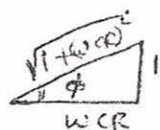
$$= \frac{\omega C V}{\sqrt{1 + \omega^2 C^2 R^2}} (\cos \omega t \cos \phi - \sin \omega t \sin \phi)$$



$$= \frac{\omega C V}{\sqrt{1 + \omega^2 C^2 R^2}} \left(\cos \omega t \cdot \left(\frac{\omega C R}{\sqrt{1 + \omega^2 C^2 R^2}} \right) - \sin \omega t \cdot \left(\frac{1}{\sqrt{1 + \omega^2 C^2 R^2}} \right) \right)$$

$$= \frac{\omega C V}{1 + \omega^2 C^2 R^2} (\omega C R \cos \omega t - \sin \omega t)$$

$$\therefore i(t) \Big|_{\substack{3 \cos t, \text{V} \\ \omega=1 \\ V=3}} = \frac{1 \cdot 1 \cdot 3}{1 + 1^2 \cdot 1^2 \cdot 5^2} (1 \cdot 1 \cdot 5 \cos t - \sin t) = \frac{3}{1.25} (.5 \cos t - \sin t)$$

$$= .12 \cos t - .24 \sin t, \text{ A}$$

$$\neq i(t) \Big|_{\substack{-2 \sin t, \text{V} \\ \omega=1 \\ V=-2}} = i(t) \Big|_{\substack{-2 \cos(t-90^\circ), \text{V} \\ \omega=1 \\ V=-2}} = \frac{1 \cdot 1 \cdot (-2)}{1.25} (.5 \cos(t-90^\circ) - \sin(t-90^\circ))$$

$$= -.08 \sin t - .16 \cos t, \text{ A}$$

$$\neq i(t) \Big|_{\substack{1.5 \cos 2t, \text{V} \\ \omega=2 \\ V=1.5}} = \frac{2 \cdot 1 \cdot 1.5}{1 + 2^2 \cdot 1^2 \cdot 5^2} (2 \cdot 1 \cdot 5 \cos 2t - \sin 2t) = .15 \cos 2t - .15 \sin 2t, \text{ A}$$

$$\neq i(t) \Big|_{\substack{-\sin 3t, \text{V} \\ \omega=3 \\ V=1}} = i(t) \Big|_{\substack{3 \cos 3(t-90^\circ), \text{V} \\ \omega=3 \\ V=1}} = \frac{3 \cdot 1 \cdot 1}{1 + 3^2 \cdot 1^2 \cdot 5^2} (3 \cdot 1 \cdot 5 \cos 3(t-90^\circ) - \sin 3(t-90^\circ)) =$$

$$= -.1385 \sin 3t - .09231 \cos 3t, \text{ A}$$

$$\therefore i(t) = -.04 \cos t - .32 \sin t + .15 \cos 2t - .15 \sin 2t - .09231 \cos 3t - .1385 \sin 3t, \text{ A}$$


$$\therefore P = (S/2) * [.04^2 + .32^2 + .15^2 + .15^2 + .09231^2 + .1385^2] = 0.44173 \text{ W (eff.)}$$

#) $|V_3|/|I_B| = 10 \text{ KVA}$
 Let $V_B = 215 \angle 0^\circ, V$

$\therefore |I_B| = \frac{10000}{215} = 46.512 \text{ A}$

$\angle_{I_B}^{V_B} = \cos^{-1} 0.6 = 53.13^\circ$

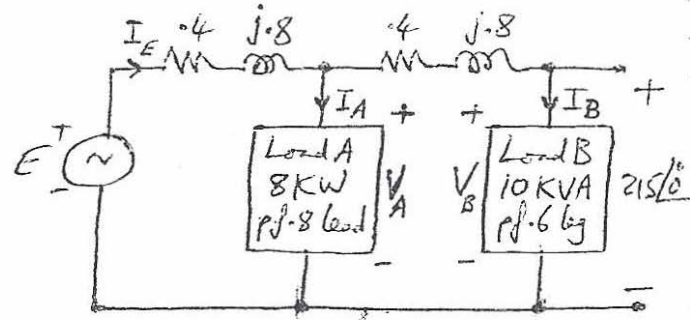$\therefore I_B = 46.512 \angle -53.13^\circ, \text{ A}$



$\therefore V_A = V_B + (0.4 + j0.8) I_B =$

$= 215 + 0.8944 \angle 63.43^\circ \times 46.512 \angle -53.13^\circ =$

$= 215 + 41.601 \angle 10.30^\circ =$

$= 215 + 40.930 + j7.4419 = 255.930 + j7.4419, V$

$= 256.04 \angle 1.67^\circ, V$

a) \therefore The terminal voltage of load A is 256.04 Volts

$\therefore |I_A| |V_A| \cos \angle_{I_A}^{V_A} = 8 \text{ KW}$

$\therefore |I_A| = \frac{8000}{256.04 \times 0.8} = 39.057 \text{ A}$

$\angle_{V_A}^{I_A} = \cos^{-1} 0.8 = 36.87^\circ$

$\therefore I_A = 39.057 \angle 1.67 + 36.87^\circ = 39.057 \angle 38.54^\circ, \text{ A}$

$\therefore I_E = I_A + I_B = 39.057 \angle 38.54^\circ + 46.512 \angle -53.13^\circ =$

$= 30.551 + j24.332 + 27.907 - j37.209 =$

$= 58.458 - j12.877 = 59.859 \angle -12.42^\circ, \text{ A}$

$\therefore E = V_A + (0.4 + j0.8) I_E = V_A + 0.8944 \angle 63.43^\circ \times 59.859 \angle -12.42^\circ =$

$= V_A + 53.540 \angle 51.01^\circ = 255.930 + j7.4419 + 33.685 + j41.616 =$

$= 289.62 + j49.057 = 293.74 \angle 9.61^\circ, V$

b) \therefore The terminal voltage of E is 293.74 Volts

$\angle_{I_E}^E = 9.61 - (-12.42) = 22.04^\circ$

c) \therefore pf at E = $\cos(22.04^\circ) = 0.9269$ lagging


d) $\therefore S_E = |E| |I_E| = 293.74 \times 59.859 = 17583 \text{ VA} = 17.583 \text{ KVA}$

e) \therefore Line losses = $0.4 |I_E|^2 + 0.4 |I_B|^2 = 0.4 [59.859^2 + 46.512^2] = 2298.6 \text{ W}$


\therefore Line losses = 2.2986 KW

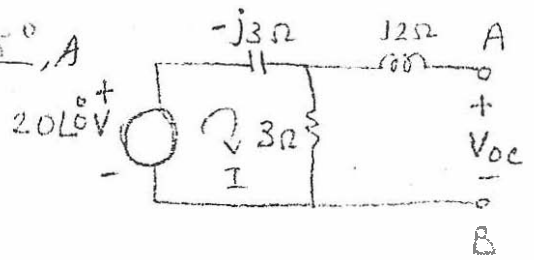(a) $I = \frac{20 \angle 0^\circ}{3 - j3} = \frac{20}{4.24 \angle -45^\circ} = 4.71 \angle 45^\circ \text{ A}$

$V_{oc} = 3I = 14.14 \angle 45^\circ \text{ V}$
 $= 10 + j10 \text{ V}$



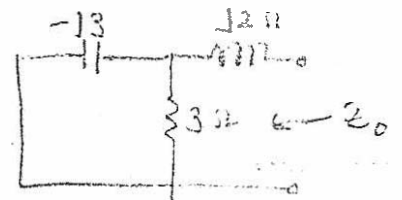
determine Z_0 , suppress the voltage source:



$Z_0 = j2 + \frac{3(-j3)}{3 - j3} = j2 + \frac{3I \cdot S}{\sqrt{2} \angle -45^\circ} = j2 + 2.12 \angle -45^\circ$
 $= j2 + 1.5 - j1.5 = 1.5 + j0.5 = 1.58 \angle 18.4^\circ \Omega$

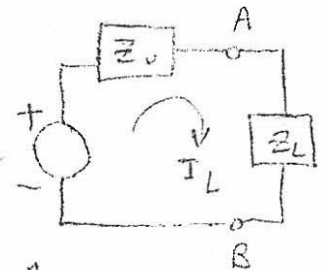(b) For max. power transfer,

$Z_L = Z_0^* = 1.5 - j0.5 \Omega = 1.58 \angle -18.4^\circ \Omega$




(c) $I_L \Big|_{p_{max}} = \frac{V_{oc}}{Z_0 + Z_0^*} = \frac{14.14 \angle 45^\circ}{1.5 + 1.5} = 4.71 \angle 45^\circ \text{ A}$

$P_{max} = |I_L|^2 R_L = (4.71)^2 (1.5) = 33.3 \text{ W}$

$$\# \quad v(t) = \frac{G}{T} t - G = G(t-1) V$$

$$v_{av} = \frac{1}{T} \int_0^T G(t-1) dt \quad T=2 \text{ sec}$$
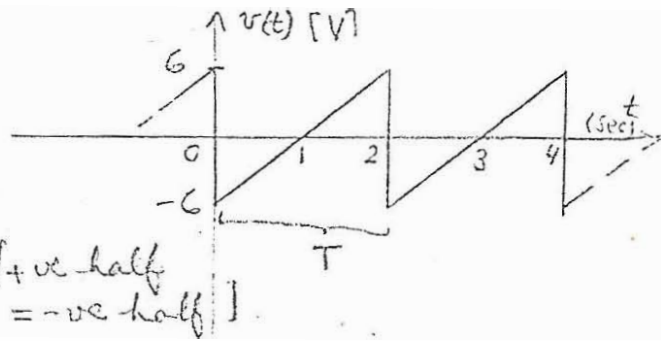
$$= \frac{G}{2} \left[\frac{t^2}{2} - t \right]_0^2 = 0 V \quad \begin{array}{l} \text{+ve half} \\ \text{-ve half} \end{array}$$



$$v_{rms} = \sqrt{\frac{1}{T} \int_0^T G^2(t-1)^2 dt} = G \sqrt{\frac{1}{T} \int_0^T (t^2 - 2t + 1) dt}$$

$$= G \sqrt{\frac{1}{T} \left[\frac{t^3}{3} - \frac{2t^2}{2} + t \right]_0^T} = G \sqrt{\frac{1}{2} \left[\frac{8}{3} - 4 + 2 \right]} = G \sqrt{\frac{1}{2} \times \frac{2}{3}}$$

$$v_{rms} = \frac{6}{\sqrt{3}} = 3.46 V$$


$$\# \quad V = 100 \angle 30^\circ V \quad \& \quad I = \frac{10}{\sqrt{2}} \angle 60^\circ A, \quad \omega = 377 \text{ rad/s}$$

(a) $\theta = 60^\circ - 30^\circ = 30^\circ$

$\therefore P = VI \cos(30^\circ) = 100 \times \frac{10}{\sqrt{2}} \times 0.866 = 612.4 W$

$Q = VI \sin(30^\circ) = 100 \times \frac{10}{\sqrt{2}} \times (+0.5) = +353.55 \text{ VAR (capacitive)}$

$VA = VI = 707 \text{ VA}$

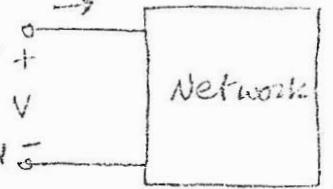


(b) $Z = R + jX = \frac{V}{I} = \frac{100 \angle 30^\circ}{\left(\frac{10}{\sqrt{2}}\right) \angle 60^\circ} = 14.14 \angle -30^\circ = 12.25 - j7.07 \Omega$

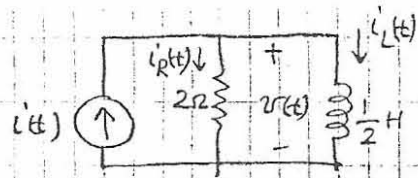(c) Since X is -ve \Rightarrow Capacitive Reactance.

$$\therefore X = X_C = \frac{1}{\omega C} = 7.07 \quad \Rightarrow C = \frac{1}{7.07 \times 377} = 375.12 \mu F$$

$$\frac{4-1}{214} \quad v_f(t) \text{ \& } i_{L_f}(t) = ?$$



$$\text{KCL} \rightarrow \frac{v}{2} + \frac{1}{L} \int v dt = i$$

$$\text{Differentiating:} \quad \frac{1}{2} \frac{dv}{dt} + 2v = \frac{di}{dt} \quad (1)$$

(a) $i = 4A \rightarrow$ Assume $v_f(t) = V_0$ (same form of excitation)
 from (1): $0 + 2V_0 = 0 \Rightarrow v_f(t) = 0$ } L is short for DC }
 $\therefore i_{L_f}(t) = i(t) = 4A$

(b) $i(t) = 2tA \rightarrow$ Assume $v_f(t) = V_1 t + V_0$ { excitation + all unique derivatives }
 from (1): $\frac{1}{2} V_1 + 2(V_1 t + V_0) = 2$

Comparing terms: $\frac{V_1}{2} + 2V_0 = 2$ & $2V_1 = 0$
 $\therefore V_1 = 0$ & $V_0 = 1V$

$$\therefore v_f(t) = 1V \quad i_{R_f}(t) = \frac{v_f(t)}{2} = \frac{1}{2}A$$

$$\text{KCL} \rightarrow i_{L_f}(t) = i(t) - i_{R_f}(t) = 2t - \frac{1}{2}A$$

(c) $i(t) = 4 + 2tA = i_1(t) + i_2(t)$

$$i_1(t) = 4A \quad \& \quad i_2(t) = 2tA$$

By superposition principle: } or follow the same procedure as in (b).

I) for $i_1(t) = 4A$, from a) $v_{f1}(t) = 0V$ & $i_{L_f1}(t) = 4A$

II) for $i_2(t) = 2tA$, from b) $v_{f2}(t) = 1V$ & $i_{L_f2}(t) = 2t - \frac{1}{2}A$


$$\therefore v_f(t) = v_{f1}(t) + v_{f2}(t) = 1V$$

$$i_{L_f}(t) = i_{L_f1}(t) + i_{L_f2}(t) = 2t + 3.5A$$

4-4
215

$v_{o_f}(t), i_f(t) = ?$

KVL $\rightarrow 100i + v_c - 9v_1 = v$

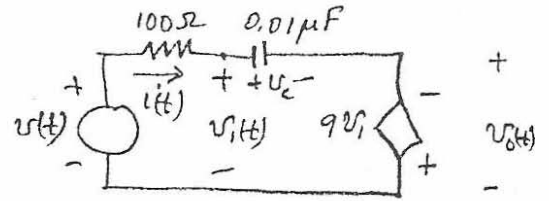

$i = i_c = C \frac{dv_c}{dt}$ and $v_1 = v - i(100)$

$\therefore 100i + v_c - 9(v - 100i) = v \Rightarrow 1000i + v_c = 10v$

$\therefore 10^{-5} \frac{dv_c}{dt} + v_c = 10v$ (1)

(a) $v = 0.1 \text{ V}$, from (1): $10^{-5} \frac{dv_c}{dt} + v_c = 1$

Assume $v_{c_f}(t) = V_0 \Rightarrow 0 + V_0 = 1 \Rightarrow V_0 = 1 \text{ V} = v_{c_f}(t)$

$i_f(t) = C \frac{dv_{c_f}}{dt} = 0$ (open ckt for DC excitation)

$\therefore v_{o_f}(t) = -9v_1 = -9v + 900i_f = -9(0.1) + 900(0) = -0.9 \text{ V}$

(b) $v = 0.2 e^{-10^5 t} \cos 10^5 t$

Assume $v_{c_f}(t) = A e^{-10^5 t} \cos 10^5 t + B e^{-10^5 t} \sin 10^5 t$

from (1)
 $2 e^{-10^5 t} \cos 10^5 t = 10^{-5} \{ (-10^5 A e^{-10^5 t} \cos 10^5 t - 10^5 B e^{-10^5 t} \sin 10^5 t) + (-10^5 A e^{-10^5 t} \sin 10^5 t + 10^5 B e^{-10^5 t} \cos 10^5 t) \} + A e^{-10^5 t} \cos 10^5 t + B e^{-10^5 t} \sin 10^5 t$

Comparing terms: $2 = -A + B + A \Rightarrow B = 2$

$0 = -A - B + B \Rightarrow A = 0$

$\therefore v_{c_f}(t) = 2 e^{-10^5 t} \sin 10^5 t, \text{ V}$


$\therefore i_f(t) = C \frac{dv_{c_f}}{dt} = 0.01 \times 10^{-6} \times 2 [-10^5 e^{-10^5 t} \sin 10^5 t + 10^5 e^{-10^5 t} \cos 10^5 t]$
 $= 0.02 e^{-10^5 t} (\cos 10^5 t - \sin 10^5 t) \text{ A}$

$\therefore v_{o_f}(t) = -9v_1 = -9v + 900i_f = -1.8 e^{-10^5 t} \cos 10^5 t + 1.8 [-e^{-10^5 t} \sin 10^5 t + 10^{-5} e^{-10^5 t} \cos 10^5 t]$

$\Rightarrow v_{o_f}(t) = -1.8 e^{-10^5 t} \sin 10^5 t, \text{ V}$

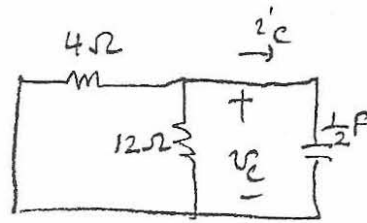4-8
216

$$\text{KCL} \rightarrow \frac{v_c}{4} + \frac{v_c}{12} + \frac{1}{2} \frac{dv_c}{dt} = 0$$



(a) $\therefore \frac{2}{3} v_c + \frac{dv_c}{dt} = 0$ (1)

$$v_{c_n}(t) = A e^{st} \Rightarrow s = -\frac{2}{3}$$

$$\therefore v_{c_n}(t) = A e^{-\frac{2}{3}t} \quad \delta \quad v_{c_f}(t) = 0 \quad (\text{force free})$$

$$\therefore v_c(t) = v_{c_f} + v_{c_n} = A e^{-\frac{2}{3}t}$$

$$i'_{c_n}(t) = \frac{1}{2} \frac{dv_{c_n}}{dt} = \frac{-A}{3} e^{-\frac{2}{3}t} = i'_c(t)$$

(b) $v_c(0) = 6 = A \Rightarrow v_c(t) = 6 e^{-\frac{2}{3}t} \text{ V}$

$$\therefore i'_c(0) = \frac{1}{2} \frac{dv_c}{dt}(0) = \frac{1}{2} \left(-\frac{12}{3} \right) = -2 \text{ A}$$

4-10
216

(a) $v_n(t) = ?$ if $i_L(0) = 10 \text{ mA}$

$$\text{KCL} \rightarrow 99 i'_L = i'_L + \frac{v}{100} = i'_L + \frac{L}{100} \frac{di_L}{dt}$$

$$\therefore \frac{2 \times 10^{-3}}{100} \frac{di_L}{dt} - 98 i'_L = 0$$


Assume $i'_L(t) = I_0 e^{st}$

$$\Rightarrow 20 \times 10^{-6} s - 98 = 0 \Rightarrow s = 4.9 \times 10^6 / \text{s}$$

$$\therefore i'_L(t) = I_0 e^{4.9 \times 10^6 t}, \quad i'_L(0) = 10^{-2} = I_0$$

$$\therefore i'_L(t) = 10^{-2} e^{4.9 \times 10^6 t}, \quad v_n(t) = L \frac{di_L}{dt} = 2 \times 10^{-3} \times 10^{-2} \times 4.9 \times 10^6 e^{4.9 \times 10^6 t}$$
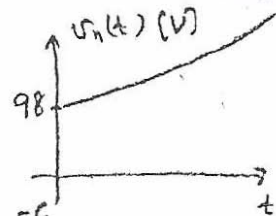
$$v_n(t) = 98 e^{4.9 \times 10^6 t} \text{ V} \quad = 98 e^{\frac{t}{\tau}} \text{ V}$$



(b) $\tau = \frac{1}{4.9 \times 10^6}, \quad t_1 = 5\tau = \frac{5}{4.9 \times 10^6} = 1.02 \times 10^{-6} \text{ s}$


$$\therefore v_n(t_1) = 98 e^5 = 14544.5 \text{ V}$$

4-13
217

$$v(t) = 12 \text{ V}, \quad t < 0$$

$$= 6 \cos t, \quad t \geq 0$$
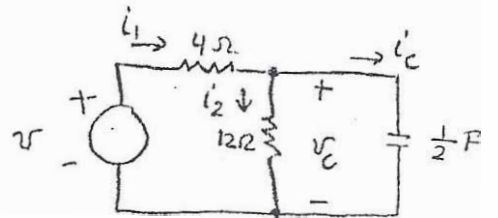
$$v_c(0^+), i_c(0^+), \frac{dv_c}{dt}(0^+) \text{ \& } \frac{di_c}{dt}(0^+) = ?$$



For $t < 0$, $i_c(0^-) = 0$ (open ckt for dc)

$$\therefore i_1(0^-) = i_2(0^-) + i_c(0^-) = i_2(0^-) = \frac{12}{4+12} \text{ A}$$

$$\therefore v_c(0^-) = i_1(0^-)(12) = \frac{12 \times 12}{16} = 9 \text{ V}$$

From principle of continuity, $v_c(0^+) = v_c(0^-) = 9 \text{ V}$.

For $t \geq 0$

$$\text{KVL} \rightarrow v(0^+) = (4) i_1(0^+) + v_c(0^+) = 6 \Rightarrow i_1(0^+) = \frac{-3}{4} \text{ A}$$

$$\text{also KVL} \rightarrow v_c(0^+) = 9 = (12) i_2(0^+) \Rightarrow i_2(0^+) = \frac{9}{12} = 0.75 \text{ A}$$

$$\text{KCL} \rightarrow i_c(0^+) = i_1(0^+) - i_2(0^+) = -0.75 - 0.75 = -1.5 \text{ A}$$

$$i_c(0^+) = C \frac{dv_c}{dt}(0^+) \Rightarrow \frac{dv_c}{dt}(0^+) = \frac{i_c(0^+)}{C} = -3.0 \text{ V/s}$$

Converting the voltage source to current source:

$$\text{KCL} \rightarrow \frac{6}{4} \cos t = \frac{v_c}{3} + i_c$$

Differentiating $-1.5 \sin t = \frac{1}{3} \frac{dv_c}{dt} + \frac{di_c}{dt} - \frac{6}{4} \cos t$


$$\therefore \frac{di_c}{dt}(0^+) = 0 - \frac{1}{3} \frac{dv_c}{dt}(0^+) = -\frac{1}{3} \times (-3) = +1 \text{ A/s}$$

4-17
217

$$v(t) = 12 \text{ V}, t < 0$$

$$= 6 \cos t \text{ V}, t \geq 0$$

(Notice the source conversion)

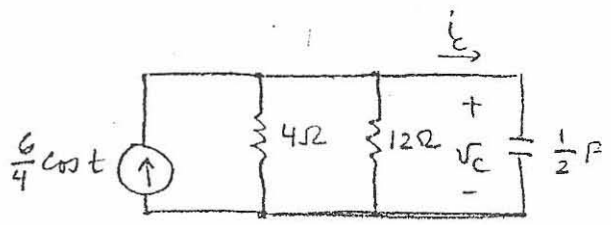

$$\text{KCL} \rightarrow \frac{6}{4} \cos t = \frac{v_c}{4//12} + i_c = \frac{v_c}{3} + C \frac{dv_c}{dt}$$

Assume $v_{c_f}(t) = A \cos t + B \sin t$

$$\therefore \frac{6}{4} \cos t = \frac{A}{3} \cos t + \frac{B}{3} \sin t + \frac{1}{2} [-A \sin t + B \cos t]$$

Comparing terms:

$$\frac{6}{4} = \frac{A}{3} + \frac{B}{2} \quad \& \quad 0 = \frac{B}{3} - \frac{A}{2}$$

$$\Rightarrow A = \frac{18}{13} \quad \& \quad B = \frac{27}{13}$$

$$v_{c_n}(t) = k e^{-t/\tau} \quad \tau = RC = (4//12) \left(\frac{1}{2}\right) = \frac{3}{2} \text{ sec}$$

$$\therefore v_c(t) = v_{c_n}(t) + v_{c_f}(t) = k e^{-\frac{2t}{3}} + \frac{18}{13} \cos t + \frac{27}{13} \sin t$$

from problem (4-13), $v_c(0) = 9$

$$\therefore 9 = k + \frac{18}{13} + 0 \Rightarrow k = \frac{99}{13}$$


$$\therefore v_c(t) = \frac{9}{13} \left[11 e^{-\frac{2}{3}t} + 2 \cos t + 3 \sin t \right] \text{ V}$$

$$i_c(t) = C \frac{dv_c}{dt} = \frac{1}{2} \times \frac{9}{13} \left[-\frac{22}{3} e^{-\frac{2}{3}t} - 2 \sin t + 3 \cos t \right]$$

$$i_c(t) = \frac{9}{26} \left[3 \cos t - 2 \sin t - \frac{22}{3} e^{-\frac{2}{3}t} \right] \text{ A}$$

4-19 / 217

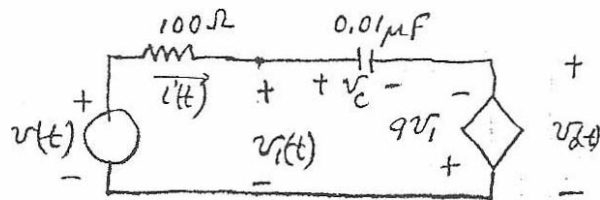(a) $v(t) = 0$, $t < 0$
 $= 0.2t$, $t > 0$
 $v_o(t) = ?$ $t > 0$



KVL $\rightarrow 10^{-5} \frac{dv_c}{dt} + v_c = 10$ [see soln of problem 4-4]

Forced response

Assume $v_{cf}(t) = V_1 t + V_0$

$\therefore (10^{-5} V_1) + (V_1 t + V_0) = 10(0.2t)$

Comparing terms: $10^{-5} V_1 + V_0 = 0$ & $V_1 = 2$ V

$\therefore V_0 = -10^{-5} V_1 = -2 \times 10^{-5}$ V

$\therefore v_{cf}(t) = 2t - 2 \times 10^{-5}$ V

Natural Response

$v_{cn}(t) = k e^{st} \rightarrow 10^{-5}s + 1 = 0 \Rightarrow s = -10^5$ V/s

$\therefore v_c(t) = v_{cn}(t) + v_{cf}(t) = k e^{-10^5 t} + 2t - 2 \times 10^{-5}$

Since $v(t) = 0$, $t < 0 \Rightarrow v_c(0^-) = v_c(0^+) = 0$

$0 = k + 0 - 2 \times 10^{-5} \Rightarrow k = 2 \times 10^{-5}$

$\therefore v_c(t) = 2 \times 10^{-5} (e^{-10^5 t} - 1) + 2t$, V

$i(t) = i_c(t) = C \frac{dv_c}{dt} = 10^{-8} [2 + 2 \times 10^{-5} \times (-10^5 e^{-10^5 t} - 0)]$
 $= 2 \times 10^{-8} (1 - e^{-10^5 t})$, A

$v_o(t) = -9v_1(t) = -9(v(t) - 100i(t)) = -1.8t + 1.8 \times 10^{-5} (1 - e^{-10^5 t})$ V

(b) $v(t) = 0$, $t < 0$ & $v(t) = 0.2e^{-10^5 t} \cos 10^5 t$, $t > 0$

From problem (4-4) , $v_{cf}(t) = 2e^{-10^5 t} \sin 10^5 t$ V

$\therefore v_c(t) = v_{cn}(t) + v_{cf}(t) = k e^{-10^5 t} + 2e^{-10^5 t} \sin 10^5 t$

Assume $v_c(0) = 0$ [uncharged capacitor] $\Rightarrow k = 0$

$\therefore v_c(t) = v_{cf}(t) = 2e^{-10^5 t} \sin 10^5 t$


$i(t) = i_c(t) = C \frac{dv_c}{dt} = 2 \times 10^{-3} e^{-10^5 t} (\cos 10^5 t - \sin 10^5 t)$

$\therefore v_o(t) = -9v_1(t) = -9(v(t) - 100i(t)) = -1.8e^{-10^5 t} \sin 10^5 t$, V

$$\frac{4-21}{217}$$

S is open for long time till closed at $t=0$ sec.

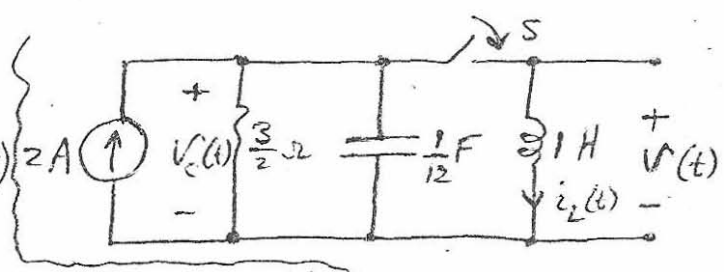∴ $V_c(0^-) = 2 \times \frac{3}{2} = 3 \text{ Volts} = V_c(0^+)$
 ∴ $i_L(0^-) = 0 \text{ Amp} \therefore V(0^-) = 0 \text{ V}$
 For $t > 0$ ∴ $V_c(t) = V(t) = V_n(t) + V_{ss}(t)$



∴ $V_n(t) \left(\frac{3}{2} \right) + \frac{1}{12} \dot{V}(t) + \frac{1}{1} \int V(t) dt = 0$

∴ $V_n + 8V_n + 12V_n = 0 \Rightarrow m^2 + 8m + 12 = 0$
 ∴ $(m+6)(m+2) = 0 \therefore m = -6 \text{ or } -2$

∴ $V_n(t) = Ae^{-6t} + Be^{-2t}$
 ∴ $V_{ss}(t) = 0$

∴ $V(t) = V_n(t) + V_{ss}(t) = Ae^{-6t} + Be^{-2t}, V$

∴ $V(0^+) = V_c(0^+) = 3 \text{ Volts} \therefore A+B = 3 \quad (1)$

∴ $i_L(t) = 2 - V(t) \left(\frac{3}{2} \right) - \frac{1}{12} \dot{V}(t)$
 $= 2 - \frac{3}{2}(Ae^{-6t} + Be^{-2t}) + \frac{1}{12}(3Ae^{-6t} + Be^{-2t})$

∴ $i_L(0^+) = 2 - \frac{3}{2}(A+B) + \frac{1}{6}(3A+B) = i_L(0^-) = 0$
 ∴ $12 - 8(A+B) + 2(3A+B) = 0 \Rightarrow 2A + 6B = 12$

∴ $A + 3B = 6 \quad (2)$

∴ $(2) - (1) \Rightarrow 2B = 3 \therefore B = \frac{3}{2}$

into (1) $\Rightarrow A = 3 - B = 3 - \frac{3}{2} = \frac{3}{2}$


∴ $V(t) = \frac{3}{2}(e^{-6t} + e^{-2t}), V$

Note:

$V(t < 0) = 0, V(0^+) = 3 \text{ V} \neq V(\infty) = 0$

∴ $V'(t) = -9e^{-6t} - 3e^{-2t} \therefore V'(0^+) = -12 \text{ V/s}$

∴ Plot of $V(t)$ is as shown here.

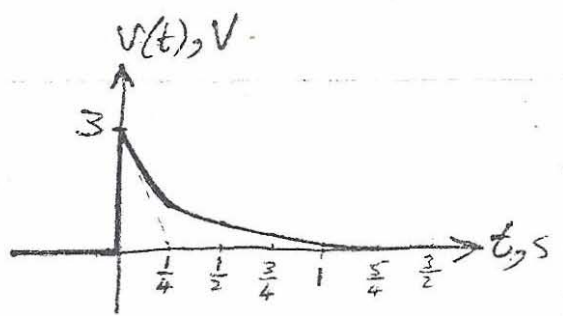

To find $i(t)$ for the given circuit and input;

$$\therefore i(t < 1) = 0 \text{ A.p}$$

$$\text{f } i(1^-) = i(1^+) = 0 \text{ A.p}$$

$$\therefore i(t \in [1, 2] \text{ sec}) = \frac{12}{1/2} + Ae^{-tR/L}$$

$$\therefore 0 = i(1^+) = 24 + Ae^{-1 \cdot 1/2 / 1}$$

$$\therefore A = -24e^{1/2}$$

$$\therefore i(t \in [1, 2] \text{ sec}) = 24(1 - e^{-(t-1)/2}) \text{ A.p}$$

$$\therefore i(2^-) = i(2^+) = 24(1 - e^{-1/2}) = 9.4434 \text{ A.p}$$



$$\therefore i(t \in [2, \infty) \text{ sec}) = \frac{0}{R} + Be^{-tR/L}$$

$$\therefore 9.4434 \text{ A.p} = i(2^+) = \frac{0}{1/2} + Be^{-2 \cdot 1/2 / 1} = 0 + Be^{-1} = Be^{-1}$$

$$\therefore B = 9.4434 e, \text{ A.p}$$

$$\therefore i(t \in [2, \infty) \text{ sec}) = 9.4434 e^{-(t-2)/2} \text{ A.p} \quad [\text{Note: } i(\infty) = 0^{\text{A}}]$$


The sketch is as shown above.

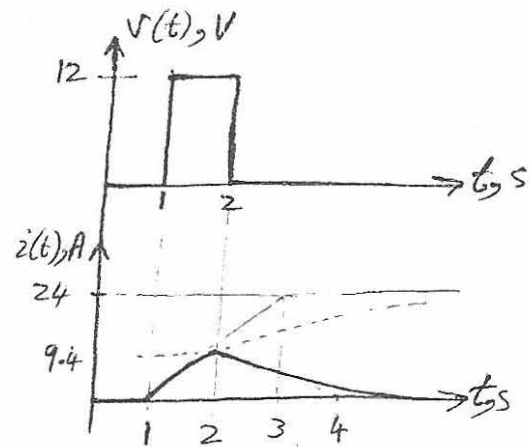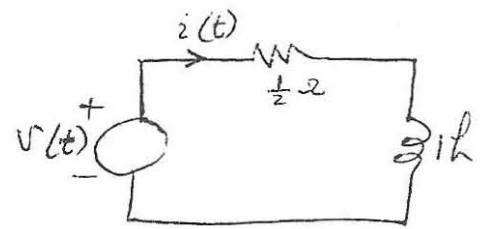


To find $Z(s)$ of the given circuit, obtain the source voltage V in terms of supplied current I .

$$\therefore V = IR + sL(I + I) = I(R + 2sL)$$
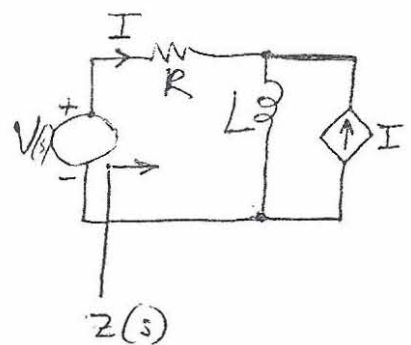
$$\therefore Z(s) = \frac{V(s)}{I(s)} = R + 2sL.$$


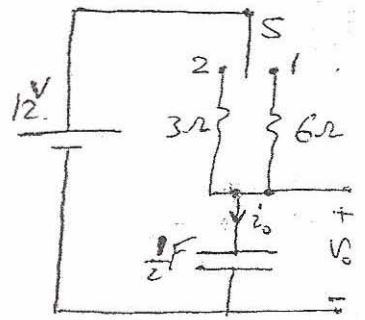
#) $V_o(t < 0) = 0$
 $V_o(t \in [0, 1]s) = 12(1 - e^{-t/RC}) = 12(1 - e^{-t/3})$, V & $i_o(t \in (0, 1)s) = 2e^{-t/3}$ A
 $\therefore V_o(1) = 12(1 - e^{-1/3}) = 3.4016$ Volts
 $\therefore V_o(t \in [1, \infty)) = 12 + Ae^{-t/1.5}$
 $\therefore V_o(1) = 3.4016 = 12 + Ae^{-1/1.5}$
 $\therefore A = (3.4016 - 12)e^{1/1.5} = -8.5984 e^{1/1.5}$ Volts
 $\therefore V_o(t \in [1, \infty)) = 12 - 8.5984 e^{-(t-1)/1.5}$, Volts
& $i_o(t \in (1, \infty)sec) = C \frac{dV_o}{dt} = 2.8661 e^{-(t-1)/1.5}$, Amp



a) \therefore at $t = 0^-$ s : $i_{6\Omega} = 0$ A, $V_{6\Omega} = 0$ V, $i_{3\Omega} = 0$ A, $V_{3\Omega} = 0$ V, $i_C = 0$ A & $V_C = 0$ V
& at $t = 0^+$ s : $i_{6\Omega} = 2$ A, $V_{6\Omega} = 12$ V, $i_{3\Omega} = 0$ A, $V_{3\Omega} = 0$ V, $i_C = 2$ A & $V_C = 0$ V
& at $t = 1^-$ s : $i_{6\Omega} = 1.433$ A, $V_{6\Omega} = 8.598$ V, $i_{3\Omega} = 0$ A, $V_{3\Omega} = 0$ V, $i_C = 1.433$ A & $V_C = 3.402$ V
& at $t = 1^+$ s : $i_{6\Omega} = 0$ A, $V_{6\Omega} = 0$ V, $i_{3\Omega} = 2.866$ A, $V_{3\Omega} = 8.598$ V, $i_C = 2.866$ A & $V_C = 3.402$ V

b) $V(t) = \begin{cases} 0 \text{ V} & \text{for } t < 0 \text{ sec} \\ 12(1 - e^{-t/3}), \text{ V} & \text{for } t \in [0, 1] \text{ sec} \\ 12 - 8.5984e^{-(t-1)/1.5}, \text{ V} & \text{for } t > 1 \text{ sec} \end{cases}$

c) The sketch is as shown here.

Note:

A corner in $V_o(t)$ plot, corresponds to a spike in $i_o(t)$ plot. This is because $i_o(t)$ is a derivative of $V_o(t)$ and at the corner of $V_o(t)$ there is a change of slope.

