

بسم الله الرحمن الرحيم

الحلول المختارة لطلاب الهندسة والعمارة

تحليل دوائر (٢)

إعداد

سلمان محمد القاسمي

الأستاذ المشارك بقسم الهندسة الكهربائية والحاسبات

بجامعة أم القرى

الطبعة الثانية

رمضان ١٤٢٢هـ - تشرين ثان ٢٠٠١


تمهيد

الحمد لله رب العالمين، والصلاة والسلام على سيد المرسلين، وعلى آله وصحبه أجمعين، وبعد: فهذه مجموعة من المسائل المحولة في مادة تحليل دوائر (٢) (EE302) لطلبة قسم الهندسة الكهربائية بكلية الهندسة والعمارة الإسلامية بجامعة أم القرى، في طبعتها الثانية، حيث أُضيف إلى طبعتها الأولى ما تحصل لدي من أعمال خلال الفترة بين الطبعتين،

وإنني إذ أشكر للطلاب التالية أسماؤهم:

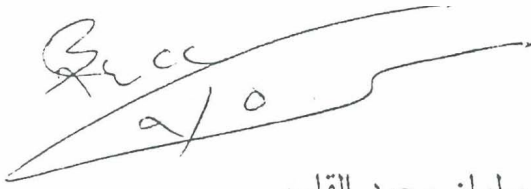- (١) فواز إبراهيم أحمد الزايدي (٤١٨٠٢٣٥٦)،
- (٢) موسى حسن عوض القثامي (٤١٨٠٢٥٥٠)،
- (٣) نزار حسين عبدالله بانبيلة (٤١٨٠٠٥٢٨)،

إذ أشكر لهم مساعدتي في تبويب مسائل الطبعتين كليهما وفهرستها، لتسهيل المراجعة فيها، وتعم الفائدة منها، لأسأل الله عز وجل أن ينفع بهذا العمل كل من يطالعه، وأن لا يحرمني ومن أعانني من مثوبته إنه سميع مجيب.



سلمان محمد القاسمي

في الثلاثاء: ١٤٢٢/٩/٥ هـ - ٢٠٠١/١١/٢٠ م

الفهرس

الصفحة	موضوعه	الباب
١	مراجعة تحليل دوائر ١	الأول
٣	دوائر الدرجة الأولى	الثاني
٨	دوائر الدرجة الثانية	الثالث
١٤	الربح والطور في دوائر المصافي	الرابع
١٩	دوائر ذوات المدخلين	الخامس
٢٣	لابلاس	السادس
٢٥	النبضات والصعقات	السابع
٣٠	المحولات والتحريض التبادلي	الثامن
٣٤	دوائر القدرة أحادية الطور	التاسع
٣٥	دوائر القدرة ثلاثية الطور	العاشر

To find currents & voltages in every branch of the shown network:

Results should be as follows:

$$I_{2\Omega} = 1 \text{ Aps } (\downarrow)$$

$$V_{2\Omega} = 2 \text{ Volts } (-)$$

$$I_{1.5\Omega} = 2 \text{ Aps } (\uparrow)$$

$$V_{1.5\Omega} = 3 \text{ Volts } (-)$$


$$I_{10V} = 1 \text{ Aps } (\leftarrow)$$

$$V_{4\Omega} = 12 \text{ Volts } (+) = V_{4A}$$

$$I_{4\Omega} = 3 \text{ Aps } (\downarrow)$$


$$I = 2 \text{ Aps } (\leftarrow) = I_{6V}$$

$$V_{3\Omega} = 6 \text{ Volts } (-)$$

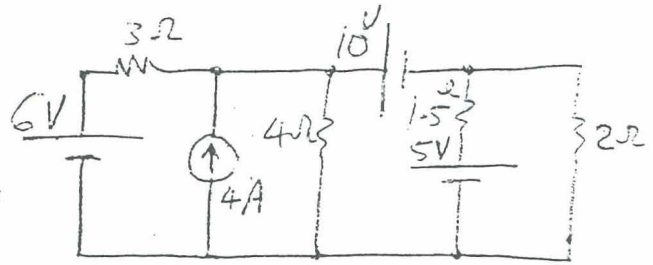


↓


To Check

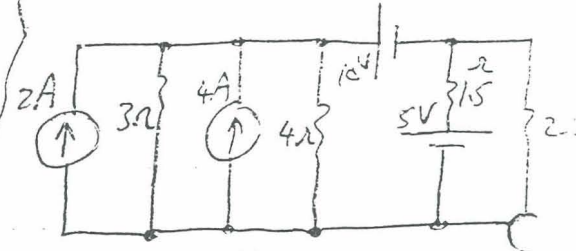


↓

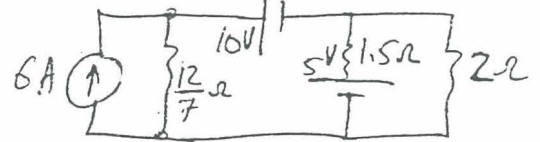


↓

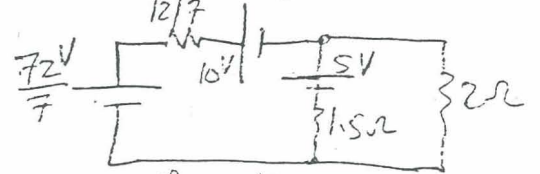


↓

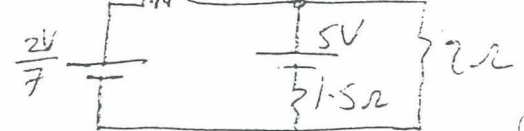

↓

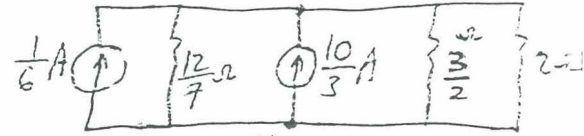


↓

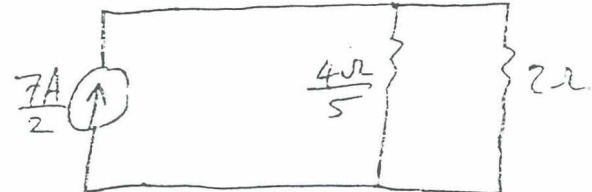

$$\therefore V_{2\Omega} = 2 * \frac{7}{2} * \frac{4/5}{2+4/5} = 2V$$
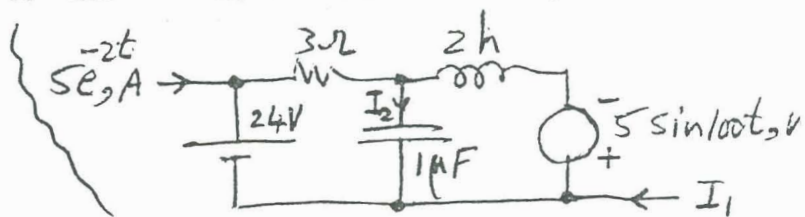
#


To find I_1 & I_2 of the shown circuit, the whole circuit could be considered as a junction where KCL gives $I_1 = -5e^{-2t}$, A.



As for I_2 , it can be obtained using superposition as:


$$I_2 = I_2|_{24V} + I_2|_{5e^{-2t}A} + I_2|_{5\sin(100t)V}$$

For $I_2|_{24V}$, circuit looks like:

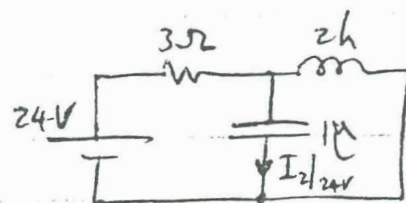


$I_2|_{24V} = 0$, since no dc current through C.

For $I_2|_{5e^{-2t}A}$, circuit looks like:

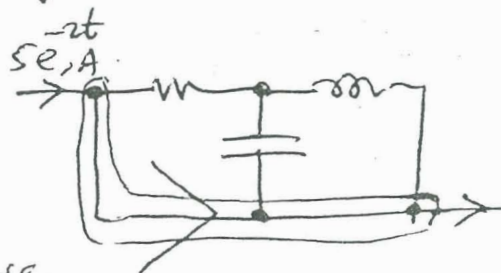

$I_2|_{5e^{-2t}A} = 0$, since there is other path with zero impedance.

For $I_2|_{5\sin(100t)V}$, circuit looks like:

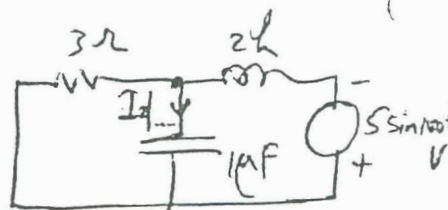


$$I_2|_{5\sin(100t)V} = \frac{-5 \angle 0}{(3 \parallel \frac{1}{j100}) + j100(2)} \cdot \frac{3}{3 + \frac{1}{j100(1\mu)}} =$$

$$= \frac{-15}{1 + j300\mu} \cdot \frac{1}{3 - j10K} = \frac{-15}{2000K} = -7.5 \mu A$$

$$I_2 = 0 + 0 + (-7.5 \mu A \sin 100t) = -7.5 \mu A \sin 100t.$$

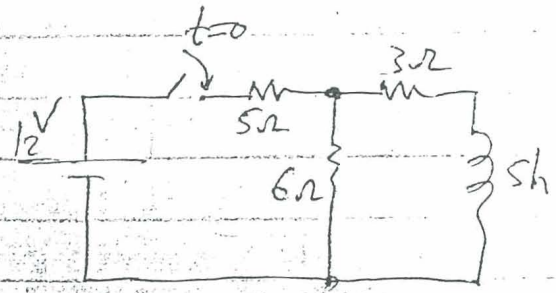For the shown circuit, the initial inductor current is zero.



$$\therefore i_{5\Omega}(0^+) = i_{6\Omega}(0^+) = \frac{12}{11} \text{ Amp}$$

$$\& i_{3\Omega}(0^+) = i_{sh}(0^+) = 0 \text{ Amp}$$

$$\& V_{sh}(0^+) = V_{6\Omega}(0^+) = 12 \cdot \frac{6}{11} = \frac{72}{11} \text{ Volts}$$

$$\therefore i'_{3\Omega}(0^+) = i'_{sh}(0^+) = \frac{V_{sh}(0^+)}{5} = \frac{72}{11(5)} = \frac{72}{55} \text{ Amp/sec}$$

$$\& (12)' = 5 i'_{5\Omega}(0^+) + 6 i'_{6\Omega}(0^+) \Rightarrow i'_{5\Omega}(0^+) = \frac{-6}{5} i'_{6\Omega}(0^+) \quad \text{--- (1)}$$

$$\& i'_{5\Omega}(0^+) = i'_{6\Omega}(0^+) + i'_{3\Omega}(0^+) \rightarrow \text{(2)} \quad \text{Solving (1) \& (2)}$$

$$\therefore \frac{-6}{5} i'_{6\Omega}(0^+) = i'_{6\Omega}(0^+) + \frac{72}{55} \Rightarrow i'_{6\Omega}(0^+) = \frac{-72}{121} \text{ Amp/sec}$$

$$\therefore i'_{5\Omega}(0^+) = \frac{432}{605} \text{ Amp/sec}$$

& The time constant of the circuit is $\tau = L / \text{resistance seen by } L$

$$= \frac{L}{5 \parallel 6 + 3} = \frac{5}{\frac{30}{11} + 3} = \frac{55}{63} \text{ sec}$$

& At steady state:

$$i_{5\Omega} = \frac{12}{5 + 6 \parallel 3} = \frac{12}{5 + \frac{18}{9}} = \frac{12}{7} \text{ Amps}$$


$$\& i_{6\Omega} = i_{5\Omega} \cdot \frac{3}{6+3} = \frac{12}{7} \cdot \frac{1}{3} = \frac{4}{7} \text{ Amps}$$

$$\& i_{3\Omega} = \frac{8}{7} \text{ Amps}$$

To solve at $t=0^+$ for

i_1' , i_2' , V_1'' & V_2''' of the shown circuit,

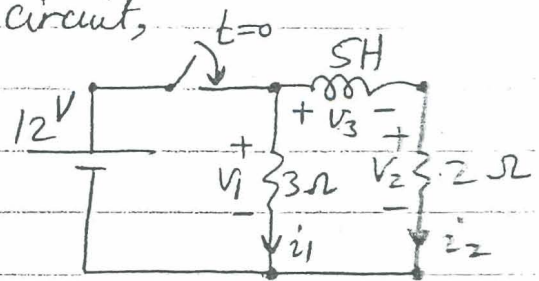a) $\therefore i_1'(0^+) = 12/3 = 4 \text{ Aps}$,
 $i_2'(0^+) = 12/5 = 2.4 \text{ Ap/sec}$,
 $V_1''(0^+) = (12)'' = 0$



$V_2'''(0^+) = 2 i_2'''(0^+) = \frac{2}{5} V_3''(0^+)$.

But $12 = V_3 + 2 i_2 \quad \therefore V_3' = -2 i_2' = -V_2'$

$\therefore V_2'''(0^+) = \frac{2}{5} (-2 i_2')' = -\frac{4}{5} \cdot i_2'' = -\frac{4}{5} \cdot V_3' = \frac{8}{25} i_2'(0^+) = \frac{8}{25} \cdot \frac{12}{5} = \frac{96}{125} = 0.768 \text{ V/s}^3$

(OR: $V_2 = 12(1 - \exp(-0.4t)) \therefore V_2'''(0^+) = 12(0.4)^3 = 0.768 \text{ V/s}^3$)

b) At steady state:


$\therefore i_1 = \text{as before unaffected} = 4 \text{ Ap}$,

$i_2 = 12/2 = 6 \text{ Aps}$,

$V_1 = \text{unaffected } 12 \text{ Volts}$ \neq


$V_2' = 0$

For the
Circuit

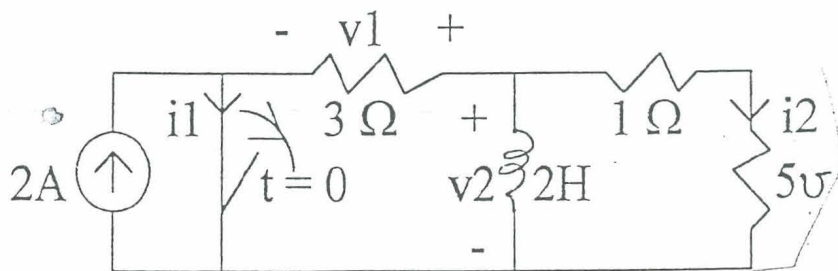

Shows,

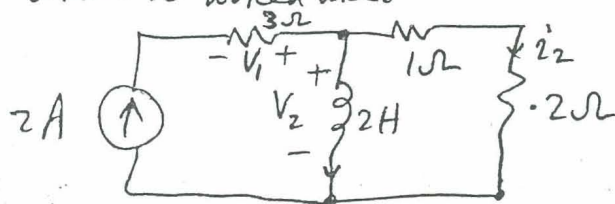- ∴ Circuit was longly having switch on,
- ∴ It was dead component-wise; till $t=0^+$, where it looked like:



- ∴ $i_1(0^+) = 0$,
- ∴ $i_2(0^+) = 2 \text{ Amp}$, giving $V_2(0^+) = 2 \cdot 4 \text{ Volts}$
- $V_1 = -3 \times 2 = -6 \text{ Volts}$ all time $\therefore V_1'(0^+) = 0$

The Circuit time constant is $\frac{2}{1.2} = \frac{5}{3} \text{ sec}$

i_2 will decay from 2 Amps at $t=0^+$ to 0 Amps at $t=\infty \therefore i_2(t) = 2e^{-.6t}$, Amps

∴ $i_2''(0^+) = 2 \times (-.6)^2 = 2 \times .36 = .72 \text{ A/s}^2$


At $t=\infty$; $V_1 =$ as before -6 Volts

∴ $V_2(\infty) = 0$ (s/c),

∴ $i_2(\infty) = 0$, shated by L;

For the shown circuit, the switch was opened for long time,

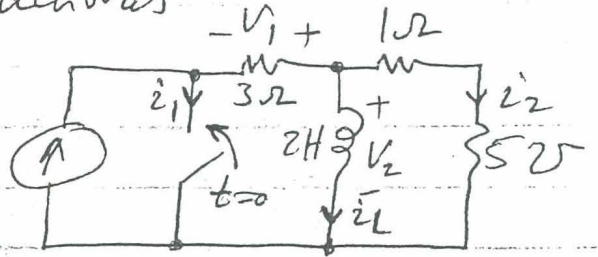
∴ $i_L(0^-) = 2 \text{ Aps} = i_L'(0^+)$ 2A



After the switch is closed at $t \geq 0^+$ the circuit looks like:

∴ i_L will see $3 \parallel 1.2 \Omega = \frac{3 \times 1.2}{4.2} = \frac{6}{7} \Omega$, with no supply.

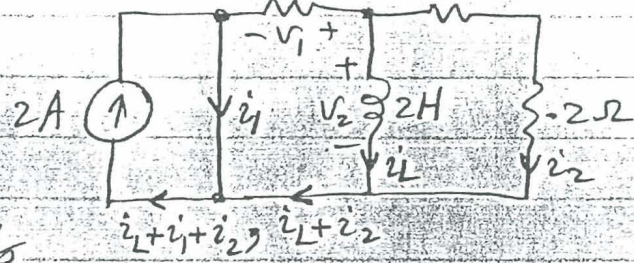(∴ $i_L(t) = 2 e^{-\frac{t}{2/(6/7)}} = 2 e^{-\frac{6t}{14}}$, Aps
 $= 2 e^{-3t/7}$, Aps



∴ $V_2(t) = 2 i_L' = 4 \times \left(-\frac{3}{7}\right) e^{-3t/7}$, Volts
 $= -\frac{12}{7} \cdot e^{-3t/7}$, Volts.

∴ $i_2(t) = \frac{V_2}{1.2} = -\frac{10}{7} e^{-3t/7}$, Aps

∴ $i_1(t) = 2 - i_L - i_2 = 2 - 2 e^{-3t/7} + \frac{10}{7} e^{-3t/7} = 2 - \frac{4}{7} e^{-3t/7}$, Aps

(∴ $V_1(t) = -3(i_L + i_2) = -3\left(2 e^{-3t/7} - \frac{10}{7} e^{-3t/7}\right) = -\frac{12}{7} e^{-3t/7}$, Volts

Note: after $t=0$ $V_1 = V_2$ as they are parallel.

∴ $i_1(0^+) = 2 - \frac{4}{7} = \frac{10}{7}$ Aps

$i_2'(0^+) = -\frac{10}{7} \times \left(-\frac{3}{7}\right) = \frac{30}{49}$ Aps/sec


$V_1''(0^+) = -\frac{12}{7} \times \left(-\frac{3}{7}\right)^2 = \frac{-108}{343}$ Volt/sec²

$V_2'''(0^+) = -\frac{12}{7} \left(-\frac{3}{7}\right)^3 = \frac{324}{2401}$ Volts/sec³.

6

(# At steadystate when $t = \infty$: $i_1 = 2 \text{ Aps}$ & $i_2 = V_1 = V_2 = 0$

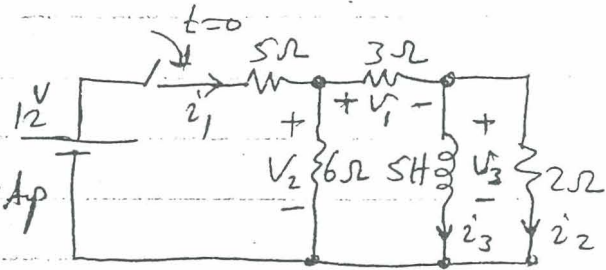To find the terms at $t=0^+$ of i_1, i_2, V_1 & V_2 , then:



a) $i_1(0^+) = \frac{12}{5 + 6 \parallel (2+3)} = \frac{132}{85} = 1.553 \text{ A}$

$\therefore i_2(0^+) = i_1(0^+) \cdot \frac{6}{6+(3+2)} = \frac{72}{85} = 0.847 \text{ A}$ { Switch was open for long time then put on at $t=0$.

$\therefore V_3(0^+) = 2 \cdot i_2(0^+) = \frac{144}{85} = 1.694 \text{ Volts}$ \therefore Circuit at 0^- was dead

$\therefore i_3'(0^+) = \frac{V_3(0^+)}{5} = \frac{144}{425} = 0.3388 \text{ Amp/sec}$ & $i_3(0^+) = 0 \text{ A}$.

But $12 = 5i_1 + 3(i_2 + i_3) + 2i_2 = 5i_1 + 5i_2 + 3i_3$

$\therefore 5i_1'(0^+) + 5i_2'(0^+) + 3i_3'(0^+) = 0$ (1)

& $i_1 = i_2 + i_3 + \frac{V_2}{6} \quad \therefore V_2 = 6(i_1 - i_2 - i_3)$ (2)

& $2i_2 = 5i_3 \quad \therefore i_3 = \frac{2}{5}i_2$ (3)

& $6(i_1 - i_2 - i_3) = 3(i_2 + i_3) + 2i_2 \quad \therefore 6i_1 = 11i_2 + 9i_3$ (4)

Solving (1) & (4) $\therefore 55i_2' + 45i_3' + 30i_2' + 18i_3' = 0 \quad \therefore i_2' = \frac{-63}{85}i_3'$

into (4) $\therefore 6 \times 85i_2' = -693i_3' + 765i_3' = 72i_3' \quad \therefore i_2' = \frac{12}{85}i_3'$ (5)

into (2) $\therefore V_2' = \frac{6}{85}(12 + 63 - 85)i_3' = \frac{6}{85} \times (-10)i_3' = \frac{-12}{17}i_3'$ (7)

& $V_1' = 3(i_2' + i_3') = (3/85)(-63 + 85)i_3' = \frac{3 \times 22}{85}i_3' = \frac{66}{85}i_3'$ (8)

b) $\therefore i_2''(0^+) = (\text{from (5)}) -\frac{63}{85} \times \frac{144}{425} = \frac{-9072}{36125} = -0.2511 \text{ Amp/sec}$ (9)

into (3) $\therefore i_3''(0^+) = 0.4i_2''(0^+) = -0.1005 \text{ Amp/sec}^2$ (10)

c) into (8) $\therefore V_1''(0^+) = \frac{66}{85}i_3''(0^+) = -0.07800 \text{ Volt/sec}^2$

From (3), (5) & (10) $\therefore i_3''' = -4i_2'' \quad \therefore i_3'''(0^+) = -4i_2''(0^+) = -4 \left(\frac{-63}{85} \right) \cdot i_3''(0^+)$
 $= -4 \left(\frac{-63}{85} \right) (-0.1005) = 0.02978 \text{ Amp/s}^3$

d) into (7) $\therefore V_2'''(0^+) = \left(\frac{-12}{17} \right) \times 0.02978 = -0.02102 \text{ V/s}^3$ (7)

(Note: It may be better to get $i_3(t) = \frac{12}{5+6 \parallel 3} \cdot \frac{6}{6+3} (1 - \exp[-\frac{t}{5 \parallel (5 \parallel (6+3)) \parallel 12}])$


$\therefore i_3(t) = \frac{8}{7} [1 - \exp(-126t/425)] \text{ A}$ Then $i_1(t) = [i_3 + (5i_3/2) + (3/6)] + \frac{5}{6}i_3 = 1.5i_3 + \frac{55}{12}i_3'$

$\therefore V_1'' = 3(i_3'' + \frac{55}{12}i_3''') \Big|_{0^+} = 3 \cdot \frac{8}{7} \cdot \left(\frac{126}{425} \right)^2 \left(-1 + \frac{55}{12} \cdot \frac{126}{425} \right) = -0.07800 \text{ V/s}^2 \quad \therefore \text{OK} \textcircled{C}$

& $V_2''' = 3(i_3''' + \frac{55}{12}i_3'''') + 5i_3'''' \Big|_{0^+} = \frac{8}{7} \cdot \left(\frac{126}{425} \right)^3 \left(3 - \frac{35}{2} \cdot \frac{126}{425} \right) = -0.02102 \text{ V/s}^3 \quad \therefore \text{OK} \textcircled{D}$

e) At $t=\infty \quad \therefore i_1 = \frac{12}{5+6 \parallel 3} = \frac{12}{7} = 1.714 \text{ A}, i_2 = 0 \text{ A}, V_1 = 12 \cdot \frac{6 \parallel 3}{5+6 \parallel 3} = 12 \cdot \frac{2}{7} = 3.429 \text{ Volts}$ & $V_2 = 0$.

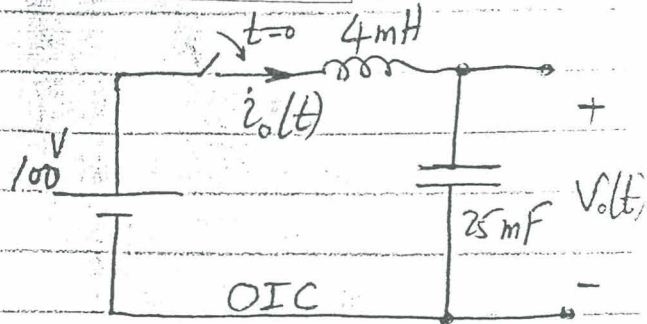a. To find first & second rates of i_o & V_o at 0^+ :



$$\therefore \dot{i}_o(0^+) = \frac{100 - 0}{4m} = 25 \text{ KA/s},$$

$$\& \dot{V}_o(0^+) = \frac{0}{25m} = 0 \text{ V/s},$$

$$\& \ddot{i}_o(0^+) = \left. \frac{(100 - V_o)'}{4m} \right|_{0^+} = \frac{-\dot{V}_o(0^+)}{4m} = 0 \text{ A/s}^2,$$

$$\& \ddot{V}_o(0^+) = \frac{\dot{i}_o(0^+)}{25m} = \frac{25K}{25m} = 1 \text{ MV/s}^2.$$

b. The circuit is in the oscillatory mode at $\text{freq} = \frac{1}{2\pi\sqrt{LC}} \Rightarrow$

Oscillation frequency is $100 \text{ rad/sec} = 15.9 \text{ Hz}$ & period = $20\pi \text{ ms}$

c. Solving the circuit $\Rightarrow 100 = 4m(25m)\ddot{V}_o + V_o = (1mD^2 + 1)V_o$

$$\therefore V_o(t) = \frac{1}{-1mD^2 + 1} \cdot (100) + A \sin 100t + B \cos 100t =$$


$$= 100 + A \sin 100t + B \cos 100t. \text{ But } V(0^+) = V(0^-) = 0 \text{ (OIC)}$$

$$\therefore V_o(t) = 100(1 - \cos 100t) + A \sin 100t. \text{ But } \dot{V}(0^+) = \frac{\dot{i}(0^+)}{25m} = \frac{\dot{i}(0^-)}{25m} = 0$$

$$\therefore A = 0 \Rightarrow V_o(t) = 100(1 - \cos 100t), \text{ Volts. Max } V_o = 200 \text{ V at } \frac{\text{odd } \pi}{100}$$

$$\therefore \dot{i}_o(t) = C \dot{V}_o(t) = 250 \sin 100t, \text{ Amp. Max } \dot{i}_o = 250 \text{ Amp at } \frac{\text{odd } \pi}{200}$$

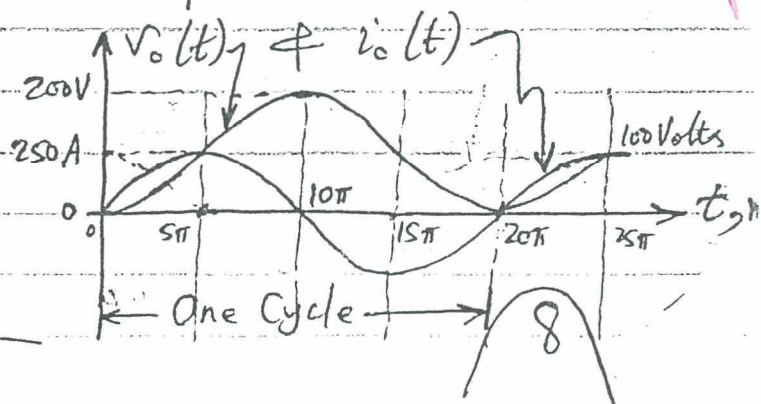d. The two responses are plotted as shown.




For the shown circuit,

$$V_c(0^-) = -50 \text{ Volts.}$$

a) To find Mode of operation:

$$(LC D^2 + RC D + 1) V_c = 0$$

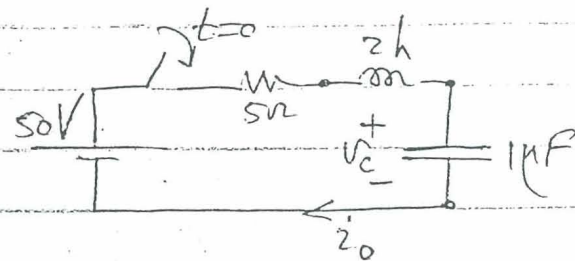

$$D = \frac{-RC \pm \sqrt{R^2 C^2 - 4LC}}{2LC} = \frac{-5 \mu \pm \sqrt{(5 \mu)^2 - 4(2)(1 \mu)}}{2(2)(1 \mu)} = \frac{-5 \pm \sqrt{25 - 8 \mu}}{4 \mu} = -1.25 \pm j 70.7 \text{ rad/s}$$

∴ Two complex roots \Rightarrow Oscillatory Mode (Underdamped)

b) Hence, $i_0(t) = (A \sin 70.7 t + B \cos 70.7 t) e^{-1.25 t}$, Amp

But $i_0(0^-) = 0$ (open circuit) $\Rightarrow B = 0$


f $V_c(0^-) = -50 \text{ V} = V_c(0^+) \Rightarrow V_L(0^+) = 100 \text{ Volts} \Rightarrow i_0'(0^+) = \frac{100}{2} = 50 \text{ A}$

∴ $50 = i_0'(0^+) = 70.7 A \Rightarrow A = \frac{50}{70.7} = 70.7 \text{ mA}$

∴ $i_0(t) = 70.7 \sin 70.7 t \cdot e^{-1.25 t}$, mA

To solve for $i(t)$:
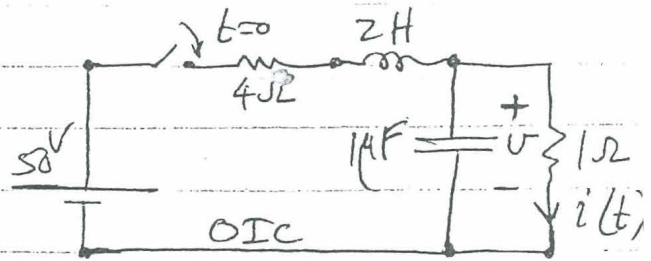
$$\begin{aligned} \infty \quad 50 &= 4(i + 1\mu V') + \\ &+ 2(i + 1\mu V') + V, \\ \text{where } i &= \frac{V}{1} = V \end{aligned}$$



$$\begin{aligned} \infty \quad 50 &= 4(V + 1\mu V') + 2(V' + 1\mu V'') + V \\ &= (2\mu D^2 + 2.000004D + 5)V. \end{aligned}$$

$$\therefore D = \frac{-2.000004 \pm \sqrt{2.000004^2 - 40\mu}}{4\mu} = -2.5, -999999.5 \approx -2.5, -1M; \text{ rad/sec}$$

$$\infty \quad V(t) = A e^{-2.5t} + B e^{-1Mt} + \frac{50}{5}$$

$$\because \text{OIC} \quad \therefore V(0) = 0 \quad \& \quad i(0) + 1\mu V'(0) = 0$$

$$\therefore A + B + 10 = 0$$

$$-2.5A - 1MB = 0 \quad \therefore A = -400,000 B$$

$$\infty \quad (1 - 400,000)B = -10 \quad \therefore B \approx 25 \mu \text{ Volt} \quad \& \quad A \approx -10 \text{ Volts}$$

$$\infty \quad V(t) = 10 - 10 e^{-2.5t} + 25 \mu e^{-1Mt}, \text{ Volts}$$

$$\infty \quad i(t) = 10 - 10 e^{-2.5t} + 25 \mu e^{-1Mt}, \text{ Amps} \approx 10(1 - e^{-2.5t}) \text{ Amp}$$

a) The circuit mode is over-damped, and it can be approximated by a first order $50\Omega - 2H$ circuit, except for that its start-off is of zero slope.

b) $\infty \quad i(t)$ is as shown


$$\infty \quad i'(t) = \text{current rise rate} =$$

$$= +25 e^{-2.5t} - 25 e^{-1Mt} \quad (\text{at } t=0, i'=0)$$


$$i' \text{ is max @ } -2.5 e^{-2.5t} + 1M e^{-1Mt} = 0 \quad \therefore 2.5 \mu \approx e^{-1Mt}$$

$$c) \therefore t = 1 \mu s \cdot \ln(400,000) = 12.9 \mu \text{ sec when } i' \text{ is at max.}$$
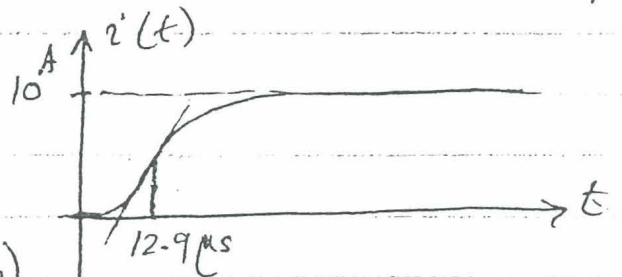
$$d) \therefore i'_{\text{max}}(12.9 \mu s) = 25 (e^{-2.5 \times 12.9 \mu} - e^{-12.9}) = 24.9991 \text{ Amp/sec}$$



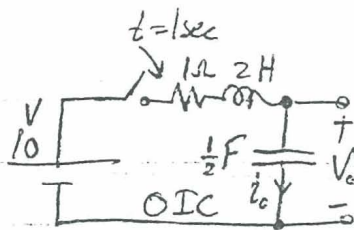To plot the responses $V_o(t)$ & $i_o(t)$ of the shown network:



$$\circ \circ V_o + 2\left(\frac{1}{2}V_o''\right) + 1\left(\frac{1}{2}V_o'\right) = 10$$

$$\circ \circ (2D^2 + D + 2)V_o = 20$$

$$\circ \circ D = \frac{-1 \pm \sqrt{1-16}}{4} = -.25 \pm j.968, \text{ rad/sec}$$

$$\circ \circ V_o(t) = 10 + e^{-.25(t-1)} \cdot [A \sin .968(t-1) + B \cos .968(t-1)]$$

$$\text{OIC} \Rightarrow B = -10 \neq A = -10 \left(\frac{.25}{.968} \right)$$

$$\circ \circ V_o(t) = 10 \left[1 - e^{-.25(t-1)} \cdot \frac{\cos .968(t-1) - \tan \left(\frac{.25}{.968} \right) \sin .968(t-1)}{\sqrt{.25^2 + .968^2}} \right]$$

$$\circ \circ V_o(t) = 10 \left[1 - 1.033 e^{-.25(t-1)} \cdot \cos \left\{ .968(t-1) + .253 \right\} \right] \text{ V}$$

$$\neq i_o(t) = 5.164 e^{-.25(t-1)} \cdot \sin \left\{ .968(t-1) \right\}, \text{ Amp.}$$

$$\circ \circ \text{Period} = \frac{2\pi}{.968} = 6.489 \text{ sec.},$$

Settlement values 10V & 0A

Maxima values are:


3.442Amps at $t = 2.622 \text{ sec}$

& 14.443Volts at $t = 4.245 \text{ sec}$

Envelope eq. is $e^{-.25(t-1)}$,


with time constant of 4sec.

These are plotted as shown.

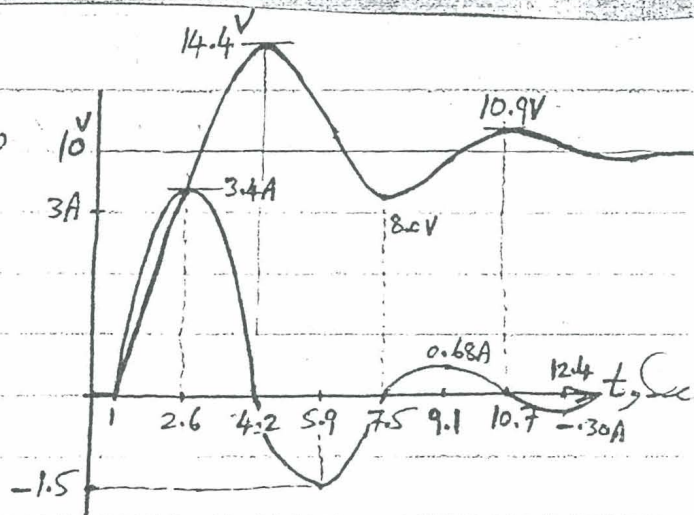

11

For the
Circuit shown:

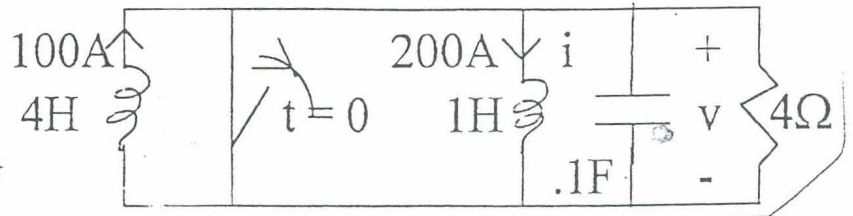

The circuit longly switched on, will have
 $V(0^-) = 0$ & the shown inductor currents. At $t=0$

$$\therefore V = 1 \cdot i' = i' \quad \& \quad V = -4 \left(i + 0.1 V' + \frac{V}{4} \right)'$$

$$= -4 i' - 0.4 V'' - V'$$

Considering i , the differential eq. is:

$$i' = -4 i' - 0.4 i''' - i'' \Rightarrow D(D^2 + 2.5D + 12.5)i = 0$$

∴ Diff. eq. order 3

But considering V , the diff. eq. is:

$$V = -4V - 0.4V'' - V' \Rightarrow (D^2 + 2.5D + 12.5)V = 0$$

the diff. eq. has been reduced to order 2,

$$\therefore D = \frac{-2.5 \pm \sqrt{6.25 - 50}}{2} = -1.25 \pm j3.31 \text{ rad/sec} \therefore \text{Voltage Under damped}$$

V will settle at 0 volts,

$$\therefore V(t) = e^{-1.25t} (A \sin 3.31t + B \cos 3.31t), \text{ Volts.}$$

putting $V(0^+) = V(0^-) = 0 \Rightarrow V(t) = A e^{-1.25t} \cdot \sin 3.31t, \text{ Volts}$

Integrating: $\therefore i = \int v dt = C + A e^{-1.25t} \cdot \frac{D+1.25}{D^2-1.25^2} \cdot \sin 3.31t$

$$\therefore i(t) = C + A e^{-1.25t} \cdot \frac{-12.5}{3.31 \cos 3.31t + 1.25 \sin 3.31t}$$


$$i(0^+) = 200 = C + A \left(\frac{3.31}{-12.5} \right) \quad \& \quad i''(0^+) = V'(0^+) = \frac{100 - 200 + 0}{1}$$

$$\therefore i''(0^+) = -1000 = A e^{-1.25(0)} \left(\frac{-1}{12.5} \right) \cdot [-3.31^3 + 1.25^2 \cdot 3.31 - 2.5 \cdot 1.25 \cdot 3.31]$$

$$\therefore A = -302.37 \text{ Volts}$$

$$\& \quad C = 120 \text{ Aps} \quad \left(\text{or equally} = \frac{100 \times 4 + 200 \times 1}{4+1} \right)$$

To solve the problem after $t=0$,

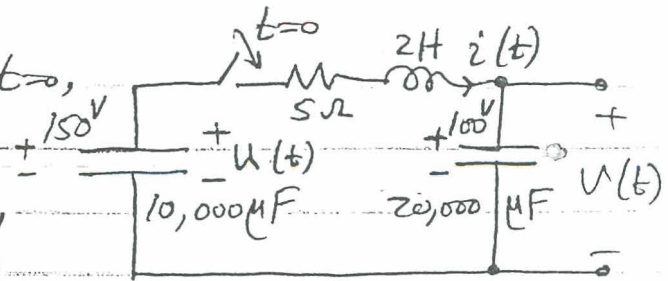

$\therefore i = .02 V'$,

$-i = .01 U' = .01 (V + 2i' + 5i)$

$\therefore -.02 V' = .01 (V' + 2 \times .02 V'' + 5 \times .02 V''')$

$\therefore 2V' + V' + .04V'' + .1V''' = 0 \Rightarrow V''' + 2.5V'' + 75V' = 0$

$\therefore (D^3 + 2.5D^2 + 75D)V = 0 \Rightarrow D(D^2 + 2.5D + 75)V = 0$

\therefore Quadratic term gives:

$D = \frac{-2.5 \pm \sqrt{6.25 - 300}}{2} = -1.25 \pm j1.25\sqrt{47} = -1.25(1 \pm j\sqrt{47})$
 $= -1.25 \pm j8.57$

$\therefore V = A + e^{-1.25t} (B_1 \sin 8.57t + B_2 \cos 8.57t)$, Volts, $t > 0$

(a) Circuit Mode is underdamped.

(b) Applying the initial conditions: $V(0^+) = 100V$, $U(0^+) = 150V + i(0^+)$

$\therefore 100 = A + B_2$ (1), $150 = 100 + 2 \times .02 V''(0^+)$ (2) $\& 0 = V'(0^+)$


But: $V'(0^+) = -1.25 B_2 + 8.57 B_1 \Rightarrow B_2 = \sqrt{47} B_1 = 6.86 B_1$ (4)

$\& V''(0^+) = -8.57^2 B_2 - 2.5 \times 8.57 B_1 + 1.25^2 B_2 \Rightarrow 800 = -46 B_2 - 2\sqrt{47} B_1$ (5)

Putting (4) in (5) $\Rightarrow 800 = -46 B_2 - 2 B_2 = -48 B_2 \Rightarrow B_2 = -800/48$


$\therefore B_1 = \frac{50}{3\sqrt{47}} = -2.43$ Volts $\& A = 100 + \frac{50}{3} = \frac{350}{3} V = -50/3$ Volts

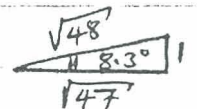$\therefore V = \frac{350}{3} + e^{-1.25t} \left(\frac{-50}{3\sqrt{47}} \sin 8.57t - \frac{50}{3} \cos 8.57t \right)$



$= \frac{50}{3} \left[7 - \frac{\sqrt{48}}{\sqrt{47}} \cdot e^{-1.25t} \cdot \left(\frac{1}{\sqrt{48}} \sin 8.57t + \frac{\sqrt{47}}{48} \cos 8.57t \right) \right]$

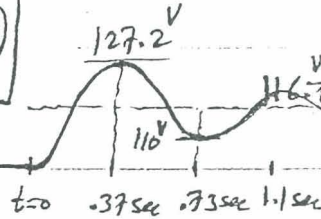$= \frac{50}{3} \left[7 - 1.01 e^{-1.25t} \cos(8.57t - 8.3^\circ) \right]$, Volts



$= 116.7 - 16.8 e^{-1.25t} \cos(8.57t - 8.3^\circ)$, Volts; plotted as shown.

(c) $\therefore i = .02 V' = +.337 e^{-1.25t} (1.25 \cos(8.57t - 8.3^\circ) + 8.57 \sin(8.57t - 8.3^\circ))$, Amps

$= \frac{20}{\sqrt{47}} e^{-1.25t} \sin 8.57t$, Amps $= 2.9173 e^{-1.25t} \sin 8.57t$, Amps.

\therefore Current rise is i'

$\therefore i' = 2.9173 e^{-1.25t} (8.57 \cos 8.57t - 1.25 \sin 8.57t) = 25.265 e^{-1.25t} \cos(8.57t + 8.3^\circ)$

This is highest when $i'' = 0 \Rightarrow 0 = -1.25 \cos(8.57t + 8.3^\circ) - 8.57 \sin(8.57t + 8.3^\circ)$


OR when $\sin 8.57t = 0 \Rightarrow t = 0$ (max) or $\frac{\pi}{8.57}$ (min)

$\therefore i'$ is max at start $\Rightarrow i$ has highest rise at start ($t=0$).

(d) $\therefore i'_{max} = i'(0) = 25$ A/sec. [Note: $(150 - 100)/2 = 50V/2H = 25$ Amp/sec]

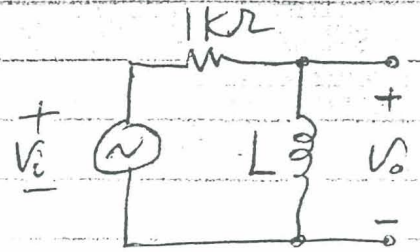a. The filter type of the circuit shown is:

High Pass with 0 gain at low frequency & Unity gain at high frequency.



b. $\left| \frac{V_o}{V_i} \right| = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}}$. Hence, corner frequency is ω_c

at $\frac{R}{\omega L} = 1$ (giving $\frac{1}{\sqrt{2}}$ gain) $\Rightarrow \omega_c = \frac{R}{L} = \frac{1k\Omega}{L}$.

Cut rate (at ω small) = cut rate of $\frac{\omega L}{R} = 20 \text{ dB/decade}$.

c. To get $f_c = 1 \text{ MHz} \Rightarrow \omega_c = 2\pi \text{ MHz} = \frac{1k\Omega}{L} \Rightarrow L = \frac{1}{2\pi \times 10^6} \text{ H} = 15.9 \mu\text{H}$

d. $\angle \frac{V_o}{V_i} = 90^\circ - \tan^{-1}\left(\frac{\omega L}{R}\right)$. Hence quadrature is obtained

between V_i & V_o at low frequency.

For the circuit shown:



a) It functions as Low Pass Filter,

b) $\frac{V_o}{V_i} = \frac{R}{R + sL} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$

c) dc gain = 1 $\equiv 0 \text{ dB}$
 hf gain = 0 $\equiv -\infty \text{ dB}$

cut-off rate @ -20 dB/decade

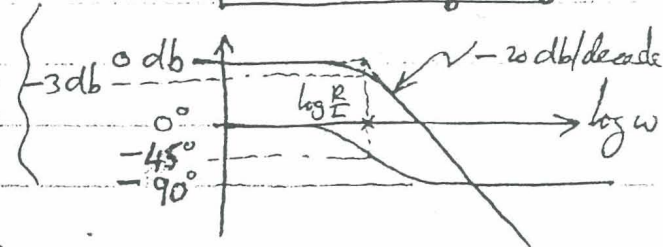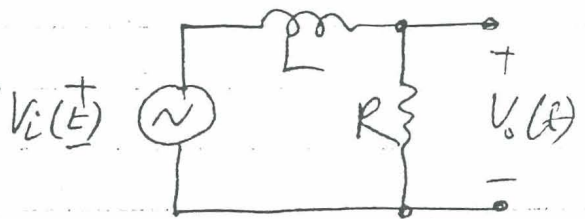d) Corner frequency = BW = $\frac{R}{2\pi L}$




For the circuit shown:

a) It functions as second-order low-pass filter,

b)
$$\frac{V_o}{V_i} = \frac{1/sC}{sL + 1/sC} = \frac{1}{1 + s^2 LC} = \frac{1}{1 - \omega^2 LC}$$

 plotted as shown:

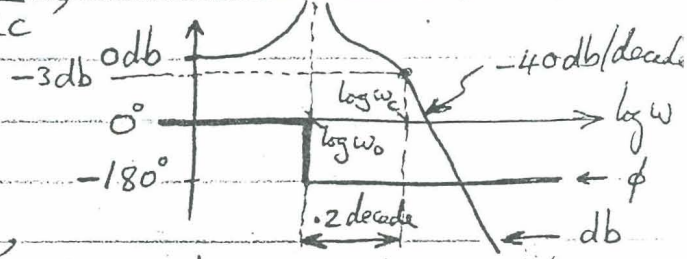
c) dc gain = 1 \equiv 0 db,
 hf gain = 0 \equiv $-\infty$ db,
 cut-off rate = -40 db/decade,




d) half-power frequency is at ω_c : $\frac{1}{\sqrt{2}} = \frac{1}{1 - \omega_c^2 LC} \rightarrow -1 + \omega_c^2 LC = \sqrt{2}$
 $\therefore \omega_c^2 LC = \sqrt{2} + 1 = 2.4142 \therefore \omega_c = 1.5538 / \sqrt{LC} = 1.5538 \omega_0$ where $\omega_0 = \frac{1}{\sqrt{LC}}$

$\therefore BW = f_c = \frac{\omega_c}{2\pi} = 0.2473 \omega_0$

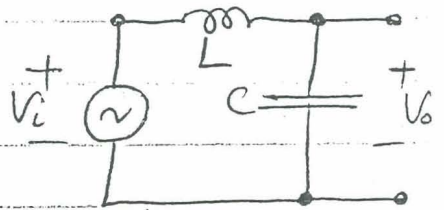e) At resonance gain goes to ∞ & ϕ reverses. This happens when $\omega = \omega_0$.



For the filter shown,

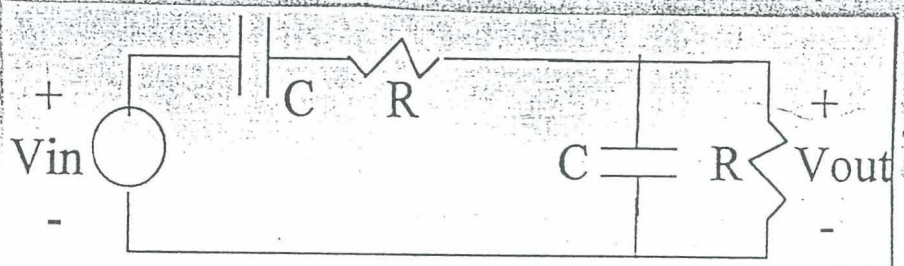

The above is a second order filter,

It blocks dc & hf signals. \therefore It is Band Pass filter,

\therefore Cutting-in rate is at 20 db/dec,

& cutting-out rate is at -20 db/dec,

dc-gain is zero,

& hf-gain is also zero,


For the circuit shown:

1. The resonant frequency is at $\omega_0 = \frac{1}{\sqrt{LC}}$

$$= \frac{1}{\sqrt{(10\text{m})(500\mu)}} \text{ rad/sec}$$

$$\therefore \omega_0 = 447.2 \text{ rad/sec}$$

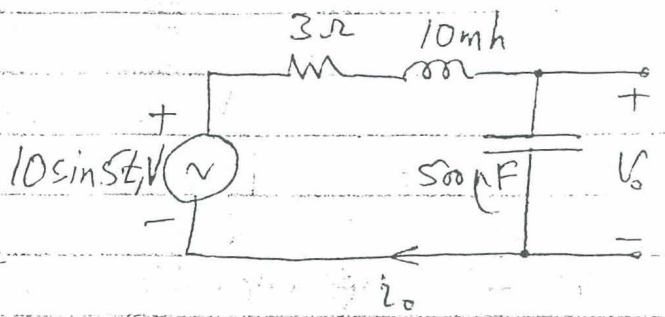Hence, the operational frequency is below resonance.



2. $i_0 = \frac{10 \angle 0^\circ}{3 + j5(10\text{m}) - j(\frac{1}{5})(\frac{1}{500\mu})} = \frac{10}{3 - j400} = .025 \angle 90^\circ \text{ A}$


\therefore 25 mA i_0 would flow at 90° lead with supply.

3. $V_0(t) \approx .025 \angle 90^\circ (-j400) \approx 10 \angle 0^\circ \approx 10 \sin 5t, \text{ Volts.}$

(circuit looks open at this frequency)

4. For V_0 to be \perp supply \therefore Supply frequency have to be equal to resonant $\Rightarrow \omega$ must equal $\omega_0 = 447.2 \text{ rad/sec.}$

For the circuit shown

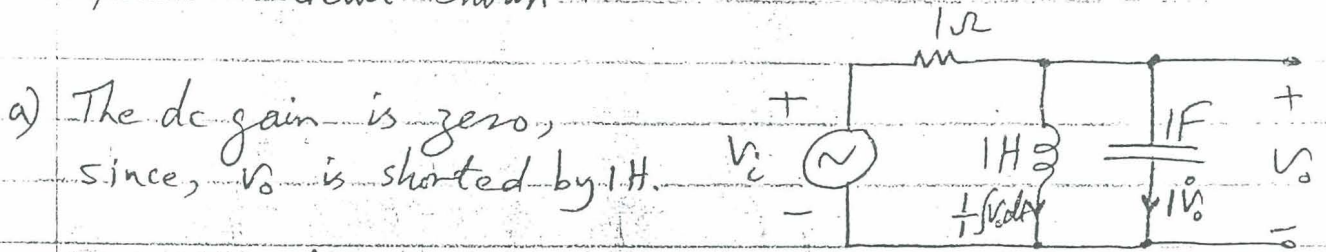

a) The dc gain is zero, since, v_o is shorted by IH.

b) The high frequency gain is zero, because v_o is shorted by IF. Hence, the network is acting as a band pass filter.

c) The differential equation is: $v_i = v_o + 1 \left(i \dot{v}_o + \frac{1}{1} \int v_o dt \right) \Rightarrow$

$$\dot{v}_i = \ddot{v}_o + \dot{v}_o + v_o \Rightarrow D v_i = (D^2 + D + 1) v_o \Rightarrow \frac{v_o}{v_i} = \frac{D}{D^2 + D + 1}$$

$$\therefore G(j\omega) = \left| \frac{v_o}{v_i} \right| = \left| \frac{j\omega}{1 - \omega^2 + j\omega} \right| = \frac{\omega}{\sqrt{(1 - \omega^2)^2 + \omega^2}}$$

Center frequency at peak gain $\Rightarrow G' = 0$

$$\therefore \frac{1}{\sqrt{(1 - \omega^2)^2 + \omega^2}} + \omega \left(-\frac{1}{2} \cdot \frac{2(1 - \omega^2)(-2\omega) + 2\omega}{[(1 - \omega^2)^2 + \omega^2]^2} \right) = 0$$

$$\therefore (1 - \omega^2)^2 + \omega^2 - \omega^2(1 - 2(1 - \omega^2)) = 0 \Rightarrow (1 - \omega^2)^2 + 2\omega^2(1 - \omega^2) = 0$$

$$\therefore (1 - \omega^2)(1 - \omega^2 + 2\omega^2) = 0 \Rightarrow (1 - \omega^2)(1 + \omega^2) = 0 \Rightarrow \omega^2 = 1 \Rightarrow \omega = 1$$

\therefore center frequency $= \omega = 1$ rad/sec

d) Hence, peak gain $= G(1) = \frac{1}{\sqrt{0^2 + 1^2}} = 1$

e) To get the quality factor, we solve $G(\omega) = \frac{G(1)}{\sqrt{2}} = \frac{1}{\sqrt{2}}$

$$\therefore \frac{\omega}{\sqrt{(1 - \omega^2)^2 + \omega^2}} = \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{1 - \omega^2}{\omega}\right)^2}} \Rightarrow \left(\frac{1 - \omega^2}{\omega}\right)^2 = 1 \quad (17)$$

$$\therefore 1 + \omega^4 - 2\omega^2 = \omega^2 \Rightarrow \omega^4 - 3\omega^2 + 1 = 0 \quad \therefore \omega^2 = \frac{3 \pm \sqrt{9 - 4}}{2} = \frac{3 \pm \sqrt{5}}{2} = \frac{3 \pm 2.236}{2}$$


$$\therefore \text{Bandwidth} = 1.618 - 0.618 = 1.000 \text{ rad/sec} \dots$$

$$\therefore \text{Quality factor} = \frac{1}{1} = 1$$

To solve the circuit opposite:

a) This circuit functions as a filter, and is categorized as:
Second order Band-pass filter.

b) Gain = $\left| \frac{V_o}{V_i}(j\omega) \right| \Rightarrow$ But

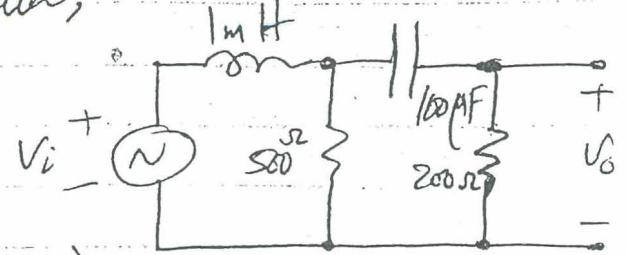

$$\frac{V_o}{V_i} = \frac{200}{200 + \frac{1}{j\omega(0.0001)}} \cdot \frac{500 \parallel \left(200 + \frac{1}{-j0.0001\omega}\right)}{0.001j\omega + \left[500 \parallel \left(200 + \frac{1}{-j0.0001\omega}\right)\right]}$$

$$= \frac{0.02j\omega}{1 + 0.02j\omega} \cdot \frac{(1 + 0.02j\omega)500}{(0.0001j\omega 500 + 1 + 0.02j\omega)(0.001j\omega) + 500(1 + 0.02j\omega)}$$

$$= \frac{j\omega 10}{(1 + j\omega(0.07)) \cdot 0.001j\omega + 500 + j\omega 10} = \frac{j\omega 10}{500 - 0.00007\omega^2 + j\omega 10.001}$$

∴ At center frequency ω_c : $500 = 0.00007\omega_c^2 \Rightarrow \omega_c = \sqrt{\frac{500}{7}} \text{ Krad/sec} = 2,673 \text{ rad/sec}$

∴ $G(\omega_c) = \frac{10}{10.001} \approx 1 = \text{peak gain}$

$$G(\omega_1, \omega_2) = \frac{1}{\sqrt{2}} = \sqrt{\frac{\omega^2 10^2}{(500 - 0.00007\omega^2)^2 + (\omega 10.001)^2}} \Rightarrow 18$$

$$200\omega_1^2 = (500 - 0.00007\omega_1^2)^2 + 100 \cdot 0.02\omega_1^2$$

$$\therefore 99.98\alpha = 250000 - 0.07\alpha + 49 \times 10^{-10}\alpha^2$$

$$\therefore 49\alpha^2 - 100.05 \times 10^{10}\alpha + 25 \times 10^{14} = 0$$


$$\therefore \alpha = \frac{100.05 \times 10^{10} \pm \sqrt{(100.05 \times 10^{10})^2 - 49 \times 10^{16}}}{98}$$

$$\therefore \alpha = \omega_1^2 = 2.042 \times 10^9 \text{ OR } 2601, \text{ rad/sec}$$

$$\therefore \omega_1 \neq \omega_2 \text{ are } 50.998 \text{ \& } 142,893 \text{ rad/sec}$$

This is plotted as shown:

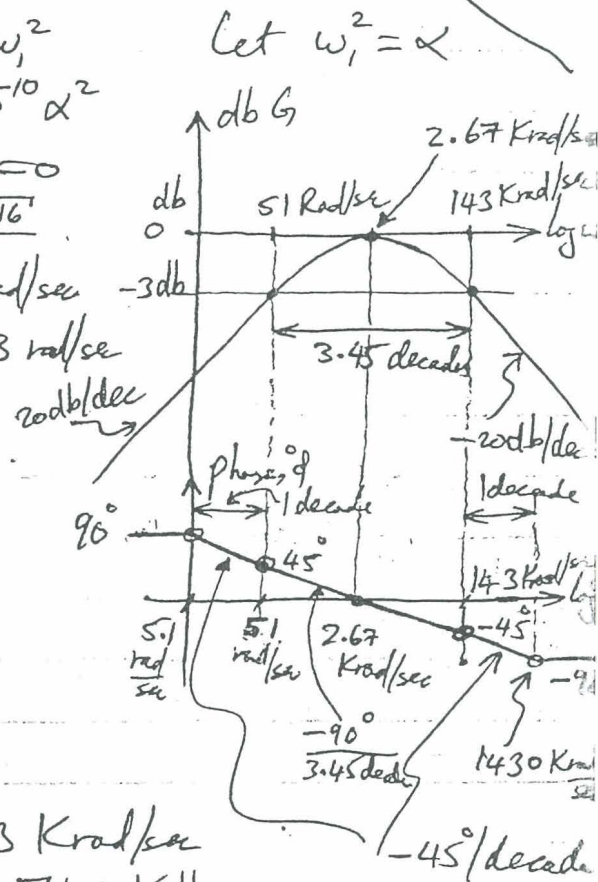c) dc gain = 0
hf gain = 0
cutting-in rate = 20db/decade
cutting-out rate = -20db/decade




d) Corner frequencies are:

$$\omega_1 = 51 \text{ rad/sec} \neq \omega_2 = 143 \text{ Krad/sec}$$

$$\text{OR } f_1 = 8.117 \text{ Hz} \neq f_2 = 22.742 \text{ KHz}$$

∴ BW = 22,742 - 8 = 22.734 KHz geometrically centered about $f_c = 425 \text{ Hz}$

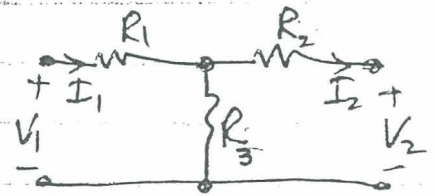To find the A matrix of the shown network, given by:




$$\begin{bmatrix} I_1 \\ V_1 \end{bmatrix} = A \begin{bmatrix} I_2 \\ V_2 \end{bmatrix} \text{ where:}$$

$$A = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix}. \quad \therefore a_{11} = \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{R_2 + R_3}{R_3} = 1 + \frac{R_2}{R_3}$$

$$a_{12} (= a_{21}) = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{R_3} \quad \& \quad a_{22} = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{R_1 + R_3}{R_3} = 1 + \frac{R_1}{R_3}$$

$$a_{21} = \left. \frac{V_1}{I_2} \right|_{V_2=0} = (-R_1 + R_2 \parallel R_3) \left(\frac{I_1}{I_2} \right) = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2 + R_3} = \frac{R_2 + R_3}{R_3} = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2 + R_3}$$

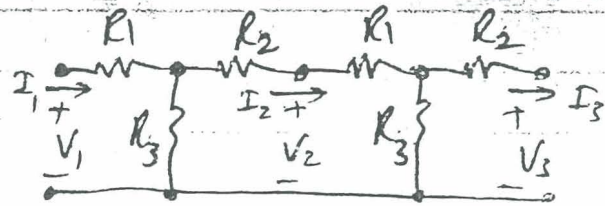Now, if two such networks are cascaded, then they can be considered as another T' as follows:



where:

$$R_4 = \frac{R_3 \cdot (R_1 + R_2)}{R_1 + 2R_3 + R_2}$$

$$\& \quad R_5 = \frac{R_3^2}{R_1 + 2R_3 + R_2}$$

New values for T' are:

$$R_1' = R_1 + R_4, \quad R_3' = R_5 \quad \& \quad R_2' = R_2 + R_4 \quad \text{Denoting:}$$

$$\begin{bmatrix} I_1 \\ V_1 \end{bmatrix} = B \begin{bmatrix} I_3 \\ V_3 \end{bmatrix}$$

$$\text{Then } B = \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \Rightarrow b_{11} = \frac{R_2' + R_3'}{R_3'}, \quad b_{12} = \frac{1}{R_3'}$$

$$b_{21} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \quad \neq b_{22} = \frac{R_1 + R_3}{R_3}$$

To check that $B = A^2$:

$$\therefore b_{11} \text{ must be } = a_{11}^2 + a_{12} a_{21}, \quad (1)$$

$$b_{12} \text{ " } = a_{12} (a_{11} + a_{22}), \quad (2)$$

$$b_{21} \text{ " } = a_{21} (a_{11} + a_{22}) \quad \neq \quad (3)$$

$$b_{22} \text{ " } = a_{12} a_{21} + a_{22}^2 \quad (4)$$

Let $\alpha = R_1/R_3$ and $\beta = R_2/R_3$

To prove (1):

$$RHS = \left(1 + \frac{R_2}{R_3}\right)^2 + \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3^2} = (1 + \beta)^2 + \alpha\beta + \beta + \alpha$$

$$LHS = \frac{R_1^2 + R_3^2}{R_3^2} = 1 + \frac{R_1 + R_3}{R_3} = 1 + \frac{R_1 + R_3 + \frac{R_1 R_2}{R_3}}{R_3} = 1 + \beta + \alpha + \frac{\alpha\beta}{R_3}$$

\therefore R.H.S of (1) = L.H.S of (1) \therefore (1) is OK, and $b_{11} = a_{11}^2 + a_{12} a_{21}$

To prove (2):

$$RHS = \frac{1}{R_3} \cdot \left(1 + \frac{R_2}{R_3} + 1 + \frac{R_1}{R_3}\right) = (2 + \alpha + \beta) / R_3$$

$$LHS = \frac{1}{R_3^2} = \frac{1}{R_5} = \frac{R_1 + 2R_3 + R_2}{R_3^2} = (2 + \alpha + \beta) / R_3$$

\therefore R.H.S of (2) = L.H.S of (2) \therefore (2) is OK $\neq b_{12} = a_{12} (a_{11} + a_{22})$

To prove (3): $RHS = (\alpha + \beta + \alpha\beta) R_3 \cdot (1 + \alpha + 1 + \beta) = (\alpha + \beta + \alpha\beta)(\alpha + \beta + 2)$

$$LHS = R_1^2 + R_2^2 + \frac{R_1 R_2}{R_3} = R_1 + R_4 + R_2 + R_4 + \frac{(R_1 + R_4)(R_2 + R_4)}{R_5} = \alpha R_3 + \beta R_3 +$$

$$+ 2 \cdot \frac{\alpha + \beta}{2 + \alpha + \beta} \cdot R_3 + \frac{\left(\alpha + \frac{\alpha + \beta}{2 + \alpha + \beta}\right) \left(\beta + \frac{\alpha + \beta}{2 + \alpha + \beta}\right)}{R_3} \cdot R_3^2 = \left[\alpha + \beta + \frac{2(\alpha + \beta)}{2 + \alpha + \beta} \right.$$

$$\left. + \alpha\beta(2 + \alpha + \beta) + \frac{(\alpha + \beta)^2}{2 + \alpha + \beta} + (\alpha + \beta)^2 \right] \cdot R_3 = R_3 \cdot \left[\alpha\beta(2 + \alpha + \beta) + \right.$$

$$\left. + \alpha + \beta + (\alpha + \beta)^2 + \frac{\alpha + \beta}{2 + \alpha + \beta} (2 + \alpha + \beta) \right] = R_3 \cdot \left[\alpha\beta(2 + \alpha + \beta) + \right.$$

$$\left. + (\alpha + \beta)(1 + \alpha + \beta + 1) \right] = R_3 \cdot (2 + \alpha + \beta)(\alpha + \beta + \alpha\beta) = RHS$$

∴ (3) is OK $\neq b_{21} = a_{21}(a_{11} + a_{22})$.

To prove, finally, (4):


$$\text{RHS} = \frac{1}{R_3} \cdot (\alpha + \beta + \alpha\beta) \cdot R_3 + (1 + \alpha)^2 = 1 + 3\alpha + \beta + \alpha\beta + \alpha^2$$

$$\begin{aligned} \text{LHS} &= \frac{R_1' + R_3'}{R_3'} = 1 + \frac{R_1 + R_4}{R_5} = 1 + \frac{(\alpha + \frac{\alpha + \beta}{2 + \alpha + \beta}) \cdot R_3}{\frac{R_3}{2 + \alpha + \beta}} = \\ &= 1 + (2 + \alpha + \beta)\alpha + \alpha + \beta = 1 + 3\alpha + \beta + \alpha\beta + \alpha^2 = \text{RHS} \end{aligned}$$

∴ (4) is OK $\neq b_{22} = a_{12}a_{21} + a_{22}^2$

∴ $B = A^2$ for the two cascaded T's.

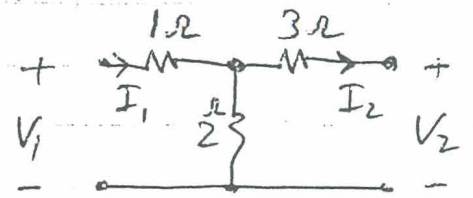To get A given as $\begin{bmatrix} I_1 \\ V_1 \end{bmatrix} = A \begin{bmatrix} I_2 \\ V_2 \end{bmatrix}$ of the network shown:



$$A = \begin{bmatrix} \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{1}{\frac{2}{2+3}} = \frac{5}{2} = 2.5 & \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{2} = 0.5 \text{ V} \\ \left. \frac{V_1}{I_2} \right|_{V_2=0} = [1 + (2 \parallel 3)] \cdot \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{11}{5} \cdot \frac{5}{2} = \frac{11}{2} = 5.5 \Omega & \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{\frac{V_2}{V_1}} = \frac{1}{\frac{2}{2+1}} = \frac{1}{\frac{2}{3}} = \frac{3}{2} = 1.5 \end{bmatrix}$$

∴ $A = \begin{bmatrix} 2.5 & 0.5 \text{ V} \\ 5.5 \Omega & 1.5 \end{bmatrix}$. For two cascaded T's, the equivalent A' matrix is given by $A' = A^2$.

$$A' = \begin{bmatrix} \frac{5}{2} & \frac{1}{2} \\ \frac{11}{2} & \frac{3}{2} \end{bmatrix} \begin{bmatrix} \frac{5}{2} & \frac{1}{2} \\ \frac{11}{2} & \frac{3}{2} \end{bmatrix} = \frac{1}{4} \begin{bmatrix} 5 & 1 \\ 11 & 3 \end{bmatrix} \begin{bmatrix} 5 & 1 \\ 11 & 3 \end{bmatrix} = \frac{1}{4} \begin{bmatrix} 36 & 8 \\ 88 & 20 \end{bmatrix} = \begin{bmatrix} 9 & 2 \text{ V} \\ 22 \Omega & 5 \end{bmatrix}$$

To find the Laplace of the given functions using rules

$$\begin{aligned} \text{a) } \therefore \alpha(t) = \cos \omega t &\Rightarrow \alpha(s) = \int_0^{\infty} e^{-st} \cos \omega t \, dt = \\ &= \frac{1}{D} e^{-st} \cos \omega t = e^{-st} \cdot \frac{1}{D-s} \cdot \cos \omega t = e^{-st} \cdot \frac{D+s}{D^2-s^2} \cdot \cos \omega t = \\ &= \frac{e^{-st}}{-\omega^2-s^2} \cdot (-\omega \sin \omega t + s \cos \omega t) \Big|_0^{\infty} = 0 + \frac{1}{s^2+\omega^2} \cdot (0+s) = \frac{s}{s^2+\omega^2} \\ \therefore \alpha(s) &= \frac{s}{s^2+\omega^2} \end{aligned}$$

$$\text{b) } \beta(t) = t \cos \omega t = t \alpha(t) = -(-t \alpha(t)).$$

$$\text{But } \mathcal{L}(-t \alpha(t)) = \frac{d}{ds} \alpha(s) = \frac{s^2+\omega^2-2s^2}{(s^2+\omega^2)^2} = -\frac{s^2-\omega^2}{(s^2+\omega^2)^2}$$

$$\therefore \beta(s) = -\left[-\frac{s^2-\omega^2}{(s^2+\omega^2)^2}\right] = \frac{s^2-\omega^2}{(s^2+\omega^2)^2}$$

$$\text{c) } \gamma(t) = (t-1) \cos \omega(t-1) = \beta(t-1).$$

$$\text{But } \mathcal{L}(\beta(t-1)) = e^{-s} \beta(s) = \frac{s^2-\omega^2}{(s^2+\omega^2)} \cdot e^{-s}$$


$$\therefore \gamma(s) = \frac{s^2-\omega^2}{s^2+\omega^2} \cdot e^{-s}$$

$$\text{d) } \delta(t) = t \cdot e^{4t} \cdot \cos \omega t = e^{4t} \cdot \beta(t).$$

$$\text{But } \mathcal{L}[e^{4t} \beta(t)] = \beta(s-4) = \frac{(s-4)^2-\omega^2}{[(s-4)^2+\omega^2]^2}$$

$$\therefore \delta(s) = \frac{(s-4)^2-\omega^2}{[(s-4)^2+\omega^2]^2}$$

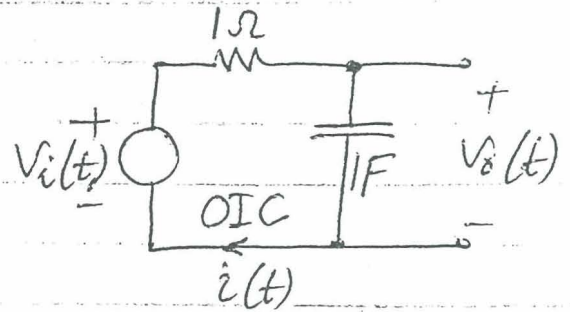
To find $V_o(t)$ by Laplace transform of the shown network for input $V_i(t)$:



$$\therefore V_i = 1 \cdot i + V_o = V_o' + V_o$$

Taking the Laplace:

$$\begin{aligned} V_i(s) &= \int_0^{10\text{m}} 100t \cdot e^{-st} dt \\ &= \int 100t \cdot d\left(\frac{e^{-st}}{-s}\right) = -100t \frac{e^{-st}}{s} \Big|_0^{10\text{m}} \\ &\quad + \int \frac{e^{-st}}{s} 100 dt = -\frac{e^{-0.01s}}{s} + \frac{100}{s} \cdot \frac{e^{-st}}{-s} \Big|_0^{10\text{m}} \\ &= -\frac{e^{-0.01s}}{s} - \frac{100}{s^2} (e^{-0.01s} - 1) = \\ &= \frac{100}{s^2} - e^{-0.01s} \left(\frac{1}{s} + \frac{100}{s^2} \right) \end{aligned}$$

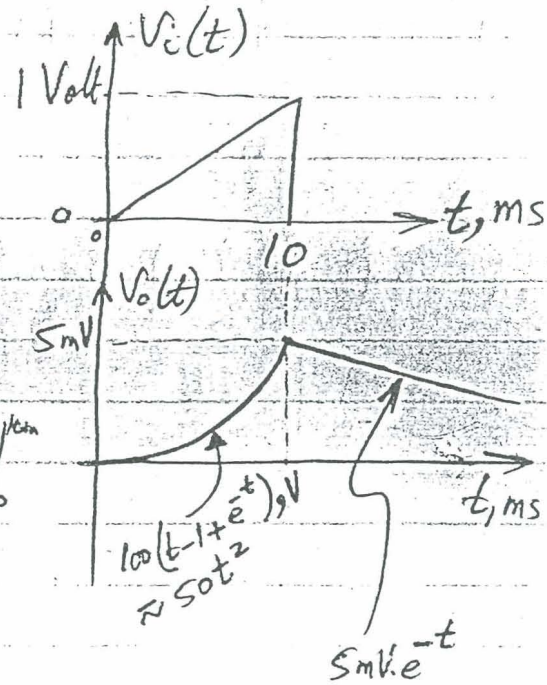

(\neq Laplace of RHS = $sV_o(s) + V_o(s) - 0 = (s+1)V_o(s)$)


$$\begin{aligned} \therefore V_o(s) &= \frac{1}{s+1} \cdot V_i(s) = \frac{100}{s^2(s+1)} - e^{-0.01s} \left(\frac{1}{s(s+1)} + \frac{100}{s^2(s+1)} \right) = \\ &= 100 \cdot \left(\frac{1}{s^2} - \frac{1}{s} + \frac{1}{s+1} \right) - e^{-0.01s} \cdot \left(\frac{100}{s^2} - \frac{100}{s} + \frac{100}{s+1} + \frac{1}{s} - \frac{1}{s+1} \right) \Rightarrow \end{aligned}$$

$$\begin{aligned} \therefore V_o(t) &= 100(t-1+e^{-t}) \cdot u(t) - u(t-0.01) \cdot (100(t-0.01) + 99e^{-t+0.01}) \\ &= \begin{cases} 100(t-1+e^{-t}) \text{ V, } t \in [0, 0.01] \text{ sec} \\ 100e^{-t} - 99e^{-0.01-t} = 0.00503e^{-t} = 5\text{mV}e^{-t}, t \in [0.01, \infty) \end{cases} \end{aligned}$$

$V_o(0.01) = 4.9834 \text{ mV}$ in both expressions. Hence $V_o(t)$ is as shown

For the circuit shown

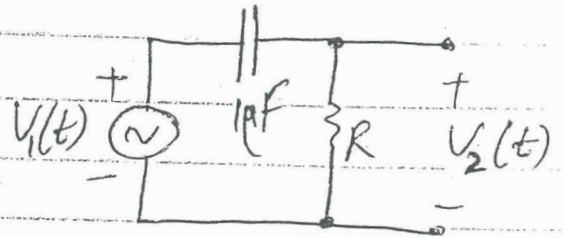
- a. The filter is a high-pass one with unity high-frequency gain and zero dc-gain.



- b. Corner frequency, f_c , is given by:

$$2\pi f_c R \times 1\mu = 1 \Rightarrow f_c = \frac{1\text{M}}{2\pi R}, \text{ Hz}$$

with cutting rate of 20db/decade.

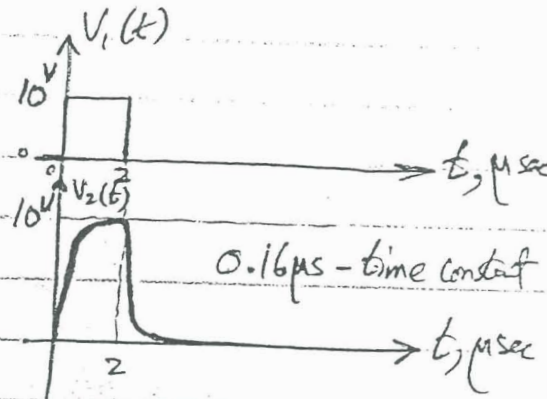

- c. For 1MHz f_c , then $2\pi R = 1$ &
 $R = \frac{1}{2\pi}$, $R = 0.1592 \Omega$

- d. For $V_1(t)$ as shown, with OIC:

then the circuit time constant is $RC = \frac{1}{2\pi} \mu\text{sec} = 0.16 \mu\text{sec}$; and the response is given by:

$$V_2(t) = 10(1 - e^{-2\pi t}), \text{ Volts for } t \in (0, 2) \mu\text{sec.}$$

$\therefore V_2(2\mu\text{sec}) = 9.999965 \approx 10 \text{ Volts (almost there)}$


$\therefore V_2(t) = 10 e^{-2\pi(t-2\mu)}, \text{ Volts for } t \geq 2\mu\text{sec.}$

The response is plotted as shown.


To find $v(t)$ for the circuit shown,

then it is a stair case wave given as shown.

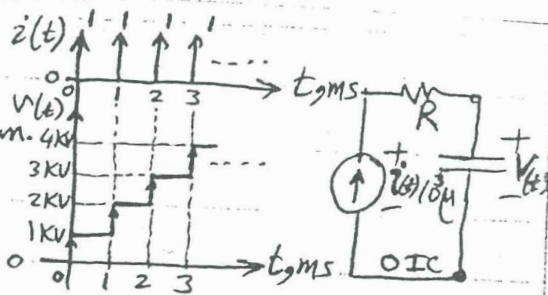Here; independant of R , every impulse gives a quota of $1 \text{ Coul} \equiv \frac{1}{10^3\mu} = 0.1 \text{KV}$ to the capacitor.



For the
Circuit shown:

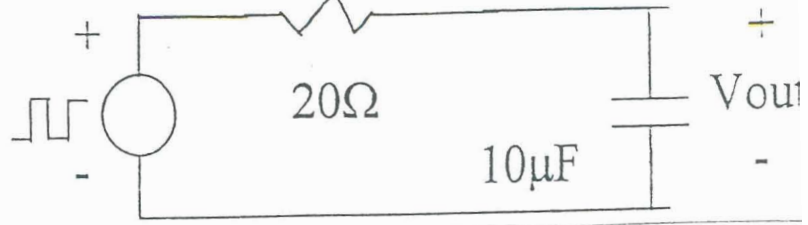


(a) V_{out} has a time constant of $RC = 0.2\text{msec}$
 \therefore To get square signal $\frac{1}{\omega} = \frac{1}{2\pi f}$ must be $\gg 0.2\text{msec}$
 \therefore choose $f \ll 2.5\text{kHz}$

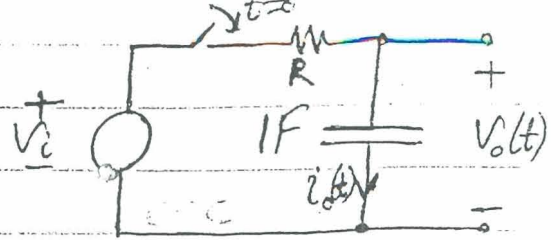(b) To get a triangular signal $\frac{1}{\omega} = \frac{1}{2\pi f}$ must be $\ll 0.2\text{msec}$
 \therefore choose $f \gg 2.5\text{kHz}$

For the shown network & signals;

$V_i(t)$ is a charge-discharge pattern given, during charge, by:



$$V_o(t) = 10 + A_1 e^{-\frac{t}{R}}, \text{ where}$$

$$A_1 = V_o(0) = 10 + A_1 \Rightarrow A_1 = A_1 - 10$$

$$\therefore V_{o,ss}(t) = 10 + (A_1 - 10) e^{-t/R}, \text{ Volts}$$

$$\therefore A_2 = V_o(1) = 10 + (A_1 - 10) e^{-1/R} \quad (1)$$

At discharge, this is given as:


$$V_{o,ss}(t) = A_2 e^{-(t-1)/R}$$

$$\therefore A_1 = V_o(3) = A_2 e^{-2/R} \quad (2)$$

Solving (1) & (2) gives:

$$A_2 = \frac{10}{1 + e^{-1/R} + e^{-2/R}} \quad \phi$$
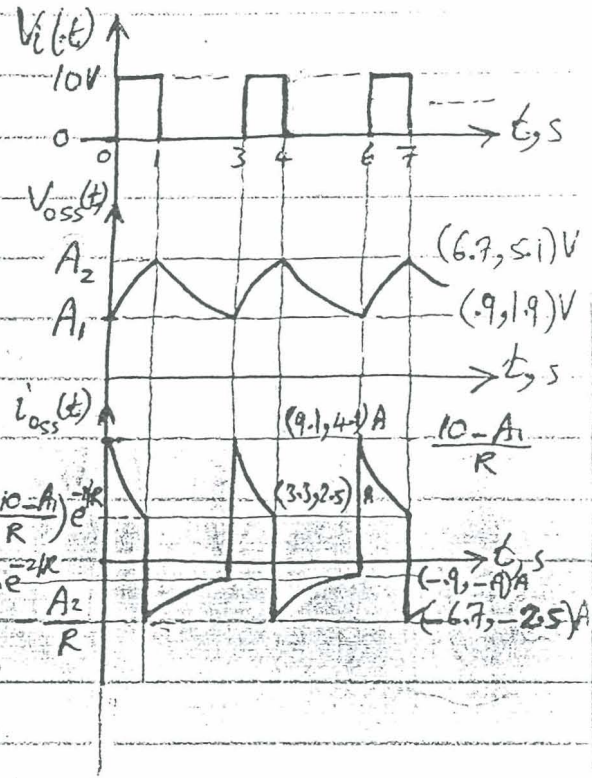
$$A_1 = \frac{10 e^{-2/R}}{1 + e^{-1/R} + e^{-2/R}}$$



The current is respectively given by:

$$i_o(t) = \frac{10 - A_1}{R} e^{-t/R} \quad \& \quad i_o(t) = -A_2 e^{-(t-1)/R}$$


These patterns are then repeated.

For $R=1$, $\therefore A_1 = 0.900$ Volts & $A_2 = 6.652$ Volts &

For $R=2$, $\therefore A_1 = 1.863$ Volts & $A_2 = 5.065$ Volts.


To find $V_{o,ss}(t)$ for the circuit shown:

then it is a decayed pattern given by:

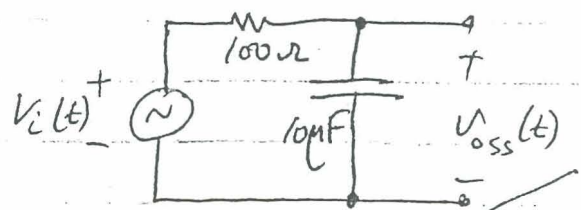


$$V_o(t) = 1582 e^{-\frac{t-k}{1ms}} = 1582 V e^{-\frac{(t-k)}{1ms}}$$

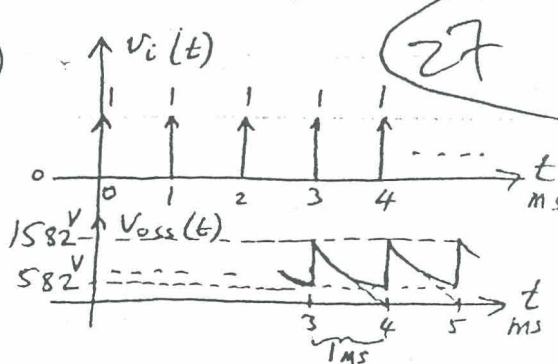where k is the time of impulse & the equation is valid till next one, provided steady-state is reached.




For the circuit shown with $V_i(t)$ being a train of unit impulses spaced one msec apart:

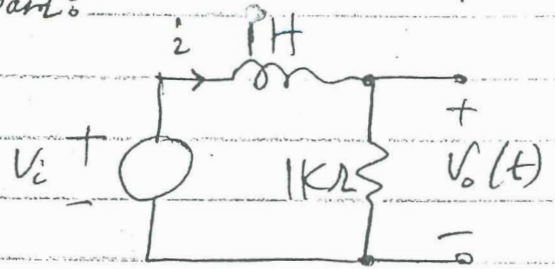∴ The coil will take the impulse voltage, δ :




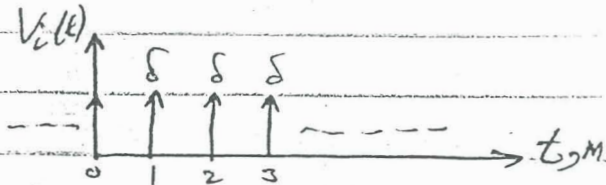∴ $\delta = L \cdot \dot{i} \Rightarrow$ integrating
 $1 = i(\text{after impulse}) - i(\text{before})$
 Assuming any-impulse time at steady-state to be α :



∴ $1 = i(\alpha^+) - i(\alpha^-)$
 let $i(\alpha^-) = A$ & $i(\alpha^+) = B$

V_i at steady state time α msec

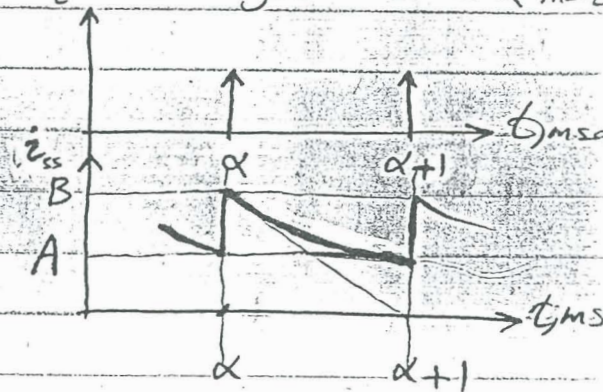

∴ $1 = B - A$ (1)
 After the impulse has gone, the coil current B will decay through the resistance

∴ $i(t) = B e^{-\frac{(t-\alpha)}{1}} = B e^{-(t-\alpha)}$, where both t & α are in msec
 When steady-state is reached $i(\alpha+1) = A$ again

∴ $A = B e^{-(\alpha+1-\alpha)} = B e^{-1} \therefore B = A e$ (2)

(1) & (2) $\Rightarrow 1 = A e - A = (e-1)A \therefore A = \frac{1}{e-1} = .582 \text{ Aps}$

∴ $B = \frac{e}{e-1} = 1.582 \text{ Aps}$.


The waveform of $i_{ss}(t)$ (at steady state) is then given by:

$$i_{ss}(t) = 1.582 e^{-(t-\alpha)}, \text{ Aps}$$


$$V_{ss}(t) = 1582 e^{-(t-\alpha)}, \text{ Volts}$$

$t \in (\alpha, \alpha+1)$

(plotted as shown.

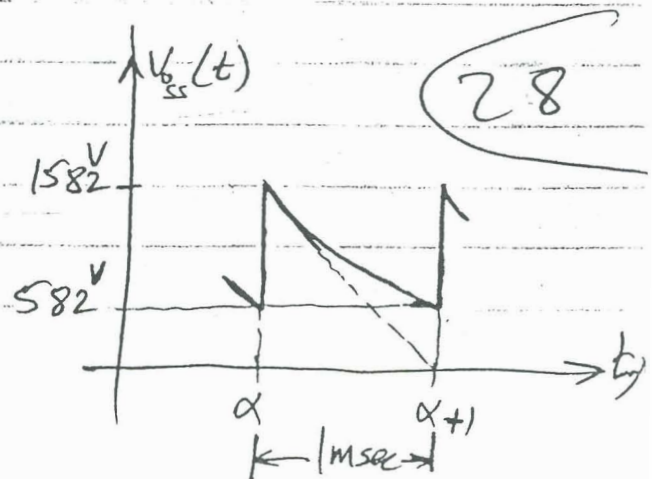

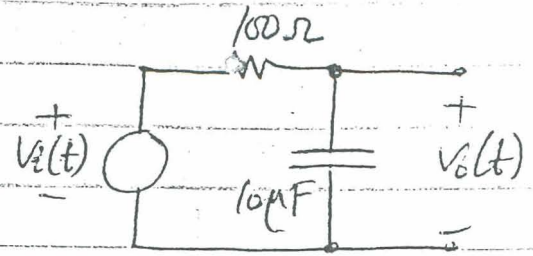For the circuit shown,
 $V_i(t)$ is given as a train of
 unit impulses spaced by 1ms.




$$\therefore V_i(t) = \sum_{k=0}^{\infty} \delta(t - k \text{ ms})$$

To find $V_o(t)$ at steady-state, $V_{o,ss}(t)$:

One $V_{o,ss}(t)$ cycle is a charge-discharge pattern of RC.
 The charge time is infinitesimally small, whereas the
 discharge time is 1msec.

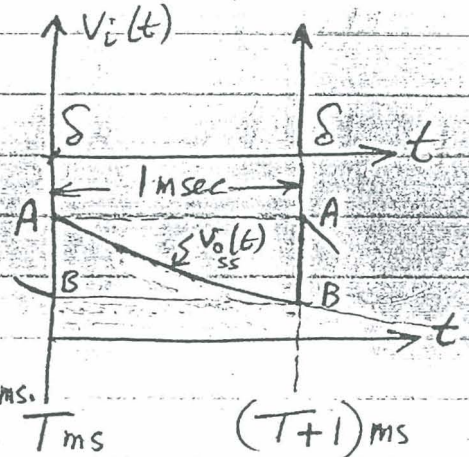Hence, one steady state
 response cycle is as shown.



Here, $V_{o,ss}(t)$ is given as:

$$V_{o,ss}(t) = A e^{-\frac{(t-T)}{RC}} = A e^{-\frac{(t-T)}{1 \text{ ms}}}, \quad t \in (T, T+1) \text{ ms}$$

$$\therefore B = V_o(T+1, \text{ms}) = A e^{-1} \Rightarrow A = e \cdot B \quad (1)$$


But, $V_i(t) = V_o(t) + 1000 \mu V_o(t)$. Integrating during the
 infinitesimally small charging time:

$$\therefore \int_{T^-}^{T^+} \delta dt = \int_{T^-}^{T^+} V_o(t) dt + 1 \text{ m} \cdot V_o(t) \Big|_{T^-}^{T^+} \Rightarrow 1 = 0 + 1 \text{ m}(A - B)$$


$$\therefore A = B + 1000 \quad (2) \quad \text{Solving (1) \& (2) } \Rightarrow$$

$$B + 1000 = eB \Rightarrow B = \frac{1000}{e-1} = 582 \text{ Volts} \Rightarrow A = 1582 \text{ Volts}$$

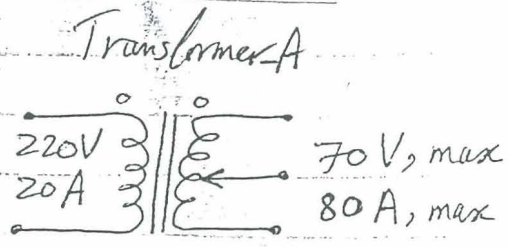
To obtain controllable 100 Amp current from 220V mains using the two transformers shown with indicated ratings, then transformer-A can not provide 100 A controlled current whereas it can provide up to 80 A controllable current.



the contrary; transformer-B

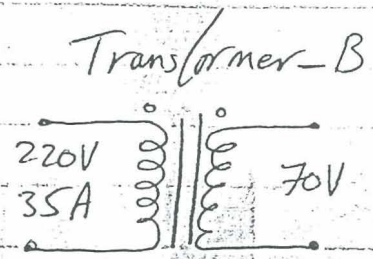

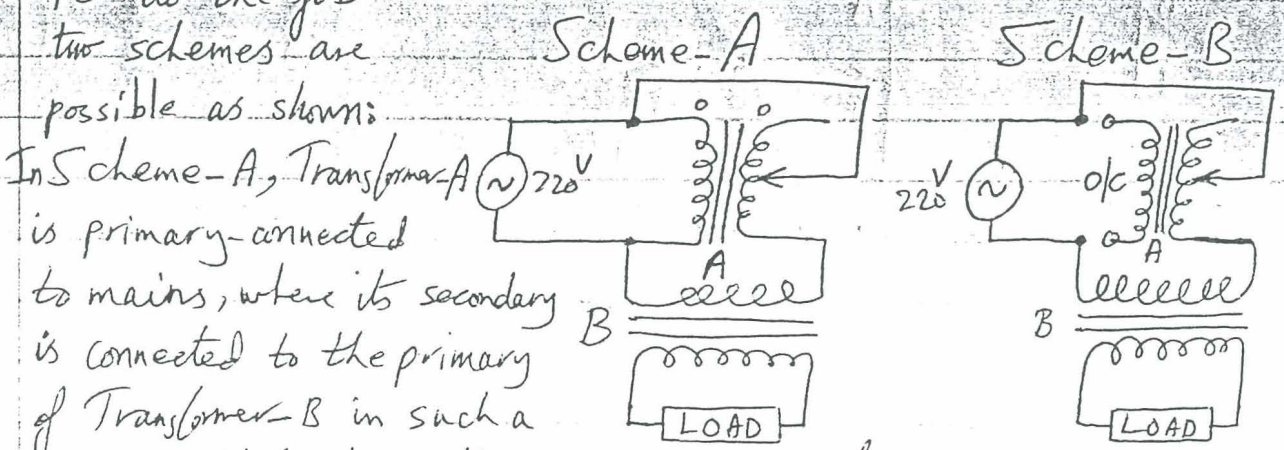can provide $\frac{220 \times 35}{70} = 110$ Amp fixed current, with no control. To do the job two schemes are possible as shown:




In Scheme-A, Transformer-A is primary-connected to mains, where its secondary is connected to the primary of Transformer-B in such a manner that the voltage across Transformer-B primary is reduced and hence the voltampere input and hence the output current to the load. Here, the dots of Transformer-B are not used.

On the other hand, Scheme-B uses the secondary of Transformer-A as inductance to decrease the voltage input to Transformer-B primary and hence controlling the load current. Here, all dots never mind.

For the two port L-circuit shown,
the z-parameters relating v's to i's as:

$$v_1 = z_1 * i_1 + z_2 * i_2, \text{ and:}$$
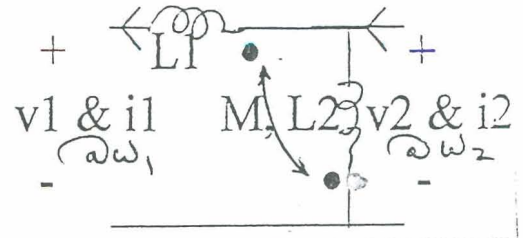
$$v_2 = z_3 * i_1 + z_4 * i_2, \text{ are:}$$



$$\begin{aligned} (a) \quad V_1 &= L_1 (-\dot{i}_1') + L_2 (\dot{i}_2 - \dot{i}_1)' - M \dot{i}_1' - M (\dot{i}_1' - \dot{i}_2)' \\ &= \underbrace{-(L_1 + L_2 + 2M)j\omega_1 \dot{i}_1'}_{z_1} + \underbrace{(L_2 + M)j\omega_2 \dot{i}_2}'_{z_2} \end{aligned}$$

$$(b) \quad V_2 = L_2 (\dot{i}_2 - \dot{i}_1)' - M \dot{i}_1' = \underbrace{-(L_2 + M)j\omega_1 \dot{i}_1'}_{z_3} + \underbrace{j\omega_2 L_2 \dot{i}_2}'_{z_4}$$


If port 2 was o/c then $\dot{i}_2 = 0$

$$\therefore V_1 = z_1 \dot{i}_1 = L_{eq} (-\dot{i}_1') = -L_{eq} j\omega_1 \dot{i}_1'$$

$$\therefore z_1 = -L_{eq} j\omega_1 \quad \therefore L_{eq} = \frac{z_1}{-j\omega_1}$$

\therefore port 1 will see inductance $L_{eq} = L_1 + L_2 + 2M$

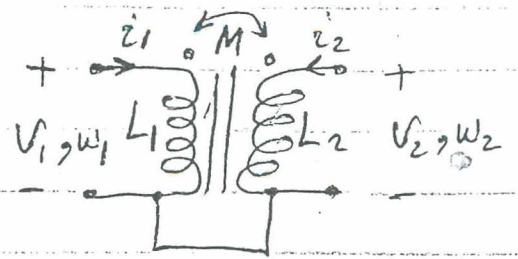For the circuit shown, to find A given by:



$$\begin{bmatrix} V_2 \\ i_2 \end{bmatrix} = A \begin{bmatrix} V_1 \\ i_1 \end{bmatrix} \text{ with sinusoidal excitations at } \omega_1 \text{ \& } \omega_2, \text{ then:}$$

$$\begin{aligned} V_1 &= L_1 i_1' + M i_2' = j\omega_1 L_1 i_1 + j\omega_2 M i_2 \Rightarrow i_2 = \frac{V_1}{j\omega_2 M} - \frac{\omega_1 L_1}{\omega_2 M} i_1 \\ \& V_2 &= L_2 i_2' + M i_1' = j\omega_2 L_2 i_2 + j\omega_1 M i_1 = \\ &= (L_2/M) V_1 + j\omega_1 [M - (L_1 L_2/M)] i_1 \end{aligned}$$


$$\therefore A = \frac{1}{j\omega_2 M} \begin{bmatrix} j\omega_2 L_2 & -\omega_1 \omega_2 (M^2 - L_1 L_2) \\ 1 & -j\omega_1 L_1 \end{bmatrix}$$

To solve the circuit opposite:

$$\therefore V = 8(i_1 - i_2) + 9(i_1 - i_3) + 4.5 i_2'$$

$$0 = 6(i_3 - i_2) + 20 i_3 - 9(i_1 - i_3) - 4.5 i_2'$$
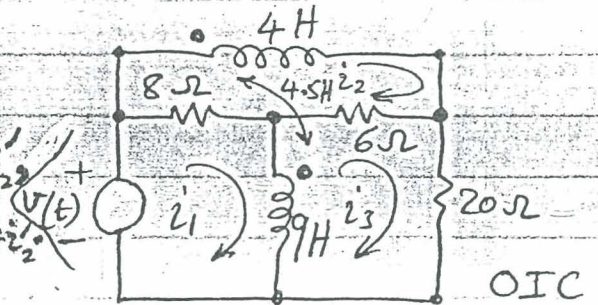
$$\& 0 = 8(i_1 - i_2) + 6(i_3 - i_2) - 4.5(i_1 - i_3) - 4 i_2'$$



$$a) \therefore \begin{bmatrix} V(t) \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 8 & -8 & 0 \\ 0 & -6 & 26 \\ 8 & -14 & 6 \end{bmatrix} \cdot \begin{bmatrix} i_1(t) \\ i_2(t) \\ i_3(t) \end{bmatrix} + \begin{bmatrix} 9 & 4.5 & -9 \\ -9 & -4.5 & 9 \\ -4.5 & -4 & 4.5 \end{bmatrix} \cdot \begin{bmatrix} i_1' \\ i_2' \\ i_3' \end{bmatrix}$$

b) Taking Laplace Transform with OIC:

$$\therefore \begin{bmatrix} V(s) \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 8+9s & -8+4.5s & -9s \\ -9s & -6-4.5s & 26+9s \\ 8-4.5s & -14-4s & 6+4.5s \end{bmatrix} \cdot \begin{bmatrix} i_1(s) \\ i_2(s) \\ i_3(s) \end{bmatrix}$$

32

$$\therefore i_3(s) = \frac{V(s) \cdot [9s(14+4s) + (6+4.5s)(8-4.5s)]}{(8+9s)(-6-4.5s)(6+4.5s) - (8-4.5s)^2(26+9s) - 81s^2(14+4s)}$$

c) Simplified by


$$i_3(s) = \frac{63s^2 + 540s + 192}{2142s^2 + 19168s + 3840} \cdot V(s) \quad \& \text{ for } V(t) = u(t) \Rightarrow V(s) = \frac{1}{s}$$

$$\therefore i_3(s) = \frac{63s^2 + 540s + 192}{2142s(s + 2050)(s + 8.7436)} = \frac{107.1}{2142s} + \frac{.02238}{s + 2050} + \frac{.0017937}{s + 8.7436}$$

$$d) \therefore i_3(t) = .05 - .02238 e^{-.2050t} + .0017937 e^{-8.7436t} \text{ Ays.}$$

To get the Z-matrix relating the V 's of the shown transformer to its i 's:

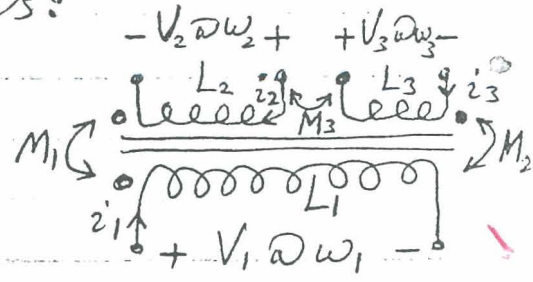∴ Let:
$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} I_1 \sin \omega_1 t \\ I_2 \sin \omega_2 t \\ I_3 \sin \omega_3 t \end{bmatrix} \Rightarrow \begin{bmatrix} i_1' \\ i_2' \\ i_3' \end{bmatrix} = j \begin{bmatrix} \omega_1 i_1 \\ \omega_2 i_2 \\ \omega_3 i_3 \end{bmatrix}$$



(a)
$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} L_1 i_1' - M_1 i_2' + M_2 i_3' \\ L_2 i_2' - M_1 i_1' - M_3 i_3' \\ L_3 i_3' - M_3 i_2' + M_2 i_1' \end{bmatrix} \quad (1) \quad \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = Z \begin{bmatrix} i_1' \\ i_2' \\ i_3' \end{bmatrix} \Rightarrow Z = \begin{bmatrix} j\omega_1 L_1 & -j\omega_2 M_1 & j\omega_3 M_2 \\ -j\omega_1 M_1 & j\omega_2 L_2 & -j\omega_3 M_3 \\ -j\omega_1 M_2 & j\omega_2 M_3 & -j\omega_3 L_3 \end{bmatrix}$$

(b) To get the inductance at port 1, when ports 2 & 3 are shorted: putting $V_2 = V_3 = 0$ in second & third row of (1):

∴
$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} L_2 & -M_3 \\ -M_3 & L_3 \end{bmatrix} \begin{bmatrix} i_2' \\ i_3' \end{bmatrix} + \begin{bmatrix} -M_1 \\ M_2 \end{bmatrix} i_1' \Rightarrow \begin{bmatrix} L_2 & -M_3 \\ -M_3 & L_3 \end{bmatrix} \begin{bmatrix} i_2' \\ i_3' \end{bmatrix} = \begin{bmatrix} M_1 \\ -M_2 \end{bmatrix} i_1'$$

∴
$$\begin{bmatrix} i_2' \\ i_3' \end{bmatrix} = \frac{1}{L_2 L_3 - M_3^2} \begin{bmatrix} L_3 & M_3 \\ M_3 & L_2 \end{bmatrix} \begin{bmatrix} M_1 \\ -M_2 \end{bmatrix} i_1' = \begin{bmatrix} L_3 M_1 - M_2 M_3 \\ M_1 M_3 - L_2 M_2 \end{bmatrix} \frac{i_1'}{L_2 L_3 - M_3^2}$$


Using this in the first row of (1):

∴
$$V_1 = L_1 i_1' + \left[M_1 (L_3 M_1 - M_2 M_3) + M_2 (M_1 M_3 - L_2 M_2) \right] \frac{i_1'}{L_2 L_3 - M_3^2} = \frac{i_1'}{L_2 L_3 - M_3^2} \cdot \left[L_1 L_2 L_3 - L_1 M_3^2 - M_1^2 L_3 + M_1 M_2 M_3 + M_1 M_2 M_3 - M_2^2 L_2 \right] =$$

∴ Inductance @ 1 when 2 & 3 are shorted = $\frac{V_1}{i_1'} = \frac{L_1 L_2 L_3 + 2 M_1 M_2 M_3 - (L_1 M_3^2 + L_2 M_2^2 + L_3 M_1^2)}{L_2 L_3 - M_3^2}$

For the power circuit shown, to find: $V_G, P_G, i_G, \eta_G, P_{Line}, V_A, P_A, Q_A$ & Z_B

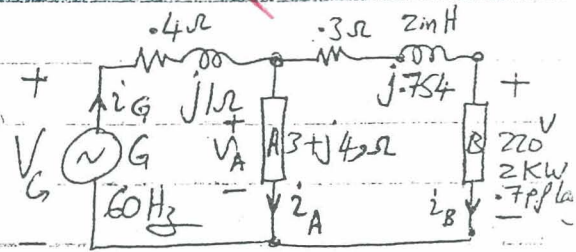The inductance of 2mH makes at 60Hz frequency, an impedance of $j\omega L = j.754\Omega$.
Taking V_B as reference:



$$\therefore i_B = \frac{2000}{220 \times 0.7} \angle -\cos^{-1} 0.7 = 12.987 \text{ Ap} \angle 45.573^\circ$$

$$\therefore Z_B = \frac{V_B}{i_B} = \frac{220 \angle 0^\circ}{12.987 \angle 45.573^\circ} = 16.94 \angle -45.573^\circ = 11.858 + j12.098 \Omega$$

$$\therefore V_A = 220 + i_B (0.3 + j.754) = 229.756 \text{ V} \angle 1.016^\circ$$

$$\therefore i_A = \frac{V_A}{3 + j4} = 45.951 \text{ Ap} \angle -52.115^\circ$$

$$\therefore P_A = i_A \cdot V_A \cdot \cos\left(\tan^{-1} \frac{4}{3}\right) = 6334.551 \text{ Watts} = 6.335 \text{ KW}$$

$$\therefore Q_A = i_A \cdot V_A \cdot \sin\left(\tan^{-1} \frac{4}{3}\right) = 8446.068 \text{ VAR} = 8.446 \text{ KVAR}$$

$$\therefore i_G = i_A + i_B = 58.872 \text{ Ap} \angle -58.675^\circ$$

$$\therefore V_G = V_A + i_G \cdot (.4 + j1) = 291.108 \text{ Volts} \angle 4.564^\circ$$


$$\therefore P_G = i_G \cdot V_G \cdot \cos \angle_{i_G}^{V_G} = 9771.530 \text{ Watts} = 9.772 \text{ KW}$$

$$\therefore P_{G_s} = \cos \angle_{i_G}^{V_G} = \cos(55.239^\circ) = .570$$

$$\therefore P_{Line} = P_G - P_A - P_B = (0.4 |i_G|^2 + 0.3 |i_B|^2) = 1436.978 \text{ W} = 1.437 \text{ KW}$$

$$\therefore \eta_G = \frac{P_A + P_B}{P_G} \times 100 = \left(1 - \frac{P_{Line}}{P_G}\right) \times 100 = 85.294\%$$

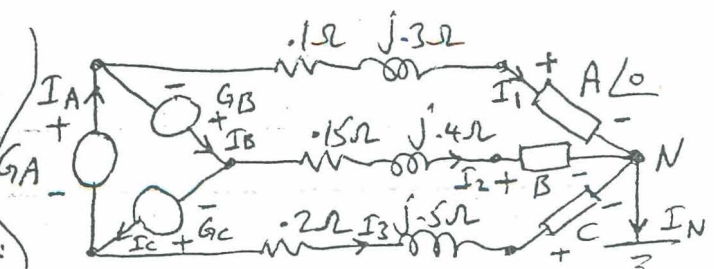To solve the circuit shown when A, B & C are symmetrical loads of 220V, 10KW & .8 pf lagging



∴ Taking A voltage as ref., then:

Each load passes $\frac{10K}{220 \times .8} = 56.82 \text{ Ap}$ at 36.9° lagging its voltage.

∴ $I_1 = 56.82 \text{ A} \angle -36.9^\circ$, $I_2 = 56.82 \text{ A} \angle -156.9^\circ$ & $I_3 = 56.82 \text{ A} \angle +83.1^\circ$ ✓

(a) $V_A = (1 + j0.3)56.82 \angle -36.9^\circ + 220 - [220 \angle 120^\circ + (-2 + j0.5)56.82 \angle 83.1^\circ] = 419.7 \text{ V} \angle -27^\circ$

& $V_B = -[(1 + j0.3)56.82 \angle -36.9^\circ + 220] + 220 \angle -120^\circ + (0.15 + j0.4)56.82 \angle -156.9^\circ = 410.8 \text{ V} \angle -146^\circ$

∴ $V_C = -(V_A + V_B) = 420.9 \text{ V} \angle 93.8^\circ$. Generator currents can be assumed symmetrical

(b) $I_A = \frac{I_1}{\sqrt{3} \angle 30^\circ} = 32.8 \text{ A} \angle -66.9^\circ$, $I_B = 32.8 \text{ A} \angle 173.1^\circ$, $I_C = 32.8 \text{ A} \angle 53.1^\circ$ ∴ $\text{pf}_{G_A} = .775$, $\text{pf}_{G_B} = .765$ & $\text{pf}_{G_C} = .758$

(c) Line losses = $56.82^2(1 + 0.15 + 0.2) = 1452.7 \text{ W}$, $I_N = V_N = 0$ lag

To find the neutral voltage and current when sound is broken:
Using superposition

$$\circ \circ V_N = V_{NA} + V_{NB} + V_{NC}$$

Let: $Z = 2.5 + j2, \Omega;$

$$Z_1 = Z_{A'} + .4 + j.6 = 5.4 + j6.6, \Omega;$$

$$Z_2 = Z_{B'} + .4 + j.6 = 4.4 + j5.6, \Omega;$$


$$Z_3 = Z_{C'} + .4 + j.6 = 6.4 + j7.6, \Omega.$$

$\circ \circ$ For sound connection:

$$\circ \circ V_{NA} = \frac{220 \angle 0^\circ * (Z \parallel Z_2 \parallel Z_3)}{Z_1 + (Z \parallel Z_2 \parallel Z_3)},$$

$$V_{NB} = \frac{220 \angle 120^\circ * (Z \parallel Z_1 \parallel Z_3)}{Z_2 + (Z \parallel Z_1 \parallel Z_3)} \neq$$
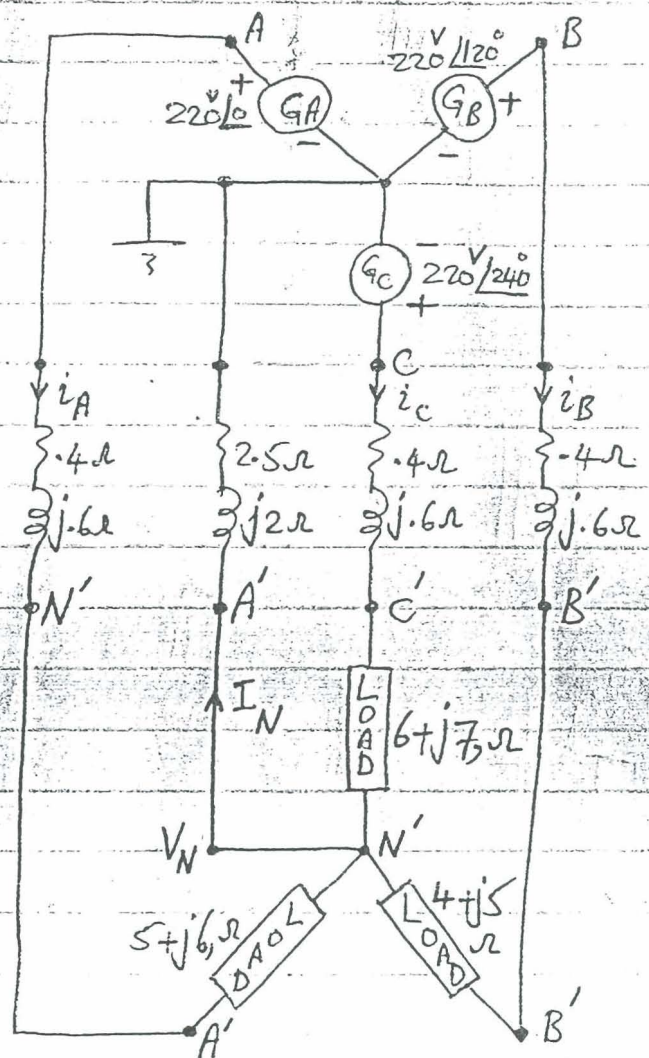
$$V_{NC} = \frac{220 \angle 240^\circ * (Z \parallel Z_1 \parallel Z_2)}{Z_3 + (Z \parallel Z_1 \parallel Z_2)}.$$



$$\circ \circ V_N = 38.689 \angle -5.5^\circ + 46.326 \angle -6.6 + 120^\circ + 33.206 \angle -4.68 + 240^\circ =$$

$$= 38.689 \angle -5.5^\circ + 46.326 \angle 113.37^\circ + 33.206 \angle 235.32^\circ =$$

$$= 11.581 \text{ Volts } \angle 83.86^\circ$$

$$\circ \circ I_N = V_N / Z = 3.617 \text{ Amp } \angle 45.20^\circ$$

\neq For broken connection; $Z = \infty$ in the above expressions:

$$\circ \circ V_N = 72.004 \angle 0.22^\circ + 86.218 \angle -0.92 + 120^\circ + 61.799 \angle 11.03 + 240^\circ =$$

$$= 72.004 \angle 0.22^\circ + 86.218 \angle 119.08^\circ + 61.799 \angle 241.03^\circ =$$

$$= 21.553 \text{ Volts } \angle 89.58^\circ$$

$$\neq I_N = 0 \text{ Amps.}$$

$$i_A = \frac{220 \angle 0^\circ - 11.581 \angle 83.86^\circ}{5.4 + j6.6} = 25.689 \text{ Ap} \angle -53.72^\circ,$$

$$i_B = \frac{220 \angle 120^\circ - 11.581 \angle 83.86^\circ}{4.4 + j5.6} = 29.593 \text{ Ap} \angle 70.01^\circ \neq$$

$$i_C = \frac{220 \angle 240^\circ - 11.581 \angle 83.86^\circ}{6.4 + j7.6} = 23.213 \text{ Ap} \angle -168.74^\circ.$$

$$\therefore P_A = 220 * 25.689 * \cos 53.72^\circ = 3343.9 \text{ W} = 3.344 \text{ KW}$$

$$P_B = 220 * 29.593 * \cos(120^\circ - 70.01^\circ) = 4186.1 \text{ W} = 4.186 \text{ KW}$$

$$P_C = 220 * 23.213 * \cos(240^\circ + 168.74^\circ) = 3368.2 \text{ W} = 3.368 \text{ KW}$$

$$P_{FA} = \cos 53.72^\circ = 0.592 \text{ lagging},$$

$$P_{FB} = \cos(120^\circ - 70.01^\circ) = 0.643 \text{ lagging} \neq$$

$$P_{FC} = \cos(240^\circ + 168.74^\circ) = 0.660 \text{ lagging}.$$

$$\text{Line Losses} = 25.689^2 * 0.4 + 29.593^2 * 0.4 + 23.213^2 * 0.4 + 3.617^2 * 0.4 \\ = 862.52 \text{ Watts}$$

a) $\therefore P_A = 3.344 \text{ KW}, P_B = 4.186 \text{ KW} \neq P_C = 3.368 \text{ KW}.$

b) $\neq P_{FA} = 0.592, P_{FB} = 0.643 \neq P_{FC} = 0.660$ all lagging.

c) $\neq \text{Line Losses} = 863 \text{ Watts}.$

d) $\neq I_N = 3.617 \text{ Amps} \neq V_N = 11.58 \text{ Volts}.$

e) $\neq I_{N_{oc}} = 0 \text{ Amps} \neq V_{N_{oc}} = 21.55 \text{ Volts}.$