

بسم الله الرحمن الرحيم

الحلول المختارة لطلاب الهندسة والعمارة
الكهربائية الصناعية

إعداد

سلمان محمد القاسمي

الأستاذ المشارك بقسم الهندسة الكهربائية والحسابات
جامعة أم القرى

الطبعة الثالثة

جمادى الآخرة ١٤٢٠ هـ - أيلول ١٩٩٩

تمهيد

الحمد لله رب العالمين، والصلوة والسلام على سيد المرسلين، وعلى آله وصحبه أجمعين، وبعد: فهذه مجموعة من المسائل والحلول في مادة الكهارب الصناعية (EE411) لطلبة قسم الهندسة الكهربائية والحواسيب بكلية الهندسة والعمارة الإسلامية بجامعة أم القرى، إخترتها لجمعها المنهج المقرر، إبان تدريسي لهذه المادة. وقد قمت بمراجعة وتنبييبها وفهرستها لتسهل المراجعة فيها وتعلم الفائدة منها وأخرجت طبعتها الأولى في شعبان ١٤١٠ هـ.

ثم زدت فيها حصيلة أخرى، مدرجاً مسائل الأبواب المقررة أولاً ثم متبعاً إياها بالحلول، وبوبتها ووضعت فهرساً لكل من المسائل والحلول وساعدني مشكوراً - جزاه الله خيراً - في دمجها وتنبييبها وفهرستها المهندس عبد الباسط زيد عابد، فخرجت طبعتها الثانية في شوال ١٤١٤ هـ.

ثم زدت فيها حصيلة ثالثة على نفس النظام، وساعدني مشكورين - جزاهما الله خيراً - في دمجها وتنبييبها وفهرستها المهندسان خالد صدقة عتيق ورامي عبدالعزيز إكرام، فخرجت في طبعتها الثالثة هذه.

والله أعلم أن ينفع بهذا العمل كل من يطالعه، وأن لا يحرمني ومن أعاذني من مثوبته في الآخرة والأولى، إنه سميع قريب مجيب.

١٤١، ١١، ٥٩

مصطلحات الكهارب الصناعية

العنوان بالإنجليزي	العنوان بالعربي
Thyristor	مفتاح (ف)
Thermal resistance	مقاومة حرارية (مح)
Degree Centigrade($^{\circ}\text{C}$)	درجة مئوية ($^{\circ}\text{م}$)
Mounted	مثبت
Heat sink	مبعد سخونة
Junction temperature	حرارة منطقة الالتحام
Ambient	ظاهريا
Drop	الساقط
SCR	مقوم سيليكوني محكم (مم)
Transistor	ناقل (ت)
i_{rms}	التيار الفعال
V_{rms}	الجهد الفعال
i_{max}	ت ع
i_{min}	ت و
i_{av}	ت ط
Period(t)	الفترة (ن)
Frequency(f)	التردد (د)
Junction	هي منطقة التلاحم بين السيليكون الغني بالبروتونان (الفقير من الكهارب)، والسيليكون الفقير من البروتونات (الغنى بالكهارب)

فهرس المسائل

الصفحة	المسائل
١	مسائل الباب الأول: المعدلات والحماية RATINGS & PROTECTION
٢	، ١-١ ، ٢-١
٣	، ٣-١
٤	، ٤-١
٥	، ٥-١
٥	مسائل الباب الثاني: مراجعة الدوائر CIRCUIT REVISION
٦	، ١-٢ ، ٢-٢
٧	، ٣-٢ ، ٤-٢ ، ٥-٢
٨	، ٦-٢ ، ٧-٢ ، ٨-٢
٩	، ٩-٢ ، ١٠-٢ ، ١١-٢ ، ١٢-٢
٩	مسائل الباب الثالث: المقطعات CHOPPERS
١٠	، ١-٣ ، ٢-٣ ، ٣-٣
١١	، ٤-٣ ، ٥-٣
١٢	، ٦-٣ ، ٧-٣ ، ٨-٣
١٣	، ٩-٣ ، ١٠-٣
١٤	، ١١-٣ ، ١٢-٣ ، ١٣-٣ ، ١٤-٣
١٥	مسائل الباب الرابع: المقلبات INVERTERS
١٥	، ١-٤ ، ٢-٤ ، ٣-٤
١٦	، ٤-٤ ، ٥-٤ ، ٦-٤ ، ٧-٤
١٧	، ٨-٤ ، ٩-٤ ، ١٠-٤ ، ١١-٤ ، ١٢-٤ ، ١٣-٤
١٨	، ١٤-٤
١٩	، ١٥-٤ ، ١٦-٤ ، ١٧-٤
٢٠	، ١٨-٤ ، ١٩-٤

الصفحة		المسائل
٢١	RECTIFIERS	مسائل الباب الخامس: المقومات
٢١		٤-٥، ٣-٥، ٢-٥، ١-٥
٢٢		٩-٥، ٨-٥، ٧-٥، ٦-٥، ٥-٥
٢٣		١٢-٥، ١١-٥، ١٠-٥
٢٤	CONVERTERS	مسائل الباب السادس: المحولات
٢٤		٢-٦، ١-٦
٢٥	CYCLO-CONVERTERS	مسائل الباب السابع: المرددات
٢٥		٢-٧، ١-٧
٢٦	FIRING & COMMUTATION CIRCUITS	مسائل الباب الثامن: دوائر الإطلاق والإغلاق
٢٦		٣-٨، ٢-٨، ١-٨

فهرس الحلول

الصفحة	الحلول
٢٧	حلول الباب الأول: المعدلات والحماية RATING & PROTECTION
٢٧	، ١-١
٢٨	، ٢-١
٣١	، ٤-١
٣٢	، ٥-١
٣٤	حلول الباب الثاني: مراجعة الدوائر CIRCUIT REVISION
٣٤	، ١-٢
٣٦	، ٢-٢ ، ٣-٢
٣٧	، ٤-٢
٣٨	، ٥-٢
٣٩	، ٦-٢
٤٠	، ١١-٢
٤١	، ١٢-٢
٤٠	حلول الباب الثالث: المقطعات CHOPPERS
٤٠	، ١-٣
٤٨	، ٢-٣
٤٩	، ٣-٣
٥٠	، ٤-٣
٥١	، ٥-٣
٥٢	، ٦-٣
٥٣	، ٧-٣
٥٤	، ٨-٣
٥٥	، ٩-٣
٥٦	، ١٠-٣
٥٨	، ١١-٣
٥٩	، ١٢-٣



الصفحة	الحلول
٦١	CHOPPERS
٦٢	١٣-٣
٦٣	١٤-٣
٦٤	٦-٤
٦٥	٧-٤
٦٦	٨-٤
٦٧	٩-٤
٦٩	١٠-٤
٧٠	١١-٤
٧١	١٢-٤
٧٢	١٣-٤
٧٣	١٤-٤
٨١	١٥-٤
٨١	١٦-٤
٨٢	١٧-٤
٨٣	١٧-٤ بـ
٨٤	١٧-٤ جـ
٨٥	١٧-٤ جـ
٨٧	١٨-٤
٨٩	١٩-٤
٩٠	RECTIFIERS
٩٠	١-٥ أـ
٩٢	١-٥ بـ
٩٤	١-٥ جـ
٩٥	٢-٥ أـ
٩٨	٥-٥ بـ ١
	٣-٣ حلول الباب الثالث: المقطعات
	٦-٤ حلول الباب الرابع: المقلبات
	٧-٤ حلول الباب الخامس: المقومات

الصفحة		الحلول
٩٩	RECTIFIERS	نتمة حلول الباب الخامس: المقومات
٩٩		، ١٠-٥
١٠٢		. ١٢-٥
١٠٤	CONVERTERS	حلول الباب السادس: المحولات
١٠٤		. ١-٦
١٠٦	CYCLO-CONVERTERS	حلول الباب السابع: المرددات
١٠٦		. ١-٧
١٠٧	FIRING & COMMUTATION CIRCUITS	حلول الباب الثامن: دوائر الإطلاق والإغلاق
١٠٧		. ٢-٨

Set One: Ratings & Protection.

- T-1] A thyristor having a thermal resistance of $0.5 \text{ }^{\circ}\text{C}/\text{W}$ is mounted on a heatsink of thermal resistance $1.0 \text{ }^{\circ}\text{C}/\text{W}$. A current I flows through the thyristor for one third of the cycle only. Calculate the maximum value of I if the junction temperature is not to exceed $125 \text{ }^{\circ}\text{C}$ in an ambient of $35 \text{ }^{\circ}\text{C}$. The voltage drop across the thyristor equals $1 + 0.01I$, Volts.

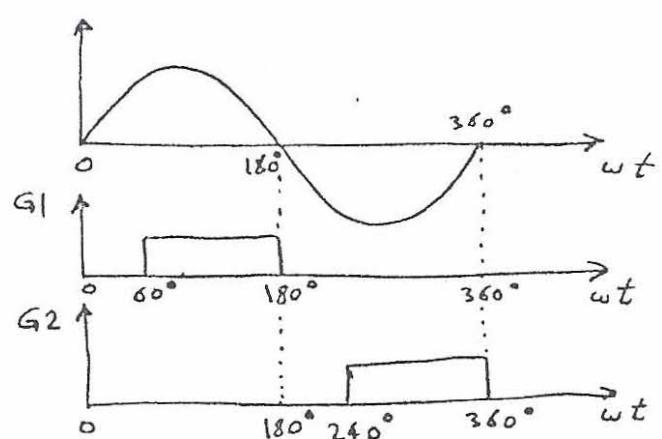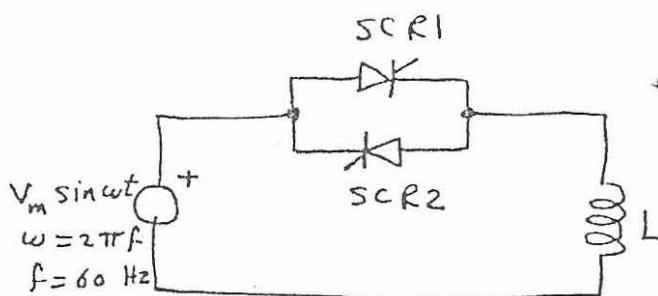- T-2] A sinusoidal supply whose frequency is 60 Hz is connected to an ideal inductor through the two SCR's 1 and 2 as shown. The gate signals G_1 and G_2 are applied to SCR1 and SCR2 respectively. Determine the turnoff times offered to SCR1 and SCR2. Sketch the voltage waveform across SCR1.



Repeat the above if G_1 is applied to SCR2 and G_2 is applied to SCR1.

1-3

Athyristor, Q, has the following ratings:

a) $i_{Fav} = 10 \text{ Amps}$,

b) $i_{F_{max}} = 100 \text{ Amps}$,

c) $V_{RB} = 300 \text{ Volts}$,

d) $V_{FB} = 100 \text{ Volts}$,

e) $V_{Fon} = 1 \text{ Volt}$,


f) $|dV/dt|_{max} = 10 \text{ V/μsec}$,

g) $|di/dt|_{max} = 1 \text{ KAmp/μsec}$,


h) $t_g = 200 \text{ ns}$,

i) $t_{on} = 10 \text{ ns}$,

j) $T_j = 150^\circ \text{C}$.

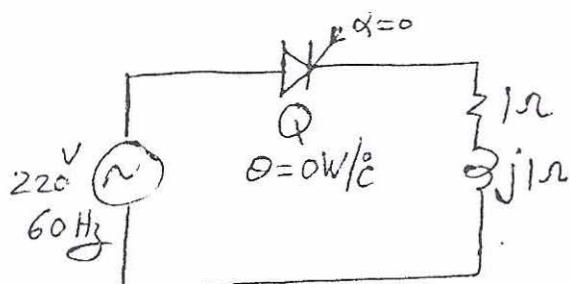

Circuit I

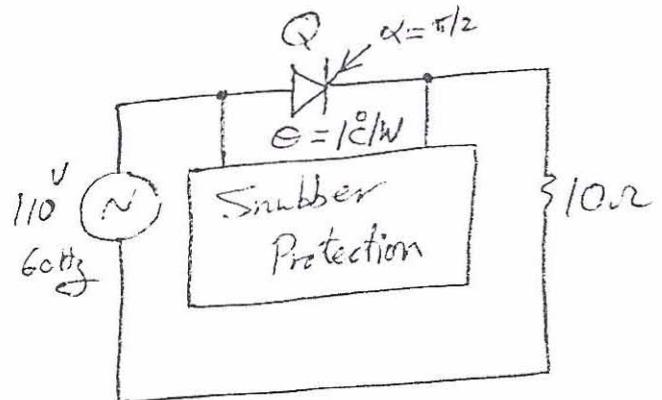

Circuit II

Will the two shown circuits that use the above thyristors operate satisfactorily? If not why?


1-4 In the Fig is

shown the voltage, v_Q , across a thyristor carrying a current i_Q during one cycle.

The thermal resistance of thyristor and heat-sink combination is $10^\circ\text{C}/\text{W}$.


In what range shall the following ratings be:

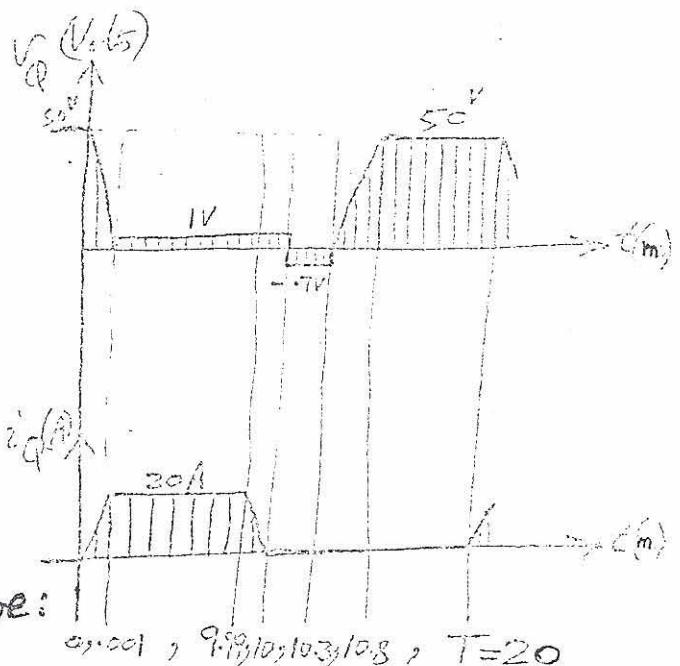- V_{FB} , the forward blocking voltage,
- V_{RB} , a reverse = = =
- V_F , a forward on-state = =
- i_{Fm} , a maximum current,
- i_{Fms} , = = = RMS = =
- i_{Fav} , a average = =
- t_{on} , the turn-on time,
- t_z , a recovery time,
- dV/dt , maximum rate of change of forward voltage,
- $dIdt$, a = = = " current rise
- T_j , the junction temperature. Assume ambient of 30°C



1-5

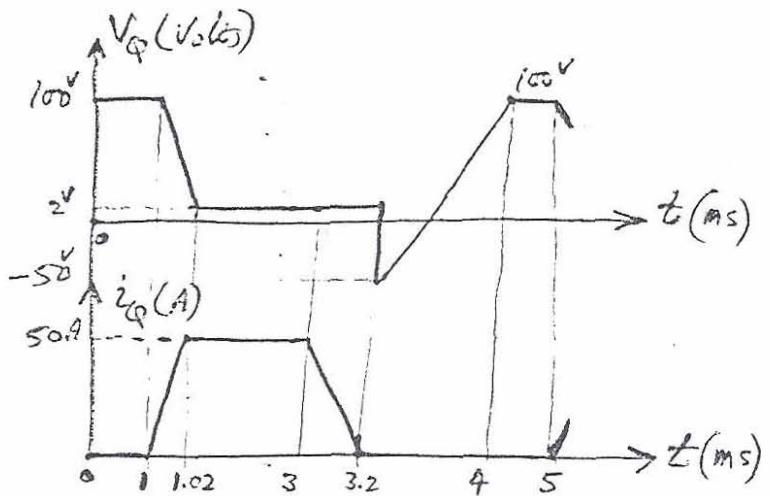
In the figure opposite, the voltage V_Q across a thyristor with current I_Q are shown for one cycle. The thermal resistance of the thyristor-heat-sink combination is $5^\circ\text{C}/\text{W}$. In what range shall the following thyristor ratings be:



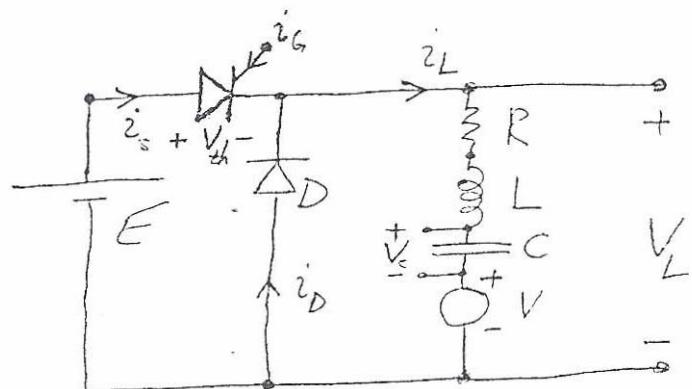
- a) V_{FB} , the forward blocking voltage,
- b) V_{RB} , = reverse = ,
- c) V_F , = forward on-state = ,
- d) i_{Fmax} , = = max. current,
- e) i_{Frms} , = = RMS = ,
- f) i_{Fav} , = = average = ,
- g) t_{on} , = turn-on time,
- h) t_g , = recovery time,
- i) dV/dt , max. rate of change of forward voltage,
- j) di/dt , = = = I_0 = current,
- k) T_j , the junction temperature assuming 25°C ambient.

Set Two: Circuit Revision.

2-1a) Find condition for the critical mode of current through the load shown in the Fig. asside.



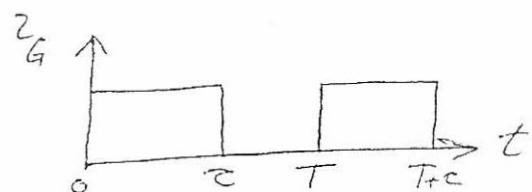
Draw waveforms of
 i , i_D , i_L , V_d , V_L & V_C .




b) What is τ_{critical} for the above part if $R = 1\Omega$, $L = 0.1$, $T = 1\text{sec}$, $C = \infty$ & $V = 0$. Draw the corresponding waves and find $i_{L,\text{av}}$, $i_{L,\text{rms}}$, $V_{L,\text{av}}$ & $V_{L,\text{rms}}$.

c) Find condition & sketch waveforms when $V = 0$.

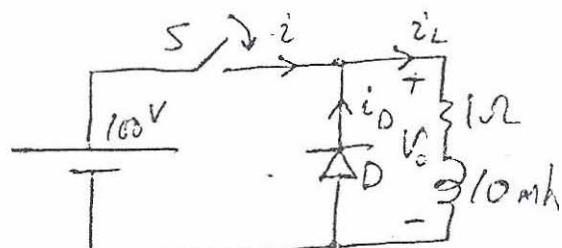
2-2 In the circuit shown, S is switched at $t=0$ when i_L was also zero. At $t=10\text{ms}$, S is opened again. Sketch to scale and find the expressions for: i , i_L , i_D & V_o .



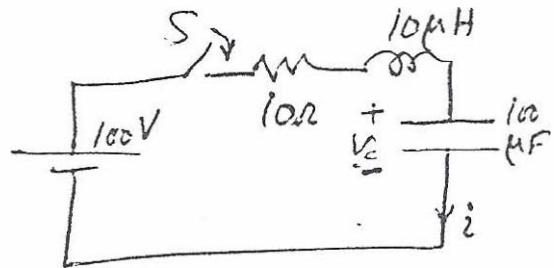
- 2-3 Determine the value of $\frac{di}{dt}$ immediately after S is put on if the initial conditions were $i=0$ & $V_c = 50$ Volt.



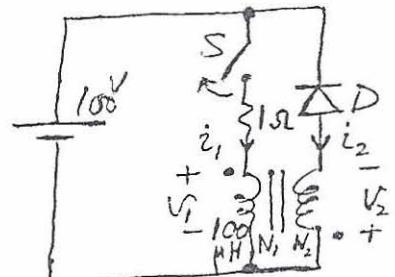- 2-4 In the circuit shown, the transformer is assumed ideal with $\frac{N_1}{N_2} = \frac{100}{300}$. S was on for very long time, then at $t=0$ it is switched off. Sketch and find the expressions for i_1 , i_2 , V_1 & V_2 .



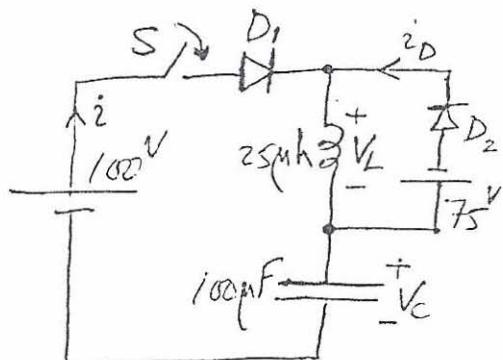- 2-5 In the circuit shown, S is switched at $t=0$, with currents in both diodes initially zero and with $-50V$ initial capacitive charge.




- a) Sketch and find expression for i , V_L , V_C & i_D


- b) Modify the circuit so that the energy supplied to the $75V$ source is pumped back to the $100V$ source without changing the time variations of i .

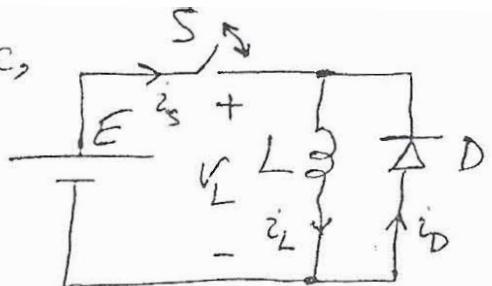2-6 For the circuit shown, with OIC, the switch is put on & off repeatedly as shown.


Sketch the waveforms for i_s , v_L , i_L & i_D . Is the operation of such circuit practical? Why?





switch state

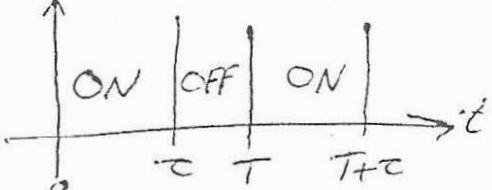

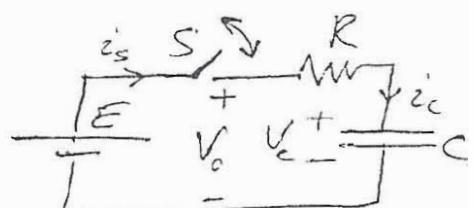2-7 Repeat the above problem for the circuit shown with waveforms of i_s , i_c , v_o & v_c .



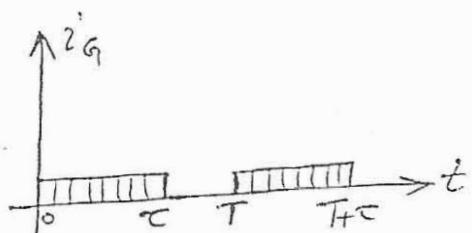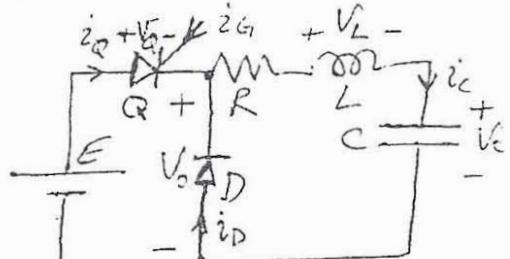2-8 For the circuit shown, with CIC, the gate current of Q is given as shown, where the end of gate pulse indicates forced commutation. Sketch waveforms for i_Q , v_Q , v_o , v_L , v_C , i_D & i_S in the case when:



- I) $R \geq 2\sqrt{L/C}$,
- II) $R = 2\sqrt{L/C}$, and
- III) $R < 2\sqrt{L/C}$. For each case, identify the condition for current mode to give:


- Continuous pattern,
- Critical pattern, and
- Discontinuous pattern. Is the circuit applicable in practise? why?

2-9

Repeat the above problem for the case when $R = 0$ (oscillatory case).


2-10

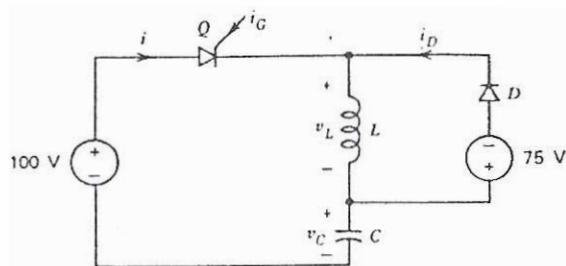In the circuit of Fig shown, $L = 30 \mu\text{H}$, $C = 120 \mu\text{F}$. If thyristor Q is turned on at $t = 0$, sketch to scale the subsequent time variations of i , v_L , v_C , and i_D . Capacitor C is initially charged to $V_{CO} = -75 \text{ V}$.



2-11

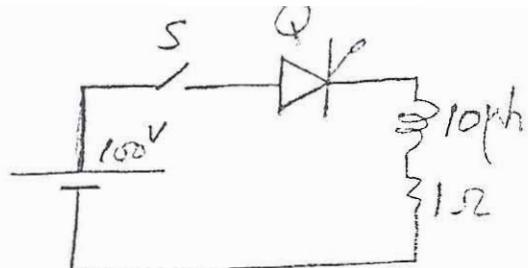In Fig the thyristor Q is not gated and have an off-state resistance of $10\text{ k}\Omega$ in the forward direction and a dV/dt limit of $50 \text{ KV}/\mu\text{sec}$. Determine, when the switch S is closed, whether or not the thyristor will turn on.




Determine, when the switch S is closed, whether or not the thyristor will turn on; and if it does, why & what rate of $dIdt$ does it start passing?

2-12

In Fig, the source is a square waveform alternating between $+100 \text{ Volts}$ & -100 Volts at 6 rpm . Sketch the waveforms when no gate is applied for Q if

I) S is put on, and

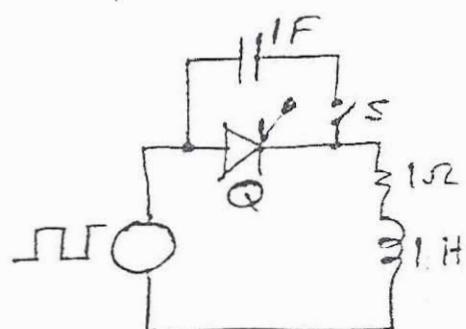II) S is put off. What difference does S makes to Q ?



Fig

Set Three: Choppers

3-1 Analyze the circuit shown in

the figure for discontinuous mode.



Sketch waveforms for:

$$i_s > i_L > i_D > V_{th} + V_L$$

Find, also, expressions for

$$i_{Lav}, i_{Lrms}$$
 & power delivered

to the load battery.

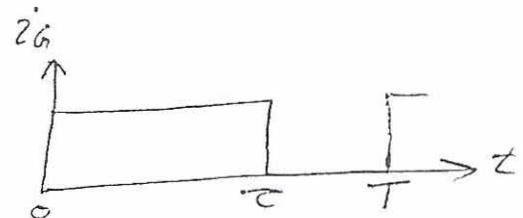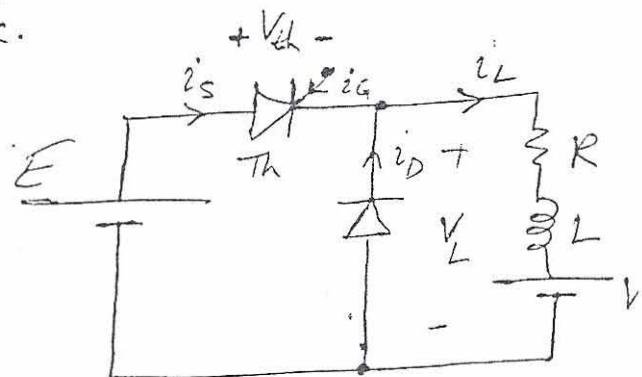

3-2 In the above figure:

$$R = 10 \Omega,$$

$$L = 10 \text{ mH},$$

$$\tau = 3 \text{ ms},$$

$$E = 10 \text{ Volts}$$

$$V = 5 \text{ Volts}.$$

a) Find $T_{critical}$,

b) IF $T_{avg} = (T_{critical} + \tau)/2$,

find %e in i_{Lav} due to linearization.

3-3 Repeat 3-1 for continuous mode.


3-4] In the circuit shown,

$$E = 600 \text{ Volt},$$

$$V = 200 \text{ Volt},$$

$$L = 1 \text{ mH}, R = 1.5 \Omega, \tau = 2.5 \text{ ms } f.$$

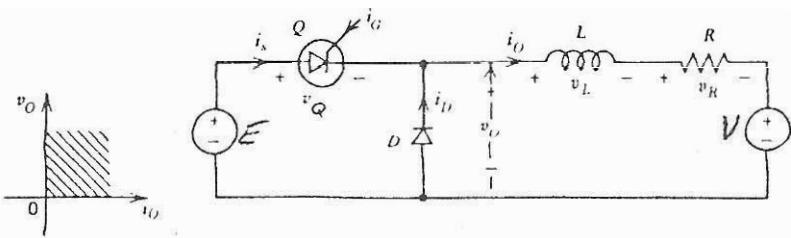$T = 4 \text{ ms}$. Show that the output current i_o is discontinuous



3-5] Draw circuit for bidirectional-current chopper-converter with positive output voltage. If the load is RL with:

$$R = 1 \Omega,$$

$$L = 1 \text{ mH},$$

$$T = 2 \text{ msec},$$


$$\tau = 0.8 \text{ ms } f$$

$$E = 100 \text{ Volts};$$

Find $i_{o_{av}}$, state current mode & commutation type.
Justify any assumptions. Can the above mentioned load condition reduce the circuit? Explain.

Sketch your waveforms for i_o 's, i_Q 's, i_D 's, v_o & i_o .

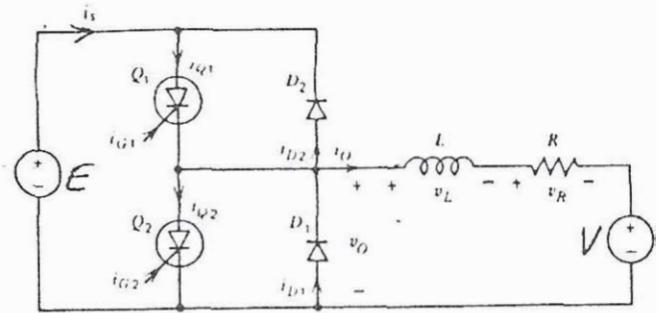3-6 In the circuit shown, $E = 600$ Volt, $V = 200$ Volt, $L = 4$ mH, $R = 1.5 \Omega$, $\tau = 2.5$ ms & $T = 4$ ms.



- (a) Calculate the average output current i_o and the average output voltage v_o .
- (b) Calculate I_{\max} and I_{\min} .
- (c) Calculate the average value of the source current i_s .
- (d) Sketch to scale the time variations of v_o , i_o , i_{Q1} , i_{Q2} , i_{D1} , i_{D2} , i_s .
- (e) Explain in what way the time variations of v_o and i_o differ from those that would be obtained with the type of chopper circuit giving positive v_o & i_o .

3-7 Sketch the circuit of a full bridge chopper feeding RL load, showing the waveforms of $i_G^{1,2}$, v_o , i_o , $i_D^{1,2}$, $i_Q^{1,2}$ & i_s . Analyze the circuit & give expressions for: $v_o(t)$, $i_o(t)$, $i_{o\text{av}}$, $i_{o\text{rms}}$, $i_{s\text{av}}$ & $i_{s\text{rms}}$ assuming large L .

3-8 Draw a half bridge chopper circuit feeding RLV load. If $E = 200$ volts, $R = 20 \Omega$, $L = 0.1$ H, $V = 50$ Volts, $\tau = 7$ ms & $T = 10$ ms, then sketch:

$$i_G^{1,2} > i_Q^{1,2} > i_D^{1,2} > i_s > i_o + V_o$$

Find, $i_{o\text{av}}$, $i_{o\text{rms}}$, K_i , $v_{o\text{av}}$, $v_{o\text{rms}} = K_v$, power delivered to V_o , power supplied by E , diode ratings for $i_{f\max}$, $i_{f\text{rms}}$ & $i_{f\text{av}}$. Justify your assumptions, mention your mode of operation.

3-9 a) Sketch the circuit of a first quadrant chopper given the following data for an RLV load:

$$E = 80 \text{ Volts},$$

$$R = 10 \Omega,$$

$$L = 50 \text{ mH},$$

$$\tau = 15 \text{ ms},$$

$$T = 25 \text{ ms} \neq$$

$$V = 30 \text{ Volts.}$$

$$I_{\min} = -\frac{V}{R} + \frac{E}{R} \cdot \frac{e^{-R\tau/L} - 1}{1 - e^{-R\tau/L}}$$

$$I_{\max} = -\frac{V}{R} + \frac{E}{R} \cdot \frac{1 - e^{-R\tau/L}}{1 - e^{-RT/L}}$$

b) Sketch the waveforms of i_o , i_Q , i_D , i_S , i_o , V_o & V_Q indicating the mode of current.

c) Find $V_{o_{av}}$, $i_{o_{av}}$, $V_{o_{rms}}$ & K_v .

3-10 Draw a Quarter Chopper to feed LV load with:

$E = 200 \text{ Volts}$, $\tau = 20 \text{ ms}$, $T = 60 \text{ ms}$, $L = 100 \text{ mH}$ and $V = 80 \text{ Volts}$. Indicate your current mode of operation and sketch the waveforms of: i_Q 's; i_Q^S ; i_D^S ; i_S ; i_o , V_Q , V_D & V_o . Find: $i_{o_{av}}$, $i_{o_{rms}}$, K_v , $V_{o_{av}}$, $V_{o_{rms}}$, K_v , power delivered to V , power supplied by E ;

diode ratings for $i_{F_{\max}}$, $i_{F_{av}}$, $i_{F_{rms}}$, I_S , τ , limited operationally?

3-11 a) Draw a half bridge chopper circuit feeding an RLV load with:

$E = 200 \text{ Volts}$, Note: $I_{\min} = -\frac{V}{R} + \frac{E}{R} \cdot \frac{e^{-i}}{e^{\frac{RT}{L}} - 1}^{\frac{RC}{L}}$
 $\tau = 7 \text{ ms}$,
 $T = 10 \text{ ms}$,
 $R = 20 \Omega$,
 $L = 1.0 \text{ henry}$
 $V = 50 \text{ Volts}$.


- b) Sketch to scale the waveforms of:
 i_G 's, i_Q 's, i_D 's, i_S , i_o , v_o & voltage v_L across L .
- c) Find i_{oav} , i_{orms} , K_i , v_{oav} , v_{orms} , K_v , power delivered to V , power supplied by E , diode ratings for i_{Fmax} , i_{Frms} & i_{Far} . Justify your assumptions if any.
- d) What mode of operation is obtained?

3-12 For the circuit shown, V_s is a 341 DCV voltage source, and Q is put on for $t = 7.00 \text{ ms}$.

The current was noted to be


continuous with min. value of $I_{\min} = 40.0 \text{ A}_{\text{av}}$.

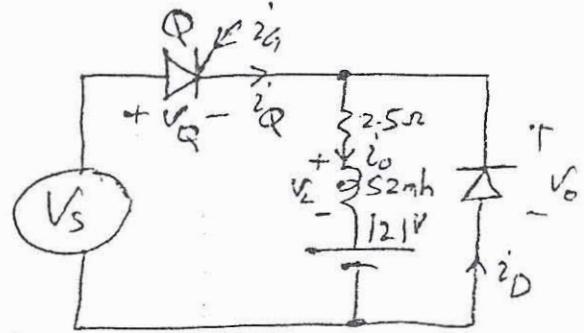1. What is the specific function of the circuit?
2. Sketch i_b , i_Q , i_o , i_D , v_o , v_Q & v_L .
3. Find the period, T , of operation, the max. current, I_{\max} , $V_{o_{\text{av}}}$, $i_{o_{\text{av}}}$, $V_{o_{\text{rms}}}$, $i_{o_{\text{rms}}}$, K_v , K_i , P_R , P_V & P_S .
4. What type of commutation is used here?
5. For Q, what are the ratings of I_{av} , I_{\max} , I_{rms} , V_{FB} , V_{RB} ?
6. For D, what are the ratings of I_{av} , I_{\max} , I_{rms} , V_{\max} ?
7. Can the current mode be discontinuous? If yes, how should L be varied?



3-13 For the circuit shown

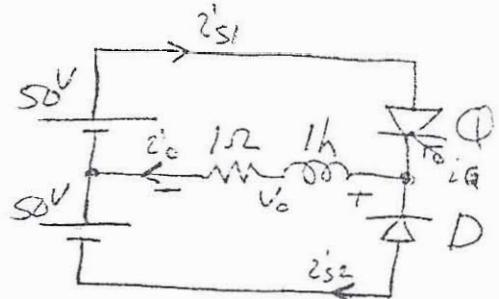- a) Classify the functions
- b) Mention the operation quadrant of i_b , v_o ,
- c) For an on state duration, $\tau = 10 \text{ ms}$, period, $T = 30 \text{ ms}$, sketch, i_b , i_{S1} , i_{S2} , i_o , v_o , v_Q , v_D and find $V_{o_{\text{av}}}$, $V_{o_{\text{rms}}}$, $i_{o_{\text{av}}}$, K_v & state mode of operation.



3-14 Draw a full bridge clapper feeding a $5\Omega - 12V$, RV load from a 100 Volt supply at a chopping rate of 1KHz. duty ratio will you require to supply 500 W average power to the 5Ω load? What power does the battery receive? What power does the source supply on average? Also find the ripple factor. Draw all associated waveforms.

Set Four: Inverters

4-1 In a sinusoidal pulse width modulated (SPWM) inverter, a triangular waveform with symmetrical peaks, P , was applied to the negative terminal of a comparator. The input signal applied to the positive terminal of the comparator is given by:

$$V_{in} = A_0 + A \sin \omega t, \text{ where}$$

$$A_0, A > 0 \quad \& \quad A_0 + A \leq P \quad \& \quad \omega = \frac{2\pi}{NT} \quad \& \\ T \text{ is the triangular period.}$$

The comparator output was used to gate the full bridge inverter switches giving a powerful output voltage V_o saturating at $\pm E$, where E is the dc supply voltage.

- I) Find $V_o(t)$
- II) Find Fourier Components of $V_o(t)$
- III) Find the distortion factor, μ .

4-2 Given $A_0 = 0 \quad \& \quad A = P$ in the above problem; Find:

- I) Fourier Components of $V_o(t)$
- II) Distortion factor, μ . And
- III) Plot the comparator inputs & output for $N = 10$

4-3 Deduce the spectrum of V_o & the distortion factor μ for:

- I) $A_0 = 0, A \ll P \& N \geq 10$
- II) $N = \infty$

4-4 Solve 4-2 for $n=2$ and phase = 0.


4-5 Repeat 4-4 for the case when the input signal lags the triangular by τ seconds, and check whether $\tau=0$ gives solution of 4-4. What should be the value of τ for n^{th} harmonic component of zero.

4-6 Sketch circuit for full bridge chopper inverter using a two-wire battery of 100 Volts, $T=1\text{ msec}$, $\tau=750\text{ usec}$, when load is RLV with $R=1\Omega$, $L=\text{very large}$ & $V=20\text{ Volts}$. Sketch: i_B 's, i_Q 's, i_D 's, V_o , i_o & i_s . Find power delivered to V & ripple factor K_r .

4-7 If SPWM was used in 4-6 with $V=0$ sketch circuit & waveforms and find the fundamental output voltage & its distortion factor.


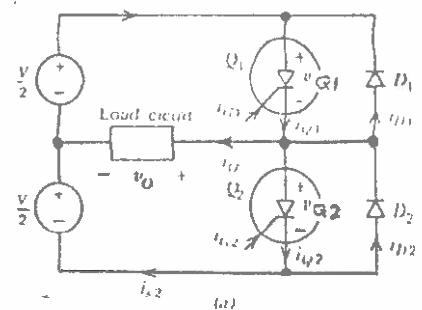
4-8 In the inverter shown $V = 500 \text{ V}$ and $T = 2000 \mu\text{s}$. The load is an RLC series circuit for which $R = 1.2 \Omega$, $\omega L = 10 \Omega$, $1/\omega C = 10 \Omega$. The gating signals are as shown.

- Sketch to scale the waveform of v_o , i_o , i_{Q1} , i_{D1} and v_{Q1} . Higher harmonics than the fundamental component may be neglected.
- Calculate the rms and average thyristor and diode currents.
- If the turn-off time of the thyristors is $50 \mu\text{s}$, state whether forced commutation will be required and determine the thyristor current at the instant of commutation.



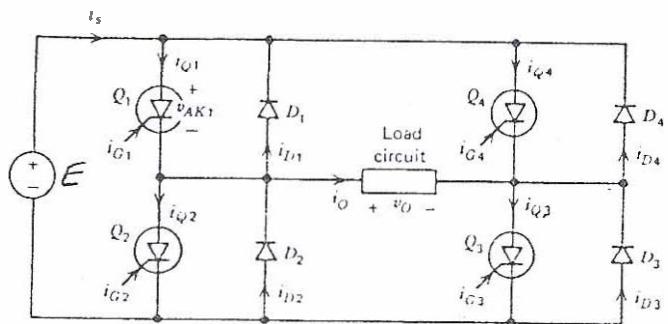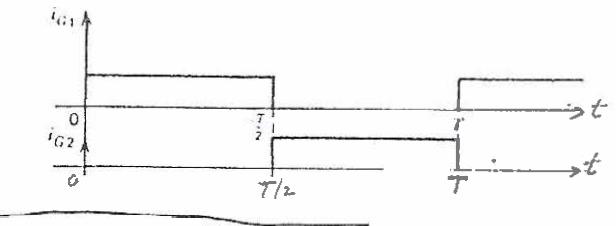4-9 The bridge inverter shown is controlled by MPWM.

Sketch gate signals for N pulses per half cycle and indicate the path of the output current, i_o . Also sketch v_o . Analyze the circuit and find the Fourier Components of v_o .



- 4-10**
- Calculate the rms values of the fundamental, fifth, and seventh harmonic components of the output voltage for a pulse width of 90° .
 - Sketch the required gating waveforms if the output voltage v_o is to be defined under all load conditions for a pulse-width of 90° .

4-11 The rms value of the fundamental component of the output in the bridge inverter of **4-9** must be $0.45E$, when E is the source voltage. Calculate the pulse-width required, sketch to scale the waveform of v_o , and determine the harmonic distortion factor K_v for voltage v_o if:

- Voltage control by single-pulse modulation is employed.
- Voltage control by multiple-pulse modulation is employed in which there are 10 pulses per half cycle of v_o .

Harmonics higher than the seventh may be neglected.

4-12 Sketch a 3-phase inverter circuit feeding a purely inductive symmetrical star load whose common point is the neutral.

If 180° scheme is employed, sketch, $i_6^>$'s, V_A , V_B , V_C , V_{AB} , V_{BC} ,

V_{CA} , V_N , V_{AN} , V_{BN} , V_{CN} , i_A , i_B , i_C , i_D 's, i_Q 's & i_S .

Show that the average power delivered by the source is $3P_0$.

4-13 Repeat **4-12** for 120° scheme (two thyristor gating) 17

4-14 Analyze the circuit for the current inverter shown in Fig. 1 aside.

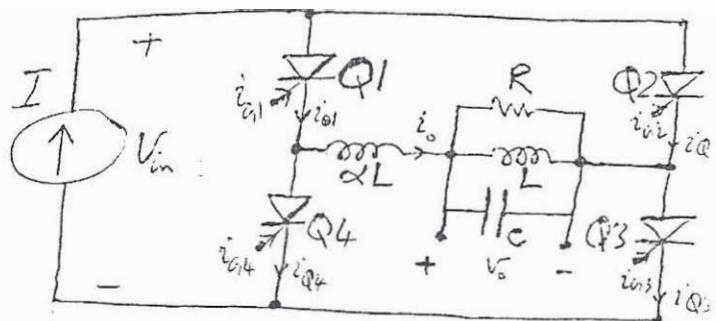


Fig. 1. Current Inverter for a Commutated Inductive Heater.

The load represents an inductive heater shunted with a commutating capacitor. The connection inductance is αL and $\alpha < 1$. The resonant frequency of the combination facilitates load commutation of the thyristors that are gated by the signals shown in Fig. 2. Use your analysis to find expressions for:

- C, the commutating capacitance giving
- Maximum output power, P.

Draw the waveforms and assume equal, t_g , for all thyristors (for $i_{Q1}, i_{Q2}, i_{Q3}, i_{Q4}, i_o, v_o + V_{in}$)

The current source is constant & continuous.

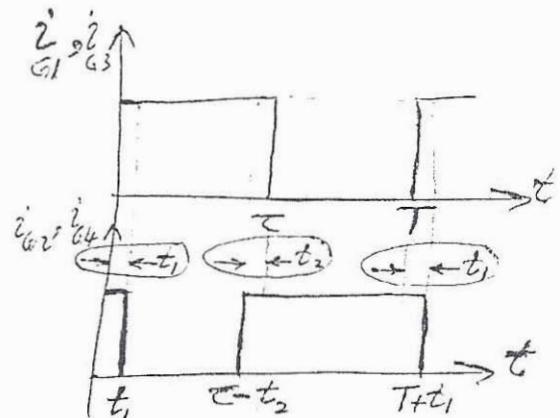



Fig. 2. Gate Signals.

4-15 Sketch circuit & waveforms for 180° scheme, 3 ϕ bridge inverter feeding a symmetrical star resistive load of $R = 2$ /phase, using 100V source. Find fundamental phase voltage & distortion factor.

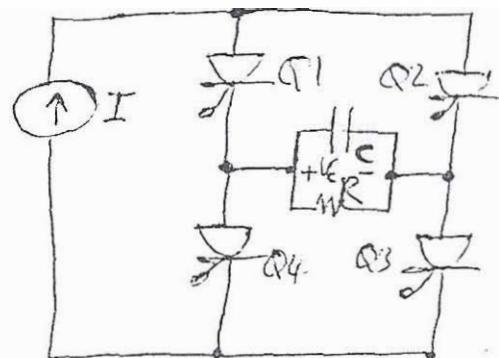4-16 The current inverter shown is used to feed the RC load with ac power at 60Hz.

$$R = 100\Omega \quad C = 1\mu F$$

Q_1 & Q_3 are turned on for one half of the cycle and Q_2 & Q_4 for the other half, then show that the four thyristors do not need forced commutation and that as soon as their gate pulses ends they turn off. Sketch to scale the time variation of V_C against i_g 's & also sketch thyristor currents, at steady state. What is the time available for turn off for thyristors?



4-17 We have a resistive load and want to supply it with an ac fundamental of 110 volts using a dc supply of 300 volts. Choose one of the following schemes, and for your scheme, sketch circuit, waveforms of $i_{g1}, i_{g2}, i_{g3}, i_{g4}$, i_o & v_o :

- Chopper inverter, giving $\frac{v_o}{v_s}$ & distortion factor of V_o .
- Single pulse modulated inverter, giving $\frac{v_o}{v_s}$ & distortion factor of i_o .
- Assuming symmetrical star, 3 ϕ inverter with $\textcircled{1} 180^\circ$ or $\textcircled{2} 120^\circ$ schemes giving %e in achievement of distortion factor of phase voltage. 19

4-18 A resistive load with parallel commutating capacitor is fed using current inverter. If $I = 50 \text{ Amp}$, $R = 10 \Omega$, $C = 400 \mu\text{F}$, $f = 200 \text{ Hz}$, then sketch the circuit showing various waveforms of i_g 's; i_Q 's; i_o ; V_Q ; V_s ; V_o . Find the power delivered to the load, the average supply voltage, V_o^{rms} , V_o^{av} , V_o^{rms} , t_r , time available for thyristor recovery; V_{FB} , V_{RB} & $\frac{dV}{dt}$ ratings of thyristors.

4-19 Draw the circuit of a full bridge current inverter feeding a $52 \parallel 11 \mu\text{F}$ load from $100 \text{ Amp DC source}$. If the operating frequency is 50 Hz , draw the associated waveforms, and find, assuming instant turn off, the recovery times of M_I of load.


Set Five: Rectifiers

5-1 Analyze the circuit

shown here for the

HWCR with:

- RLV load
- RL load
- R load.

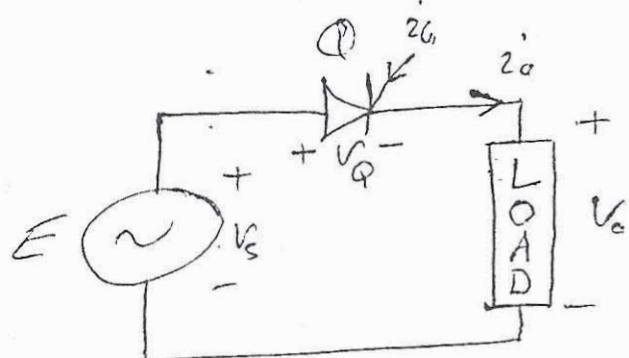

Sketch the waveforms of:

v_s , i_0 , i_o , v_o , v_Q and

find expressions for:


$i_o(t)$, $v_o(t)$, P , $i_{o\text{av}}$, $V_{o\text{av}}$, $i_{o\text{rms}}$, $V_{o\text{rms}}$, K_i & K_v for $P_{o\text{av}}$.
where β is the extinction angle obtained through natural commutation

5-2 Repeat 5-1 for the case of forced commutation at β . Mention the required modification to your load circuit if any. Sketch your circuit.

5-3 Repeat 5-1 parts (a) & (b) when L is very large

5-4 Repeat 5-2 part (a) & (b) when L is very large.

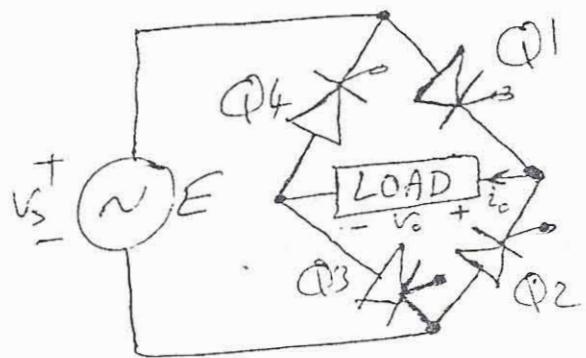5-5 Analyze the FWCR shown here for the case when $Q_1 \neq Q_3$ are both fired at α & $Q_2 \neq Q_4$ are both fired at $\pi + \alpha$. All thyristors are line commutated, and current is



- a) Discontinuous, and
- b) Continuous. Load is
 - I) RLV load,
 - II) RL load &
 - III) R load.

For each case, draw: i_b^s , i_Q^s , V_S , V_o & i_o .

Find expression for: V_{av} , i_{oav} & K_v .

5-6 Repeat **5-5** for the case when $Q_3 \neq Q_4$ are replaced by diodes $D_3 \neq D_4$ respectively.

5-7 Repeat **5-5** when force commutation is used, sketch your circuit and mention any modification.

5-8 Repeat **5-6** when force commutation is used, sketch circuit.

5-9 For all the preceding four problems repeat for L very large. (22)

- 5-10 a) Draw the circuit for 3 ϕ HWCR with RL load, using symmetrical gating at α ,
 b) Sketch all the associated waveforms, and
 c) Give range of α for continuous load current.
 d) Find $V_{o\text{ar}}$ &
 e) Find $i_{o\text{ar}}$.

5-11 Repeat 5-10 for 3 ϕ FWCR.

- 5-12 For the circuit shown V_s is $341 \sin 120\pi t$, Volts, and Q is fixed at $\alpha = 90^\circ$.
1. What is the specific function of the circuit? What is the control range of α ?
 2. Sketch V_s , i_6 , i_Q , i_C , i_D , V_o & V_Q for the current mode of operation. Mention it.
 3. What is the conduction times of both Q & D? What type of commutation is used?
 4. Find $V_{o\text{ar}}$, $i_{o\text{ar}}$, $V_{o\text{rms}}$ & power delivered to V.
 5. For Q find t_g , V_{FB} & V_{KB} & for D find P_J & T_J given 25°C ambient, $0.5^\circ\text{C}/\text{W}$ cooling & V_F


Set Six: Converters

6-1 Analyze the converter shown for RL load.

Give range of α , assuming symmetrical

gating. Sketch: v_s , i_g 's, i_Q 's, v_o , i_o + v_Q .

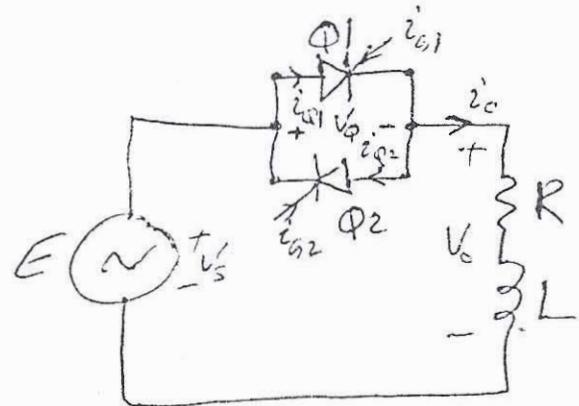Find expressions for: $v_{o\text{rms}}$, $i_{o\text{rms}}$, $P_{o\text{av}}$ + pf .




6-2 If α was 90° in the above problem, sketch the above mentioned waveforms and find values for the above mentioned expressions.


Set Seven: Cycloconverters.

7-1

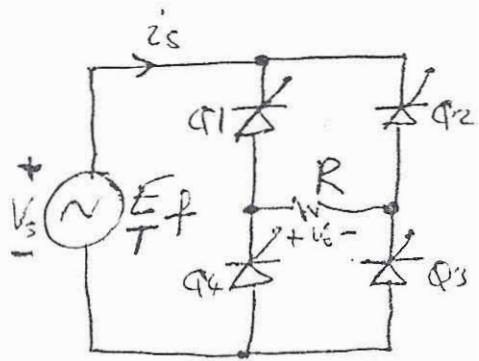- a) Name the function of the circuit shown for the given gate signals.



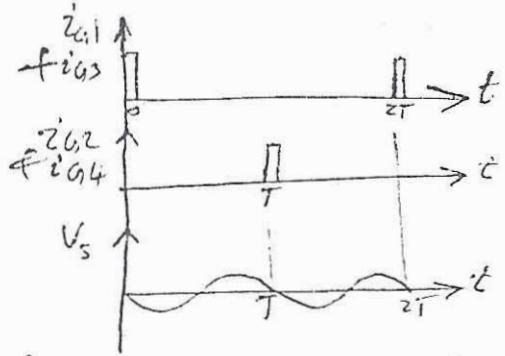- b) Sketch all the waveforms
 c) Find the fundamental output current,
 d) Find the power,
 e) Find the power factor,
 f) Find the fundamental power factor,
 g) Find the distortion factor of the output.
 h) What is the disadvantage of the circuit from the supply point of view?



7-2

- Draw a circuit that can supply a resistive load by controlled ac supply at 300 Hz using 3³ supply at 60 Hz. Sketch the waveforms of i_Q 's, i_o , v_o for symmetrical gating at α . Mention control range of α and the corresponding value of the fundamental output voltage. Also get expression for the voltage distortion factor.

Set Eight: Firing & Commutation Circuits.

8-1

Draw a circuit that can generate a train of pulses using 741 amplifier, 311 comparator & discrete capacitors & resistors. Analyze your circuit showing the relationships governing the period of your train & width of pulse. How can you change these two parameters. Sketch any relevant waveforms.

8-2


In the circuit shown, $E = 600 \text{ Volts}$,

$$L' = 42 \mu\text{h},$$

$$C' = 6 \mu\text{F},$$

$$T = 2.5 \text{ ms} \text{ &}$$

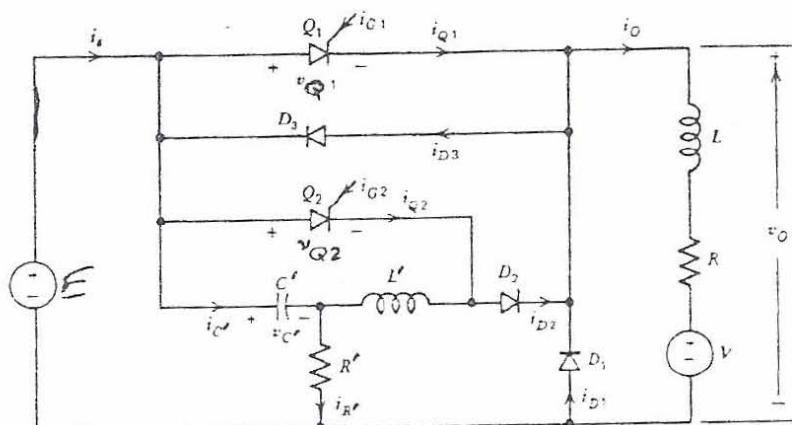i_o at instant of commutation is 150 Amp. Explain the circuit in general and then, for the given values :



(a) Calculate the time t_q available for turn-off of thyristor Q_1 .

(b) Calculate the total commutation interval t_c .

(c) Sketch to scale the time variations of i_C , i_{Q2} , i_{D2} , i_{Q1} , i_{D1} , v_C , v_{Q1} & v_{Q2} .

(d) Determine the time available for turn-off of thyristor Q_2 .

8-3

For the circuit shown in 8-2 C' was $1 \mu\text{F}$.

What would happen, show the corresponding curves & figs.

$$[1-1] \quad \text{Total thermal resistance} = 0.5 + 1 = 1.5 \text{ }^{\circ}\text{C}/\text{W}$$

$$\therefore P_{\text{thyristor,av}} = \frac{1}{T} \int_0^T i_t^2 \cdot v_{th} dt = \frac{1}{T} \int_0^{T/3} I \cdot (1 + 0.01I) dt = \\ = I(1 + 0.01I) \frac{T/3}{T} = I(1 + 0.01I)/3$$

$$\therefore [I(1 + 0.01I^2)/3] * 1.5 = 125 - 35 = 90$$

$$\therefore I + 0.01I^2 = 90 * 3 / 1.5 = 180$$

$$\therefore I^2 + 100I - 18000 = 0$$

$$\therefore I = \frac{-100 \pm \sqrt{100^2 + 4(18000)}}{2} = \frac{-100 \pm \sqrt{82,000}}{2} = 93.2 \text{ OR } -193.2$$

\therefore Maximum value of I is 93.2 Amps since thyristor can't allow negative currents.

1-3 ① The output is half sinusoid, approximately.

a) $i_{o_{\text{avg}}} = \frac{2\sqrt{2}E * \pi}{2\pi R^2} = \frac{\sqrt{2}E}{\pi R} = \frac{\sqrt{2} * 220}{\pi * 1} = 99.035 \text{ Amps} > 100 \text{ Amps } (\because X)$

b) $i_o = i_o(\delta)$ where $i_o(0) = 0$.

$$\therefore i_o(\omega t) = \frac{\sqrt{2}E}{Z} \left[\sin(\omega t - \phi) + \sin \phi \cdot e^{-\alpha t / \tan \beta} \right]$$

$$\therefore i_o(\delta) = 0 = \frac{\sqrt{2}E}{Z} \left[\cos(\delta - \phi) + \sin \phi e^{-\delta / t_{\text{on}} \cdot \frac{1}{\tan \beta}} \right]$$

$$\therefore \cos(\delta - \phi) = \cos \phi \cdot e^{-\delta / t_{\text{on}} \cdot \frac{1}{\tan \beta}}$$

$$\therefore \delta = t_{\text{on}}^{-1} \frac{1}{\tan \beta} = 45^\circ = \frac{\pi}{4} \text{ rad} \therefore \sqrt{2} e^{\delta} \cos(\delta - \pi/4) - 1 = 0 \quad \therefore \delta = 2.2841 \text{ rad}$$

$$\therefore i_{o_{\text{max}}} = i_o(\delta) = \frac{\sqrt{2} * 220}{\sqrt{2}} \left[\sin(2.2841 - \pi/4) + \frac{1}{\sqrt{2}} e^{-2.2841} \right] = 235.3 \text{ Amps}$$

$$\therefore i_{o_{\text{max}}} = 235.3 \text{ Amps} > 100 \text{ Amps} \quad (\because X)$$

c) Q will have to withstand the negative half cycle of supply.

$$\therefore V_{R_{\text{max}}} = \sqrt{2}E = \sqrt{2} * 220 = 311.13 \text{ Volts} > 300 \text{ Volts } (\because X)$$

d) Q is blocking no forward voltage since $\alpha = 0$ $(\because \text{OK})$

e) (OK)

f) $\frac{dV}{dt} = 0$ (since $\alpha = 0$) $\leq 10 \text{ V/μsec}$ $(\because \text{OK})$

g) $\left. \frac{di}{dt} \right|_{\text{max}} = i_o(0) = \frac{\sqrt{2}E}{Z} (\cos \phi + \sin \phi e^{0^\circ} (-\alpha t / \tan \beta)) = 0 \quad (\because \text{OK})$

h) Q will extinct at β given by:

$$\sqrt{2} e^{\beta} \sin(\beta - \pi/4) + 1 = 0 \quad \therefore \beta = 3.9407 \text{ rad}$$

$\therefore Q$ will remain reverse biased between β & 2π

$$\therefore \text{Should recover in } \frac{2\pi - \beta}{\omega} = 6.214 \times 10^3 \text{ sec} = 6.214 \text{ msec}$$

$$\therefore t_{off} = 6.214 > t_g = 20 \text{ ns} \quad (\because \text{OK})$$

$$\# i) f = 60 \text{ Hz} \Rightarrow T = 16.6 \text{ msec} \ggg t_{on} \quad (\because \text{OK})$$

$$\# j) \text{ power dissipated in } Q = \frac{1}{2\pi} * 1V * 235.3 * \frac{2}{\pi} * \pi A = 74.9 \text{ W}$$

$$\therefore \text{Temperature rise} \approx \frac{75}{Q} = \infty \quad \therefore Q \text{ will boil mad.} \quad (\because X)$$

$\therefore Q$ will not operate satisfactorily, since it fails in:
a, b, c & j.

② The output is exactly one quarter sinusoid.

$$\# a) \therefore i_{o_{min}} = \frac{2\sqrt{2}E \pi/2}{2\pi^2 R} = \frac{E}{\sqrt{2}\pi R} = \frac{110}{\sqrt{2}\pi * 10} = 2.476 \text{ Amps} < 10 \quad (\because \text{OK})$$

$$\# b) \therefore i_{o_{max}} = \sqrt{2}E/R = \frac{\sqrt{2} * 110}{10} = 15.56 \text{ Amps} < 100 \quad (\because \text{OK})$$

$\# c) Q$ will have to withstand the negative half of supply cycle.

$$\therefore V_{R_{min}} = \sqrt{2}E = 155.6 \text{ Volts} < 300 \text{ Volts} \quad (\because \text{OK})$$

$\# d) Q$ will have to withstand half the positive half cycle.

$$\therefore V_{F_{max}} = 155.6 \text{ Volts} > 100 \text{ Volts} \quad (\because X)$$

$\# e) (\text{OK})$

8) $\frac{dV}{dt}$ is worst (at $\omega t = 0$) = $V_2 E \omega = \sqrt{2} * 110 * 2\pi * 60$
 $= 58.65 \text{ KV/sec} < 10 \text{ V/msec}$ ($\therefore \text{OK}$)
 (no need for the snubber circuit).

9) $dI/dt = \infty$ ($\therefore \text{X}$)

1) Q will extinct at π \therefore It has $\frac{2\pi - \pi}{\omega}$ to recover = 8.33 ms

$\therefore t_{off} = 8.33 \text{ ms} > 200 \text{ ns}$ ($\therefore \text{OK}$)

i) $f = 60 \text{ Hz} \neq T = 16.7 \text{ ms} \ggg 1 \text{ ns}$ ($\therefore \text{OK}$)

j) Power dissipated in Q $\approx \frac{1}{2\pi} * 1V * \dots = \pi$

\therefore Temperature rise = $2.5 \text{ W} * \frac{1^\circ \text{C}}{\text{W}} = 2.5^\circ \text{C}$

\therefore Junction temperature = Ambient + $2.5 \approx 30 + 2.5 = 32.5^\circ \text{C}$

$\therefore 32.5^\circ \text{C} < 150^\circ \text{C}$ ($\therefore \text{OK}$).

\therefore Q will not operate satisfactorily, since it fails in:

d \neq g.

1-4 a) V_{FB} = forward blocking voltage = 50 Volts

∴ V_{FB} rating of the thyristor must be ≥ 50 Volts

b) V_{RB} = reverse blocking voltage = 0.7 Volts

∴ V_{RB} rating of the thyristor must be ≥ 0.7 Volts

c) V_F = forward on-state voltage = 1 Volt

d) $i_{F_{max}}$ = maximum forward current = 20 Amp

∴ $i_{F_{max}}$ rating of the thyristor must be ≥ 20 Amp

e) $i_{F_{rms}} = \text{forward rms current} = \sqrt{\frac{1}{20} \left(\frac{1}{3} * 20^2 * 0.001 + 20^2 * 9.989 + \frac{1}{3} * 20^2 * 0.1 \right)}$

$$= \sqrt{199.853} = 14.137 \text{ Amp. } (\text{Note: } i_{F_{rms}} \approx 20 * \sqrt{\frac{t_{on}}{T}} = \frac{20A}{\sqrt{2}})$$

∴ $i_{F_{rms}}$ rating of the thyristor must be ≥ 14.137 Amp.

f) $i_{F_{av}} = \text{average forward current} = \frac{1}{20} \left(\frac{1}{2} * 20 * 0.001 + 20 * 9.989 + \frac{1}{2} * 20 * 0.1 \right)$

$$= 9.9945 \text{ Amp } (\text{Note } i_{F_{av}} \approx 20 * \frac{t_{on}}{T} = 10 \text{ Amp})$$

∴ $i_{F_{av}}$ rating of the thyristor must be ≥ 9.9945 Amp.

g) $t_{on} = \text{turn on time} = 0.001 \text{ ms} = 1 \mu\text{sec}$

∴ t_{on} rating of the thyristor must be $\leq 1 \mu\text{sec}$

- h) $t_g = \text{recovery time} = 0.3 \text{ ms} = 300 \mu\text{sec}$
 ∵ t_g rating of the thyristor must be $\leq 300 \mu\text{s}$
- i) $\frac{dV}{dt}_{\text{max}} = \text{maximum rate of change of forward voltage} = \frac{50V}{0.5ms} = 100 \text{ KV/sec}$
 ∵ $\frac{dV}{dt}_{\text{max}}$ rating of the thyristor must be $\geq 100.0 \text{ KV/sec.}$
- j) $\frac{di}{dt}_{\text{max}} = \text{maximum rate of change of forward current} = \frac{20A}{0.001ms} = 20 \text{ KA/ms}$
 ∵ $\frac{di}{dt}_{\text{max}}$ rating of the thyristor must be $\geq 20 \text{ KA/ms.}$
- k) Power consumed by thyristor $= \frac{1}{T} \int_{0}^{T} i_Q \cdot V_Q dt =$
 $= \frac{1}{20} \left[\int_{0}^{0.01} \left(\frac{20}{0.001} t \right) \cdot \left(50 - \frac{49}{0.001} t \right) dt + 20 \times 1 \times 9.989 + \int_{9.99}^{10} \frac{20(10-t)}{0.01} \times 1 dt \right]$
 $= \frac{1}{20} \left[\int_{0}^{0.01} (10t^2 - 9800t^3) dt + 199.78 + \left[\frac{20(10-t)^2}{2} \right]_{9.99}^{10} \right] =$
 $= \frac{1}{20} \left[10 \frac{t^3}{3} - 9800 \frac{t^4}{4} \Big|_0^{0.01} + 199.78 + K \cdot 0 \right] =$
 $= \frac{1}{20} \left[10 \frac{0.001^3}{3} - 9800 \frac{0.001^4}{4} + 199.78 + 0 \right] =$
 $= \frac{1}{20} \left[0.00000333 - 0.00000245 + 199.78 \right] = \frac{1}{20} (0.00000088 + 199.78) = 10.003 \text{ Watt}$
 (Note $\pi 20 \times 1 \times \frac{1}{20} = 10 \text{ Watt}$)
- ∵ $\frac{T_j - 30}{10.003} = 10 \Rightarrow T_j = 30 + 100.03 = 130.03^\circ\text{C}$
- ∵ $T_j = \text{junction temperature} = 130.03^\circ\text{C.}$
- ∵ T_j rating of the thyristor must be $\geq 130.03^\circ\text{C}$

$$1-5) a) V_{FB} \geq 100 \text{ Volts}$$

$$b) V_{RB} \geq 50 \text{ Volts}$$

$$c) V_F = 2 \text{ Volts}$$

$$d) i_{F_{\max}} \geq 50 \text{ Amp}$$

$$e) i_{F_{rms}} \geq \sqrt{\frac{1}{4} \int_0^4 i_Q^2 dt} = \frac{1}{4} \cdot \sqrt{\left[\frac{1}{3} \cdot 0.02 \cdot 50^2 + 1.98 \cdot 50^2 + \frac{1}{3} \cdot 2 \cdot 2 \cdot 50^2 + 0 \right]} = 35.8 \text{ A}$$

$$\therefore i_{F_{rms}} \geq 36 \text{ Amp}$$

$$f) i_{F_{av}} \geq \frac{1}{4} (\frac{1}{2} \cdot 0.02 \cdot 50 + 1.98 \cdot 50 + \frac{1}{2} \cdot 2 \cdot 50) = 26.13 \text{ Amp}$$

$$\therefore i_{F_{av}} \geq 26 \text{ Amp.}$$

$$g) t_{on} \leq 0.02 \text{ ms} = 20 \mu\text{sec}$$

$$h) t_g \leq \frac{50}{100+50} \cdot (4 - 3.2) = 0.26 \text{ ms} = 267 \mu\text{sec.}$$

$$i) \left| \frac{di}{dt} \right|_{\max} \geq \frac{150}{4-3.2} \cdot \frac{V}{ms} = 187.5 \text{ KV/sec}$$

$$j) \left| \frac{di}{dt} \right|_{\max} \geq \frac{50A}{0.02ms} = 2.5 \text{ MA/sec} = 2.5 \text{ A}/\mu\text{sec}$$

$$k) P_Q = \frac{1}{4} \int_0^4 i_Q V_Q dt \approx \frac{1}{4} \cdot \left[0 + \frac{2}{3} \cdot 0.02 \cdot \frac{100}{2} \cdot \frac{50}{2} + 1.98 \cdot 2 \cdot 50 + \frac{1}{2} \cdot 2 \cdot 2 \cdot 50 \right] = \frac{1}{4} \cdot (16.67 + 198 + 10) = 56.16 \text{ Watt} = \frac{\Delta T_j}{5}$$

$$\therefore \Delta T_j = 5 \cdot 56.16 = 280.83 \text{ } ^\circ\text{C} = T_j - 25 \text{ } ^\circ\text{C}$$

∴ $T_j \geq 306 \text{ } ^\circ\text{C}$, max. junction-temperature rating of thyristor.

To find the ratings of Q
surviving the shown voltage
and current waveforms:

$$\therefore I_{Q_{\text{max}}} > 30 \text{ A},$$

$$I_{Q_{\text{AV}}} > \frac{30}{5} = 6 \text{ Amp},$$

$$I_{Q_{\text{rms}}} > 30\sqrt{\frac{1}{5}} = 13.4 \text{ A},$$

$$I_{\text{break}} = \begin{cases} -10\mu\text{A} \text{ } \square -10\text{V} \\ 30\text{mA} \text{ } \square 250\text{V} \end{cases},$$

$$V_{Q_{\text{FB}}} > 250 \text{ V},$$

$$V_{Q_{\text{RB}}} > 100 \text{ V}$$

$$V_{Q_{\text{on}}} = 1.5 \text{ V}, \quad \left| \frac{dV_Q}{dt} \right|_{\text{max}} > \frac{250 + 100}{10 \text{ ms}} = 35 \text{ V/ms}$$


$$t_g < 20 + 10 * \frac{100}{350} = 22.86 \text{ ms}$$

$$t_{on} < 10\mu\text{s}$$


$$\left| \frac{di_Q}{dt} \right|_{\text{max}} > \frac{30 \text{ A}}{10\mu\text{s}} = 3 \text{ A}/\mu\text{s}$$

$$P_{Q_{\text{av}}} > \frac{45}{5} + \frac{7.5}{5} = 10.5 \text{ W}$$
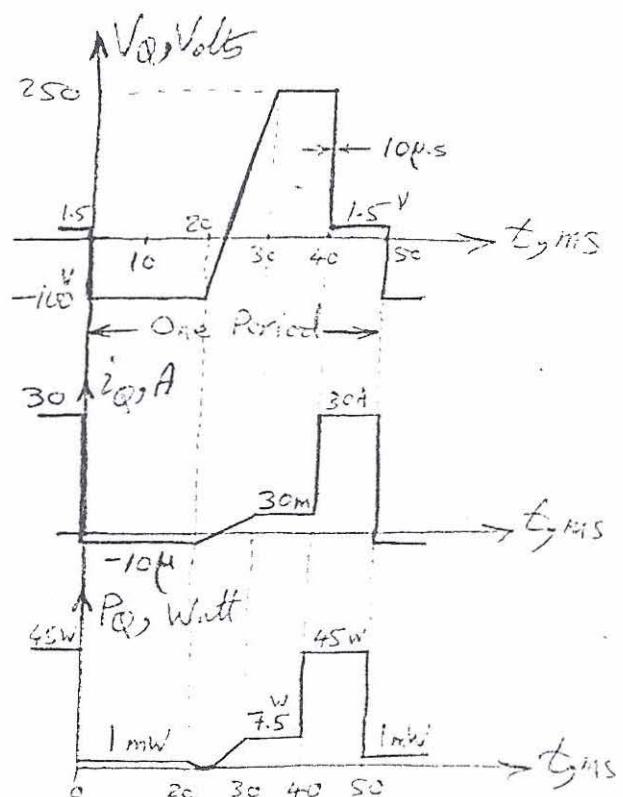
$$\therefore T_j > \frac{10.5}{1} + 25 = 35.5^\circ\text{C}$$



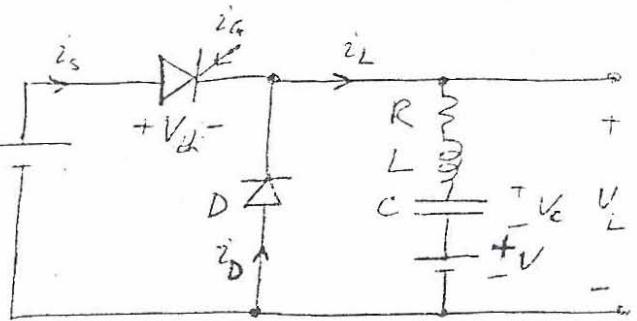2-1 a) Critical mode of current occurs when the current, i_L , starts from zero, at the instant the thyristor is fired on, and increases till it is shut down whereby it will flow through the diode



till it reaches zero again just at the instant the thyristor is fired again for the next cycle. The associated waveforms are shown in the figure aside for one steady-state cycle.

Note that i_L is always positive & hence V_C is going to charge up in every cycle till it reaches $E-V$ whereby no current will flow in the thyristor. To avoid this case C must be ∞ such that $\frac{dV_C}{dt} = \frac{i_L}{C} = 0$

\therefore For critical mode to happen, $C = \infty$ i.e. short-circuited. Hence, $V_C = 0$ (say) as shown.


Now, during $t \in [0, \tau]$:

$$\therefore i_L(t) = \frac{E-V}{R} + A e^{-Rt/L} \quad \text{f. since } i_L(0) = 0 \quad \therefore A = \frac{V-E}{R}$$

$$\therefore i_L(t) = \frac{E-V}{R} \left(1 - e^{-Rt/L} \right) \quad (1)$$

$$\therefore i_L(\tau) = \frac{E-V}{R} \left(1 - e^{-R\tau/L} \right). \quad (2)$$

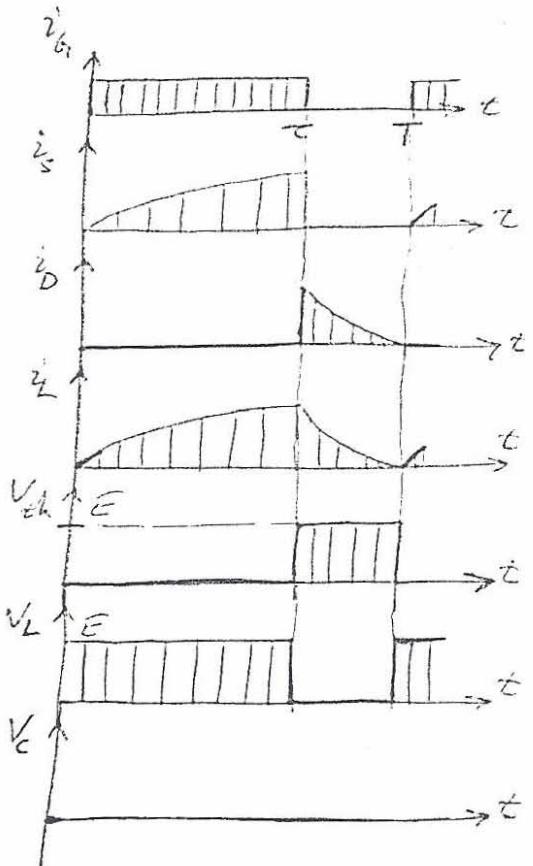When the thyristor is switched off, D becomes on during $t \in [\tau, T]$. Hence:



$$i_L(t) = \frac{-V}{R} + Be^{-Rt/L} \quad \text{& since } i_L(t) = \frac{E-V}{R} (1 - e^{-Rt/L})$$

$$\therefore \frac{E-V}{R} (1 - e^{-Rt/L}) = \frac{-V}{R} + Be^{-Rt/L}$$

$$\therefore B = \left[\frac{E-V}{R} (1 - e^{-Rt/L}) + \frac{V}{R} \right] \cdot e^{Rt/L}$$

$$\therefore i_L(t) = \frac{-V}{R} + \left[\frac{E-V}{R} (1 - e^{-Rt/L}) + \frac{V}{R} \right] e^{-R(t-\tau)/L} \quad (3)$$

Now the mode of current is critical when $i_L(T) = 0$

$$\therefore 0 = \frac{-V}{R} + \left[\frac{E-V}{R} (1 - e^{-R\tau/L}) + \frac{V}{R} \right] e^{-R(T-\tau)/L} \quad (4)$$

$$\text{OR: } 0 = -V + E (1 - e^{-R\tau/L}) e^{-R(T-\tau)/L} + V e^{-RT/L}$$

$$\therefore V (1 - e^{-RT/L}) = E \cdot e^{-R(T-\tau)/L} + (1 - e^{-R\tau/L})$$

$$\text{OR } 2V \cdot e^{-RT/2L} \sinh(RT/2L) = 2E e^{-R(T-\tau)/L} \cdot e^{-R\tau/2L} \cdot \sinh(R\tau/2L)$$

$$\text{OR } V e^{(RT/2L)} \sinh(RT/2L) = E e^{(R\tau/2L)} \sinh(R\tau/2L) \quad (5)$$

\therefore Eq. 5, also, must be satisfied to get critical mode for i_L .

b) If $V=0$ in (5) then $E e^{(R\tau/2L)} \sinh(R\tau/2L)$ must be zero

$\therefore R\tau/2L = 0 \quad \therefore \tau = 0$ (limit case, or no operation)

$$\therefore i_{L_{\text{av}}} = i_{L_{\text{rms}}} = V_{L_{\text{av}}} = V_{L_{\text{rms}}} = 0$$

c) If $V=0$, C must be ∞ & hence as before $\tau_{\text{out}} = \infty$

\therefore Again we have limit case & $i_L(t) = V(t) = 0$

2-2

At $t \in [0, 10]$ msec

$$\therefore i_L^{(0)} = i_L(0) = \frac{100}{1} + Ae^{-1t/0.01} \\ = 100 + A e^{-10t} \text{ Amps}$$

$$\therefore i_L(0) = 0 \quad \therefore A = -100$$

$$\therefore i_L(t) = 100(1 - e^{-100t}) \text{ Amps}, t \in [0, 10] \text{ msec}$$

$$\therefore i_L(10 \text{ msec}) = 100(1 - e^{-100 \times 10 \times 10^{-3}}) = \\ = 100(1 - e^{-1}) = 63.2 \text{ Amps}$$

When S is off the diode is on \therefore at $t \in [10 \text{ msec}, \infty)$:

$$\therefore i_L(t) = Be^{-1t/10 \times 10^{-3}} = \\ = Be^{-100t}$$

$$\therefore i_L(10 \text{ ms}) = 63.2$$

$$\therefore 63.2 = Be^{-100(10 \text{ ms})}$$

$$\therefore B = 63.2 \cdot e^{100(10 \text{ ms})}$$



$$\therefore i_L(t) = 63.2 e^{-100(t-10 \text{ ms})} \text{ Amps}, t \in [10 \text{ ms}, \infty)$$

2-3

$$100 = 10\mu \dot{i} + V_c + 10i$$

$$\therefore V_c = 50 \text{ V} \quad \dot{i} \approx 0 \quad \Rightarrow \quad 100 = 10\mu \dot{i} + 50 + 0 \Rightarrow \dot{i} = \frac{50}{10\mu} \cdot \frac{A}{S}$$

$$\therefore \left. \frac{di}{dt} \right|_{t=0} = 5 \text{ A}/\mu\text{s}$$

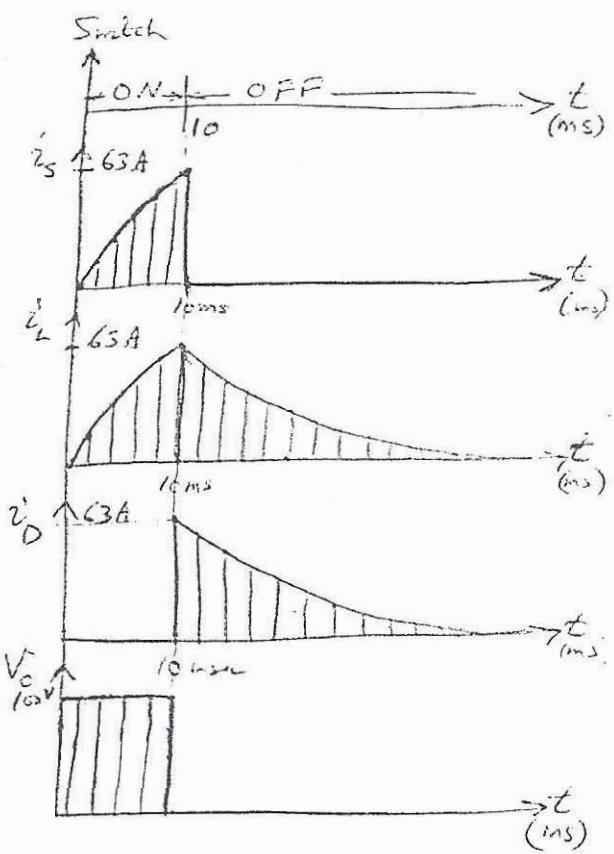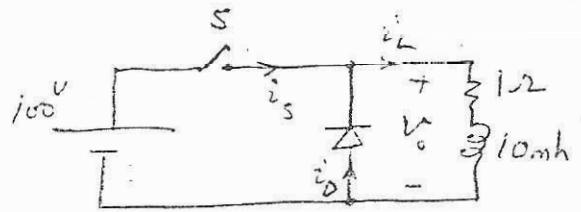


2-4

$$i_1(0^-) = \frac{100V}{100} = 100 \text{ Amp} \Rightarrow V_1(0^-) = 0 \Rightarrow V_2(0^-) = 0 \Rightarrow i_2(0^-) = 0$$

At $t = 0^+$, the circuit referred to primary would like:

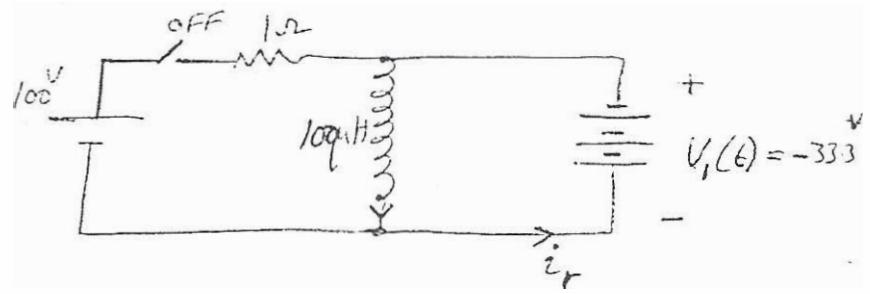The reason is due to transforming negative voltage that makes the diode on.



$$\therefore V_2(t) = -100V$$

$$\therefore V_1(t) = -100 * \frac{N_1}{N_2} = -100 * \frac{100}{300} = -\frac{100}{3} = -33.3 \text{ Volts}$$

$$\therefore -i_2 = i_r \frac{N_1}{N_2} = i_r * \frac{100}{300} = i_r / 3$$


$$\text{Now } i_r = 100 \text{ Amp} - \frac{33.3V}{100 \mu\text{h}} t = \left[100 - 333 \times 10^6 t (\text{sec}) \right] \text{ Amps}$$

$$\therefore i_r \text{ will stop at } t = \frac{100}{333 \times 10^6} = 300 \text{ m sec}$$

The waveforms are shown here.

Note:

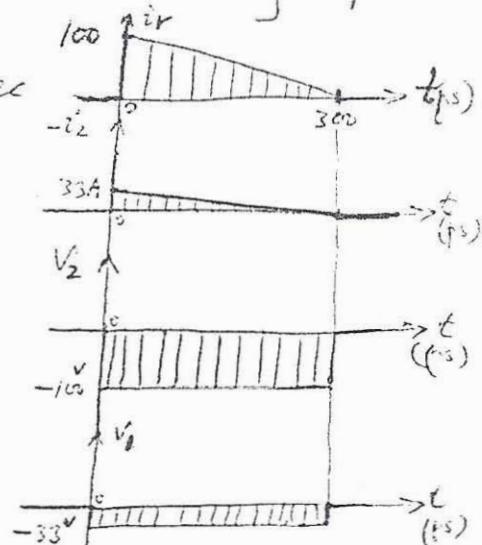- After $t = 300 \mu\text{s}$ Current i_2 tries to reverse. This makes the diode off. Hence, $V_2 = 0$ again.
- Hence $V_1 = 0$ again. So is i_r .
- As for i_1 it is zero throughout.



2-5

$$\text{a) } V_c(t) = \frac{\frac{1}{sC}}{\frac{1}{sC} + sL} \cdot 100 = \frac{1}{s^2 L C + 1} \cdot 100 \\ = \frac{1}{2500 \mu^2 s^2 + 1} \cdot 100$$

$$= 100 + A \sin \frac{t}{50\mu} + B \cos \frac{t}{50\mu} \\ = 100 + A \sin 2\omega K t + B \cos 2\omega K t$$

$$\therefore V_c(0) = -50 = 100 + B \quad B = -150 \text{ volts}$$

$$\therefore i(0) = 0 = C \dot{V}_c(0) = 100 \mu \times 2\omega K \times A \Rightarrow A = 0$$

$$\therefore V_c(t) = 100 - 150 \cos 2\omega K t \text{ volts}$$

$$V_L = 100 - V_c(t) = 150 \cos 2\omega K t \text{ volts.}$$

$$\text{f. } i(t) = C \dot{V}_c(t) = 100 \mu \times 150 \times 2\omega K \times \sin 2\omega K t$$

$$\therefore i(t) = 300 \sin 2\omega K t = i_L(\text{Amps}), \text{ period} = 100\pi / 100\mu = 314.16 \mu\text{sec}$$

These expressions are valid as long as $V_L > -75^\circ$ ($i < D_2$ is off). (Fig. 1).

$$\text{i.e. till: } 150 \cos 2\omega K t = -75 \Rightarrow t' = \frac{1}{2\omega K} \cos^{-1} \frac{-1}{2}$$

$$\text{i.e. till } t = t' = 104.72 \mu\text{sec}$$

After that V_L is clamped to -75 volts and D_2 becomes on. (Fig. 2).

$$\text{f. } V_c = 100 + 75 = 175 \text{ volts}$$

$$\therefore i = C \dot{V}_c = 0$$

$$\text{f. } i_D = i_L \text{ governed by:}$$

$$25\mu i = -75 \Rightarrow i = \frac{-75}{25\mu} (t - t') + I$$

$$\therefore i_D(t) = i(t) = 300 \sin(2\omega K t + 104.72\mu) = I$$

$$\therefore I = 259.81 \text{ Amps}$$

$$\therefore i_L(t) = i_D(t) = 259.81 - 3M(t - 104.72\mu)$$

$$\text{f. } V_L = -75 \text{ volts} \quad \text{f. } V_c = 175 \text{ volts, valid for } t \geq t' \text{ till } t = t'' \text{ where } i_L(t'') = 0 \therefore t'' = 191.32 \mu\text{s}$$

At $t > 191.32 \mu\text{s}$ D_2 is off, D_1 is also off $\text{f. } i = i_D = i_L = 0$

$\text{f. } V_c$ keeps at 175 volts $\text{f. } V_L = 0$.

The waveforms are as shown.

(b) The energy trapped in the inductance could be returned to the 100V source if a transformer is used as shown,

where the secondary circuit referred to primary is just as before but the 75V source is now replaced by $100 N_1 / N_2$

\therefore Choose the transformer turns ratio to be $\frac{N_1}{N_2} = \frac{75}{100} = 3/4$.



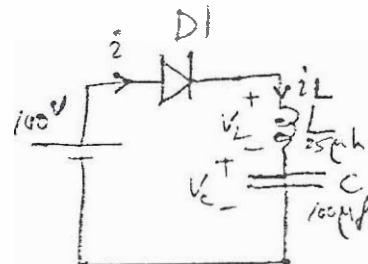
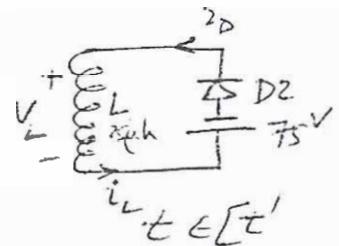


Fig. 1. $t \in [0, t']$

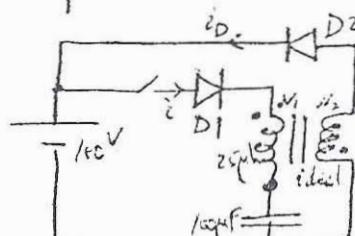

$t \in [t']$

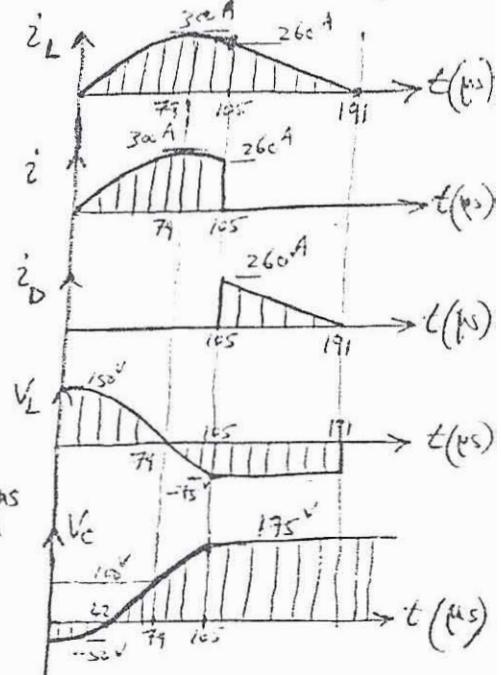

2-10

$$L = 30 \mu H$$

$$C = 12.0 \mu F$$

$$E = 100 \text{ Volts}$$

$$V = 75 \text{ Volts}$$

$$V_{C_0} = -75 \text{ Volts}$$

This is the same as

problem $\frac{6}{72}$ but values
are different.

V_L will make part of oscillation
till it reaches V whereby it
is held constant at V and the
inductor current decays to 0.

$$\text{Let } \omega = 1/\sqrt{LC} = 16.6 \text{ Krad/sec}$$

$$\therefore V_C(t) = E + A \sin \omega t + B \cos \omega t$$

$$\text{at } V_{C_0} = V_C(0) = E + B \Rightarrow B = -E + V_{C_0}$$

$$\text{at } i(0) = \infty = C V_C(t) \Big|_{t=0}$$

$$\therefore \omega A = 0 \Rightarrow A = 0$$

$$\begin{aligned} \therefore V_C(t) &= E - (E - V_{C_0}) \cos \omega t \\ &= E (1 - \cos \omega t) + V_{C_0} \cos \omega t \\ &= 100 - 175 \cos \omega t. \end{aligned}$$

$$\text{at } V_L(t) = 100 - V_C = 175 \cos \omega t \quad \text{at } i_L(t) = C V_C(t) = 350 \sin \omega t$$

$$V_L(t_1) = -75 = 175 \cos \omega t_1$$

$$\therefore t_1 = 120.8 \text{ usec} \quad \text{at } i_L(t_1) = 316.2 \text{ Amps} \quad \text{at } V_C(t_1) = 175 \text{ Volts}$$



$$\text{at } T = 2\pi/\omega = 377.0 \text{ usec.}$$

The i_L decrease linearly to zero whereas $V_L = -75^V$ and $V_L = 175^V$

$$\therefore i_L = -\frac{75}{30} (t - t_1) + i_L(t_1) = -2.5 (t(\mu s) - 120.8) + 316.2 \text{ Amps}$$

$$\therefore i_L(t_2) = 0 \Rightarrow t_2 = 247.3 \text{ usec.}$$

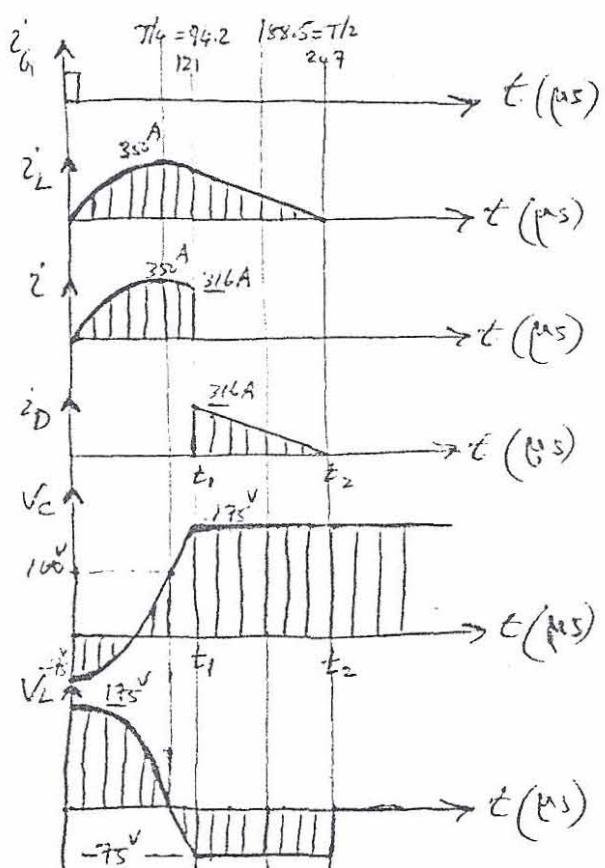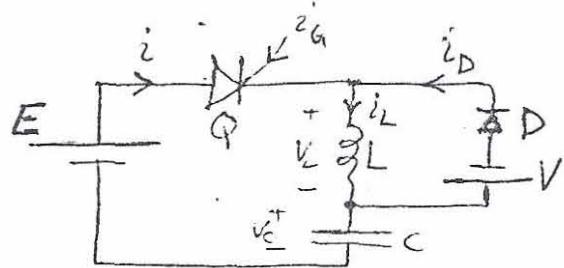At $t > t_2$ all waveforms are zero except $V_C = 175 \text{ Volts}$.



2-11

The equivalent circuit at A-state is as shown.

Assuming S is put on at $t=0$, then it's an RL circuit with time constant

$$\frac{L}{R} = \frac{10\text{H}}{1000\Omega} \approx 1.0 \text{ nsec}$$

$$\therefore i_o(t) = \frac{100}{10001} + Ae^{-\frac{t}{1n}}, \text{ Amp}$$

$$\because i_o(0) = 0 \quad \therefore A = -\frac{100}{10001} \approx 10 \text{ mA}$$

$$\therefore i_o(t) \approx 10(1 - e^{-t/1n}), \text{ mA}$$

$$\therefore V_Q(t) = 10K * 10m(1 - e^{-t/1n}) = \\ = 100(1 - e^{-t/1n}), \text{ Volts}$$



$$\therefore \frac{dV_Q(t)}{dt} = 100 * (-e^{-t/1n}) * (-\frac{1}{1n}) \\ = 100G e^{-t/1n}, \text{ V/s} \\ = 100e^{-t/1n}, \text{ KV/μs}$$

\therefore Worst dV/dt is at start when $t=0$, whereby $\frac{dV_Q}{dt} = 100K/\mu s$


$\therefore Q$ can withstand $50 \text{ KV}/\mu s$, then the value indicated above will cause it to fire, as soon as S is put on.
Hence, when S is put on Q becomes on without gating.
This is because of the inherent capacitance of Q.

The initial rate of load current is $\frac{di_o(0)}{dt} = \frac{dV_Q(0)}{dt}/10K = 10A/\mu s$

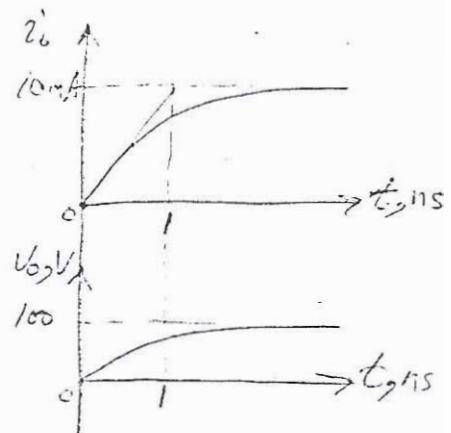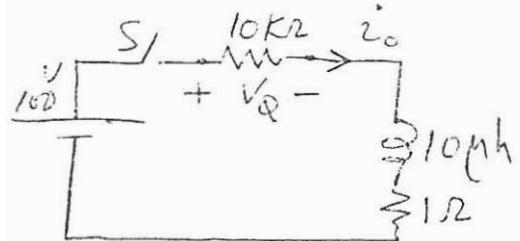(Note $\frac{di_o(0)}{dt}$ is also obtained by $\frac{100V}{10\mu h} = 10A/\mu s$).



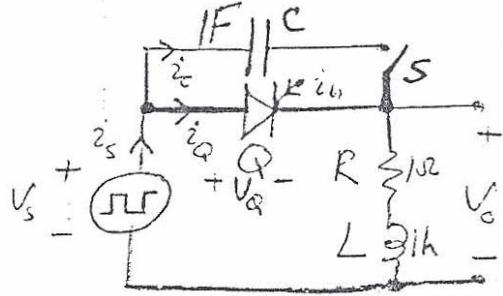2-12 (i) When the thyristor Q is not gated, it remains off. Hence, for the case when the switch S is put on, V_s sees an RLC series circuit.



$$\therefore V_s(t) = \begin{cases} E & \text{for } t \in [0, T/2) \\ -E & \text{for } t \in [T/2, T] \end{cases}$$

where T is the period of V_s

$$\therefore V_c(t) = V_Q(t) = \begin{cases} E + e^{-t/2} (A_1 \sin(\sqrt{3}t/2) + A_2 \cos(\sqrt{3}t/2)) & t \in [0, T/2) \\ -E + e^{-(t-T)/2} (B_1 \sin(\sqrt{3}(t-T)/2) + B_2 \cos(\sqrt{3}(t-T)/2)) & t \in [T/2, T] \end{cases}$$

The waveforms at steady-state are as shown where: $V_c(t)$ is smooth due to continuity of $V_c(t) + \dot{V}_c(t)$; and during one half-cycle of input, V_c makes $\frac{\sqrt{3}T/2}{2\pi} \times \frac{60}{6 \times 2} = 0.69$ cycle > 1 cycle. Hence, the RLC dynamic oscillations will not show very clearly during a half cycle input step. Also note that $i_c(t)$ is continuous but not smooth, hence, $V_c(t)$ is not continuous. Due to symmetry of both half-cycles:

$$\therefore V = V_c(t) = E + e^{-T/4} (A_1 \sin \frac{\sqrt{3}T}{4} + A_2 \cos \frac{\sqrt{3}T}{4}) = -E + B_2 \quad (1)$$

$$\therefore -V = V_c(0) = V_c(T) = E + A_2 = -E + e^{-T/4} (B_1 \sin \frac{\sqrt{3}T}{4} + B_2 \cos \frac{\sqrt{3}T}{4}) \quad (2)$$


$$\text{From (1)} \Rightarrow \therefore B_2 = E + V \quad (3)$$

$$\text{into (2)} \Rightarrow \therefore B_1 = [(E-V)e^{-T/4} - (E+V)\cos \frac{\sqrt{3}T}{4}] / \sin \frac{\sqrt{3}T}{4} \quad (4)$$

$$\text{From (2)} \Rightarrow \therefore A_2 = -E - V = -B_2 \quad (5)$$

$$\text{into (1)} \Rightarrow \therefore A_1 = [-(E-V)e^{-T/4} + (E+V)\cos \frac{\sqrt{3}T}{4}] / \sin \frac{\sqrt{3}T}{4} = -B_1 \quad (6)$$

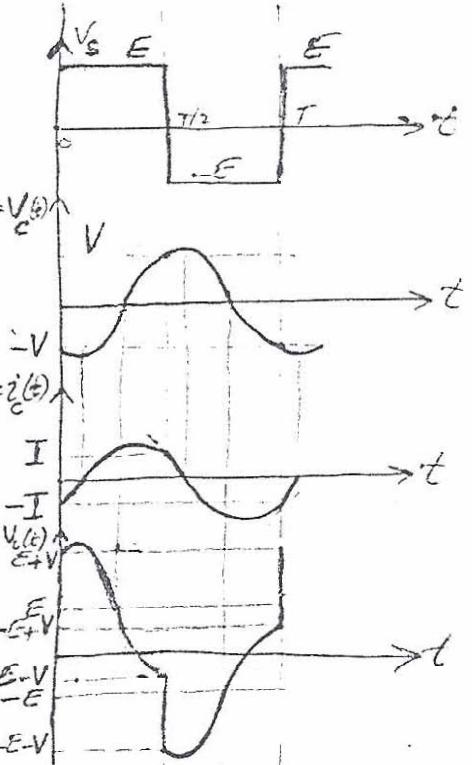Hence, one half-cycle is enough and other could be obtained using symmetry. (4)



And since $i_c(t) = \frac{dV_c(t)}{dt} = \dot{V}_c(t)$

$$\therefore I = i_c\left(\frac{T}{2}\right) = \dot{V}_c\left(\frac{T}{2}\right) = e^{-\frac{t}{2}} \left[\left(A_1/2 - \sqrt{3}A_2/2 \right) \sin\left(\frac{3\pi t}{2}\right) + \left(-A_2/2 + \sqrt{3}A_1/2 \right) \cos\left(\frac{3\pi t}{2}\right) \right]$$

$$= e^{-\frac{T}{4}} \cdot \left[-\frac{A_1 + \sqrt{3}A_2}{2} \cdot \sin\frac{\sqrt{3}T}{4} + \frac{\sqrt{3}A_1 - A_2}{2} \cdot \cos\frac{\sqrt{3}T}{4} \right] \quad (7)$$

$$\therefore -I = i_c(0) = \dot{V}_c(0) = \frac{\sqrt{3}A_1 - A_2}{2} \quad (8)$$

(5) + (6) into (7) + (8) gives: (Note: $T = \frac{60 \text{ sec}}{6} = 10 \text{ sec.}$)

$$0 = A_1 \left[\left\{ -\sin\left(\frac{3\pi}{4}\right) + \sqrt{3} \cos\left(\frac{3\pi}{4}\right) \right\} e^{-\frac{T}{4}} + \sqrt{3} \right] + A_2 \left[\left\{ -\sqrt{3} \sin\left(\frac{3\pi}{4}\right) - \cos\left(\frac{3\pi}{4}\right) \right\} e^{-\frac{T}{4}} - 1 \right]$$

$$= A_1 \left[2 \cos\left(\frac{\sqrt{3}\pi}{4} + \frac{\pi}{6}\right) \cdot e^{-\frac{T}{4}} + \sqrt{3} \right] - A_2 \left[2 \sin\left(\frac{\sqrt{3}\pi}{4} + \frac{\pi}{6}\right) \cdot e^{-\frac{T}{4}} + 1 \right]$$

$$= 1.7552 A_1 - 0.83747 A_2$$

$$= 1.7552 [13.532 E - 12.723 V] - 0.83747 [-E - V] =$$

$$= 24.589 E - 21.503 V$$

$$\therefore V = \frac{24.589 E + 100}{21.503} = 114.35 \text{ Volts} \quad (9)$$

$$\text{into (5)} \Rightarrow \therefore A_2 = -B_2 = -214.35 \text{ Volts} \quad (10)$$

$$\text{into (6)} \Rightarrow \therefore A_1 = -102.28 \text{ Volts} \quad (11)$$

\therefore The equation of $V_c(t)$ in the first symmetrical half is given by:

$$V_c(t) = V_q(t) = 100 - e^{-\frac{t}{2}} \left[102.28 \sin\left(\frac{\sqrt{3}\pi}{2} t\right) + 214.35 \cos\left(\frac{\sqrt{3}\pi}{2} t\right) \right], \text{ Volts}$$

$$\text{Using (8), (10) & (11):} \quad (12)$$

$$\therefore I = -18.602 \text{ Amperes.} \quad (13)$$

The equation for $i_c(t)$ in the first symmetrical half is given by:

$$i_c(t) = i_s(t) = e^{-\frac{t}{2}} \left[236.77 \sin\left(\frac{\sqrt{3}\pi}{2} t\right) + 18.602 \cos\left(\frac{\sqrt{3}\pi}{2} t\right) \right], \text{ Amp, } t \in [0, T] \quad (14)$$

These values modify the waveforms shown earlier to be as indicated beside. Note that i_Q is zero, and that:

$$V_c(0) = -114.35 \text{ Volts},$$

$$\dot{V}_c(0) = i_c(0) = 18.602 \text{ Amp or } V/s,$$

$V_c(t)$ is zero at $t = 1.2686 \text{ sec}$,

$$\dot{V}_c(1.2686) = i_c(1.2686) = 116.31 \text{ Amp or } V/s,$$

$V_c(t)$ is max. at $t = 3.5371 \text{ sec}$,

$$i_c(3.5371) = 0,$$

$$V_c(3.5371) = 135.09 \text{ Volts},$$

$$V_c(5) = -V_c(0) = 114.35 \text{ Volts},$$

$$\dot{V}_c(5) = i_c(5) = -\dot{V}_c(0) = -i_c(0) = -18.602, \text{ Amp or } V/s$$

$i_c(t)$ is max. at $t = 1.1187 \text{ sec}$,

$$i_c(1.1187) = 117.57 \text{ Amp},$$

$$i_c(1.1187) = 0 \text{ Amp/s}$$

$$V_c(1.1187) = -17.565 \text{ Volts},$$

$i_c(t)$ is min. at $t = 4.7463 \text{ sec}$,

$$i_c(4.7463) = -19.167 \text{ Amp},$$

$$i_c(4.7463) = 0 \text{ Amp/s}, \text{ and}$$

$$V_c(4.7463) = 119.17 \text{ Volts}.$$

Also note the corner points at $i_S(t)$ curve.



Zeros of $i_S(t)$ occurs at $t = 2.3279 \text{ sec}$ & 7.3279 sec .

Hence, for Q, it is forward biased during $t \in [1.27, 6.27] \text{ sec}$, and in this interval the max. dV/dt is occurring at start when $t = 1.27 \text{ sec}$ with value of 116.31 V/sec

II) When Q is integrated and S is off then,

$$i_S(t) = i_c(t) = i_Q(t) = V_S(t) = 0.$$

Hence, $V_Q(t) = V_S(t)$ as shown.

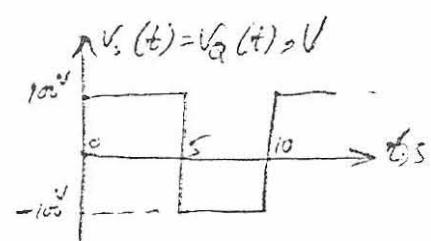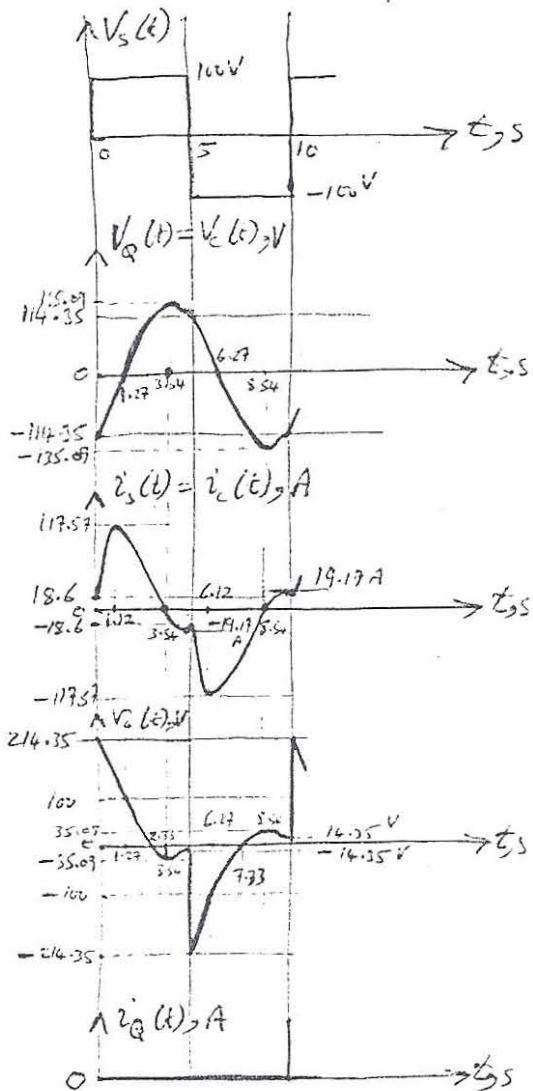

Hence, for Q, it is forward biased during $t \in [0, 5] \text{ sec}$ and in this interval max. dV/dt is at start with value of infinity. This value causes Q to be on at the start of interval although gate is

absent. Hence, current will flow into the load through Q. When the input reverses at $t=5$ sec current will try to reverse with the result of commutating the thyristor. Waveforms are hence obtained as shown.

Note that the load current is exponential with time constant of $L/R = 1$ sec and that almost it reaches its steady-state value of 100 Amp at the end of $t=5$ sec, i.e:

$$i_Q(t) = 100(1 - e^{-t}), \text{ Amp}, t \in [0, 5] \text{ sec}$$

$$+ i_Q(5) = 99.33 \text{ Amp} \approx 100 \text{ Amp}$$

After $t=5$ sec, $i_Q(t)$ is given by

$$i_Q(t) = -100 + A_3 e^{-(t-5)}, \text{ Amp}, \text{ where}$$


$$i_Q(5) = 99.33 = -100 + A_3 \therefore A_3 = +199.33 \text{ Amp}$$

$$\therefore i_Q(t) = -100 + 199.33 e^{-(t-5)}, \text{ Amp}, t \in [5, t_c], \text{ where}$$

$$i_Q(t_c) = 0 \quad \therefore t_c = 5.6898 \text{ sec after which } i_Q(t) = 0.$$


$$\therefore i_Q(t) = \begin{cases} 100(1 - e^{-t}), \text{ Amp}, & t \in [0, 5] \text{ sec} \\ -100 + 199.33 e^{-(t-5)}, \text{ Amp}, & t \in [5, 5.6898] \text{ sec} \\ 0, \text{ Amp}, & t \in [5.6898, 10] \text{ sec} \end{cases}$$

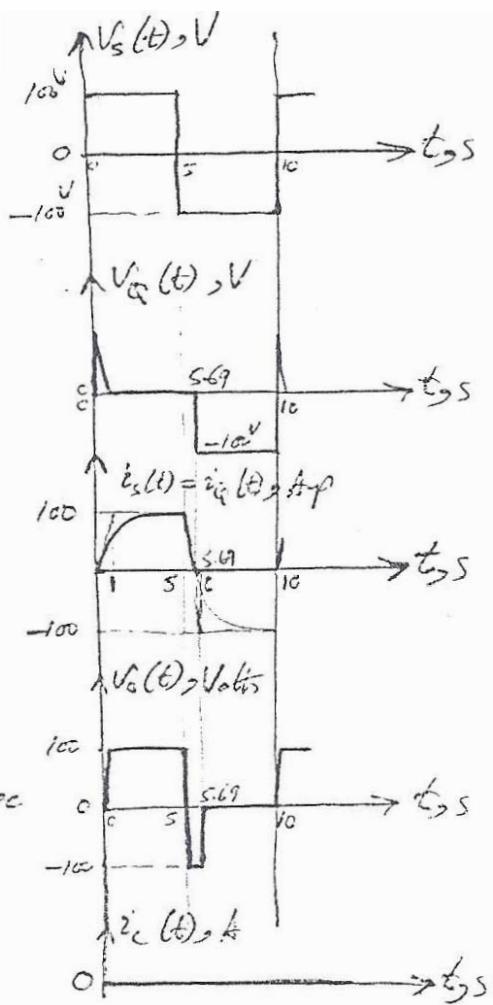Hence, S introduces a snubber capacitor that protects against $\infty \frac{di}{dt}$ rate at start of input positive step, with the result of Q being brought on only through gating current.



3-1

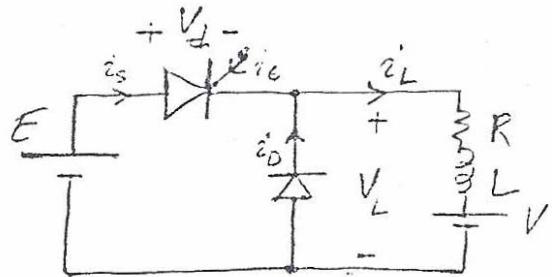Since current mode is discontinuous, then current starts at steady state from zero when gate pulse is applied.



$$\therefore i_L(t) = \frac{E-V}{R} + A e^{-Rt/L}$$

$$\text{for } t=0 = \frac{E-V}{R} + A$$

$$\therefore i_L(t) = \frac{E-V}{R} (1 - e^{-Rt/L}), t \in [0, \tau]$$

$$\therefore i_L(\tau) = I = \frac{E-V}{R} (1 - e^{-R\tau/L}) \quad (1)$$

for For $t \in (\tau, t_0]$

$$\therefore i_L(t) = B e^{-R(t-\tau)/L} - \frac{V}{R}$$

$\approx i_L(\tau) = I$ the current continuity.

$$\therefore i_L(\tau) = I = B - \frac{V}{R}$$


$$\therefore B = I + \frac{V}{R}$$

$$\therefore i_L(t) = \left(I + \frac{V}{R} \right) e^{-R(t-\tau)/L} - \frac{V}{R} \quad t \in (\tau, t_0]$$

$$\therefore i_L(t_0) = 0 = \left(I + \frac{V}{R} \right) e^{-R(t_0-\tau)/L} - \frac{V}{R}$$

$$\therefore (V+IR) = V e^{R(t_0-\tau)/L} \quad \therefore \frac{t_0-\tau}{L/R} = \ln \left(1 + \frac{IR}{V} \right)$$
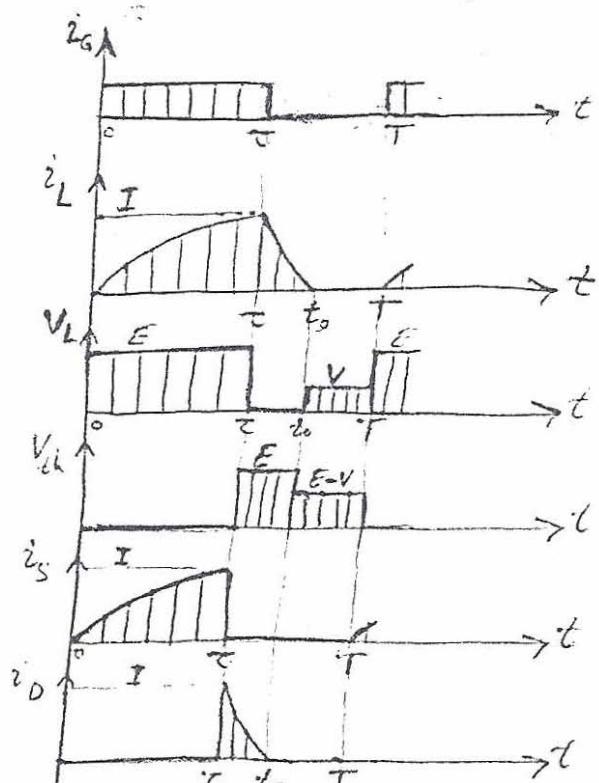
$$\therefore t_0 = \tau + \frac{L}{R} \ln \left(1 + \frac{IR}{V} \right)$$



45

But, from (1) :

$$1 + \frac{IK}{V} = 1 + \frac{E-V}{V} \cdot (1 - e^{-Kt/L}) = \left(\frac{E}{V} - 1 \right) e^{-Kt/L} + \frac{I}{V}$$

$$\therefore t_0 = \tau + \frac{L}{R} \ln \left[\frac{E}{V} \left(1 - e^{-K\tau/L} \right) + e^{-K\tau/L} \right] \quad (3)$$

Hence: to get discontinuous mode we must have:

$T \geq t_0$. where t_0 as given in (2) or (3)

The current $i_L(t) = 0 \quad \text{in } t \in [t_0, T]$.

$$\begin{aligned} i_{L_{av}} &= \frac{1}{T-t_0} \int_{t_0}^T i_L(t) dt = \\ &= \frac{1}{T-t_0} \left[\int_{t_0}^{\tau} i_L(t) dt + \int_{\tau}^{t_0} i_L(t) dt \right] \\ &= \frac{1}{T-t_0} \left[\int_{t_0}^{\tau} \frac{E-V}{R} (1 - e^{-K(t-\tau)/L}) dt + \int_{\tau}^{t_0} \left[\left(I + \frac{V}{R} \right) e^{-K(t-\tau)/L} - \frac{V}{R} \right] dt \right] \\ &= \frac{1}{T-t_0} \left[\frac{E-V}{R} \left(t + \frac{L}{R} e^{-K(t-\tau)/L} \right) \Big|_{t_0}^{\tau} + \left[\left(I + \frac{V}{R} \right) \frac{e^{-K(t-\tau)/L}}{-K/L} - \frac{V}{R} \right] \Big|_{\tau}^{t_0} \right] = \\ &= \frac{1}{T-t_0} \left[\frac{E-V}{R} \cdot \left(\tau + \frac{L}{R} e^{-K(\tau-t_0)/L} - \frac{L}{R} \right) + \left(I + \frac{V}{R} \right) \frac{L}{R} \cdot \left(1 - e^{-K(\tau-t_0)/L} \right) - \frac{V}{R} (t_0 - \tau) \right] \\ &= \frac{1}{T-t_0} \left[\frac{E-V}{R} \cdot \tau - \frac{IL}{R} + \left(I + \frac{V}{R} \right) \cdot \frac{L}{R} \cdot \left(1 - \frac{V}{V+IK} \right) - \frac{V}{R} \cdot \frac{L}{R} \ln \left(1 + \frac{IK}{V} \right) \right] \\ &= \frac{1}{T-t_0} \left[\frac{E-V}{R} \cdot \tau - \frac{IL}{R} + \frac{L}{R^2} \cdot IR - \frac{VL}{R^2} \ln \left(1 + \frac{IK}{V} \right) \right]. \end{aligned}$$

$$\therefore i_{L_{av}} = \frac{E-V}{R} \cdot \frac{\tau}{T-t_0} - \frac{V}{R} \cdot \frac{L}{RT-t_0} \cdot \ln \left(1 + \frac{IK}{V} \right) \quad (4)$$

\therefore power delivered to load battery, $P_d = i_{L_{av}} \cdot V =$

$$= V \cdot \left(\frac{E-V}{R} \cdot \frac{\tau}{T-t_0} - \frac{V}{R} \cdot \frac{L}{RT-t_0} \cdot L \cdot \left(1 + \frac{IK}{V} \right) \right) \quad (5)$$

for $i_{L_{rms}}$

$$\begin{aligned}
i_L^2 &= \frac{1}{T} \int_0^T i_L^2(t) dt = \frac{1}{T} \left[\int_0^{\tau} i_L^2(t) dt + \int_{\tau}^{t_0} i_L^2(t) dt \right] = \\
&= \frac{1}{T} \left[\left(\frac{E-V}{R} \right)^2 \left(t + \frac{2L}{R} e^{-Rt/L} - \frac{L}{2R} e^{-2Rt/L} \right)_0^{\tau} + \right. \\
&\quad \left. + \left(I + \frac{V}{R} \right)^2 \cdot \frac{e^{-2R(t-\tau)/L}}{-2R/L} \int_{\tau}^{t_0} + \left(\frac{V}{R} \right)^2 t \Big|_{\tau}^{t_0} - \frac{2V}{R} \left(I + \frac{V}{R} \right) \frac{e^{-R(t-\tau)/L}}{-R/L} \right] \\
&= \frac{1}{T} \left[\left(\frac{E-V}{R} \right)^2 \left(\tau + \frac{2L}{R} (e^{-R\tau/L} - 1) - \frac{L}{2R} (e^{-2R\tau/L} - 1) \right) + \left(\frac{V}{R} \right)^2 (t_0 - \tau) + \right. \\
&\quad \left. + \left(I + \frac{V}{R} \right)^2 \cdot \frac{L}{2R} \cdot \left(1 - e^{-2R(t_0-\tau)/L} \right) - \frac{2V}{R} \left(I + \frac{V}{R} \right) \cdot \frac{L}{R} \left(1 - e^{-R(t_0-\tau)/L} \right) \right] \\
&= \frac{1}{T} \left[\left(\frac{E-V}{R} \right)^2 \left\{ \tau + \frac{2L}{R} \cdot \left(-\frac{IR}{E-V} \right) - \frac{L}{2R} \left(\frac{IR}{E-V} - 1 \right)^2 + \frac{L}{2R} \right\} + \left(\frac{V}{R} \right)^2 (t_0 - \tau) + \right. \\
&\quad \left. + \left(I + \frac{V}{R} \right)^2 \cdot \frac{L}{2R} \cdot \left(1 - \frac{V^2}{(V+IR)^2} \right) - \frac{2V}{R^2} (IR+V) \cdot \frac{L}{R} \cdot \left(1 - \frac{V}{V+IR} \right) \right] = \\
&= \frac{1}{T} \left[\left(\frac{E-V}{R} \right)^2 \left\{ \tau + \frac{L}{2R} - \frac{2IL}{E-V} - \frac{I^2 RL}{2(E-V)^2} + \frac{LI}{E-V} - \frac{L}{2R} \right\} + \left(\frac{V}{R} \right)^2 (t_0 - \tau) + \right. \\
&\quad \left. + \frac{(IR+V)L}{2R^3} \cdot \frac{IR(2V+IR)}{(V+IR)^2} - \frac{2VLIR}{R^3} \right] = \\
&= \frac{1}{T} \left[\left(\frac{E-V}{R} \right)^2 \left\{ \tau - \frac{I^2 RL + 2LI(E-V)}{2(E-V)^2} \right\} + \left(\frac{V}{R} \right)^2 (t_0 - \tau) + \right. \\
&\quad \left. + \frac{IL(2V+IR)}{2R^2} - \frac{2VIL}{R^2} \right] = \frac{1}{T} \left[\left(\frac{E-V}{R} \right)^2 \tau + \left(\frac{V}{R} \right)^2 (t_0 - \tau) + \right. \\
&\quad \left. - \frac{I^2 RL + 2LI(E-V) - 2LIV - 2ILV - I^2 LR + 4VIL}{2R^2} \right] = \\
&= \frac{1}{T} \left[\left(\frac{E-V}{R} \right)^2 \tau + \left(\frac{V}{R} \right)^2 (t_0 - \tau) - \frac{LIE}{R^2} \right] = \\
&= \left(\frac{E-V}{R} \right)^2 \frac{\tau}{T} + \left(\frac{V}{R} \right)^2 \left(\frac{t_0 - \tau}{T} \right) - \frac{E}{R} \cdot I \cdot \frac{L}{RT}
\end{aligned}$$

$$i_L^2 = \sqrt{\left(\frac{E-V}{R} \right)^2 \frac{\tau}{T} + \left(\frac{V}{R} \right)^2 \frac{L}{RT} \ln \left(1 + \frac{IR}{V} \right) - \left(\frac{EI}{R} \right) \frac{L}{RT}} \quad (6)$$

$$\boxed{3-2} \text{ a) } T_{\text{critical}} = t_0 \text{ of } \boxed{3-1} = \tau + \frac{L}{R} \ln \left[\frac{E}{V} \left(1 - e^{-RT/L} \right) + e^{-RT/L} \right] = \\ = 3.66794 \text{ msec} \quad (\text{see Eq. 3 in } \boxed{2-6}).$$

$$\therefore T_{\text{critical}} = 3.66794 \text{ msec}$$

$$\text{b) } T = (T_{\text{critical}} + \tau)/2 = 3.334 \text{ msec} \quad \therefore \text{ Continuous Mode.}$$

$$\therefore I_{\text{min}} = -\frac{V}{R} + \frac{E}{R} \cdot \frac{e^{RT/L} - 1}{e^{RT/L} + 1} = 0.20556 \text{ Amp}$$

$$\therefore I_{\text{max}} = \frac{V}{R} + \frac{E}{R} \cdot \frac{1 - e^{-RT/L}}{1 + e^{-RT/L}} = 0.48534 \text{ Amp}$$

$$\therefore i_{L_{\text{av}}} \text{ (by linearization)} = \frac{I_{\text{max}} + I_{\text{min}}}{2} = 0.34545 \text{ Amp}$$

$$i_{L_{\text{av}}} \text{ (actual)} = \frac{E - V}{R} \cdot \frac{\tau}{T} - \frac{V}{R} \cdot \left(1 - \frac{\tau}{T} \right) = 0.39982 \text{ Amps}$$



$$\therefore \% \text{ error in } i_{L_{\text{av}}} \text{ due to linearization} = \left| 1 - \frac{0.34545}{0.39982} \right| * 100 = 13.6\%$$

(Note: the actual value for $i_{L_{\text{av}}}$ is easy to calculate, without referring to the current expression by using superposition. For dc, L looks short circuit and hence voltage across R is found from the waveform of the load voltage, hence $i_{L_{\text{av}}}$ is obtained. You can also get it by integration, but this is long and avoidable).

3-3

A first quadrant chopper supplies positive load voltage and positive load current. It has three modes of operation, Discontinuous, Critical & Continuous, depending upon load currents.

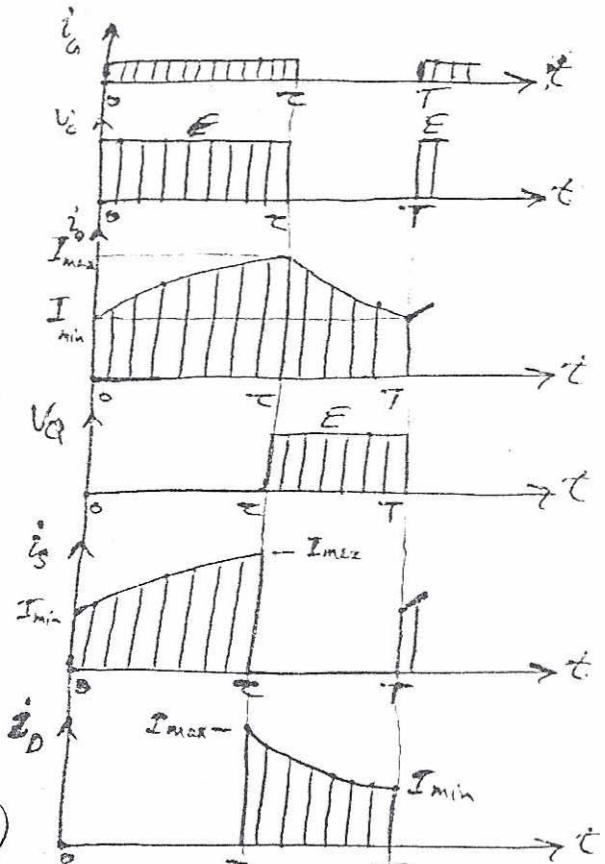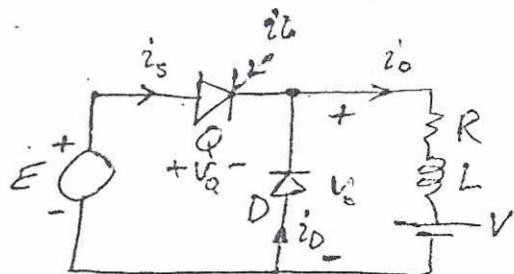- 1) The discontinuous mode is analyzed in [3-1].
- 2) The critical mode is a limit case of [3-1] and can be obtained when T is made $\rightarrow t_0$ in Eq. 2 of [3-1]
- 3) The continuous mode is considered here for analysis.



$$i_o(t) = I_{min} e^{-Rt/L} + \frac{E-V}{R} (1 - e^{-Rt/L}) \quad t \in [0, \tau]$$

$$\therefore I_{max} = i_o(\tau) = I_{min} e^{-R\tau/L} + \frac{E-V}{R} (1 - e^{-R\tau/L}) \quad (1)$$

$$\text{f } i_o(t) = I_{max} e^{-R(t-\tau)/L} - \frac{V}{R} (1 - e^{-R(t-\tau)/L}) \quad t \in [\tau, T]$$

$$\therefore I_{min} = i_o(T) = I_{max} e^{-R(T-\tau)/L} - \frac{V}{R} (1 - e^{-R(T-\tau)/L}) \quad (2)$$

Solving (1) & (2) together gives:

$$I_{min} = -\frac{V}{R} + \frac{E}{R} \cdot \frac{e^{R\tau/L} - 1}{e^{RT/L} - 1} \quad (3)$$

$$I_{max} = -\frac{V}{R} + \frac{E}{R} \cdot \frac{e^{R\tau/L} - 1}{e^{RT/L} - 1} \cdot e^{R(T-\tau)/L} \quad (4)$$

The waveforms are as shown above.

Assuming a chopping period, $T \ll L/R$, the current pattern $i_i(t)$ can be considered triangular.

$$\therefore I_{\text{av}} = (I_{\max} + I_{\min})/2 \quad (5)$$

$$\text{&} I_{\text{rms}} = \sqrt{I_{\text{av}}^2 + \left(\frac{I_{\max} - I_{\min}}{2\sqrt{3}}\right)^2} \quad (6)$$

Other parameters can be obtained very easily.

(Note: the critical mode is also a limit case of continuous mode, and is obtained by letting $I_{\min} = 0$, i.e

$$T_{\text{critical}} = \frac{L}{R} \ln \left[\frac{E}{V} \cdot (e^{RCL} - 1) + 1 \right]. \quad (7)$$

The expression is just the same as the one obtained earlier:

$$T_{\text{critical}} = \tau + \frac{L}{R} \ln \left[1 + \frac{I_{\max} \cdot R}{V} \right]. \quad (8)$$

$$\boxed{3-4} \quad E = 600V, V = 200V, L = 1mH, R = 1.5 \Omega, T = 4ms \\ \text{if } \tau = 2.5ms$$

To judge mode of operation find T_{critical} :


$$(7) \Rightarrow T_{\text{critical}} = \frac{1m}{1.5} \ln \left[\frac{600}{200} \cdot (e^{2.5 \times 1.5} - 1) + 1 \right] = 3.222 \text{ msec}$$

Since $T = 4ms \quad \therefore T > T_{\text{critical}} \quad \therefore \text{Discontinuous mode.}$

(Note: you can also judge it by I_{\min} being negative)

$$(3) \Rightarrow I_{\min} = -\frac{200}{1.5} + \frac{600}{1.5} \cdot \frac{e^{2.5 \times 1.5} - 1}{e^{4 \times 1.5} - 1} = -92.1 \text{ Amp} \quad \therefore \text{OK} \quad 50$$

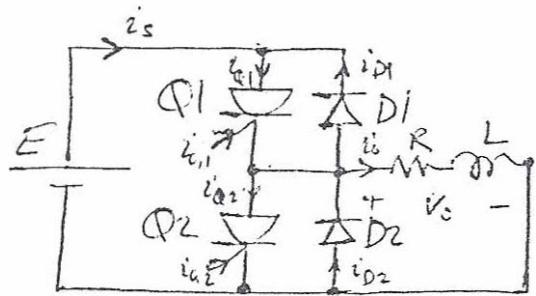- 3-5 The circuit for bidirectional current chopper-converter with positive output is shown aside.
 $\therefore R = 1\Omega$, $L = 1\text{mH}$, $T = 2\text{ms}$
 $\tau = 0.8\text{ms}$ & $E = 100\text{Vdc}$.



$$\therefore I_{\min} = \frac{E}{R} \cdot \frac{e^{\frac{RT}{L}} - 1}{e^{\frac{R(T-\tau)}{L}} - 1} = 19.182\text{Amp}$$


& $I_{\max} = I_{\min} \cdot e^{\frac{R(T-\tau)L}{2}} = 63.686\text{Amp}$

Since I_{\min} is positive then D_1 & Q_2 could be taken out of the circuit without harm.
The current mode is always continuous.
& Commutation type is forced.
The waveforms are as shown.

$$\therefore V_{o_{av}} = \frac{100 \times 0.8}{2} = 40\text{Volts}$$

$$\therefore i_{o_{av}} = \frac{40V}{1\Omega} = 40\text{Amps}$$

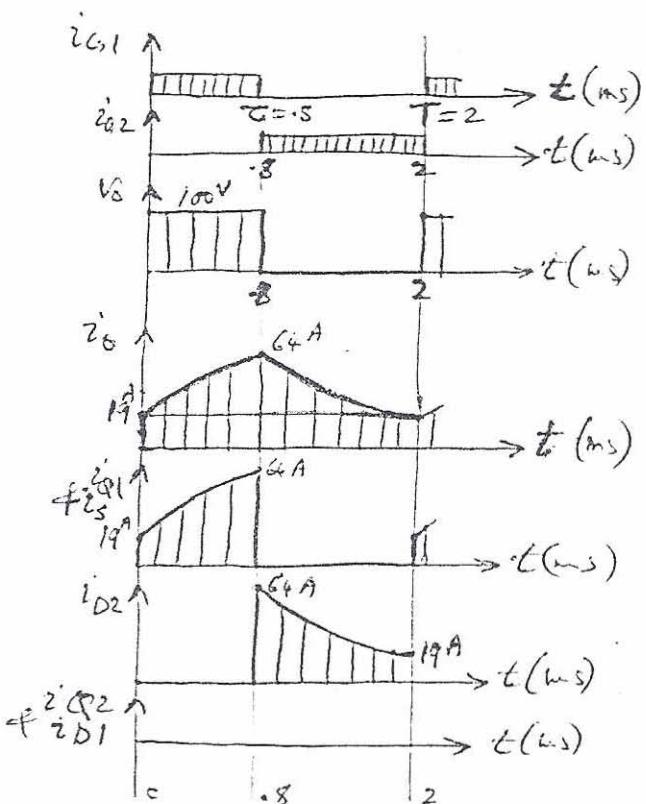(Note one could assume linear segments since $\frac{L}{R} = 1\text{msec}$
Comparable to τ & $T-\tau$, $\therefore i_{o_{av}} \approx \frac{I_{\min} + I_{\max}}{2} = 41.434\text{Amp}$ or $2 = 3.67$)



The circuit and waveforms of a half-bridge chopper with $R = 10 \Omega$, $L = 100 \text{ mH}$, $\tau = 5 \text{ ms}$, $T = 7 \text{ ms}$ & $E = 100 \text{ Volts}$; are as shown; where:

$$I_n = \frac{100}{10} \cdot \frac{e^{\frac{-5t}{10}} - 1}{e^{\frac{-7t}{10}} - 1} = 6.40 \text{ A}$$

$$\therefore I_x = \frac{100}{10} + (6.4 - \frac{100}{10}) e^{\frac{-5t}{10}} = 7.82 \text{ A}$$

$$V_L = L \frac{di}{dt} \approx \begin{cases} -i \cdot \frac{7.82 - 6.40}{0.005} = 28.34 \text{ V} \\ \text{for } t \in (0, 5) \text{ ms} \end{cases}$$

$$\text{level segments, } \begin{cases} -i \cdot \frac{7.82 - 6.40}{0.002} = -70.84 \text{ V} \\ (\approx 28.34 - 100 \text{ V}) \text{ for } t \in (5, 7) \text{ ms.} \end{cases}$$

Or, exactly, exponential segments with:

$$V_L(0^+ \text{ ms}) = 100 - 10 \cdot 6.40 = 36.01 \text{ Volts,}$$

$$\text{and } V_L(5^- \text{ ms}) = 100 - 10 \cdot 7.82 = 21.34 \text{ Volts,}$$

$$V_L(5^+ \text{ ms}) = 0 - 10 \cdot 7.82 = -78.16 \text{ Volts,}$$

$$\text{and } V_L(7^- \text{ ms}) = 0 - 10 \cdot 6.40 = -63.99 \text{ V.}$$

Line segments could be assumed since, $L/R = 10 \text{ ms} > T$.

$$\therefore V_{\text{com}} = 100 \cdot 5/7 = 71.43 \text{ Volts,}$$

$$i_{\text{com}} = V_{\text{com}}/R = 7.14 \text{ Amps}$$

$$P_{\text{avr}} \approx \frac{78.2 + 64.0}{2} \cdot \frac{5}{7} = 50.8 \text{ W}$$

$$(\text{or } \approx i_{\text{com}}^2 R = 510 \text{ W})$$

$$I_{xQ1} = 7.8 \text{ A}, I_{avQ1} = \frac{7.14 \cdot 5}{7} = 5.10 \text{ A,}$$



$$V_{xQ1} = -100 \text{ V}, V_{avQ1} = 100 \cdot 2/7 = 28.6 \text{ V,}$$

$$I_{xD2} = 7.8 \text{ A}, I_{avD2} = 7.14 \cdot 2/7 = 2.04,$$

$$V_{xD2} = 100 \text{ V}, V_{avD2} = 100 \cdot 5/7 = 71.4 \text{ V.}$$

As for D1 & Q2, they are not in use.
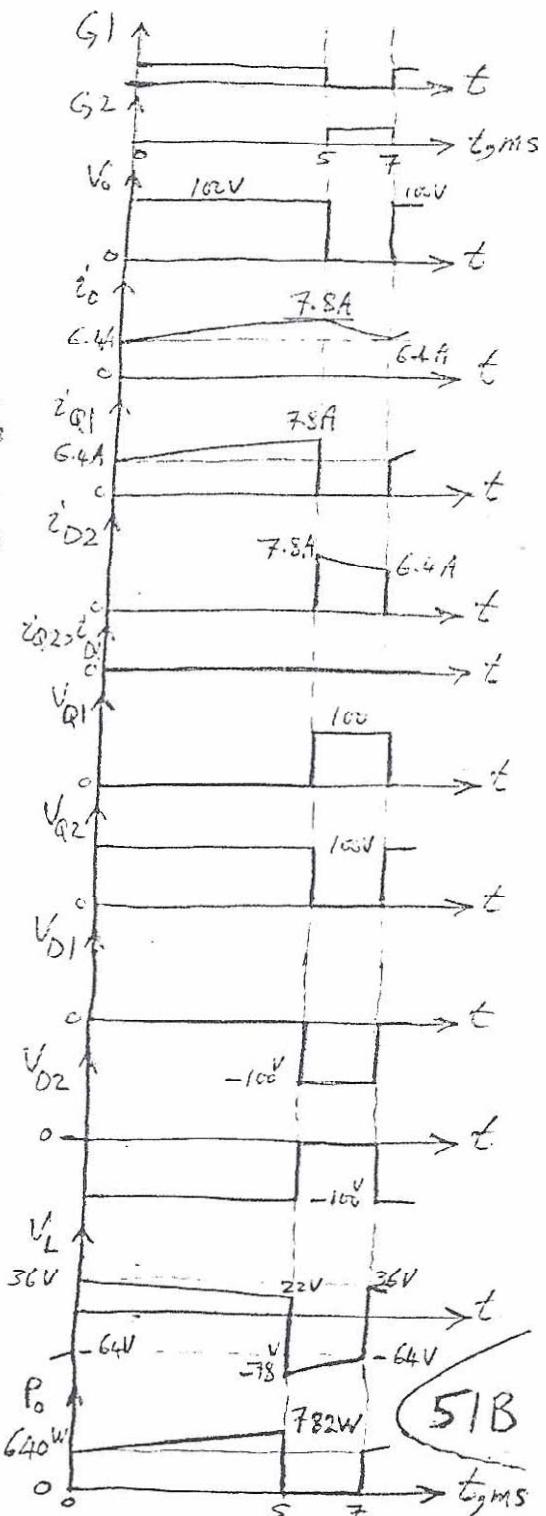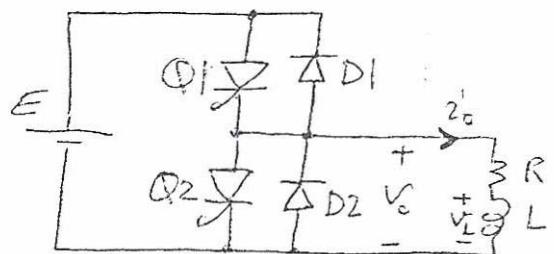
$$K_i = \frac{2ac}{Z_{dc}} = \frac{(7.82 - 6.40)/2\sqrt{3}}{7.14} = 5.73 \%$$



3-6

$$E = 600 \text{ volts}$$


$$V = 200 \text{ volts}$$

$$L = 4 \text{ mH}$$

$$R = 1.5 \Omega$$

$$T = 4 \text{ ms}$$

$$\tau = 2.5 \text{ ms}$$

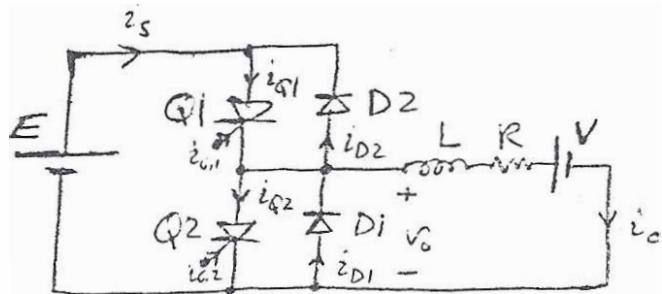

$$\therefore a) i_{\text{avg}} = I_o = \left(\frac{E - V}{T} - \frac{V}{R} \right)$$

$$= \left(600 - \frac{200}{4} \right) / 1.5 = 116.7 \text{ Amp}$$

$$\therefore V_o = V = \frac{E - V}{T} = \frac{600 - 200}{4} = 375 \text{ Volts.}$$

$$b) I_{\text{max}} = \frac{-V}{R} + \frac{E}{R} \cdot \frac{e^{RQ/L} - 1}{e^{RT/L} - 1} \cdot e^{\frac{R(T-\tau)}{L}} =$$

$$= \frac{-200}{1.5} + \frac{600}{1.5} \cdot \frac{e^{1.5 \times 2.5/4} - 1}{e^{1.5 \times 4/4} - 1} \cdot e^{1.5 \times 1.5/4}$$

$$= 179.92 \text{ Amps}$$

$$c) I_{\text{min}} = \frac{-V}{R} + \frac{E}{R} \cdot \frac{e^{RQ/L} - 1}{e^{RT/L} - 1}$$

$$= \frac{-200}{1.5} + \frac{600}{1.5} \cdot \frac{e^{1.5 \times 2.5/4} - 1}{e^{1.5 \times 4/4} - 1} = 45.15 \text{ Amps.}$$

c) Since $L/R = 4/1.5 = 2.7 \text{ msec} > \tau$
we can assume linear pattern of
current segments.

$$\therefore i_{\text{avg}} \approx \frac{I_{\text{max}} + I_{\text{min}}}{2} \cdot \frac{\tau}{T} = \frac{179.92 + 45.15}{2} \cdot \frac{2.5}{4}$$

$$= 70.34 \text{ Amps.}$$


(Note: the accurate answer is

$$i_{\text{avg}} = \frac{1}{4} \int_{0}^{2.5} \left[45.15 e^{-1.5t/4} + \frac{600 - 200}{1.5} \left(1 - e^{-1.5t/4} \right) \right] dt$$

$$= \left[-221.51 \cdot \frac{e^{-1.5t/4}}{-1.5/4} + 266.67 t \right]_{0}^{2.5} / 4$$

$$= [59070 (e^{-1.5 \times 2.5/4} - 1) + 266.67 \times 2.5] / 4 = 76.82 \text{ Amps.}$$

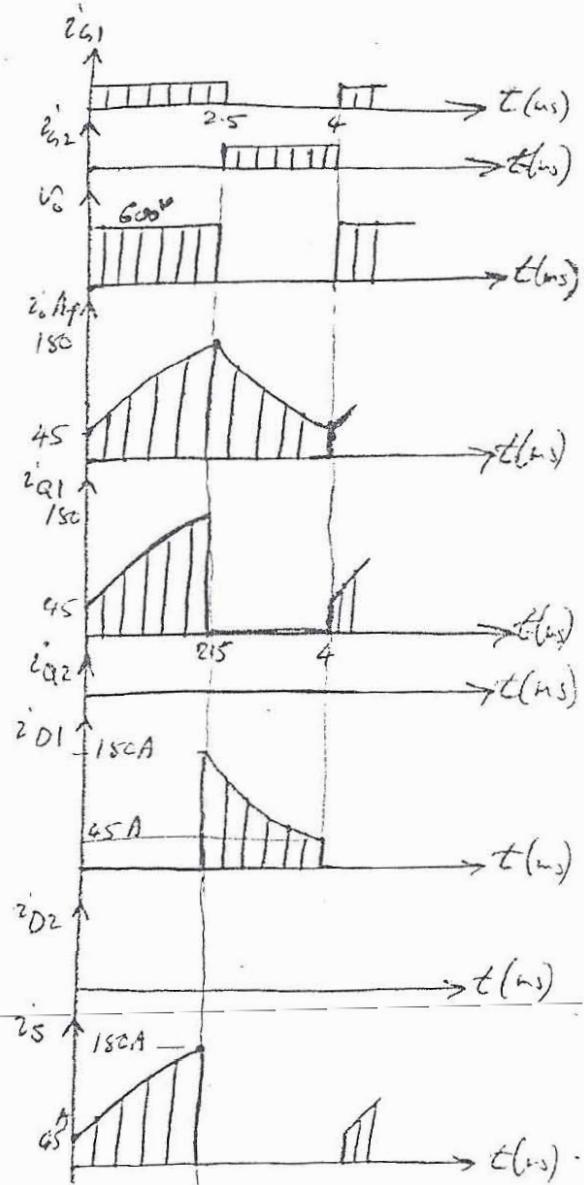e) No difference, since ~~Q2~~ \neq D2 are not in operation, for the given data



3-7

Consider the analysis of full bridge choppers feeding RL loads. The figs shows circuit and waveforms relevant.

Here:

$$v_s(t) = \begin{cases} E & t \in (0, \tau) \\ -E & t \in (\tau, T) \end{cases}$$

$$+ i_c = \begin{cases} I_{\min} e^{-Rt/L} + \frac{E}{R} (1 - e^{-Rt/L}), & t \in (0, \tau) \\ I_{\max} e^{-R(t-\tau)/L} - \frac{E}{R} (1 - e^{-R(t-\tau)/L}), & t \in (\tau, T) \end{cases}$$

$$\therefore I_{\max} = i_c(\tau) = I_{\min} e^{-R\tau/L} + \frac{E}{R} (1 - e^{-R\tau/L})$$

$$+ I_{\min} = i_c(T) = I_{\max} e^{-R(T-\tau)/L} - \frac{E}{R} (1 - e^{-R(T-\tau)/L})$$

Solving together:

$$I_{\max} = \frac{E}{R} \cdot \frac{e^{RT/L} - 2e^{-R\tau/L} + 1}{e^{RT/L} - 1}$$

$$+ I_{\min} = \frac{-E}{R} \cdot \frac{e^{RT/L} - 2e^{-R\tau/L} + 1}{e^{RT/L} - 1}$$

For large inductance, we can assume linear segments.

$$\therefore i_{c_{av}} \approx \frac{I_{\max} + I_{\min}}{2} \quad (i_{c_{av}} = \frac{E(2\tau - T)}{R \cdot T})$$



$$+ i_{c_{rms}} \approx \sqrt{i_{c_{av}}^2 + \left(\frac{I_{\max} - I_{\min}}{2\sqrt{3}} \right)^2}$$

$$\therefore i_{s_{av}} \approx \left(\frac{I_{\max} + I_{\min}}{2} \right) \frac{\tau}{T} + \left(\frac{-I_{\max} - I_{\min}}{2} \right) \left(\frac{T-\tau}{T} \right)$$

$$= \left(\frac{I_{\max} + I_{\min}}{2} \right) \left(\frac{\tau}{T} - \frac{T-\tau}{T} \right)$$

$$= \left(\frac{I_{\max} + I_{\min}}{2} \right) \left(\frac{2\tau}{T} - 1 \right)$$
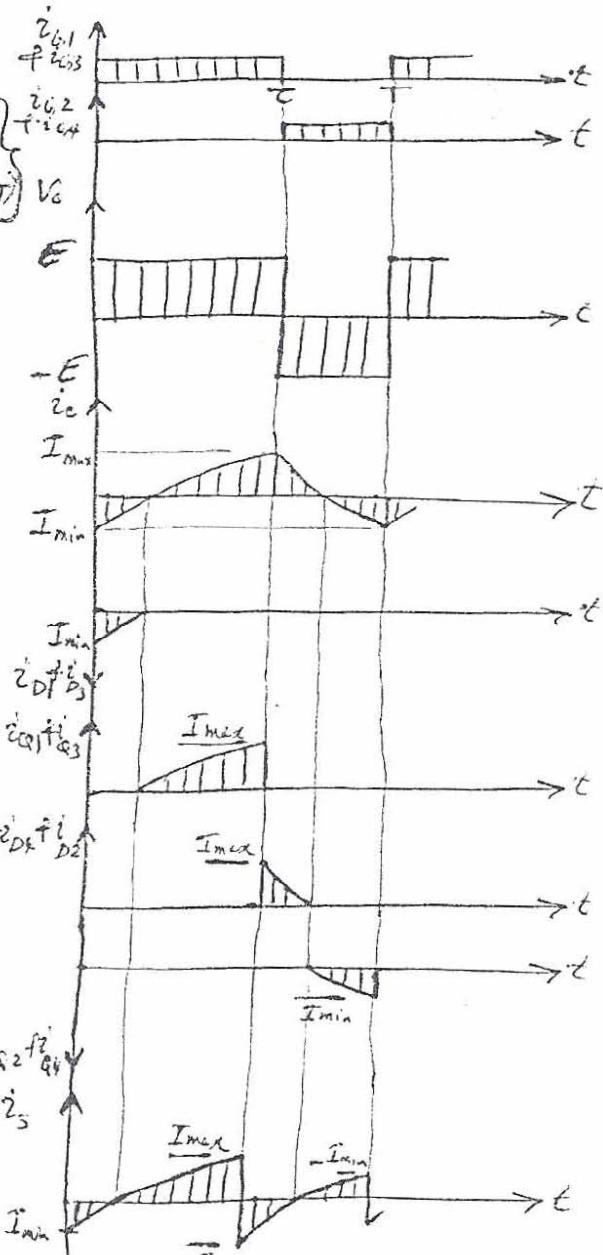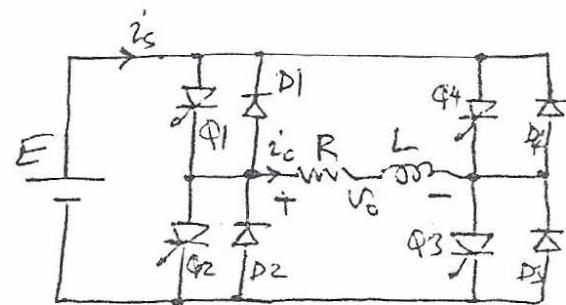
$$+ i_{s_{rms}}^2 \approx i_{s_{av}}^2 + \left(\frac{I_{\max} - I_{\min}}{2\sqrt{3}} \right)^2 \cdot \left(\frac{\tau}{T} + \frac{T-\tau}{T} \right) \Rightarrow i_{s_{rms}} \approx \sqrt{i_{s_{av}}^2 + \left(\frac{I_{\max} - I_{\min}}{2\sqrt{3}} \right)^2}.$$



$$3-8 \quad I_{\min} = -\frac{50}{20} + \frac{200}{20} \cdot \frac{e^{-1}}{e^{2000/100} - 1}$$

$$= 2.28193 \text{ Amps}$$

$$I_{\max} = \frac{-50}{20} + \frac{200}{20} \cdot \frac{e^{-2000/100} - 1}{e^{-2000/100} - 1} \cdot e^{2000/100}$$

$$= 6.21324 \text{ Amps}$$

$$\therefore \frac{L}{R} = \frac{100 \text{ mH}}{20 \Omega} = 5 \text{ msec}$$

is comparable to τ &
 $T-\tau$ (i.e. 7 ms & 3 ms)

\therefore The exponential segment
 could be assumed linear.
 The waveforms are as shown.

$$\# i_{\text{avg}} \approx \frac{2.28193 + 6.21324}{2} = 4.24758 \text{ A}$$

$$\text{OR } i_{\text{avg}} = \frac{(200 \times 7 - 50)}{20} = 4.5 \text{ Amp (exact)}$$

(% error = 5.61% \therefore assumption justified)

$$\# i_{\text{rms}} \approx \sqrt{4.5^2 + \left(\frac{6.21324 - 2.28193}{2\sqrt{3}} \right)^2} = 4.64090 \text{ A}$$

$$\text{OR } i_{\text{rms}}^2 = \frac{\text{Power supplied by source - power consumed by battery}}{IR} \text{ (exact)}$$

$$\# P_E = \text{power supplied by } E = 200 \times \frac{1}{10} \int [2.28193 e^{-20t/100} + \frac{200-50}{20} (1 - e^{-20t/100})] dt = 20 \left[2.28193 \frac{e^{-20t/100}}{-2} + 7.5 (t - \frac{e^{-20t/100}}{2}) \right] = 20 \left[2.28193 \left(\frac{1-e^{-14}}{2} \right) + 7.5 \left(7 - \frac{1-e^{-14}}{2} \right) \right] = 656.8688 \text{ Watts (exact)}$$

$$\text{OR } P_E \approx 200 \times \frac{2.28193 + 6.21324}{2} \times \frac{7}{10} = 594.6616 \quad (\% \text{ error} = 9.47\%)$$

$$\# P_V = \text{power delivered to } V = 50 \times 4.5 = 225 \text{ Watts (exact)}$$

$$\therefore i_{\text{rms}} = \sqrt{(656.8688 - 225)/20} = 4.64687 \text{ Amps (exact)}$$

(% error (of approximate value of 4.64090) = 0.13%).

$$\# \therefore K_i = \frac{i_{\text{avg}}}{i_{\text{rms}}} = \sqrt{\frac{i_{\text{avg}}^2 - i_{\text{min}}^2}{i_{\text{max}}^2}} = \sqrt{\left(\frac{i_{\text{avg}}}{i_{\text{rms}}}\right)^2 - 1} = \sqrt{0.6634^2 - 1} = 0.2576 = 25.76\%$$


$$\# \text{ if } V_{o_{\text{avg}}} = 200 \times 7/10 = 140 \text{ volts}$$

$$\# \text{ if } V_{o_{\text{rms}}} = 200 \sqrt{\frac{7}{10}} = 167.3320 \text{ volts}$$


$$\# \therefore K_v = \sqrt{\left(\frac{V_{o_{\text{avg}}}}{V_{o_{\text{rms}}}}\right)^2 - 1} = 0.6547 = 65.47\%$$

D1 is not needed & for D2: $i_F \geq 6.21324 \text{ Amp}$, $i_F \geq 4.24758 \times \frac{3}{10} = 1.2743 \text{ Amp}$
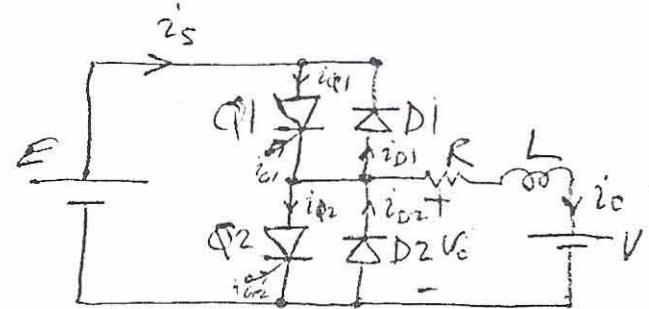
$$\# \text{ if } i_{F_{\text{rms}}} \geq \sqrt{4.24758^2 + \left(\frac{6.21324 - 2.28193}{2\sqrt{3}} \right)^2} = 2.40810 \text{ Amp. Current Mode is continuous.}$$



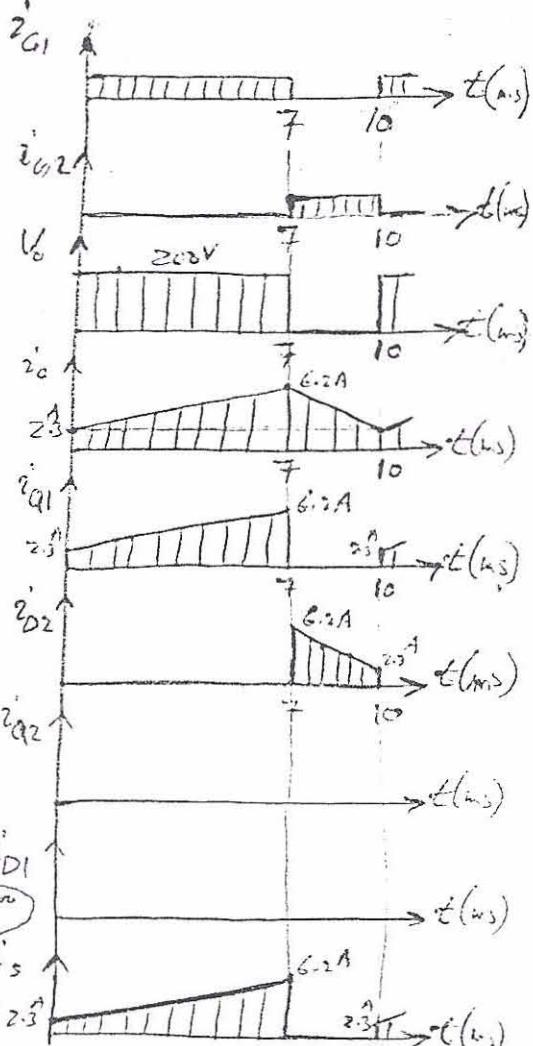
$$E = 200 \text{ V}, V = 50 \text{ V}, R = 20 \Omega, L = 1 \text{ H}, T = 7 \text{ ms}, T = 10 \text{ ms}$$



54

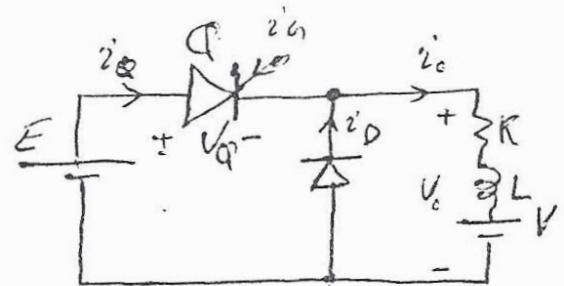3-9 a) $E = 80 \text{ Volts}$,
 $R = 10 \Omega$,
 $L = 50 \text{ mH}$,
 $\tau = 15 \text{ ms}$,
 $T = 25 \text{ ms}$ &

$V = 30 \text{ Volts}$, with circuit as shown.



b) $\therefore I_{\min} = \frac{-30}{10} + \frac{80}{10} \cdot \frac{e^{\frac{10+15}{50}} - 1}{e^{\frac{10+25}{50}} - 1} = -1.9642 \text{ Amps}$

Since no path is available for negative current,
 \therefore Mode is discontinuous.

The waveforms are as shown ($i_s = i_Q$)

$$\therefore i_o(t) = \frac{80 - 30}{10} (1 - e^{-\frac{10+t}{50}}), (t \leq 15 \text{ ms}) \\ = 5(1 - e^{-\frac{t}{5}}) \text{ Amp}, t \in [0, 15] \text{ ms}$$

$$\therefore I = i_o(15) = 5(1 - e^{-3}) = 4.75 \text{ II Amp}$$

$$\therefore i_o(t) = I e^{-\frac{10(t-15)}{50}} - \frac{30}{10}(1 - e^{-\frac{(t-15)}{50}}) = \\ = -3 + 7.75 II e^{\frac{(15-t)}{5}} \text{ A}, t \in [15, t_0] \text{ ms.}$$

$$\therefore i_o(t_0) = 0 \Rightarrow t_0 = 19.7461 \text{ ms.}$$

$i_o(t) = 0$ for $t \in [t_0, 25]$ ms.

c) $\therefore V_{o_{\text{avg}}} = \frac{1}{25} \times [80 \times 15 + 30 \times (25 - 19.7461)] = \\ = 54.3047 \text{ Volts.}$


$i_o = \frac{54.3047 - 30}{10} = 2.4305 \text{ Amps.}$

$V_{o_{\text{rms}}}^2 = \frac{1}{25} [80^2 \times 15 + 30^2 \times (25 - 19.7461)] = 4024.141 \text{ V}^2$

$$\therefore V_{o_{\text{rms}}} = \sqrt{V_{o_{\text{rms}}}^2 - V_{o_{\text{avg}}}^2} = 63.4755 \text{ Volts}$$

$$\therefore V_{o_{\text{ac}}} = \sqrt{V_{o_{\text{rms}}}^2 - V_{o_{\text{avg}}}^2} = 32.8655 \text{ Volts}$$

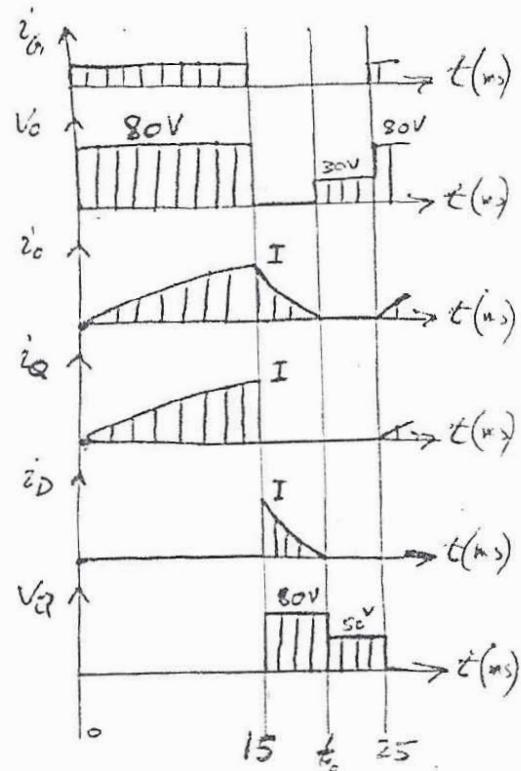
$$\therefore K_r = \frac{V_{o_{\text{ac}}}}{V_{o_{\text{avg}}}} = .6053 = 60.53 \%$$



SS
3

3-10
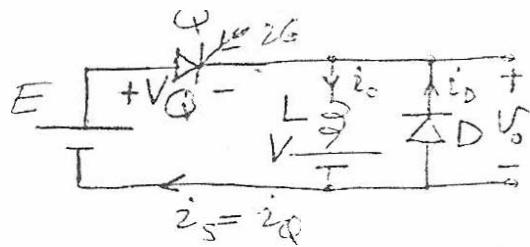
$$E = 200 \text{ Volts}, \\ \tau = 20 \text{ ms}, \\ T = 60 \text{ ms}, \\ L = 100 \text{ mH} \quad \& \\ V = 80 \text{ Volts}.$$



Assume $i_L(0) = I_0 > 0$

$$\therefore i_L(\tau) = I_0 + \frac{E-V}{L} \cdot \tau$$

$$\therefore i_L(T) = I_0 + \frac{E-V}{L} \cdot \tau - \frac{V}{L} (T-\tau)$$

$$= I_0 + \frac{E\tau - VT}{L} = I_0 + \Delta I$$

where $\Delta I = \frac{E\tau - VT}{L}$. (1)

For stable operation, ΔI must be ≤ 0 ; because if it was positive then the current at the end of a cycle would be more than its value at the beginning. This would cause the current to increase unstably


reaching after few cycles to very large values and hence

the circuit becomes in-operational. You can equally argue it by saying that the energy pumped to L during the on-state (56) should be pumped out before (or just at) the end of the cycle.

If ΔI were equal to zero, continuous or critical mode occurs; whereas for $\Delta I < 0$, the current collapses to discontinuous mode.

For our case; $\Delta I = \frac{200 \cdot 20 - 80 \cdot 60}{100} = -8 \text{ Amp} < 0 \Rightarrow I_0 = 0 \text{ A}$.

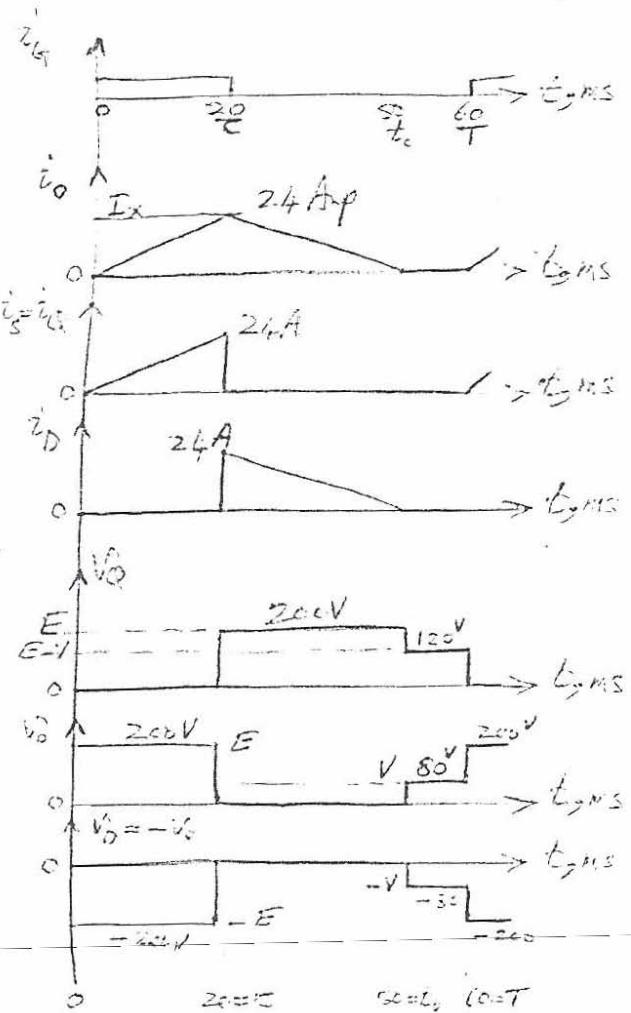∴ Current mode is discontinuous, with extinction at $t_0 = \frac{E}{V} = \frac{200}{80} = 25 \text{ ms}$. This results in the indicated waveforms, with $I_x = \frac{E-V}{L} \cdot \tau = 24 \text{ Amp}$.



$$\therefore i_{\text{com}} = \frac{24+50}{2+60} = 10 \text{ Amp.}$$

$$\therefore i_{\text{rms}} = \sqrt{\frac{24^2+50}{3+60}} = 4\sqrt{10} = 12.6497 \text{ Amp}$$

$$\therefore K_i = \frac{i_{\text{com rms}}}{i_{\text{com}}} = \sqrt{\left(\frac{i_{\text{rms}}}{i_{\text{com}}}\right)^2 - 1} = 0.7746 = 77.46\%$$

$$\therefore V_{\text{com}} = \frac{200 \times 20 + 80 \times 10}{60} = 80 \text{ Volts}$$

$$\therefore V_{\text{rms}} = \sqrt{\frac{200^2 \times 20 + 80^2 \times 10}{60}} = 144.42 = 120 \text{ Volts}$$

$$\therefore K_v = \sqrt{\left(\frac{V_{\text{rms}}}{V_{\text{com}}}\right)^2 - 1} = 1.12 = 112\%$$

$$P_r = V \cdot i_{\text{com}} = 80 \times 10 = 800 \text{ Watt} = P_E \text{ because } I_L^2 = 0$$

$$(\text{check: } P_E = E \cdot i_{\text{com}} = 200 \times \frac{24+20}{2+60} = 800 \text{ W} \therefore \text{OK})$$

$$\therefore i_{DF_{\text{max}}} = 24 \text{ Amp.}$$

$$\therefore i_{DF_{\text{ar}}} = \frac{24+30}{2+60} = 6 \text{ Amp.}$$

$$\therefore i_{DF_{\text{rms}}} = \sqrt{\frac{24^2+30}{3+60}} = 96 = 4\sqrt{6} = 9.798 \text{ Amp}$$


Yes, τ is limited operationally by Eq (1) to

$$\text{give } \Delta I = \frac{E_C - VT}{L} \leq 0 \Rightarrow E_C \leq VT$$

$$\therefore \tau \in [0, \frac{VT}{E_C}] \equiv [0, 24] \text{ ms.}$$

In case this limit is violated, current will rise gradually to ∞ .

3-11(a)

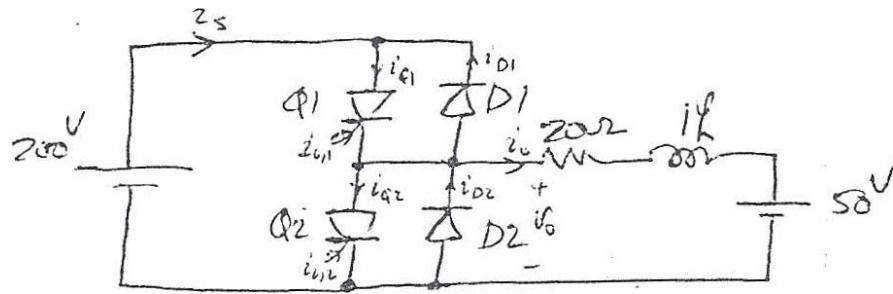

$$b) I_{min} = -\frac{50}{20} + \frac{200}{20} \cdot \frac{e^{14} - 1}{e^{12} - 1}$$

$$= 4.287 \text{ Amp}$$

$$I_{max} = -\frac{50}{20} + \frac{200}{20} \cdot \frac{e^{14} - 1}{e^{12} - 1} \cdot e^{06}$$

$$= 4.707 \text{ Amp}$$

Time-constant of current $= \frac{L}{R}$

$$= \frac{1}{20} = 50 \text{ ms} \gg \tau \text{ & } T - \tau$$

∴ Segments could be assumed linear.
and waveforms are as shown.

$$V_L = V_o - V - i_o R, \text{ with linear segments}$$


$$V_L(0^+) = 200 - 50 - 4.287 \cdot 20 = 64.25 \text{ V}$$

$$V_L(7^-) = 200 - 50 - 4.707 \cdot 20 = 55.86 \text{ V}$$

$$V_L(7^+) = 0 - 50 - 4.707 \cdot 20 = -144.14 \text{ V}$$

$$V_L(10^-) = 0 - 50 - 4.287 \cdot 20 = -135.75 \text{ V}$$

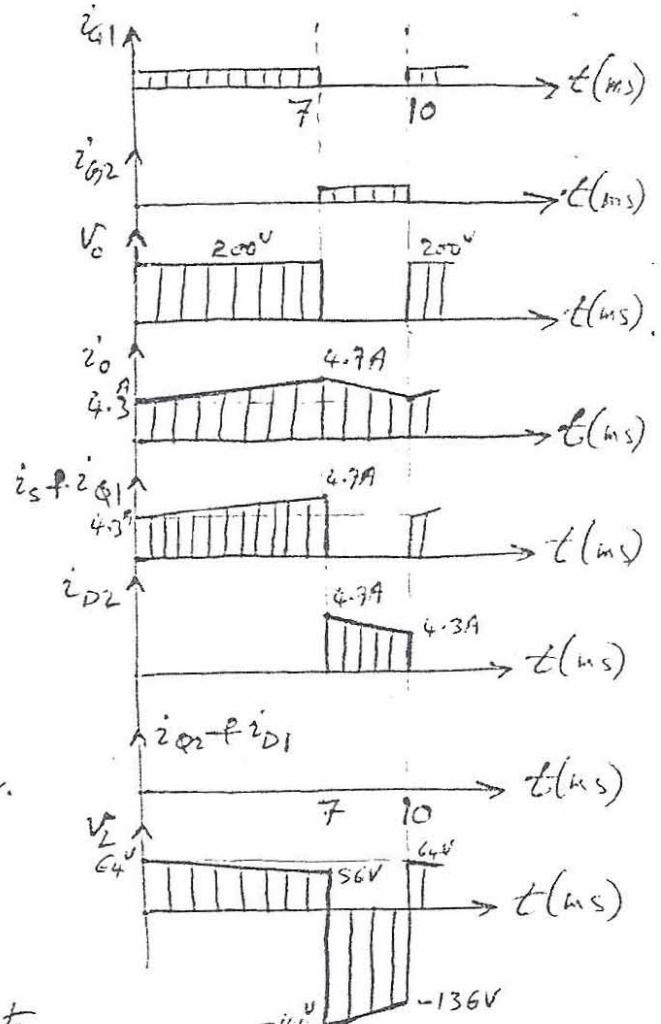- c) $V_{avg} = 140 \text{ Volt} \quad , \quad V_{rms} = 167.33 \text{ Volt.} \quad \& \quad K_v = 65.5 \%$
 $i_{avg} = 4.50 \text{ Amp} \quad , \quad i_{rms} = \sqrt{4.5^2 + (4.707 - 4.287)^2} = 4.502 \text{ Amp} \quad \& \quad K_i = 2.69 \%$
 $P_v = 225 \text{ Watt} \quad , \quad P_E = 225 + 4.502^2 \cdot 20 = 630.3 \text{ Watt, D1 is not required as Q2}$
 $i_{Fmax} \text{ for } D2 \geq 4.7 \text{ Amp} \quad \& \quad i_{Frms} \text{ for } D2 \geq 4.502 \cdot \sqrt{3} = 2.466 \text{ Amp} \quad \& \quad i_{Favg} \geq 1.35 \text{ A}$
- d) Current Mode is continuous.



3-12i. The circuit is a first quadrant chopper feeding RLV Load.

2. Waveforms are as shown,

assuming linear segments for

$$\text{current due to } \frac{L}{R} = \frac{52}{2.5} = 20.8 \text{ ms} > \tau = 7 \text{ ms.}$$

3. During $t \in [0, \tau]$:

$$\therefore i_o(t) = \frac{341 - 121}{2.5} \left(1 - e^{-2.5t/52\text{ms}} \right) + 40 e^{-2.5t/52\text{ms}}$$

$$\therefore I_N = i_o(0) = 40 \text{ A}$$

$$\therefore I_X = i_o(\tau) = i_o(7 \text{ ms}) = 53.72 \text{ Ap}$$

During $t \in [\tau, T]$:

$$\therefore i_o(t) = \frac{-121}{2.5} \left(1 - e^{-2.5(t-7\text{ms})/52\text{ms}} \right) + 53.72 e^{-2.5(t-7\text{ms})/52\text{ms}}$$

$$\therefore I_N = i_o(T) = 40 \text{ A} \Rightarrow T = 10.00 \text{ msec}$$

$$\therefore V_{o_{av}} = 341 \times \frac{7}{10} = 238.7 \text{ V}_{AC}$$

$$\therefore i_{o_{av}} = \frac{238.7 - 121}{2.5} = 47.08 \text{ Ap}$$


$$\therefore V_{o_{rms}} = 341 \sqrt{\frac{7}{10}} = 285.3 \text{ V}_{AC}$$

$$\therefore i_{o_{ac}} \approx \frac{I_X - I_N}{2\sqrt{3}} = \frac{53.72 - 40.0}{2\sqrt{3}} = 3.961 \text{ Ap}$$

$$\therefore i_{o_{rms}} = \sqrt{i_{o_{av}}^2 + i_{o_{ac}}^2} = \sqrt{47.08^2 + 3.961^2} = 47.25 \text{ Ap}$$

$$\therefore K_r = \sqrt{\left(\frac{V_{o_{rms}}}{V_{o_{av}}}\right)^2 - 1} = \sqrt{\left(\frac{285.3}{238.7}\right)^2 - 1} = 0.6546 = 65.46\%$$
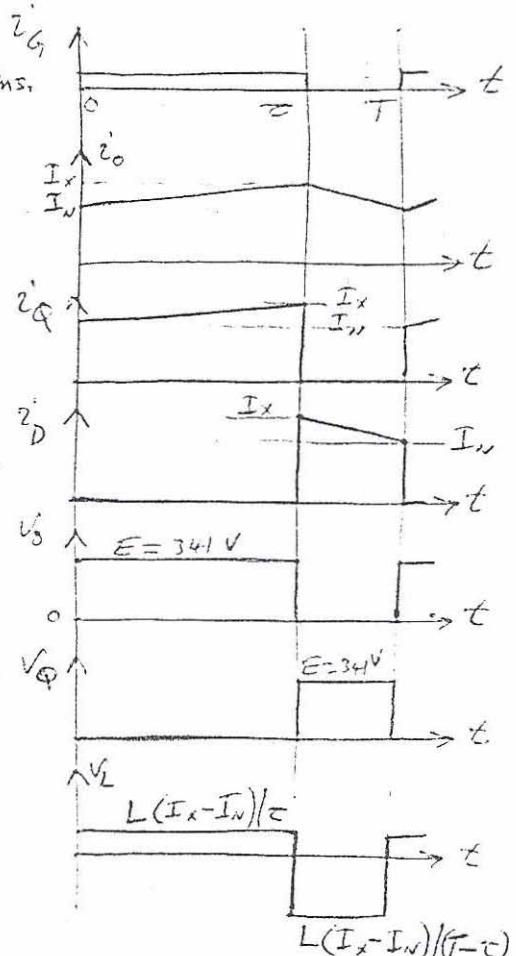
$$\therefore K_i = \frac{i_{o_{ac}}}{i_{o_{av}}} = \frac{3.961}{47.08} = 0.08413 \approx 8.41\%. \quad 59$$



$$P_R = i_{o_{rms}}^2 \cdot R = 47.25^2 \cdot 2.5 = 5581.4 \text{ W} = 5.581 \text{ kW}$$

$$P_V = i_{o_{av}} \cdot V = 47.08 \cdot 121 = 5696.68 = 5.697 \text{ kW}$$

$$\therefore P_S = P_R + P_V = 5.581 + 5.697 = 11.278 \text{ kW}$$

$$\begin{aligned} \text{(or equally)} : P_S &\approx E \cdot i_{o_{av}} = E \cdot \frac{I_X + I_N}{2} \cdot \frac{\epsilon}{T} = \\ &= 341 \cdot \frac{53.72 + 40}{2} \cdot \frac{7}{10} = 11185 \text{ W} = 11.185 \text{ kW} \end{aligned}$$

4. Forced Commutation is used here.

5. For Q:

$$I_{av} = \frac{I_X + I_N}{2} \cdot \frac{\epsilon}{T} = \frac{53.72 + 40}{2} \cdot \frac{7}{10} = 32.80 \text{ Ap}$$

$$I_{rms} = i_{o_{rms}} \sqrt{\frac{\epsilon^2}{T}} = 47.25 \sqrt{7} = 39.53 \text{ Ap}$$

$$I_{max} = I_X = 53.72 \text{ Ap}$$

$$V_{FB} = 341 \text{ Volts}$$

$$V_{KB} = 0 \text{ Volts}$$

6. For D:

$$I_{av} = \frac{I_X + I_N}{2} \cdot \frac{T - \tau}{T} = \frac{53.72 + 40}{2} \cdot \frac{3}{10} = 14.06 \text{ Ap}$$

$$I_{rms} = i_{o_{rms}} \sqrt{\frac{\epsilon^2}{T}} = 47.25 \sqrt{3} = 25.88 \text{ Ap}$$

$$V_{max} = 341 \text{ Volts}$$

7. The current mode can be discontinuous by reducing the value of the inductance L

3-13(a) The circuit is a half bridge chopper that can supply the load with ± 50 DCV but with positive load currents only.

b) $i_o > 0 \rightarrow V_o$ can be either positive or negative.

c) It is very likely, due to $\tau:T$ ratio; that the current mode is discontinuous. To check this, assume $i_o(0) = 0$

$$\therefore i_o(t) = \frac{50}{R} (1 - e^{-t}), A_p, t \in [0, \tau]$$

$$\therefore i_o(\tau) = 50 (1 - e^{-\tau}) , A_p = 0.49751 A_p = 497.51 \text{ mA}$$

$$\therefore i_o(t) = -50 + A e^{-(t-\tau)}, \text{ with}$$

$$i_o(\tau) = i_o(\tau) = 497.51 \text{ mA}$$



$$\therefore A = 50.49751 A_p$$

$$\therefore i_o(t) = -50 + 50.49751 e^{-(t-\tau)}, A_p, t \in [\tau, t_x]$$

$$\text{where } i_o(t_x) = 0 \quad \therefore t_x = \ln\left(\frac{50.49751}{50}\right) + \tau = 0.01995 \text{ ms}$$

$\therefore t_x = 19.9 \text{ msec}$, and hence, i_o is given by:
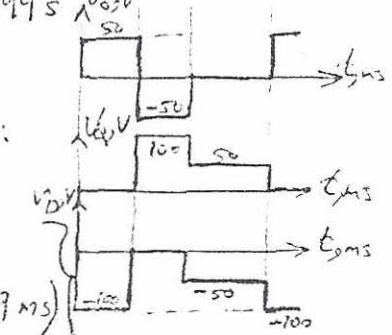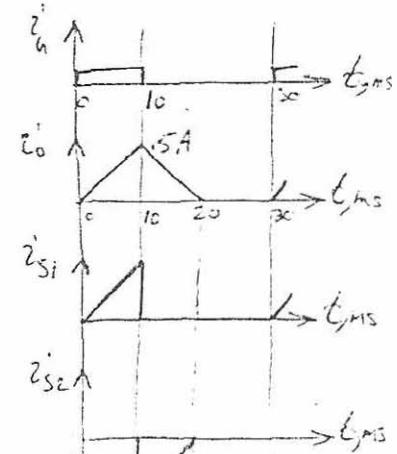
$$\therefore i_o(t) = \begin{cases} 50 (1 - e^{-t}), A, t \in [0, 10 \text{ ms}] \\ -50 + 50.49751 e^{-(t-\tau)}, A, t \in [10 \text{ ms}, 19.9 \text{ ms}] \\ 0, A, t \in [19.9 \text{ ms}, 30 \text{ ms}] \end{cases}$$



Hence, current mode is discontinuous. This illustrates the waveforms above. Note that, because $L/R = 1 \text{ sec} \gg \tau, T$, then linear segments appear for the currents. Hence, $V_{o,an} = 50 \left(\frac{10 - 9.9 + 0}{30} \right) = 0.1650 \text{ Volts}$

$$\therefore i_{o,an} = \frac{V_{o,an}}{R} = \frac{0.1650}{R} = 0.1650 A = 165.0 \text{ mA}$$

$$\text{and } V_{o,av}^2 = 50^2 \left(\frac{10 + 9.9 + 0}{30} \right)^2 = 1658.42 \Rightarrow V_{o,av} = 40.72 \text{ Volts. (61)}$$

$$\therefore K_v = \frac{V_{o,av}}{V_{o,an}} = \sqrt{\left(\frac{V_{o,av}}{V_{o,an}}\right)^2 - 1} = \sqrt{\left(\frac{40.72}{0.165}\right)^2 - 1} = 246.8 \quad (\text{Too High}).$$

$$3-14 \quad f_{\text{chopping}} = 1 \text{ kHz}$$


$$\therefore T = 1 \text{ msec}$$

Let Q1 & Q3 be on for τ ,

i.e. The avg power delivered to SR resistor is P_5

given by
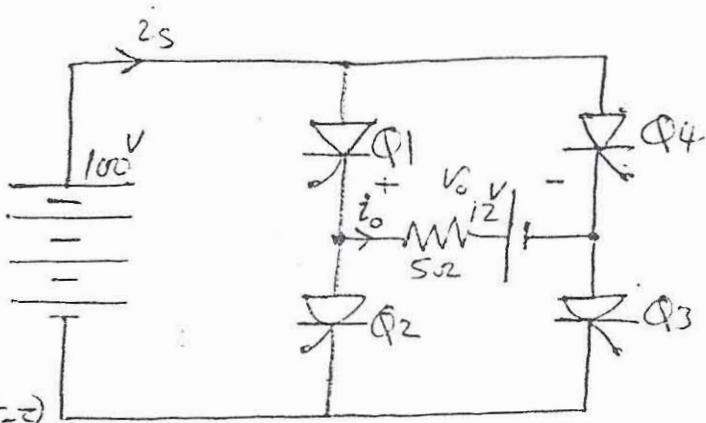
$$P_5 = \frac{(100 - i_2)^2}{5} \times \frac{\tau}{T} + \frac{(100 + i_2)^2}{5} \frac{(T-\tau)}{T}$$



$$= 2508.8 - 960 \alpha, \text{ where}$$

α is the duty ratio $\frac{\tau}{T}$

$$\therefore P_5 = 500 \text{ W}$$

$$\therefore \alpha = \frac{2508.8 - 500}{960} = 2.0925 > 1$$

\therefore If Q1 & Q3 were on for $\tau \neq \frac{T}{2}$

then Q2 & Q4 are brought on to end of T,
it is impossible to supply power less than

$2508.8 - 960 = 1548.8 \text{ W}$. To supply power less than this to
the SR load resistor, SPWM scheme is adopted with symmetrical
on-duration of $\tau/2$ as shown

$$\therefore P_5 = \frac{88^2}{5} \cdot \frac{\tau/2}{T} + \frac{112^2}{5} \cdot \frac{\tau/2}{T} = 2028.8 \alpha$$

$$\therefore \alpha = \frac{500}{2028.8} = 0.24645$$

$$\therefore P_{12} = 12 \left[\frac{88 - 112}{5} \cdot \frac{\tau/2}{T} \right]$$

$$= 12 \left(-\frac{24}{5} \right) \times \frac{\alpha}{2} = -28.8 \times 0.24645$$

$= -7.0978 \text{ Watt} \quad \therefore \text{Battery supplies } 7.1 \text{ W}$



$$P_{\text{source}} = P_{100} = P_5 + P_{12} = 500 - 7.0978 = 492.9 \text{ W}$$

$$V_{\text{rms}} = \sqrt{12^2(1-\alpha) + 100^2\alpha} = 50.725 \text{ V}, V_{\text{avg}} = 12(1-\alpha) = 9.043 \text{ V}$$

$$I_{\text{rms}} = \sqrt{\frac{500}{5}} = 10 \text{ A}, i_{\text{avg}} = \frac{7.0978}{12} = 0.5915 \text{ A}$$

$$\therefore K_r = \sqrt{(V_{\text{avg}}/V_{\text{rms}})^2 - 1} = 5.520. (\text{very high ripple})$$

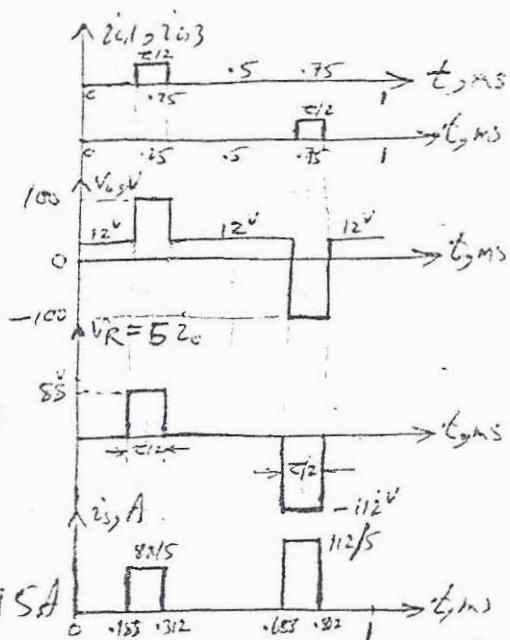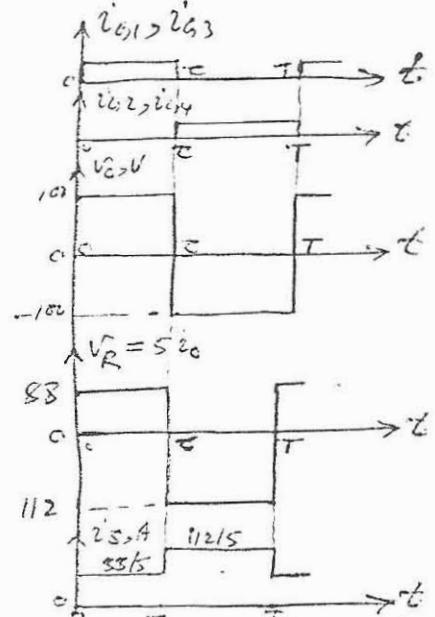
$$\& K_i = \sqrt{\left(\frac{i_{\text{avg}}}{i_{\text{rms}}}\right)^2 - 1} = 16.88 \quad (\text{very high ac components}).$$



62

$$4-4 \quad V_+(t) = \begin{cases} \frac{4P}{T} \cdot t, & t \in [0, \frac{T}{4}] \\ -\frac{4Pt}{T} + 2P, & t \in [\frac{T}{4}, \frac{3T}{4}] \\ \frac{4Pt}{T} - 4P, & t \in [\frac{3T}{4}, \frac{5T}{4}] \\ -\frac{4Pt}{T} + 6P, & t \in [\frac{5T}{4}, \frac{7T}{4}] \\ \frac{4Pt}{T} - 8P, & t \in [\frac{7T}{4}, 2T] \end{cases}$$
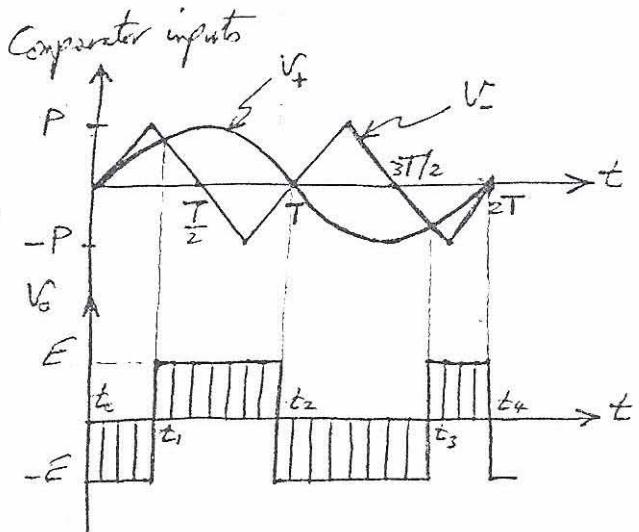
$$+ V_-(t) = P \sin(\frac{2\pi}{T} t) = P \sin(\pi t/T)$$



$$\therefore V_o(t) = \begin{cases} -E & t \in [t_0, t_1] \cup [t_2, t_3] \\ E & t \in [t_1, t_2] \cup [t_3, t_4] \end{cases}$$

where t_0, t_1, t_2, t_3 & t_4 are the solutions of $V_+(t) = V_-(t)$
 (Note that there are four solutions per fundamental period, i.e. double the frequency ratio). Finding these solutions:

$$\begin{aligned} \text{f. } \frac{4Pt_0}{T} = P \sin(\pi t_0/T) &\Rightarrow f(t_0/T) = \sin(\pi t_0/T) - 4t_0/T = 0 \quad \therefore \frac{t_0}{T} = 0 \\ \text{f. } -\frac{4Pt_1}{T} + 2P = P \sin(\pi t_1/T) &\Rightarrow f(t_1/T) = \sin(\pi t_1/T) + 4t_1/T - 2 = 0 \quad \therefore \frac{t_1}{T} = 0.29846 \\ \text{f. } +\frac{4Pt_2}{T} - 4P = P \sin(\pi t_2/T) &\Rightarrow f(t_2/T) = \sin(\pi t_2/T) - 4\frac{t_2}{T} + 4 = 0 \quad \therefore \frac{t_2}{T} = 1.000 \\ \text{f. } -\frac{4Pt_3}{T} + 6P = P \sin(\pi t_3/T) &\Rightarrow f(t_3/T) = \sin(\pi t_3/T) + 4\frac{t_3}{T} - 6 = 0 \quad \therefore \frac{t_3}{T} = 1.70154 \\ \text{f. } t_4 = t_0 + 2T = 2T \quad (\text{Note: you can find only one iteration and use symmetry}) \end{aligned}$$

$$\begin{aligned} \text{I) } \therefore \text{ Since } V_o(2T-t) = -V_o(t) &\quad \therefore V_{o,\text{avg}} = 0 \quad \text{f. } V_o(t) = \sum_{n=1}^{\infty} a_n \sin(n\omega t + b_n) \\ \text{ where } \omega = \frac{2\pi}{2T} = \frac{\pi}{T}, \quad \therefore \cos n\omega(2T-t) &= \cos n\omega t \quad \therefore b_n = 0 \\ \therefore \sin n\omega(2T-t) = -\sin n\omega t &\quad \therefore a_n = \frac{2}{2T} \int_0^{2T} V_o(t) \sin n\omega t dt = \frac{1}{T} * 2 \int_0^T V_o(t) \sin n\omega t dt \\ &= 2 * \int_0^1 V_o(\frac{x}{T}) \sin(n\frac{\pi}{T}x) dx = 2 \left(\int_{-0.29846}^{0.29846} - \int_{0.29846}^1 \right) E \sin(n\pi x) dx = \\ &= 2E \left[\frac{-\cos n\pi x}{n\pi} \Big|_0^{0.29846} + \frac{\cos n\pi x}{n\pi} \Big|_{-0.29846}^1 \right] = \frac{2E}{n\pi} \left[1 - 2\cos(n\pi * 0.29846) + \cos n\pi \right] = a_n \end{aligned}$$

$$\begin{aligned} \text{II) } \therefore V_{o,\text{rms}} &= \sqrt{\frac{2E}{\pi}} / \sqrt{-2 \cos 2.9846\pi} = 0.532712 E \quad \text{f. } \therefore V_{o,\text{tot,rms}} = E \\ \therefore \text{v}_r &= \sqrt{1 - 0.532712^2} = 0.846297 \end{aligned}$$

4-6

$$E = 100 \text{ Volts}$$

$$T = 1 \text{ ms}$$

$$\tau = 0.75 \text{ ms}$$

$$R = 1.2$$

L = very large

$$V = 20 \text{ Volts}$$

$\therefore L$ is very large,

\therefore exponential segments could be assumed linear (ripple very small).

$$\begin{aligned} \therefore V_{o_{\text{avg}}} &= [E\tau - E(T-\tau)]/T \\ &= \frac{E}{T}(2\tau - T) = 50 \text{ Volts} \end{aligned}$$

$$\therefore i_{o_{\text{avg}}} = \frac{V_{o_{\text{avg}}} - V}{R} = 30 \text{ Amps}$$

\therefore power delivered to $V = i_{o_{\text{avg}}} \cdot V = 600 \text{ W}$

The waveforms are all shown here.

$$\begin{aligned} \therefore i_s &= i_{Q1} + i_{Q4} - i_{D1} - i_{D4} = \\ &= i_{Q1} - i_{D4} \text{ as shown.} \end{aligned}$$



(Note: D1, Q2, D3 & Q4 are not required.)

As for Kv :

$$\begin{aligned} Kv &= \frac{V_{o_{\text{avg}}}}{V_{o_{\text{rms}}}} = \sqrt{\frac{V_{o_{\text{avg}}}^2 - V_{o_{\text{avg}}}^2}{V_{o_{\text{avg}}}^2}} = \\ &= \sqrt{\left(\frac{V_{o_{\text{avg}}}}{V_{o_{\text{avg}}}}\right)^2 - 1} = 1. \end{aligned}$$

$$\therefore V_{o_{\text{rms}}} = E = 100 \text{ Volts} \quad \text{and} \quad V_{o_{\text{avg}}} = 50 \text{ Volts}$$
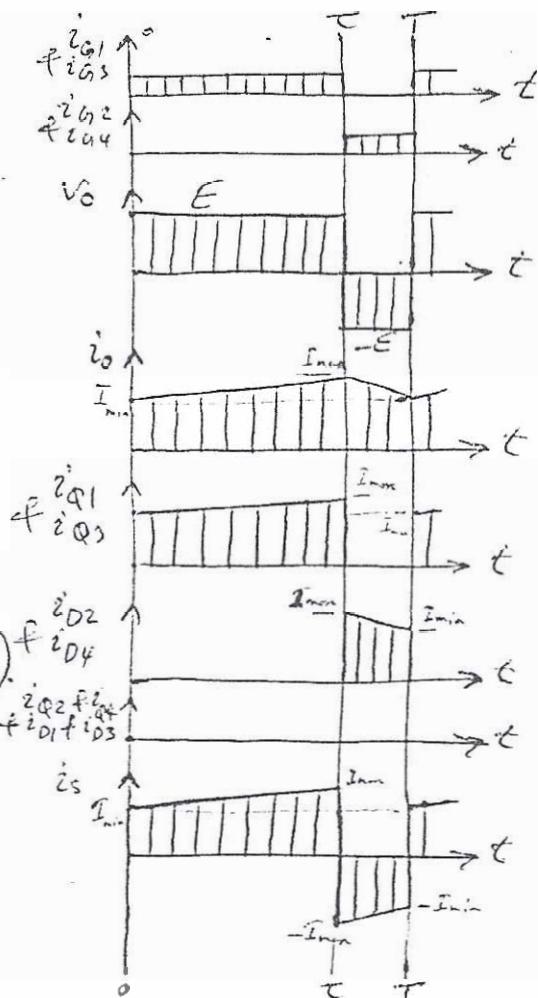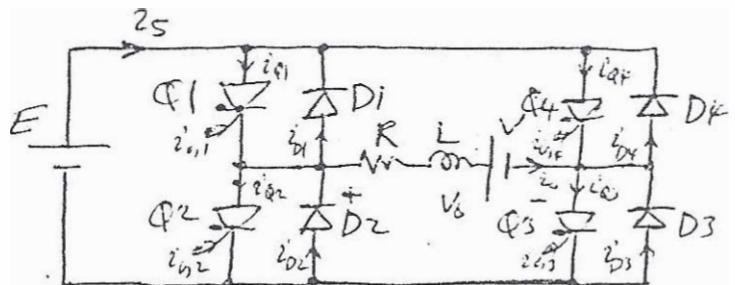
$$\therefore Kv = \sqrt{\left(\frac{100}{50}\right)^2 - 1} = \sqrt{3} = 1.732 = 173.2\% \text{ (very high ripple)}$$



4-7

$$E = 100 \text{ Volts}$$

$$T = 1 \text{ msec}$$

$$\tau = 0.75 \text{ msec} \quad (\frac{\tau}{T} = \frac{3}{4})$$

$$R = 1.2$$

L = very large

∴ SPWM

∴ Waveforms are as shown

∴ L is very large,

∴ i_s can be assumed as straight line segments, as shown.

As for i_s :

$$i_s = i_{Q1} + i_{Q4} - i_{D1} - i_{D4}$$

To give the shape shown.



$$V_o \text{ fundamental} = \frac{4E}{\pi f_2} \sin \frac{\pi C}{2T}$$

$$= 83.18 \text{ Volts}$$

$$M_v = \frac{V_o \text{ rms}}{V_{o \text{ rms}}} = \sqrt{1 - \left(\frac{V_o \text{ fundamental}}{V_{o \text{ rms}}} \right)^2},$$

$$\therefore V_{o \text{ rms}} = E \sqrt{\frac{C}{T}} = 86.60 \text{ Volts}$$

$$\therefore M_v = 0.2784 = 27.84\%$$

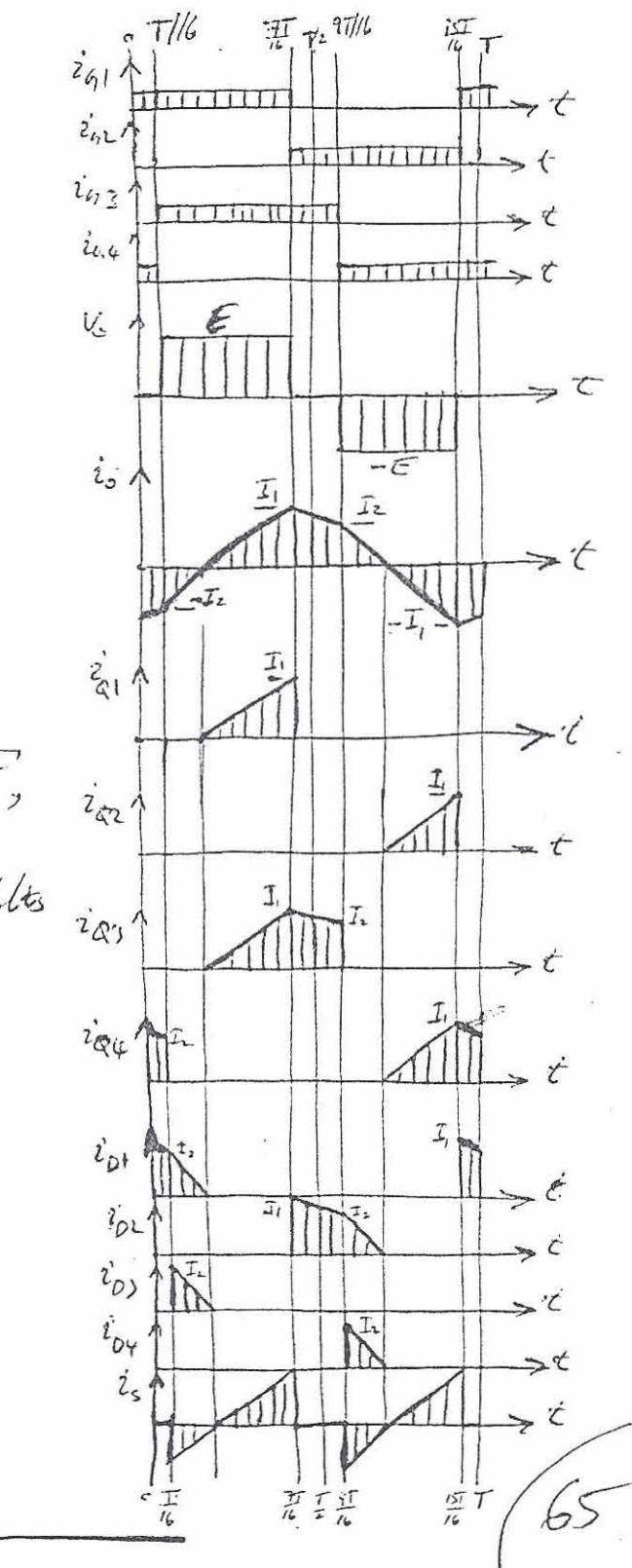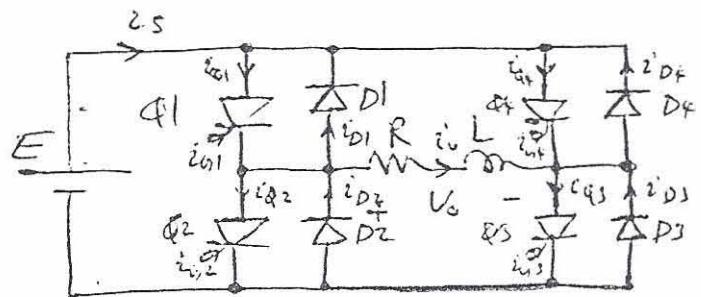

4-8

$$V = 500 \text{ volts}$$

$$T = 2 \text{ ms}$$

$$R = 1.2 \text{ } \Omega$$

$$\omega = \frac{2\pi}{T}$$

$$\omega L = 10 \text{ } \Omega$$

$$\frac{1}{\omega C} = 10 \text{ } \Omega$$

$$t_g = 50 \text{ } \mu\text{sec}$$

a) Since higher harmonics can be neglected,

$$\therefore V_o \approx V_m \sin \omega t = \bar{V}_o \text{, where:}$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{2 \text{ ms}} = \pi \text{ Krad/sec,}$$

$$\text{f} \quad V_m = \frac{2}{T} \int_{0}^T V_o(t) \sin \omega t \, dt$$

$$= \frac{2}{2\pi/\omega} \cdot 2 \int_{\frac{\pi}{2}}^{\frac{\pi}{2}} \sin \omega t \, dt =$$

$$= \frac{\omega}{\pi} \cdot \frac{2V}{2} \cdot \frac{-\cos \omega t}{\omega} \Big|_{\frac{\pi}{2}}^{\frac{\pi}{2}} = \frac{V}{\pi} (-\cos \frac{\pi}{2} + 1)$$

$$= \frac{V}{\pi} (-\cos(\frac{2\pi}{T} \cdot \frac{T}{2}) + 1) = \frac{V}{\pi} (-\cos \pi + 1) = \frac{2V}{\pi}$$

$$\therefore \bar{V}_o = \frac{1000}{\pi} \sin \pi t \text{ (ms)} \quad \text{volts} = 318.31 \sin \pi t$$

$$\therefore i_o \approx \bar{i}_o = \frac{318.31}{\sqrt{1.2^2 + (10 - 1)^2}} \sin \left\{ \pi t - t_g - \frac{1}{1.2} \right\} =$$



$$= 265.26 \text{ Amp} \sin \pi t \text{ (ms)}$$

$$\text{b) } i_{Q1_{av}} = i_{Q2_{av}} = \frac{2}{\pi} \times 1 \times 265.26 / 2 = 84.43 \text{ Amps}$$

$$\text{f} \quad i_{Q1_{rms}} = i_{Q2_{rms}} = \frac{265.26}{\sqrt{2} \cdot \sqrt{2}} = 132.63 \text{ Amps}$$

$$\text{f} \quad i_{D1_{av}} = i_{D2_{av}} = i_{D1_{rms}} = i_{D2_{rms}} = 0 \text{ Amps}$$

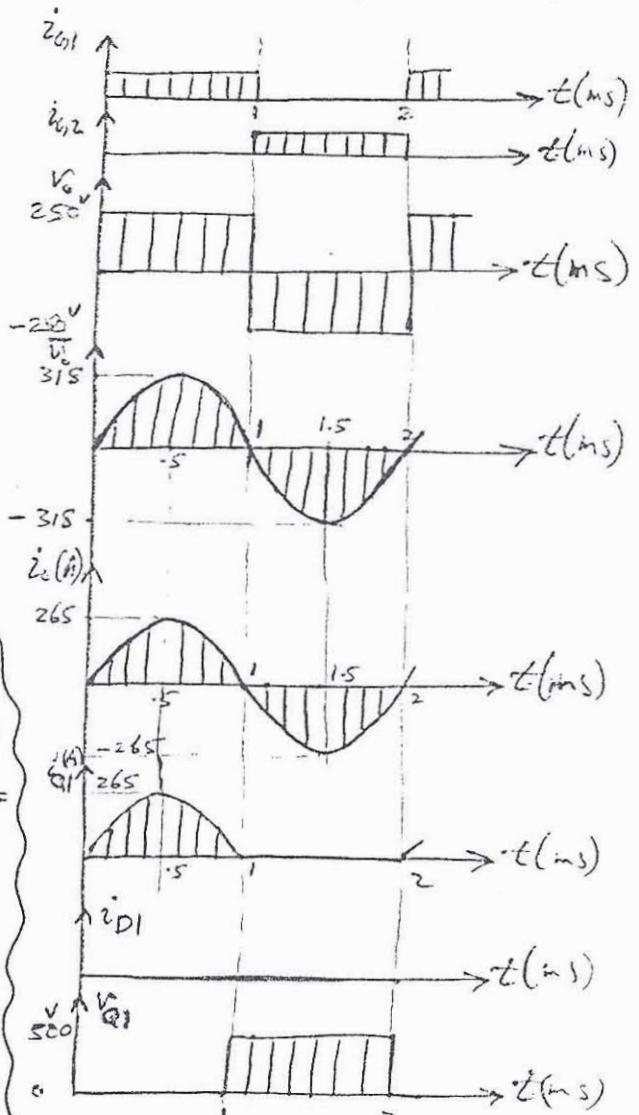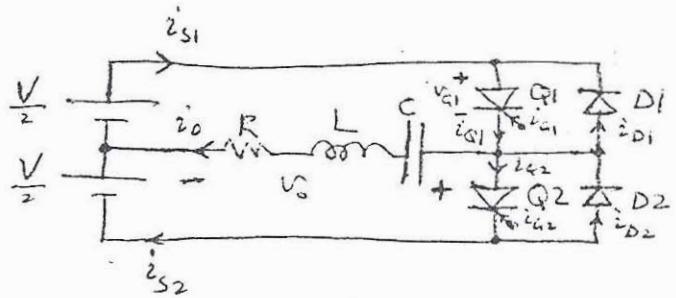c) Since phase lead = 0 > $t_g = 50 \mu\text{sec}$; then forced commutation is required to provide recovery, though commutation current is zero Amps.



66

4-9

Consider the inverter circuit shown, and let the gate signals of Q_2 & Q_4 be the complements of those of Q_1 & Q_3 respectively.

Now, if gate signals of Q_1 & Q_3 were as shown, the output voltage will be a multiple pulse width modulation of the input supply E ; proving bidirectionality.

The timing of all signals can be controlled to

give the desired multiple pulse width modulated output.

We will consider the case of equally-spaced N pulses per half cycle having centred symmetry to make life simpler.

$$\therefore V_o(t + \frac{T}{2}) = -V_o(t)$$

$$\begin{aligned} \text{# } V_o(t) &= E & \text{for } t \in \left[\frac{(2k-1)T-\tau}{4N}, \frac{(2k-1)T+\tau}{4N} \right] \quad k=1, \dots, N \\ &= -E & \text{for } t \in \left[\frac{(2k-3)T+\tau}{4N}, \frac{(2k-1)T-\tau}{4N} \right] \end{aligned}$$

where τ is the total energizing period in one whole cycle $\in [0, T]$.

$$\therefore V_o(t) = V_{o\text{av}} + \sum_{n=1}^{\infty} (a_n \sin n\omega t + b_n \cos n\omega t), \text{ where } \omega = \frac{2\pi}{T}$$



\because Symmetrical $\therefore V_{o\text{av}} = 0 + b_n = 0$ for all n & a_n for even n

$$\therefore V_o(t) = \sum_{n=1, \text{ odd}}^{\infty} a_n \sin \left(\frac{2n\pi t}{T} \right)$$

$$\begin{aligned} \therefore a_n &= \frac{2}{T} \int_0^T V_o(t) \sin \left(\frac{2n\pi t}{T} \right) dt = \frac{2}{T} * 2 \int_{\frac{(2k-1)T-\tau}{4N}}^{\frac{(2k-1)T+\tau}{4N}} V_o \sin \left(\frac{2n\pi t}{T} \right) dt = \\ &= \frac{4}{T} \sum_{k=1}^N \int_{\frac{(2k-1)T-\tau}{4N}}^{\frac{(2k-1)T+\tau}{4N}} E \sin \left(\frac{2n\pi t}{T} \right) dt = \frac{4E}{T} \sum_{k=1}^N \left[\frac{-\cos \left(\frac{2n\pi t}{T} \right)}{\frac{2n\pi}{T}} \right]_{\frac{(2k-1)T-\tau}{4N}}^{\frac{(2k-1)T+\tau}{4N}} \end{aligned}$$

$$= \frac{2E}{n\pi} \sum_{k=1}^N -\cos \left\{ \frac{2n\pi[(2k-1)T+\tau]}{4NT} \right\} + \cos \left\{ \frac{2n\pi[(2k-1)T-\tau]}{4NT} \right\} =$$

67

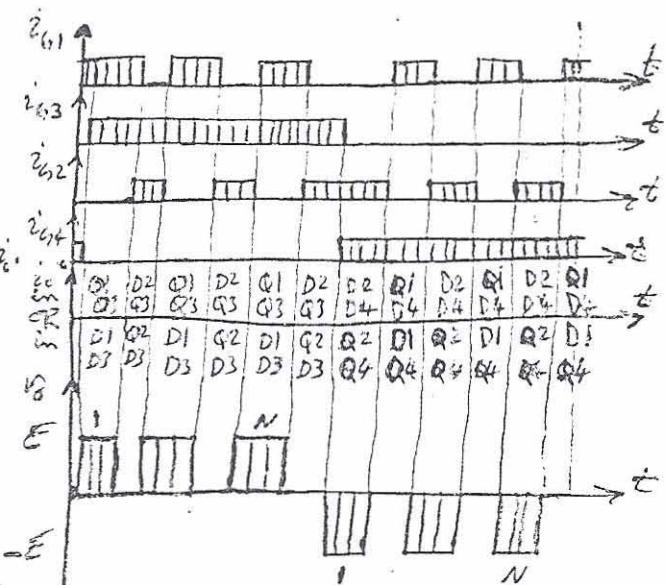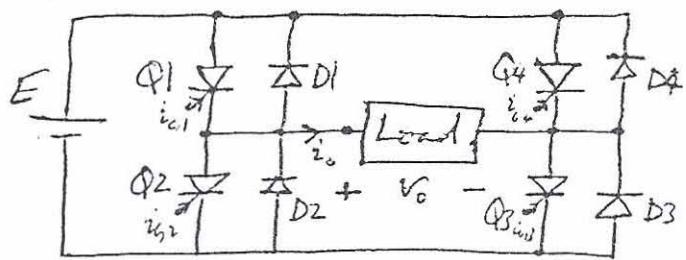

$$= \frac{2E}{n\pi} \sum_{k=1}^N 2 \sin \left\{ \frac{n\pi(2k-1)}{2N} \right\} \sin \left(\frac{n\pi c}{2NT} \right)$$

$$= \frac{4E}{n\pi} \cdot \sin \left(\frac{n\pi c}{2NT} \right) \cdot \sum_{k=1}^N \sin \left\{ \frac{n\pi}{2N}(2k-1) \right\}$$

(Let's revise complex theory to find $\sum_{m=1}^M \sin m\theta = S$.

$$\text{Let } z = e^{j\theta} \quad \therefore z^m = e^{jm\theta} = \cos m\theta + j \sin m\theta$$

$$\therefore S = \sum_{\substack{m=1 \\ \text{odd}}}^M \operatorname{Im} z^m = \operatorname{Im} \sum_{\substack{m=1 \\ \text{odd}}}^M z^m = \operatorname{Im} (z^1 + z^3 + \dots + z^M).$$

$$\text{Now, let } \bar{S} = z + z^3 + \dots + z^M = \sum_{\substack{m=1 \\ \text{odd}}}^M z^m$$

$$\therefore z^2 \bar{S} - \bar{S} = z^3 + z^5 + \dots + z^{M+2} - z - z^3 - z^5 - \dots - z^M =$$

$$= z^{M+2} - z$$

$$\therefore \bar{S}(z^2 - 1) = z^{M+2} - z \quad \Rightarrow \quad \bar{S} = \frac{z^{M+2} - z}{z^2 - 1}$$

$$\therefore S = \operatorname{Im} \bar{S} = \operatorname{Im} \left(\frac{z^{M+2} - z}{z^2 - 1} \right) = \operatorname{Im} \left[\frac{\cos(M+2)\theta + j \sin(M+2)\theta - \cos\theta - j \sin\theta}{\cos 2\theta + j \sin 2\theta - 1} \right]$$

$$= \operatorname{Im} \left[\frac{\{\cos(M+2)\theta - \cos\theta\} + j \{\sin(M+2)\theta - \sin\theta\}}{(\cos 2\theta - 1)^2 + (\sin 2\theta)^2} \cdot \{(cos 2\theta - 1) - j \sin 2\theta\} \right]$$

$$= \frac{(\cos 2\theta - 1)\{\sin(M+2)\theta - \sin\theta\} - \sin 2\theta \{\cos(M+2)\theta - \cos\theta\}}{\cos^2 2\theta - 2 \cos 2\theta + 1 + \sin^2 2\theta} =$$

$$= \frac{\cos 2\theta \sin(M+2)\theta - \sin 2\theta \cos(M+2)\theta - \cos 2\theta \sin\theta + \sin 2\theta \cos\theta - \sin(M+2)\theta + \sin\theta}{2 - 2 \cos 2\theta} =$$

$$= \frac{\sin(M+2-2)\theta + \sin(2\theta - \theta) - \sin(M+2)\theta + \sin\theta}{2(1 - \cos 2\theta)} =$$

$$= \frac{\sin(M+1-1)\theta - \sin(M+1+1)\theta + 2\sin\theta}{2 \cdot 2 \sin^2 \theta} = \frac{-2 \cos(M+1)\theta \sin\theta + 2\sin\theta}{4 \sin^2 \theta} =$$

$$= \frac{1 - \cos(M+1)\theta}{2 \sin\theta} \quad \therefore S = \sum_{\substack{m=1 \\ \text{odd}}}^M \sin m\theta = \frac{1 - \cos(M+1)\theta}{2 \sin\theta}.$$

$$\therefore a_n = \frac{4E}{n\pi} \cdot \sin \left(\frac{n\pi c}{2NT} \right) \cdot \left[\sum_{k=1}^N \sin \left\{ (2k-1) \left(\frac{n\pi}{2N} \right) \right\} \right] =$$

$$= \frac{4E}{n\pi} \cdot \sin \left(\frac{n\pi c}{2NT} \right) \cdot \left[\sum_{\substack{m=2k-1=1 \\ \text{m odd}}}^{M=2N-1} \sin m \left(\frac{n\pi}{2N} \right) \right] = \frac{4E \sin \left(\frac{n\pi c}{2NT} \right) \times [1 - \cos M\pi]}{n\pi \times 2 \sin \left(\frac{n\pi}{2N} \right)}$$

$$= \frac{4E}{n\pi} \cdot \sin \left(\frac{n\pi c}{2NT} \right) / \sin \left(\frac{n\pi}{2N} \right).$$

(68)

∴ The fundamental output voltage, $V_{o1\text{rms}} = \frac{4E}{\pi\sqrt{2}} \cdot \sin\left(\frac{\pi c}{2NT}\right) / \sin\left(\frac{\pi}{2N}\right)$

+ The total output voltage, $V_{o\text{tot rms}} = E \cdot \sqrt{\frac{c}{T}}$,

$$\text{giving a distortion factor, } \mu_v = \frac{V_{o\text{ harmonics rms}}}{V_{o\text{ tot rms}}} = \sqrt{\frac{V_{o\text{ harmonics rms}}^2 - V_{o1\text{ rms}}^2}{V_{o\text{ tot rms}}^2}} \\ = \sqrt{1 - \left(\frac{V_{o\text{ rms}}}{V_{o\text{ tot rms}}}\right)^2} = \sqrt{1 - \left(\frac{2\sqrt{2} \cdot \sqrt{\frac{T}{c}} \cdot \frac{\sin(\pi c/2NT)}{\sin(\pi/2N)}}\right)^2}$$

Hence, the two parameters c & N facilitate control over μ_v .

If $N=1$, then single pulse modulation is used. Hence,

$$a_n = \frac{4E}{n\pi} \cdot \sin\left(\frac{n\pi c}{2T}\right) / \sin\left(\frac{n\pi}{2}\right) = (-1)^{\frac{n-1}{2}} \cdot \frac{4E}{n\pi} \cdot \sin\left(\frac{n\pi c}{2T}\right)$$

+ $V_{o1\text{ rms}} = \frac{4E}{\pi\sqrt{2}} \cdot \sin\left(\frac{\pi c}{2T}\right)$

+ $\mu_v = \sqrt{1 - \frac{8T}{\pi^2 c} \cdot \sin^2\left(\frac{\pi c}{2T}\right)}$

4-10 a) for $\delta = 90^\circ \Rightarrow c = \frac{T}{2}$


∴ $a_n = (-1)^{\frac{n-1}{2}} \cdot \frac{4E}{n\pi} \cdot \sin\left(\frac{n\pi}{4}\right)$

∴ $V_{o1\text{ rms}} = \frac{4E}{\pi\sqrt{2}} \cdot \sin\left(\frac{\pi}{4}\right) = 0.63662E$

+ $V_{o3\text{ rms}} = \frac{4E}{3\pi\sqrt{2}} \cdot \sin\left(\frac{3\pi}{4}\right) = 0.21221E$

+ $V_{o5\text{ rms}} = \frac{4E}{5\pi\sqrt{2}} \cdot \left| \sin\left(\frac{5\pi}{4}\right) \right| = 0.12732E$

+ $V_{o7\text{ rms}} = \frac{4E}{7\pi\sqrt{2}} \cdot \left| \sin\left(\frac{7\pi}{4}\right) \right| = 0.09095E$

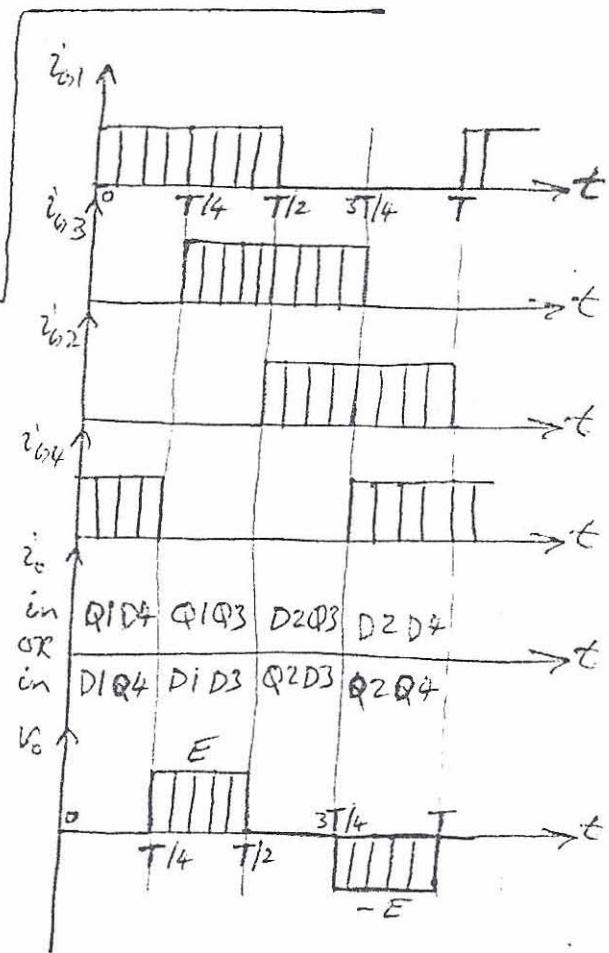

+ b) The gating waveforms indicated earlier will be for this case as shown above.


4-11 a) Single pulse modulation:

$$\therefore V_{o1, \text{rms}} = \frac{4E}{\pi\sqrt{2}} \cdot \sin\left(\frac{\pi\tau}{2T}\right) = 0.45E$$

$$\therefore \sin\left(\frac{\pi\tau}{2T}\right) = \frac{-45\sqrt{2}}{4} = 0.49982$$

$$\therefore \frac{\tau}{T} = \frac{2}{\pi} \cdot \sin^{-1} 0.49982 = 0.33320 \approx \frac{1}{3}$$
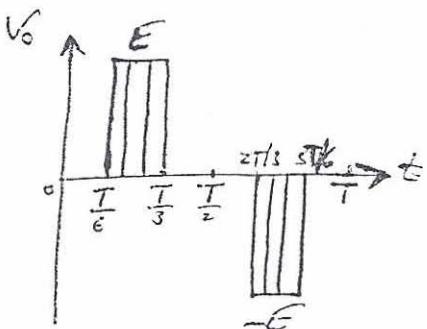
$$\therefore \tau \approx \frac{T}{3} \Rightarrow \delta \approx 60^\circ, \text{ width of a pulse.}$$



$$+ V_{o1, \text{det rms}} = E \sqrt{\frac{\tau}{T}} \left(\frac{E}{\sqrt{3}} \right) = 0.57724E$$

$$\therefore M_r = \sqrt{1 - \left(\frac{0.45}{0.57724} \right)^2} = 0.62631$$

$$+ K_r = \sqrt{\left(\frac{0.57724}{0.45} \right)^2 - 1} = 0.80340$$

b) Multiple pulse width modulation; N=10:

$$\therefore V_{o1, \text{rms}} = \frac{4E}{\pi\sqrt{2}} \cdot \sin\left(\frac{\pi\tau}{2NT}\right) / \sin\left(\frac{\pi}{2N}\right) = 0.45E$$

$$\therefore \sin\left(\frac{\pi\tau}{2NT}\right) = \frac{\pi\sqrt{2} \cdot 0.45}{4} \cdot \sin\left(\frac{\pi}{2N}\right) = 0.07819$$


$$\therefore \frac{\tau}{T} = \frac{20}{\pi} \cdot \sin^{-1} 0.07819 = 0.49828 \approx \frac{1}{2}$$

$$\therefore \tau \approx \frac{T}{2} \Rightarrow \delta \approx \frac{90^\circ}{10} = 9^\circ, \text{ width of a pulse.}$$

$$+ V_{o1, \text{det rms}} = E \sqrt{\frac{\tau}{T}} \left(\sqrt{\frac{E}{\tau}} \right) = 0.70589E$$


$$\therefore M_r = \sqrt{1 - \left(\frac{0.45}{0.70589} \right)^2} = 0.77046$$
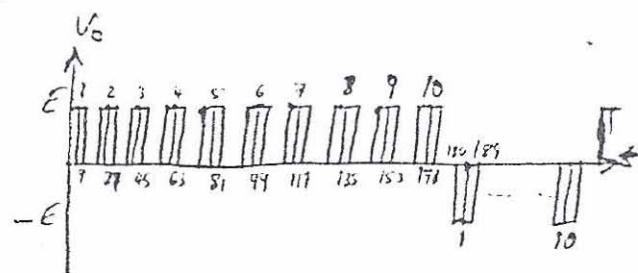
$$+ K_r = \sqrt{\left(\frac{0.70589}{0.45} \right)^2 - 1} = 1.2086$$



4-12

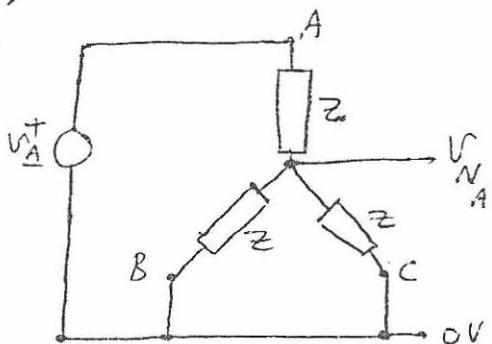Assuming symmetrical star loads, the waveforms are as shown. The potential of N relative to the negative battery terminal could be found by superposition and phasor analysis is as follows:



$$\frac{V_{NA}}{V_A} = \frac{(-z/z)}{(-z/z) + z} = \frac{-z/2}{z/2 + z} = \frac{1}{3}$$

$$\text{Likewise } \frac{V_{NB}}{V_B} = \frac{1}{3} = \frac{V_{NC}}{V_C}$$

$$V_N = V_{NA} + V_{NB} + V_{NC} = \frac{1}{3} (V_A + V_B + V_C)$$

Hence, $V_{AN} = V_A - V_N$ as shown, other phase voltages has $\pm T/3$ phase shift. To calculate i_A , we assume that current initially at L is providing symmetry, i.e. $i_A(0) = \frac{-ET}{9L}$, slopes = $\frac{V_{AN}}{L}$.

other i_B & i_C currents have $\pm T/3$ shift.

As for i_S : $i_S = i_{Q1} + i_{Q3} + i_{Q5} - i_{D1} - i_{D3} - i_{D5}$

as shown, where $I = ET/18L$

$$P_A = \frac{1}{T} \int_0^T V_{AN} i_A dt = \frac{1}{T} \int_0^T \text{odd} * \text{even} = 0$$

$P_B = P_A + P_C = 0$ (consistent with the fact that L loads dissipate no power). OK.

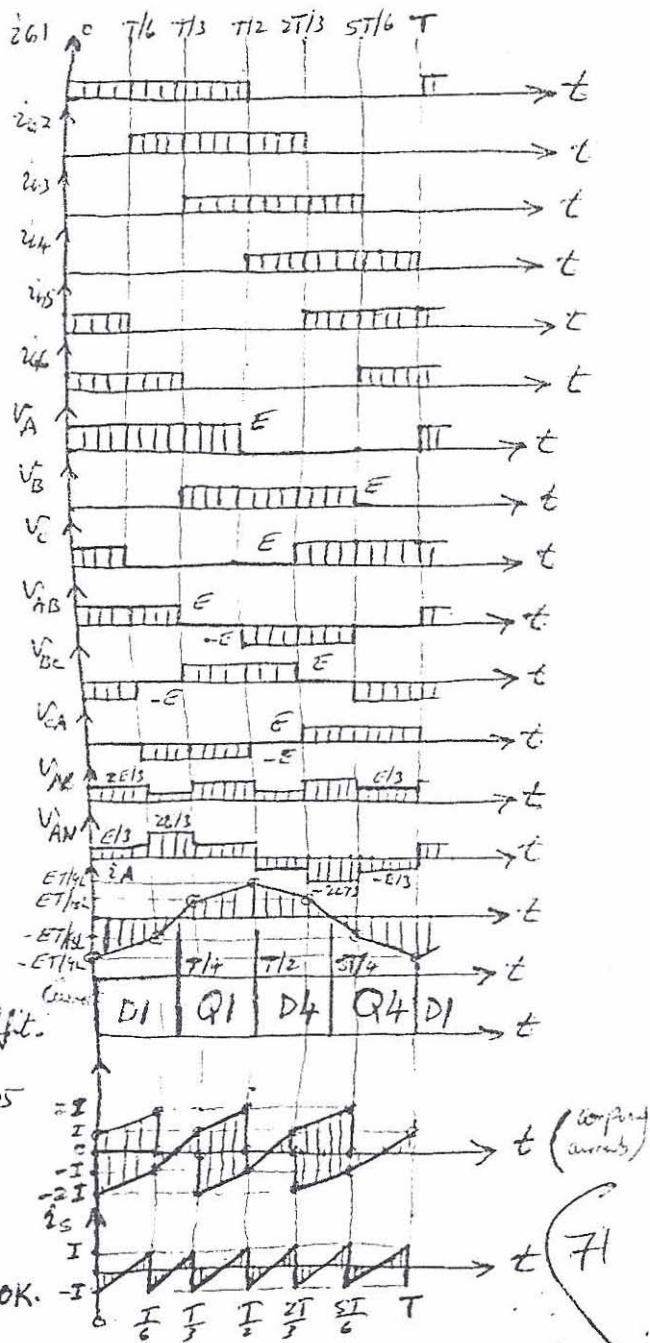
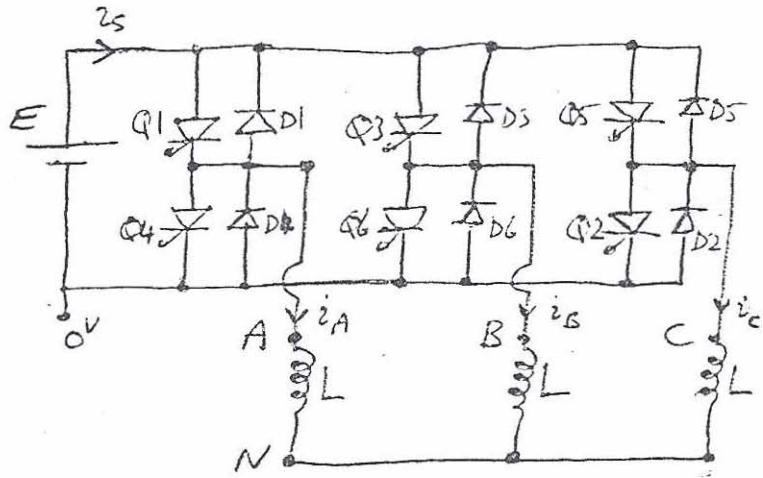


Fig 13

Assuming symmetrical star loads, with circuit as in Fig 12 above, the waveforms are as shown.

The slope at the indeterminate interval is decided by the load. Due to load being inductive, the load currents at instants of commutating Q1, Q3 & Q5 will have to freewheel through D4, D6 & D2 respectively. Likewise, at commutation of Q4, Q6 & Q2 through D1, D3 & D5 respectively. This gives the shapes shown of V_A , V_B & V_C . The potential of V_N is obtained as before as:


$$V_N = \frac{V_A + V_B + V_C}{3}, \text{ and is as shown.}$$

Hence, V_{AN} , V_{BN} & $V_{CN} = V_c - V_N$ are as shown. Note the $\frac{T}{2}$ shifts.

Also note that the presence of freewheeling diodes makes the conduction effectively for half cycle, so that the previous case waveforms show up again with $T/6$ phase shift.

Again initial state currents are assumed to preserve symmetry hence, i_A , i_B & i_C are as shown, where $I = ET/18L$.

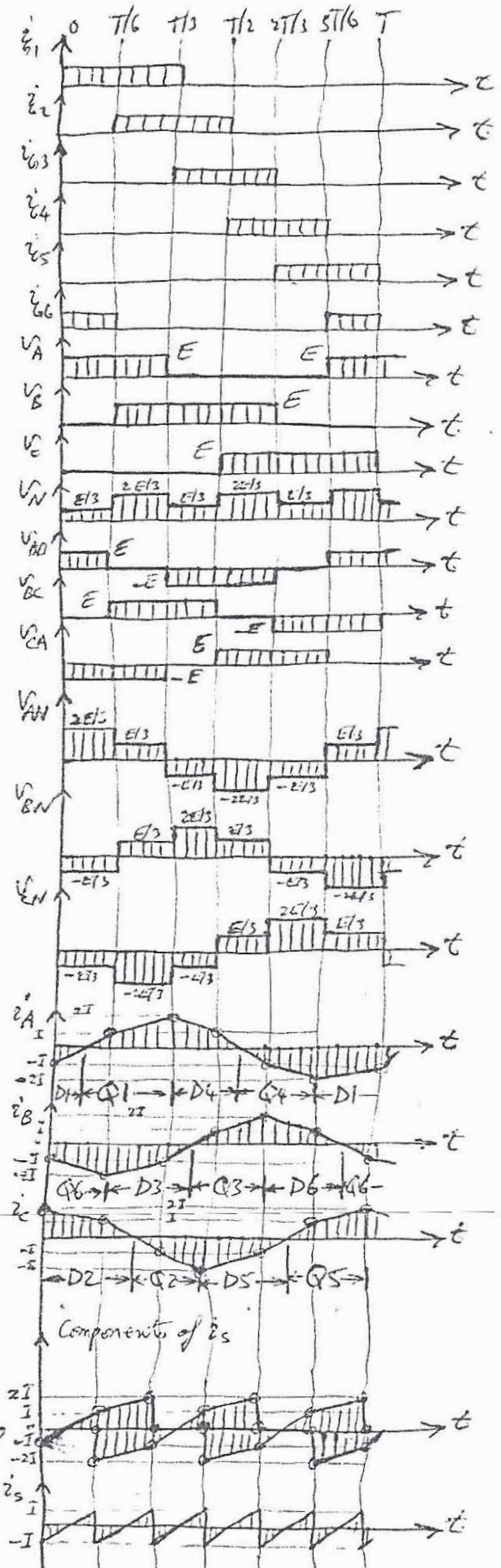Again, $i_S = i_Q + i_{Q3} + i_{Q5} - i_{D1} - i_{D3} - i_{D5}$ and is obtained from components as shown. Note the $\frac{T}{6}$ phase shift compared to the one obtained earlier. As before power consumed is zero.



72




4-14

The load commutation in the current inverter shown, is caused by the capacitor.


When current flows into the capacitor the voltage across it will build up, hence making a forward bias to the thyristors not in conduction. When these thyristors are gated, the current will divert its flow and a short circuit will occur to the load combination. This short circuit will force the commutation of the thyristors at conduction and hence half a cycle is complete. The same would happen in the other half cycle. If the gating of the thyristors not in conduction was delayed, a voltage reversal (due to oscillation) may occur and commutation is not possible because these thyristors have not been turned on to short the load combination.

The importance of lead inductances is during the commutation interval whereby, the current rate of change is so high that the lead inductances cause a substantial voltage drop.

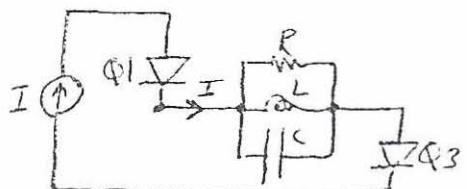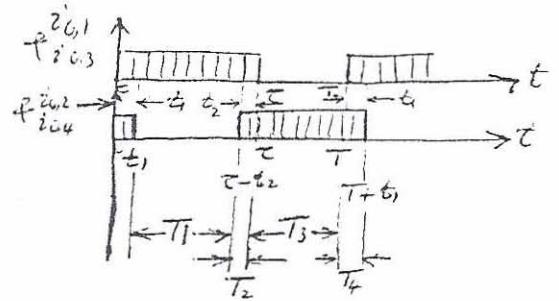
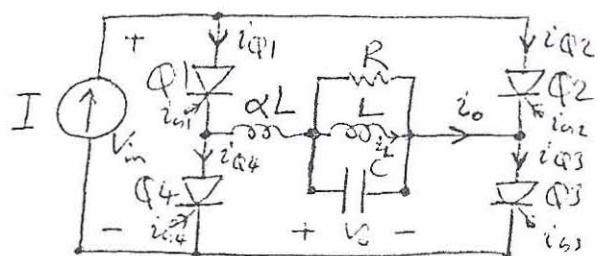
Assuming ideal components, the circuit will look like the following at various instants of time, with shown rectifiers fully on.



$$t \in T_1 = (t_1, t - t_2)$$

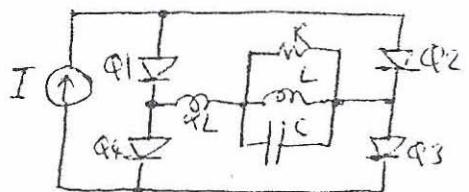

$$t \in T_2 = [t - t_2, t]$$

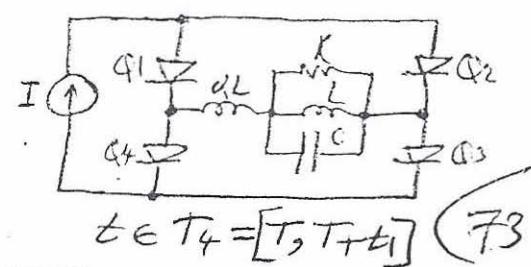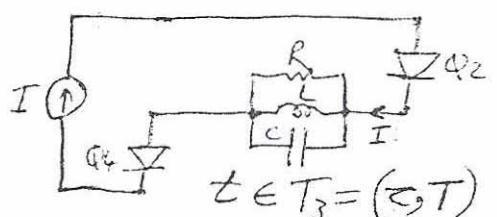

$$t \in T_4 = [T_3, T + t_1] \quad (73)$$

Now, assuming $\alpha \ll \omega$ which is a practically justified assumption, then the commutation time becomes too small that the load inductance during this commutation interval could be considered as a current source passing the same value of pre-commutation current. Let us analyze the circuit for each time interval.

at $t \in T_1$, the initial i_L & V_o are assumed to be $I_1 + V_1$

$$\therefore I(s) = V_o(s) \cdot \left(\frac{1}{R} + \frac{1}{sL} + \frac{1}{sC} \right) = V_o(s) \cdot \frac{s^2 L C R + s L + R}{s L R}$$

$$\therefore V_o(s) = \frac{s L R}{s^2 L C R + s L + R} \cdot I(s)$$

$$\therefore s = \frac{-L \pm \sqrt{L^2 - 4LCR^2}}{2LCR} \quad \text{∴ load mode is resonating}$$

$$\therefore s = \frac{-L \pm j\sqrt{4LCR^2 - L^2}}{2LCR} = -\frac{1}{2CR} \pm j\sqrt{\frac{1}{LC} - \left(\frac{1}{2CR}\right)^2} = -\sigma \pm j\omega$$

$$\therefore \sigma = \frac{1}{2CR} \quad \text{and} \quad \omega = \sqrt{\frac{1}{LC} - \left(\frac{1}{2CR}\right)^2} = \sqrt{\frac{1}{LC} - \sigma^2}$$

$$\therefore V_o(t) = \frac{s L R}{s^2 L C R + s L + R} \cdot I = \left[A_1 \sin \omega(t-t_1) + B_1 \cos \omega(t-t_1) \right] e^{-\sigma(t-t_1)}$$

$$\therefore V_o(t_1) = V_1 = B_1$$

$$\therefore V_o(t) = \left[A_1 \sin \omega(t-t_1) + V_1 \cos \omega(t-t_1) \right] e^{-\sigma(t-t_1)} \quad t \in T_1 \quad (1)$$

$$\therefore i_o(t) = I \quad t \in T_1 \quad (2)$$

$$\therefore i_L(t_1) = I - \frac{V_o(t_1)}{R} - C \dot{V}_o(t_1) = I - \frac{V_1}{R} - C(-\sigma V_1 + \omega A_1) = I,$$

$$\therefore A_1 = \frac{I - I_1 - \sigma C V_1}{\omega C} \quad (3)$$

$$\therefore V_o(t-t_1) = V_2 = \left[A_1 \sin \omega(t-t_1-t_2) + V_1 \cos \omega(t-t_1-t_2) \right] e^{-\sigma(t-t_1-t_2)} \quad (4)$$

$$\therefore i_L(t-t_2) = I_2 = I - \sigma C V_2 - \omega C e^{-\sigma(t-t_1-t_2)} \cdot \left[A_1 \cos \omega(t-t_1-t_2) - V_1 \sin \omega(t-t_1-t_2) \right] \quad (5)$$

\leftarrow At $t \in T_2$, with $\alpha \ll 1$ then commutation time is very short, during which, the load inductance current, i_L , could be assumed constant at I_2 , hence appearing as a current source. The capacitor voltage could also be assumed constant, with value $V_2 > 0$ to enable Q2 + Q4 to fire.

$$\therefore i_L(t) = I_2 \quad t \in T_2 \quad (6)$$

$$\leftarrow V_o(t) = V_2 \quad t \in T_2 \quad (7)$$

$$\leftarrow -\dot{i}_o \cdot \alpha L = V_o$$

$$\therefore i_o = \int -\frac{V_o}{\alpha L} dt = -\frac{V_2}{\alpha L} \cdot t + A_3$$

$$\therefore i_o(\tau - t_2) = I \quad \therefore I = -\frac{V_2}{\alpha L} \cdot (\tau - t_2) + A_3$$

$$\therefore A_3 = I + \frac{V_2}{\alpha L} (\tau - t_2)$$

$$\therefore i_o(t) = \frac{V_2}{\alpha L} (\tau - t_2 - t) + I \quad t \in T_2 \quad (8)$$

\therefore The condition for t_2 is that $i_o(\tau) = -I$

$$\therefore -I = \frac{V_2}{\alpha L} (\tau - t_2 - \tau) + I \Rightarrow -2I = -\frac{V_2 t_2}{\alpha L}$$

$$\therefore t_2 = \frac{2 \alpha L I}{V_2} \quad (9)$$

\leftarrow At $t \in T_3$, the initial i_o & V_o are respectively $I_2 + V_2$.

\therefore Like the analysis of T_1 :

$$\therefore i_o(t) = -I \quad t \in T_3 \quad (10)$$

$$\leftarrow V_o(t) = [A_2 \sin \omega(t-\tau) + V_2 \cos \omega(t-\tau)] \cdot e^{-\sigma(t-\tau)}, t \in T_3 \quad (11)$$

$$\text{where: } A_2 = -(I + I_2 + \sigma C V_2) / \omega C \quad (12)$$

$$\therefore V_o(t) = V_1 = [A_2 \sin \omega(T-t) + V_2 \cos \omega(T-t)] e^{-\sigma(T-t)} \quad (13)$$

$$\nexists i_L(t) = I_1 = -I - \omega C V_1 - \omega C e^{-\sigma(T-t)} [A_2 \cos \omega(T-t) - V_2 \sin \omega(T-t)] \quad (14)$$

\therefore At $t \in T_4$, like for $t \in T_2$; but $V_1 < 0$ for Q1 + Q3 to flow.

$$\therefore i_L(t) = I_1 \quad t \in T_4 \quad (15)$$

$$\nexists V_o(t) = V_1 \quad t \in T_4 \quad (16)$$

$$\nexists i_o(t) = \frac{V_1}{\alpha L} \cdot (T-t) - I \quad t \in T_4 \quad (17)$$

Hence, the condition for t_1 is that $i_o(t+t_1) = I$

$$\therefore t_1 = \frac{-2\alpha L I}{V_1} \quad (V_1 < 0) \quad (18)$$

This completes one cycle at steady state.

Now, we want to find $I_1, V_1, I_2 \& V_2$ in terms of given parameters. This is done by solving (3), (4), (5), (12), (13) & (14) together.

(3) & (4) gives:

$$V_2 e^{\sigma(\tau-t_1-t_2)} \cdot \omega C = I \sin \omega(\tau-t_1-t_2) - I_1 \sin \omega(\tau-t_1-t_2) + V_1 \left[\omega C \cos \omega(\tau-t_1-t_2) - \omega C \sin \omega(\tau-t_1-t_2) \right]$$

$$\text{Let } t_+ = \tau - t_1 - t_2$$

$$\therefore V_2 e^{\sigma t_+} \cdot \omega C = I \sin \omega t_+ - I_1 \sin \omega t_+ + V_1 (\omega \cos \omega t_+ - \sigma \sin \omega t_+) \quad (19)$$

\nexists (3) & (5) gives:

$$I_2 + \sigma C V_2 = I \left(1 - e^{-\sigma t_+} \cos \omega t_+ \right) + I_1 e^{-\sigma t_+} \cos \omega t_+ + V_1 e^{-\sigma t_+} \left(\omega \sin \omega t_+ + \sigma \cos \omega t_+ \right) \quad (20)$$

76

Let $t_+ = T - \tau$

$\therefore (12) + (13)$ gives:

$$V_1 e^{\frac{\sigma t}{\omega C}} = -I_1 \sin \omega t_+ - I_2 \sin \omega t_+ + CV_2 (\omega \cos \omega t_+ - \sigma \sin \omega t_+) \quad (21)$$

$+ (12) - (14)$ gives

$$I_1 + \sigma CV_1 = I_1 (e^{-\frac{\sigma t}{\omega C}} - 1) + I_2 e^{-\frac{\sigma t}{\omega C}} \cos \omega t_+ + CV_2 e^{-\frac{\sigma t}{\omega C}} (\omega \sin \omega t_+ + \sigma \cos \omega t_+) \quad (22)$$

For maximum power delivered to R , then the following conditions must be met:

- I) $t_+ = t_- = t_0$ i.e. $\tau - t_1 - t_2 = T - \tau \Rightarrow \tau = \frac{T + t_1 + t_2}{2}$
- II) $t_+ + t_- \approx \frac{2\pi}{\omega}$ i.e. $T - t_1 - t_2 \approx \frac{2\pi}{\omega} \Rightarrow T \approx \frac{2\pi}{\omega} + t_1 + t_2$
 $\therefore 2t_2 \approx \frac{2\pi}{\omega} \Rightarrow t_2 \approx \pi/\omega$. Let $t_0 = \frac{\pi - \delta}{\omega}$.

The above conditions implies that the behaviour of the circuit during T_1 is just same as during T_3 & T_2 as T_4 with opposite sense, i.e. symmetrical.

$$\therefore V_1 = -V_2 \quad \text{and} \quad I_1 = -I_2$$

$\therefore (19) + (21)$ become the same as:

$$-V_1 e^{\frac{\sigma t_0}{\omega C}} \stackrel{(+\delta)}{\approx} I_1 \sin \omega t_0 - I_1 \sin \omega t_0 + CV_1 \left(\omega \cos \omega t_0 - \sigma \sin \omega t_0 \right)$$

$$\therefore -V_1 e^{\frac{\sigma t_0}{\omega C}} \approx -CV_1 \omega + \delta (I_1 - I_1)$$

$$\text{or } \omega C V_1 (1 - e^{\frac{\sigma t_0}{\omega C}}) \approx +\delta (I_1 - I_1) \Rightarrow V_1 \approx \frac{-\delta (I_1 - I_1)}{\omega C (e^{\frac{\sigma t_0}{\omega C}} - 1)} \quad (23)$$

$+ (20) + (22)$ become the same as:

$$I_1 + \sigma CV_1 = I_1 (1 - e^{-\frac{\sigma t_0}{\omega C}}) + I_2 e^{-\frac{\sigma t_0}{\omega C}} \stackrel{(-1)}{\approx} CV_1 e^{-\frac{\sigma t_0}{\omega C}} (\omega \sin \omega t_0 + \sigma \cos \omega t_0)$$

$$\approx I_1 (1 + e^{-\frac{\sigma t_0}{\omega C}}) - I_2 e^{-\frac{\sigma t_0}{\omega C}} - CV_1 e^{-\frac{\sigma t_0}{\omega C}}$$

$$\therefore (I_1 + \sigma CV_1) (e^{-\frac{\sigma t_0}{\omega C}} - 1) \approx I_1 (1 + e^{-\frac{\sigma t_0}{\omega C}}) \Rightarrow I_1 + \sigma CV_1 = \frac{e^{-\frac{\sigma t_0}{\omega C}} - 1}{1 - e^{-\frac{\sigma t_0}{\omega C}}} \cdot I_1 \quad (24)$$

Solving (23) & (24):

$$\begin{aligned}\therefore I_1 + \omega C \left(\frac{-\delta(I - I_1)}{\omega(e^{\sigma t_0} - 1)} \right) &= \frac{e^{\sigma t_0} + 1}{1 - e^{\sigma t_0}} \cdot I \\ \therefore I_1 \left[1 + \frac{\omega \delta}{\omega(e^{\sigma t_0} - 1)} \right] &= \frac{-\omega C \delta + \omega C + \omega C e^{\sigma t_0}}{(1 - e^{\sigma t_0}) \omega C} \cdot I \\ \therefore I_1 \approx \frac{1 + e^{\sigma t_0}}{1 - e^{\sigma t_0}} I &= \frac{e^{\sigma t_0} + 1}{e^{\sigma t_0} - 1} \cdot (-I) \\ \therefore I_1 = -I \cdot \frac{e^{\sigma \pi / \omega}}{e^{\sigma \pi / \omega} - 1} &\quad (25)\end{aligned}$$

$$(23) \Rightarrow \therefore V_1 = \frac{-\delta}{\omega C} \cdot \left(\frac{I + I \cdot \frac{e^{\sigma \pi / \omega} + 1}{e^{\sigma \pi / \omega} - 1}}{e^{\sigma \pi / \omega} - 1} \right) = \frac{-\delta I (e^{\sigma \pi / \omega} - 1 + e^{\sigma \pi / \omega} + 1)}{\omega C (e^{\sigma \pi / \omega} - 1)^2}$$

$$\therefore V_1 = \frac{-2\delta I e^{\sigma \pi / \omega}}{\omega C (e^{\sigma \pi / \omega} - 1)^2} = \frac{-\delta I}{2\omega C \sinh^2(\frac{\sigma \pi}{2\omega})} \rightarrow \delta > 0 \quad (26)$$

(9) & (18) both become:

$$t_2 = t_1 = t_c = \frac{2\alpha L I}{V_2} = \frac{2\alpha L I}{-V_1} = \frac{2\alpha L I}{+\delta I} \left(2\omega C \sinh^2(\frac{\sigma \pi}{2\omega}) \right)$$

$$\therefore t_c = +4\alpha \omega L C \sinh^2(\frac{\sigma \pi}{2\omega}) / \delta \quad , \quad \delta > 0 \quad (27)$$

$$\therefore T = \frac{I + t_1 + t_2}{2} = \frac{I}{2} + t_c \approx T/2 \quad , \quad \text{since } t_c \ll \ll T$$

$$\therefore T \approx \frac{2\pi}{\omega} + 2t_c \approx \frac{2\pi}{\omega} \quad , \quad \text{since } t_c \ll \ll T$$

$$\therefore \omega = \frac{2\pi}{T} = \sqrt{\frac{1}{LC} - \left(\frac{1}{2R}\right)^2} \Rightarrow \frac{4\pi^2}{T^2} = \frac{1}{LC} - \frac{1}{4R^2C^2}$$

$$\therefore \frac{1}{C} = \frac{-\frac{1}{L} \pm \sqrt{\frac{1}{L^2} + 4 \cdot \frac{1}{4R^2} - \frac{4\pi^2}{T^2}}}{-2/4R^2} = \frac{2R^2}{L} \pm \sqrt{\left(\frac{2R^2}{L}\right)^2 - 16\pi^2 R^2/L^2/T^2}$$

$$= \frac{2R}{TL} \cdot \sqrt{T^2 R^2 - 4\pi^2 L^2}$$

$$\therefore C = \frac{TL}{2R} \cdot \frac{1}{RT \pm \sqrt{R^2 T^2 - 4\pi^2 L^2}} = \frac{TL}{2R} \cdot \frac{RT \pm \sqrt{R^2 T^2 - 4\pi^2 L^2}}{4\pi^2 L^2} \quad (78)$$

$$\# \therefore C, \text{ the commutating capacitor} = \frac{TL}{8\pi^2 LR} \cdot (RT \pm \sqrt{R^2 T^2 - 4\pi^2 L^2}) \quad (28)$$

The power maximized, P , is given by using (i) :

$$\begin{aligned}
 P &= \frac{1}{T} \int_0^T V_o^2(t)/R dt = \frac{2}{RT} \int_{t_c}^{T/2} V_o^2(t) dt \approx \frac{2}{RT} \int_{t_c}^{T/2} [A_1 \sin \omega(t-t_c) + V_i \cos \omega(t-t_c)]^2 dt \\
 * e^{-2\zeta\omega(t-t_c)} dt &= \frac{2}{RT} \int_{t_c}^{T/2} [A_1^2 (1 - \cos 2\omega(t-t_c)) + V_i^2 (1 + \cos 2\omega(t-t_c)) + \\
 &\quad + 2A_1V_i \frac{\sin 2\omega(t-t_c)}{2}] \cdot e^{-2\zeta\omega(t-t_c)} dt = \\
 &= \frac{2}{RT} \cdot \left[\frac{A_1^2 + V_i^2}{\zeta} e^{-2\zeta\omega(t-t_c)} + e^{-2\zeta\omega(t-t_c)} \frac{(A_1^2/2)(2\omega \sin 2\omega(t-t_c) - 2\zeta \cos \omega(t-t_c))}{-4\omega^2 - 4\zeta^2} \right. \\
 &\quad \left. + (V_i^2/2)(2\omega \cos 2\omega(t-t_c) - 2\omega \sin \omega(t-t_c)) + A_1V_i (2\omega \cos \omega(t-t_c) + 2\zeta \sin \omega(t-t_c)) \right] \\
 &\approx \frac{2}{RT} \cdot \left[\frac{A_1^2 + V_i^2}{4\zeta} (1 - e^{-2\zeta\pi/\omega}) + \frac{(-A_1^2\zeta + V_i^2 + 2A_1V_i\omega)e^{-2\zeta\pi/\omega}}{4(\omega^2 + \zeta^2)} \right] \\
 &= \frac{(1 - e^{-2\zeta\pi/\omega})}{2RT} \cdot \left[\frac{A_1^2 + V_i^2}{\zeta} + \frac{(-A_1^2 + V_i^2)\zeta + 2A_1V_i\omega}{\omega^2 + \zeta^2} \right]
 \end{aligned}$$

but:

$$A_1 = \frac{I - I_1 - \omega C V_i}{\omega C} \approx \frac{I - I_1}{\omega C} = \frac{I + \frac{I(e^{\zeta\pi/\omega} + 1)}{(e^{\zeta\pi/\omega} - 1)}}{\omega C} = \frac{2e^{\zeta\pi/\omega} \cdot I}{(e^{\zeta\pi/\omega} - 1)\omega C} = \frac{e^{\zeta\pi/\omega} I}{\omega C \sinh(\zeta\pi/\omega)}$$

$$\therefore A_1^2 + V_i^2 \approx A_1^2 \quad \therefore -A_1^2 + V_i^2 \approx -A_1^2$$

$$\begin{aligned}
 \therefore P &\approx \frac{1 - e^{-2\zeta\pi/\omega}}{2RT} \cdot \left[\frac{1}{\zeta} - \frac{1}{\omega^2 + \zeta^2} \right] A_1^2 = \frac{\sinh(\zeta\pi/\omega)}{RT e^{\zeta\pi/\omega}} \cdot \left[2RC - \frac{L}{2RC} \right] A_1^2 \\
 &= \frac{\sinh(\zeta\pi/\omega)}{2R^2 C T e^{\zeta\pi/\omega}} \cdot (4R^2 C^2 - L) \cdot \frac{4e^{2\zeta\pi/\omega} I^2}{\omega^2 C^2 (e^{\zeta\pi/\omega} - 1)^2}
 \end{aligned}$$

$$\therefore \text{Max. power, } P = (4R^2 C - L) I^2 \sinh(\zeta\pi/\omega) / 2R^2 C T e^{\zeta\pi/\omega} \sinh(\frac{\zeta\pi}{2})$$

$$\text{or } P = \frac{4R^2 C - L}{R^2 C^2 T} \cdot \coth(\frac{\zeta\pi}{2}) \cdot I^2 = \frac{4R^2 C - L}{R^2 C^2 T \cdot \frac{4LCR^2 - L^2}{4L^2 C^2 R^2}} \cdot \coth(\frac{\zeta\pi}{2}) \cdot I^2$$

$$\# \therefore P = 4L I^2 \coth(\frac{\zeta\pi}{2}) / T \quad (29)$$

As for waveforms:

$$i_{Q1} = i_{Q3} \text{ for all } t$$

$$\nexists i_{Q2} = i_{Q4} \text{ for all } t$$

during $t \in T_2$

$$\therefore I = i_{Q1} + i_{Q2}$$

$$\nexists i_{Q1} = i_{Q4} + i_c = i_{Q2} + i_c$$

$$\therefore I = i_{Q2} + i_c + i_{Q1} = 2i_{Q2} + i_c$$


$$\therefore i_{Q2} = \frac{I - i_c}{2} = \frac{I - I - (\zeta - t_2 - t)V_2/\omega L}{2} \\ = +(\frac{\zeta}{2} - t)V_2/2\omega L$$

$$\therefore i_{Q2}(t) = \frac{\delta(\zeta - t/T_2)}{4\omega LC \sinh^2(\zeta\pi/2\omega)} \cdot I, t \in T_2$$

$$V_L = 0 \text{ for } t \in T_2$$

$$\nexists V_L(t) = V_c(t) \text{ for } t \in T_1$$
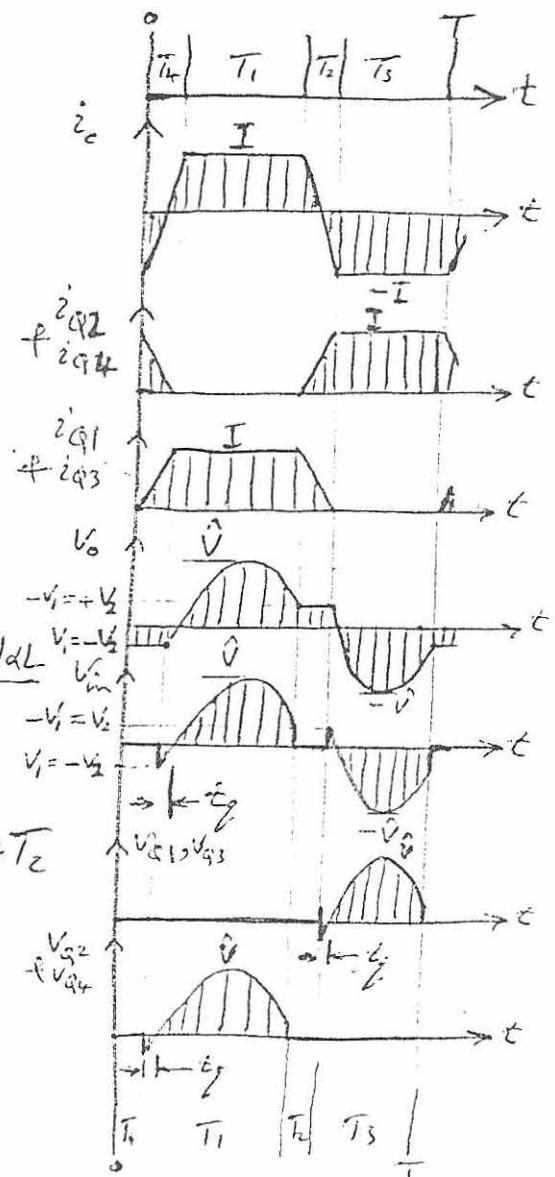
$$\nexists i_{Q1} = i_{Q3} = i_c = I \text{ for } t \in T_1$$



$$\hat{V} = V_c(t) \underset{\text{max}}{\approx} A_1 e^{-\zeta\pi/2\omega} = \frac{2e^{-\zeta\pi/2\omega} I}{(e^{-\zeta\pi/2\omega} - 1)\omega c} e^{-\zeta\pi/2\omega} = \frac{I}{\omega c \sinh(\zeta\pi/2\omega)} \quad (30)$$

$$\text{From (1)} \quad \therefore V_c(t_1 + t_2) = 0$$

$$\therefore A_1 \sin \omega t_2 + V_c \cos \omega t_2 = 0 \quad \therefore \tan \omega t_2 = -\frac{V_c}{A_1} = (\text{From (26) if } A_1 \neq 0)$$

$$= \frac{\delta I}{2\omega c \sinh^2(\zeta\pi/2\omega)} \cdot \frac{\omega c \sinh(\zeta\pi/2\omega)}{I e^{-\zeta\pi/2\omega}} = \frac{\delta e^{-\zeta\pi/2\omega}}{2 \sinh(\zeta\pi/2\omega)} = \frac{\delta}{e^{\zeta\pi/2\omega} - 1}$$

$$\# \therefore \delta = (e^{\zeta\pi/2\omega} - 1) \cdot \tan \omega t_2 \ll \pi \quad (31)$$

This closes all the expressions for the problem.

4-15 Since load is resistive, then no need for the six freewheeling diodes and the bridge becomes as shown here.

The neutral voltage V_N is again, due to symmetry, given by:

$$V_N = \frac{1}{3} (V_A + V_B + V_C)$$

The waveforms are as shown.

The source current i_s is:

$$i_s = i_{Q1} + i_{Q5} + i_{Q3}$$

where i_{Q1}, i_{Q5} & i_{Q3} are the positive parts of i_A, i_B & i_C respectively (i_{Q4}, i_{Q2} & i_{Q6} are respectively the negative)

$\therefore i_s$ is obtained as shown (constant)

$$\therefore V_s(t) = a_n \sin n\omega t + b_n \cos n\omega t$$

$b_n = 0$ due to symmetry.

$$\therefore a_n = \frac{2}{T} \int_0^T V_{AN}(t) \sin n\omega t dt =$$

$$= \frac{3}{T} \int_0^{T/4} V_{AN}(t) \sin n\omega t dt =$$

$$= \frac{8E}{T} \left[\int_{(E/3)}^{(E/3)} \sin n\omega t dt + \int_{(2E/3)}^{(2E/3)} \sin n\omega t dt \right] =$$

$$= \frac{E \cdot 8}{3T} \left[-\frac{\cos n\omega t}{n\omega} \Big|_{(E/3)}^{(E/3)} - 2 \frac{\cos n\omega t}{n\omega} \Big|_{(2E/3)}^{(2E/3)} \right] =$$

$$= \frac{8E}{3n\omega T} \left[1 - \cos(n\omega T/6) - 2 \cos(n\omega T/4) + 2 \cos(n\omega T/6) \right]$$



$$= \frac{8E}{3n\omega T} \left[1 + \cos(n\pi/3) - 2 \cos(n\pi/2) \right]$$

$$\therefore a_1 = \frac{4E}{3\pi} (1 + \cos \pi/3 + 0) = \frac{4E}{3\pi} (1 + \frac{1}{2}) = \frac{2E}{\pi}$$

$$\therefore \text{phase fundamental} = \frac{RE}{\pi} = \frac{V_L + 100}{\pi} = 45.0 \text{ Volts}$$

$$\text{phase rms} = \sqrt{\frac{1}{T} \left[\left(\frac{E}{3}\right)^2 I_0 + \left(\frac{2E}{3}\right)^2 I_0 \right]} = \frac{\sqrt{2} E}{3}$$
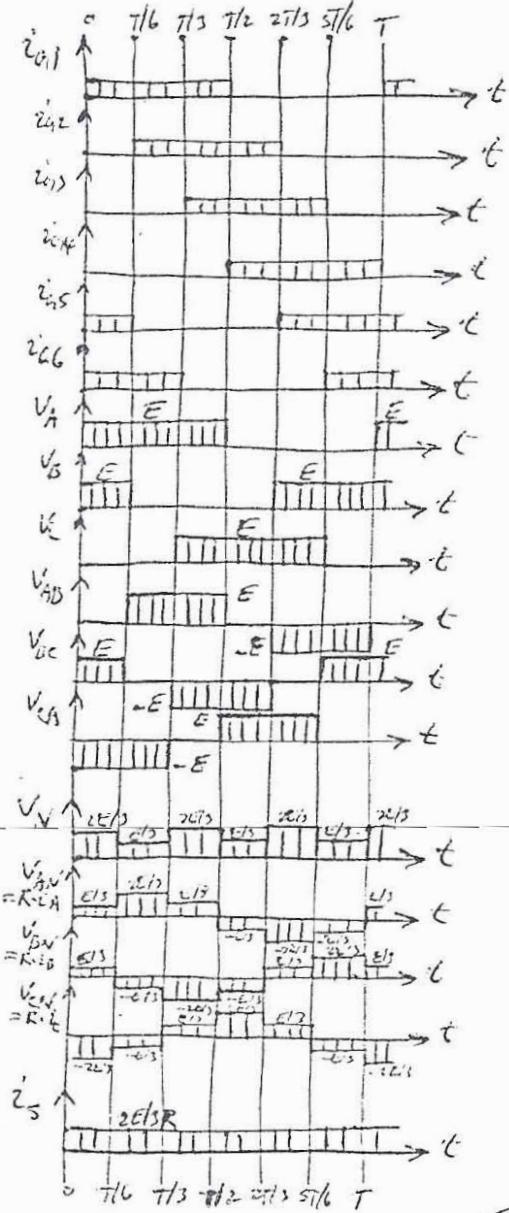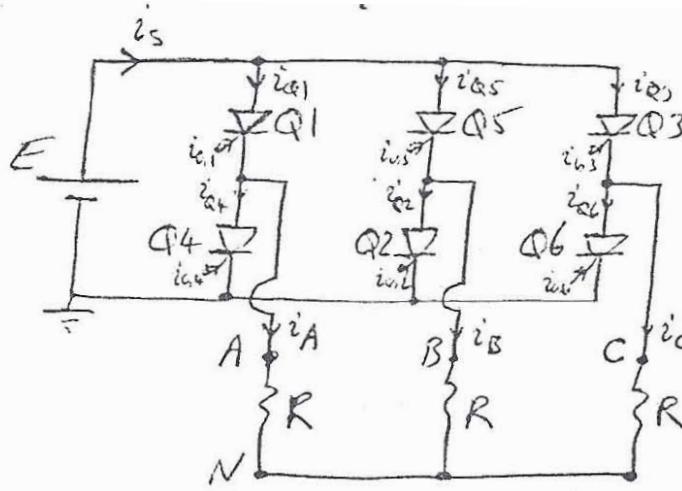
$$\therefore \text{phase distortion} = \frac{V_{L \text{ fundamental}}}{V_{L \text{ rms}}} = \sqrt{1 - \left(\frac{R_L I_0}{V_{L \text{ rms}}}\right)^2} = \sqrt{1 - \frac{9}{16}} = 0.297 \approx 30\%$$



81A

4-16

$$f = 60 \text{ Hz} \Rightarrow T = 16.67 \text{ ms}$$

$$R = 100 \Omega \quad L = 1 \mu\text{H}$$

Circuit shown gives the waveforms indicated.

When Q_1 & Q_3 are turned on at $t=0$, the source charges C up so that as soon as Q_2 & Q_4 are gated, C discharges through $Q_4 Q_3$ causing Q_3 to be off and through $Q_1 Q_2$ causing Q_1 to be off. This makes I to recharge C with opposite sense till Q_1 & Q_3 are gated again at $t=T$ whereby a similar procedure ensures the turn off of Q_2 & Q_4 .



Hence, no forced commutation is required. Since $RC = 100 \mu\text{s}$ and $T \gg RC$; then waveform of V_C looks rectangular as shown with equations:

$$V_C(t) = IR(1 - e^{-t/RC}) \quad t \in [0, T/2]$$

$$V_C \text{ is zero at } t = RC \ln 2 = 69.3 \mu\text{s}$$

This is also the time during which thyristors are reversed biased after being put off.

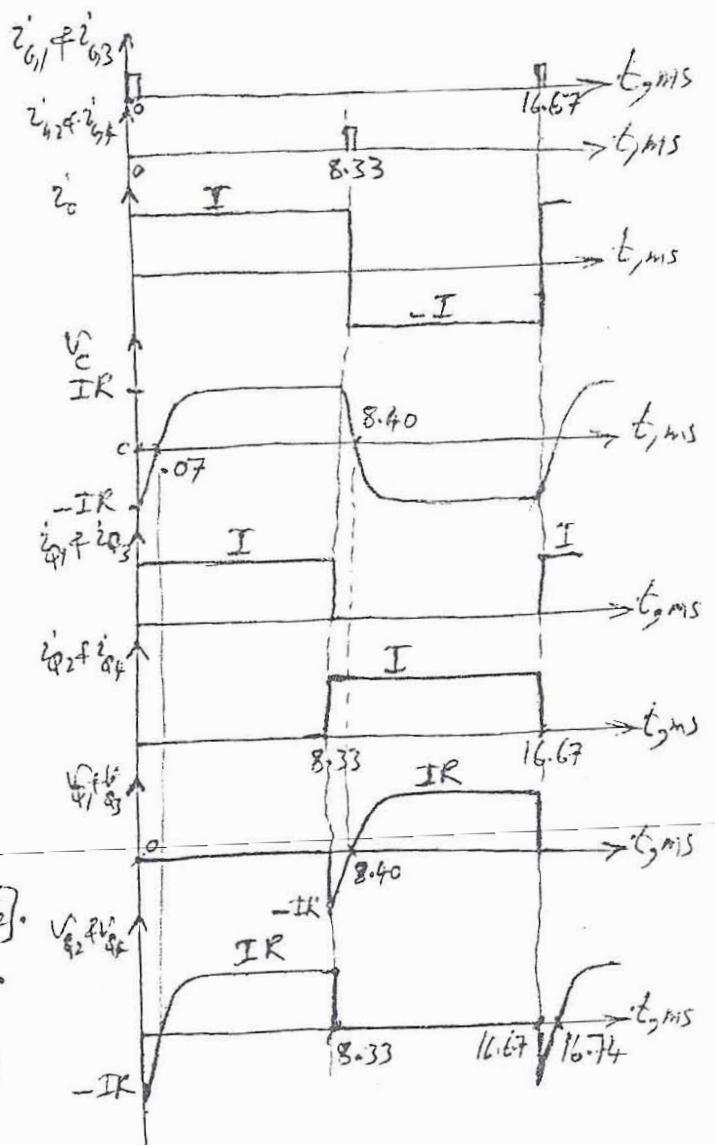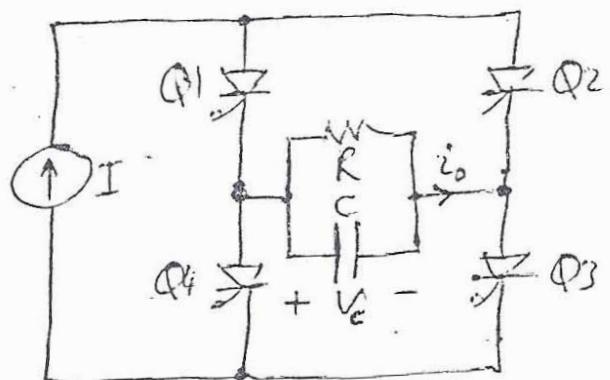$\therefore t_g$ must be $\leq 69.3 \mu\text{s}$.



81B

4-17-a

Chopper inverter:

The circuit is as shown aside where no diodes are required since no inductance is present.

The output fundamental is given by:

$$V_o(t)_{\text{fundamental}} = a \sin\left(\frac{2\pi t}{T}\right) + b \cos\left(\frac{2\pi t}{T}\right)$$

$$\begin{aligned} \therefore a &= \frac{2}{T} \int_0^T V_o(t) \sin\left(\frac{2\pi t}{T}\right) dt = \\ &= \frac{2}{T} \left[\int_0^{\frac{T}{2}} E \sin\left(\frac{2\pi t}{T}\right) dt - \int_{\frac{T}{2}}^T E \sin\left(\frac{2\pi t}{T}\right) dt \right] = \\ &= \frac{2E}{T} \left[\frac{-\cos(2\pi t/T)}{2\pi/T} \Big|_0^{\frac{T}{2}} + \cos(2\pi t/T) \Big|_{\frac{T}{2}}^T \right] = \\ &= \frac{E}{\pi} \left[1 - \cos(2\pi/2) + 1 - \cos(2\pi T/T) \right] = \\ &= \frac{2E}{\pi} \left(1 - \cos\left(\frac{2\pi T}{T}\right) \right). \end{aligned}$$

$$\begin{aligned} \therefore b &= \frac{2}{T} \int_0^T V_o(t) \cos\left(\frac{2\pi t}{T}\right) dt = \\ &= \frac{2}{T} \left[\int_0^{\frac{T}{2}} E \cos\left(\frac{2\pi t}{T}\right) dt - \int_{\frac{T}{2}}^T E \cos\left(\frac{2\pi t}{T}\right) dt \right] = \\ &= \frac{2E}{T} \left[\frac{\sin(2\pi t/T)}{2\pi/T} \Big|_0^{\frac{T}{2}} - \sin(2\pi t/T) \Big|_{\frac{T}{2}}^T \right] = \\ &= \frac{E}{\pi} \left[\sin(2\pi/2) - 0 - 0 + \sin(2\pi T/T) \right] = \\ &= \frac{2E}{\pi} \sin(2\pi T/T). \end{aligned}$$

$$\begin{aligned} \therefore V_o^2_{\text{fundamental rms}} &= \left(\frac{a}{\sqrt{2}}\right)^2 + \left(\frac{b}{\sqrt{2}}\right)^2 = \frac{1}{2}(a^2 + b^2) = \frac{1}{2} \cdot \left(\frac{2E}{\pi}\right)^2 \left((1 - \cos(2\pi T/T))^2 + \sin^2(2\pi T/T) \right) = \\ &= \frac{2E^2}{\pi^2} \cdot (1 - 2\cos(2\pi T/T) + \cos^2(2\pi T/T) + \sin^2(2\pi T/T)) = \frac{4E^2}{\pi^2} (1 - \cos(2\pi T/T)) = \frac{8E^2}{\pi^2} \sin^2\left(\frac{\pi T}{2}\right) \end{aligned}$$



$$\therefore V_o^2_{\text{fundamental rms}} = \frac{2\sqrt{2}E}{\pi} \sin\left(\frac{\pi T}{2}\right) \Rightarrow \frac{2\sqrt{2} * 300}{\pi} \sin\left(\frac{\pi T}{2}\right) = 110 \Rightarrow \frac{\pi T}{2} = 0.41946 \text{ OR } 2.72214$$

$$\# \therefore \frac{\pi}{T} = 0.13352 \text{ OR } 0.86648$$

$$\# \therefore V_o^2_{\text{rms}} = (E^2 \tau + E^2 (T-\tau))/T = E^2 \therefore V_o_{\text{rms}} = E \quad \# V_o = (E\tau - E(T-\tau))/T = E(\frac{\pi T}{2} - 1) = \pm E \cdot 0.73297$$

$$\# \therefore \# = \frac{V_o^2_{\text{harmonics rms}}}{V_o^2_{\text{rms ac}}} = \frac{V_o^2_{\text{rms}} - V_o^2_{\text{ac}} - V_o^2_{\text{fundamental}}}{V_o^2_{\text{rms}} - V_o^2_{\text{ac}}} = \sqrt{1 - \left(\frac{110}{300}\right)^2 \cdot \frac{1}{(1 - 0.73297)^2}} = 0.84230 = 84.23\%$$

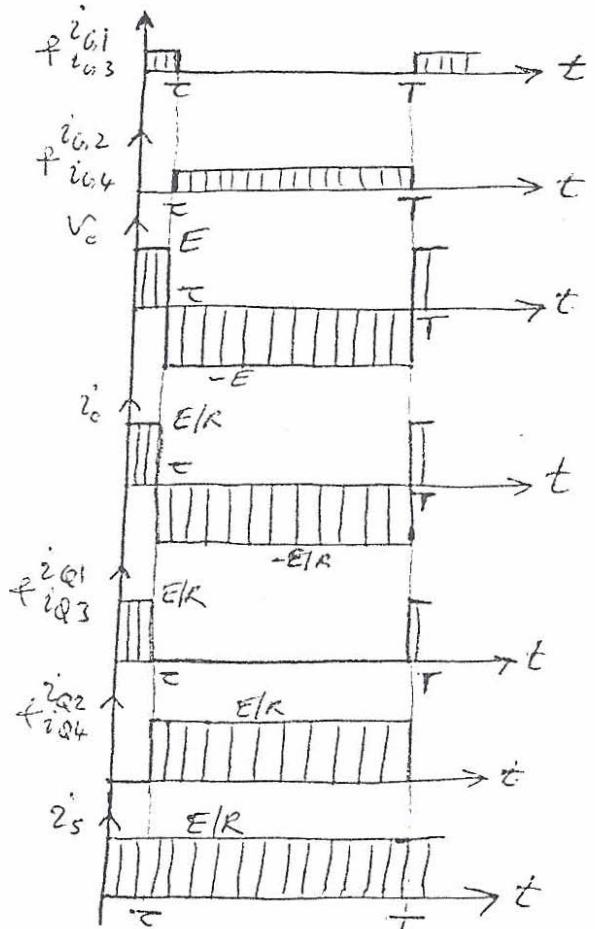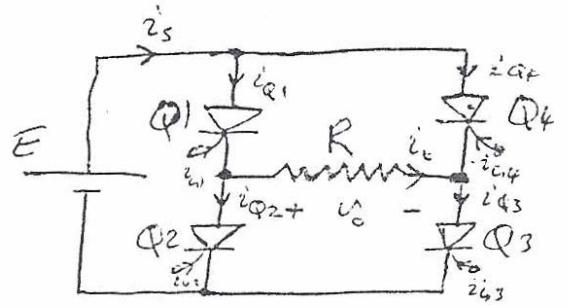
\therefore The distortion factor is 84.23%.



82

4-17-b Single pulse width-modulated inverter:

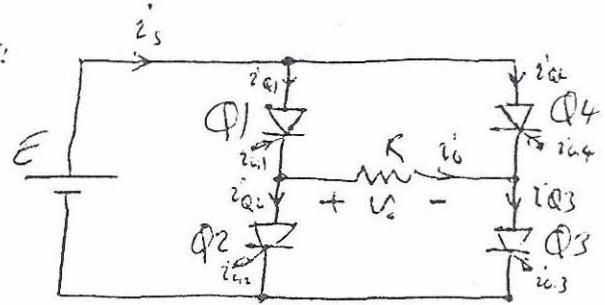The circuit is as shown with no diodes as before. The gating needs not to be as complex as for RL load, but rather simpler as shown.



The output fundamental is given by:

$$V_o(t)_{\text{fundamental}} = A \sin\left(\frac{2\pi t}{T}\right)$$


$$\text{where } A = \frac{4E}{\pi} \sin\left(\frac{\pi C}{2T}\right)$$

$$\therefore V_o(t)_{\text{fundamental rms}} = \frac{2\sqrt{2}E}{\pi} \sin\left(\frac{\pi C}{2T}\right)$$

$$\therefore \frac{2\sqrt{2} \times 300}{\pi} \sin\left(\frac{\pi C}{2T}\right) = 110$$

$$\therefore \pi CT = 0.41946 \text{ OR } 2.72214$$
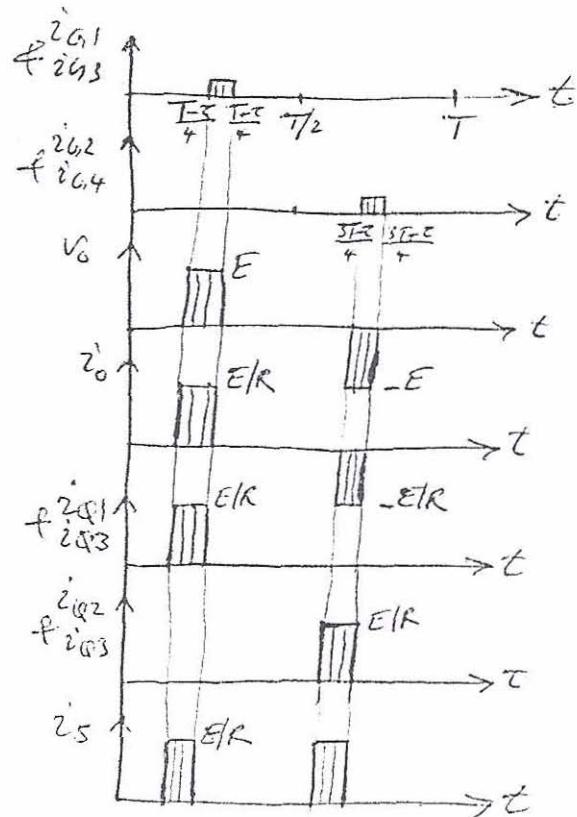
$$\therefore \frac{C}{T} (\leq 1) = 0.26703, \text{ the other answer } = 1.73297 > 1 \text{ is rejected since } \frac{C}{T} \in [0, 1].$$



$$\# \therefore \frac{C}{T} = 0.26703 \quad (\text{i.e. } 1.3352T \text{ duration at each half cycle symmetrically}).$$

$$\therefore V_o(t)_{\text{rms}}^2 = (E^2 \tau/2 + E^2 \tau/2)/T = \left(\frac{E^2 C}{T}\right) \quad \therefore V_o(t)_{\text{rms}} = E \sqrt{\frac{C}{T}} = 300 \sqrt{0.26703} = 155.026$$

$$\# \therefore M_r = \frac{V_o(t)_{\text{harmonics rms}}}{V_o(t)_{\text{rms}}} = \sqrt{1 - \left(\frac{V_o(t)_{\text{fundamental rms}}}{V_o(t)_{\text{rms}}}\right)^2} = \sqrt{1 - \left(\frac{110}{155.026}\right)^2} = 0.70465 \approx 70.5\%$$

\therefore The distortion factor is 70.5%. (less distorted than part (a)).

$\#$ Since resistive load; then waveform of i_o is same as that of V_o .

$$\therefore M_I = M_r = 70.5\%.$$

4-17c-I 3φ Invert. with 180° scheme:

The circuit is as shown with no diodes as before. Waveforms are also as shown, where:

$$V_N \text{ (by symmetry)} = \frac{1}{3}(V_A + V_B + V_C)$$

$$\therefore i_s = i_{Q1} + i_{Q3} + i_{Q5}$$

The fundamental phase voltage, $V_{AN, \text{fundamental}}(t)$, is given by:

$$V_{AN, \text{fundamental}}(t) = a \sin\left(\frac{2\pi t}{T}\right) + b \cos\left(\frac{2\pi t}{T}\right)$$

$$\text{when: } a = \frac{2}{T} \int_0^T V_{AN}(t) \sin\left(\frac{2\pi t}{T}\right) dt$$

$$= \frac{2}{T} \times 2 \int_0^{T/2} V_{AN}(t) \cdot \sin\left(\frac{2\pi t}{T}\right) dt =$$

$$\frac{4}{T} \times 2 \int_0^{T/4} V_{AN}(t) \sin\left(\frac{2\pi t}{T}\right) dt =$$

$$= \frac{8}{T} \left[\int_0^{T/6} V_{AN}(t) \sin\left(\frac{2\pi t}{T}\right) dt + \int_{T/6}^{T/4} V_{AN}(t) \sin\left(\frac{2\pi t}{T}\right) dt \right] =$$

$$= \frac{8}{T} \left[\int_0^{T/6} \sin\left(\frac{2\pi t}{T}\right) dt + \int_{T/6}^{T/4} \frac{2E}{3} \sin\left(\frac{2\pi t}{T}\right) dt \right] =$$

$$= \frac{8E}{3T} \left[-\cos\left(\frac{2\pi t}{T}\right) \Big|_0^{T/6} - 2\cos\left(\frac{2\pi t}{T}\right) \Big|_{T/6}^{T/4} \right] =$$

$$= \frac{4E}{3\pi} \left[1 - \cos\left(\frac{\pi}{3}\right) + 2 \cos\left(\frac{\pi}{2}\right) \right]$$

$$= \frac{4E}{3\pi} \left(1 + \cos\frac{\pi}{3} \right) = \frac{4E}{3\pi} \left(1 + \frac{1}{2} \right) = \frac{2E}{\pi}$$

$$\therefore b = (\text{by symmetry}) \quad 0$$

$$\therefore V_{AN, \text{fundamental}}(t) = \frac{2E}{\pi} \sin\left(\frac{2\pi t}{T}\right)$$

Other phases fundamentals are same but


$$\text{with } \pm 120^\circ \text{ shifts if } V_{phase} = \frac{\sqrt{2}E}{\sqrt{3}} = 135.047 \text{ V}$$

$$\# \therefore \% \text{ distortion} = + 22.77 \%$$


$$\therefore V_{phase, rms} = \sqrt{\left(\frac{E}{3}\right)^2 + \left(\frac{2E}{\pi}\right)^2 + \frac{2}{3} \left(\frac{2E}{\pi}\right)^2} = \frac{E}{3} \sqrt{\frac{2}{3} + \frac{4}{3}} = \frac{\sqrt{2}E}{3}$$

$$\# \therefore M_r (\text{of phase voltage}) = \sqrt{1 - \left(\frac{E}{\sqrt{2}E/3}\right)^2} = 0.2968 = 29.68\%$$

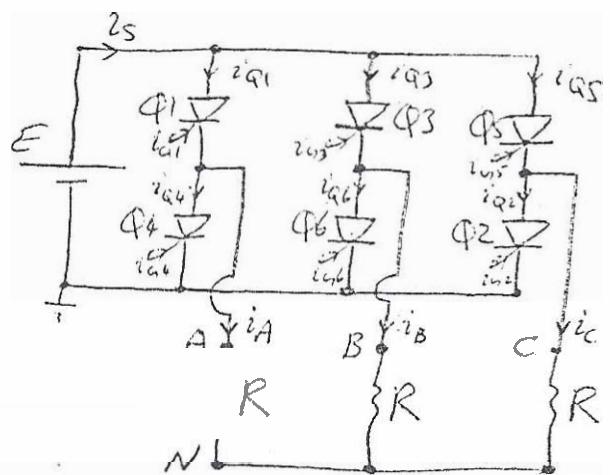\therefore The phase voltage distortion factor is about 30%. (less distorted than both part ④ + part ⑤).



$$E = 300 \text{ V}$$

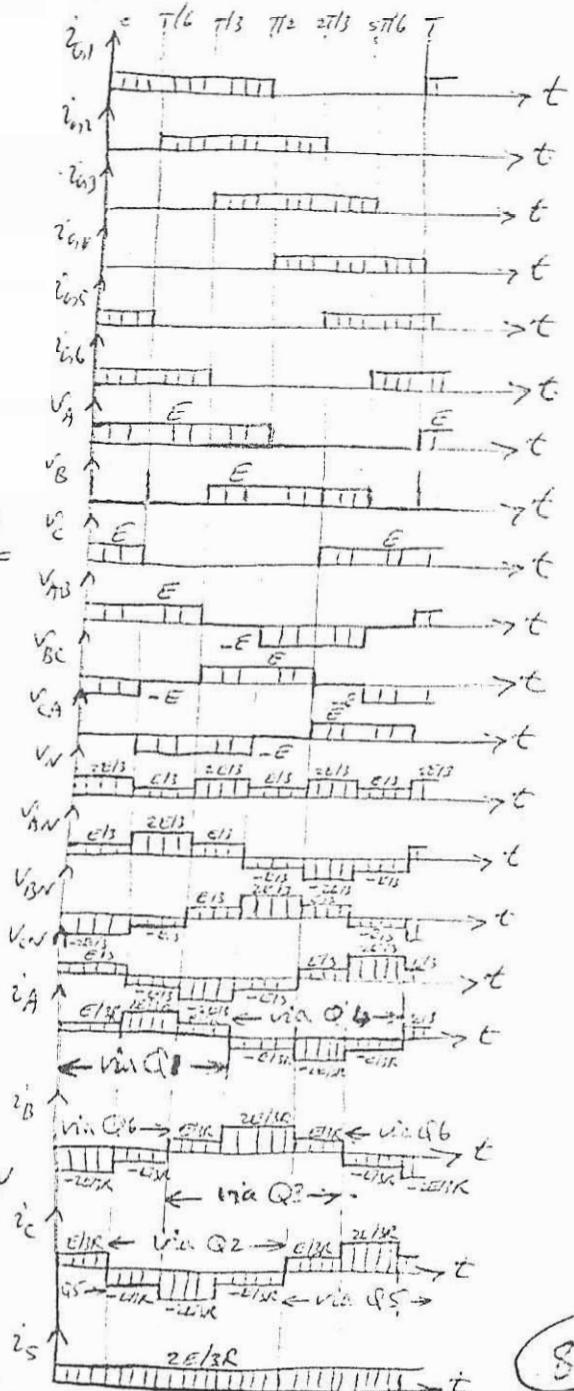

(S4)

4-17-C-II 3φ-Inverter with 120° scheme:

The circuit is as in part (I) but with waveforms as shown here.

The voltage during the indeterminate interval of one terminal is obtained by the average of the other two terminal voltages due to the resistive symmetry of the star load. The voltage is $E/2$.

$$\text{Again, } V_N = (\text{by symmetry}) \frac{1}{3} (V_A + V_B + V_C) \\ = E/2 \text{ all times.}$$

$\nabla i_s = i_{Q1} + i_{Q3} + i_{Q5} = \frac{E}{2R} \text{ all times}$

The fundamental phase voltage is:

$$V_{B,\text{fundamental}}(t) = a \sin\left(\frac{2\pi t}{T}\right) + b \cos\left(\frac{2\pi t}{T}\right)$$

$a = 0$ by symmetry.

$b = \frac{2}{T} \int_0^T V_{B,N}(t) \cos\left(\frac{2\pi t}{T}\right) dt =$

$$= \frac{4\sqrt{2}}{T} \int_0^{T/4} V_{B,N}(t) \cos\left(\frac{2\pi t}{T}\right) dt =$$

$$= \frac{8}{T} \int_0^{T/6} \left(-\frac{E}{2}\right) \cos\left(\frac{2\pi t}{T}\right) dt =$$

$$= -\frac{4E}{T} \left[\frac{\sin(2\pi t/T)}{2\pi/T} \right]_0^{T/6} =$$

$$= -\frac{2E}{\pi} \cdot \left(\sin\left(\frac{\pi}{3}\right) - 0 \right) = -\frac{E\sqrt{3}}{\pi}$$

$$\therefore V_{B,\text{fundamental}}(t) = -\frac{\sqrt{3}}{\pi} E \cdot \cos\left(\frac{2\pi t}{T}\right) \quad \nabla \text{ other phases fundamentals are}$$



same but with shifts of $\pm 120^\circ$. Hence, $V_{\text{phase fundamental rms}} = \sqrt{\frac{3}{2}} \cdot \frac{E}{\pi} = 116.95$

$\nabla \therefore \% e \text{ in achievement} = +6.322\% \text{ (better than I).}$

$\nabla V_{\text{phase rms}} = \sqrt{\left(\frac{E}{2}\right)^2 \times \frac{4}{6}} = \frac{E}{\sqrt{6}}$

$\nabla \therefore K_v \text{ (of phase voltage)} = \sqrt{1 - \left(\frac{\frac{E}{\sqrt{6}}}{\frac{E}{\sqrt{2}}}\right)^2} = \sqrt{1 - \left(\frac{3}{\pi}\right)^2} = .2968 = 29.68\%$

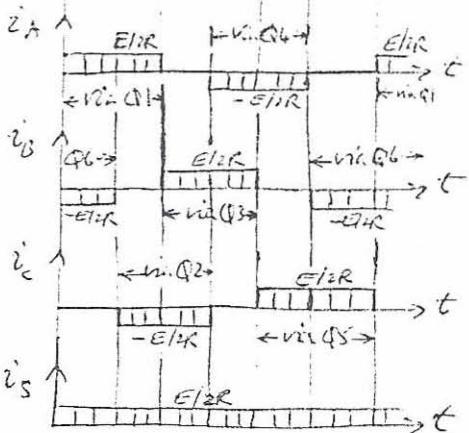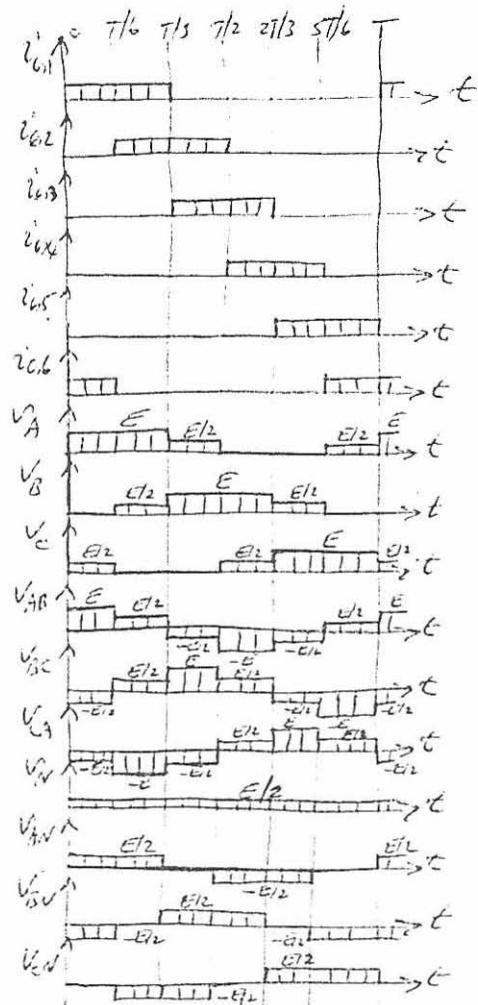\therefore The phase voltage distortion factor is about 30% (same as I).



(Note you can also calculate $V_{\text{rms, fundamental}}$ using shifting of formula

$a_1 = \frac{4E}{\pi} \sin\left(\frac{\pi t}{T}\right)$ of SPWM, by shifting to the right, through


$\frac{T}{12}$, $v_{AN}(t)$ into the waveform shown in the figure as v'_{AN} .

\therefore SPWM formula applies with $E = 150$, $T = \frac{2I}{3}$:

$$\therefore a_1|_{v'_{AN}} = \frac{600}{\pi} \sin\left(\frac{\pi t}{\frac{2I}{3}}\right) = \frac{300\sqrt{3}}{\pi} \text{ Volts.}$$

\therefore Since shifting does not change peak.

$$\therefore a_1|_{v'_{AN}} = \hat{V}_{AN \text{ fundamental}} = \frac{300\sqrt{3}}{\pi} \text{ Volts} = V_{AN \text{ fundamental rms}}$$

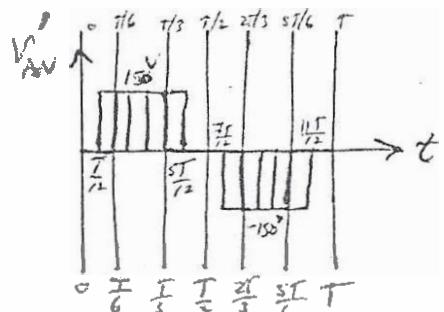

$$\therefore V_{\text{rms, fundamental}} = \underline{a_1|_{v'_{AN}} \div \sqrt{2}} = \frac{300\sqrt{3}}{\pi} \div \sqrt{2} = 116.95 \text{ Volts} \quad \therefore \text{OK}.$$

$$4-18 \quad I = 50 \text{ A}_p$$


$$R = 10 \Omega$$

$$C = 400 \mu\text{F}$$

$$f = 200 \text{ Hz}$$

$$\therefore T = 5 \text{ msec}$$
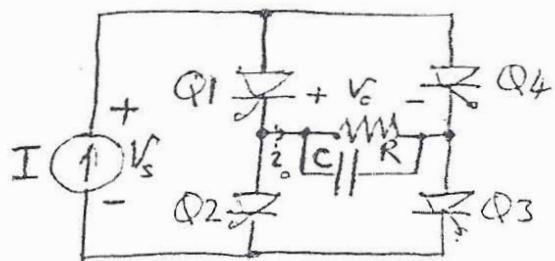
$$\therefore \omega = 2\pi f = 400 \text{ rad/sec}$$



\therefore Circuit is as shown

$$\text{Since } RC = 4 \text{ ms} > \frac{T}{2} = 2.5 \text{ ms}$$

\therefore Exponential variations could be assumed linear and hence waveforms are as shown, where:

$$V(t) = -Ee^{-\frac{t}{RC}} + IR(1 - e^{-\frac{t}{RC}}), t \in (0, T/2)$$

$$\therefore v(t) = -v(t - T/2)$$

$$\therefore E = v(T/2) = -Ee^{-T/2RC} + IR(1 - e^{-T/2RC})$$

$$\therefore E = IR \cdot \frac{1 - e^{-T/2RC}}{1 + e^{-T/2RC}} = 151.35 \text{ V}$$

$$\therefore \theta_0 = 2\pi f \cdot RC \cdot \ln\left(\frac{E+IR}{IR}\right) = 0.4231 \text{ rad}$$

$$\therefore P_R = P_K \approx \frac{E^2}{3R} = 763.61 \text{ Watts}$$


(Note: Exact value of R is:

$$P_K = \frac{1}{T} \int_0^T \frac{V^2(t)}{R} dt = \frac{1}{\pi_0} \int_0^{\pi_0} \frac{V^2(\omega t)}{R} d\omega =$$

$$= \frac{1}{\pi R} \cdot \left[I^2 R^2 \theta + (E+IR) e^{-\frac{2\pi}{\omega RC}} + \right.$$

$$\left. - \frac{2IR(E+IR)}{-i/\omega CR} \cdot e^{-\frac{\theta}{\omega CR}} \right]_{0}^{\pi_0}$$
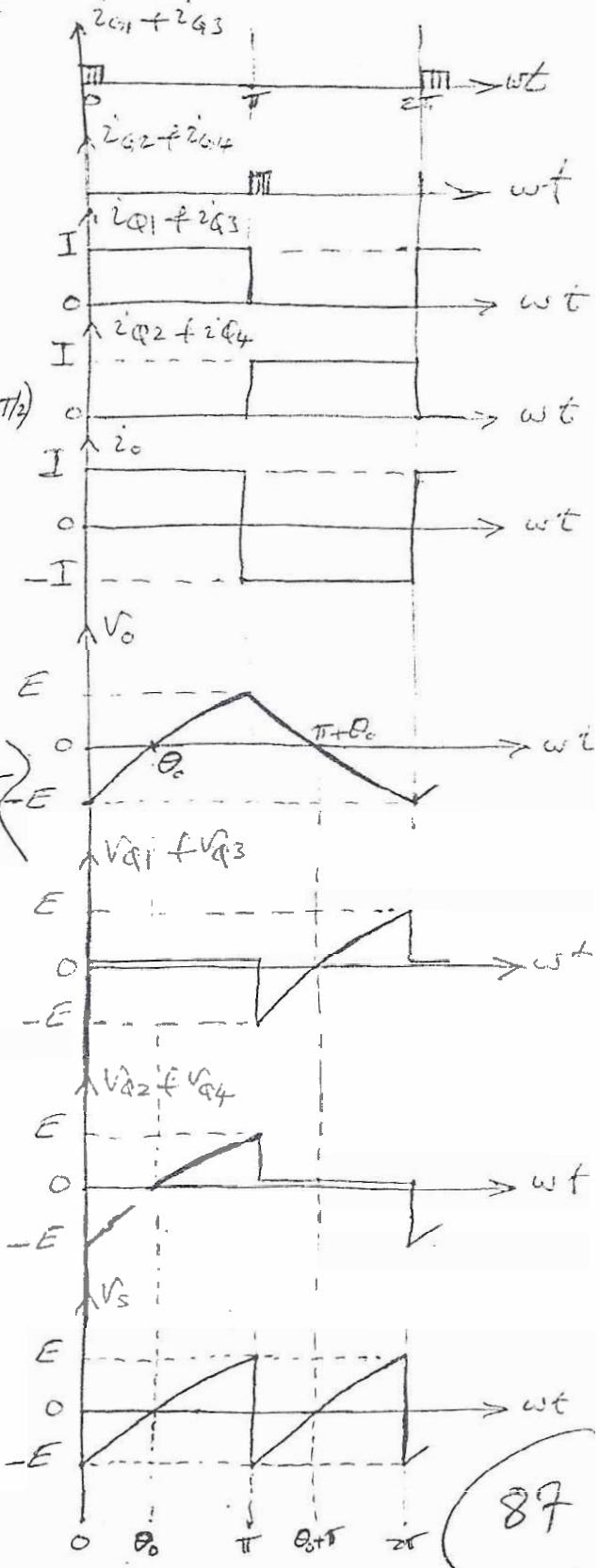
$$= 783.22 \text{ Watts if } \theta = 2.5 \text{ rad}$$



87

$$\text{f } P_I = P_o \approx 763.61 \text{ Watts}$$

$$\therefore V_{S_{av}} = \frac{P_I}{I} \approx \frac{763.61}{50} = 15.272 \text{ Volts}$$

(Note: The exact value of $V_{S_{av}}$ can be obtained in two ways:

$$\text{i) } V_{S_{av}} = \frac{P_I}{I} = \frac{P_E}{I} = \frac{783.22}{50} = 15.664 \text{ Volts}$$

$$\text{ii) } V_{S_{av}} = \frac{1}{\pi} \int_0^{\pi} v_s(\omega t) dt = \frac{1}{\pi} \left[IR\theta + (IR+E)e^{-\theta/\omega CR} \right]_0^{\pi} = 15.664V$$

both ways give an error of 2.5% due to non-linearity)

$\text{f As for } V_{o_{rms}}, \text{ this could be found from: } V_o(t) \approx a \cos \omega t,$

$$\text{where: } a = \frac{2}{2\pi} \int_0^{2\pi} V_o(\omega t) \cos \omega t dt = \frac{2}{\pi} \int_0^{\pi} (-E + \frac{2E}{\pi} \cdot \theta) \cos \theta d\theta = \\ = \frac{2E}{\pi} \left[-\sin \theta + \frac{2}{\pi} (\theta \sin \theta + \cos \theta) \right]_0^{\pi} = \frac{2E}{\pi} \cdot \frac{2}{\pi} (-1-1) = \frac{-8E}{\pi^2}$$

$$\therefore V_{o_{rms}} \approx \frac{a}{\sqrt{2}} = 4\sqrt{2}E/\pi^2 = 86.75 \text{ Volts} \quad (\text{exact} = \frac{2\sqrt{2}IK/\pi}{\sqrt{1+(\omega CR)^2}} = \frac{87.83}{\sqrt{1+(0.02)^2}} = 87.83 \text{ Volts}, \epsilon = 1.2\%)$$

$\text{f } V_{o_{av}} = 0 \text{ since } V_o(t) \text{ is symmetrical.}$

$$\text{f } V_{o_{rms}} = \sqrt{RP_o} \approx \sqrt{7636.1} = 87.38 \text{ Volts} \quad (\text{exact} = 88.50, \epsilon = 1.3\%)$$

$$\text{f } C_v = \frac{V_{o_{rms}}}{V_{o_{av}}} = \sqrt{1 - \left(\frac{V_{o_{rms}}}{V_{o_{av}}} \right)^2} \approx 0.120 = 12.0\%$$

$$\text{f } t_g \text{ of thyristor must be } < \frac{\theta_c}{\omega} = \frac{4.231\pi}{400\pi} = 1.058 \text{ msec}$$

$$\text{f } V_{QFB} = V_{QRB} = E = 151.35 \text{ Volts. This is min. required rating}$$

$$\text{f } \frac{dV_Q}{dt} = \frac{dV_o}{dt} \left(\frac{\theta_c}{\omega} \right) = (E + IR) \cdot e^{-\theta_c/\omega CR} = 125000V/s = 0.125 \frac{V}{\mu s}$$

$$\therefore \frac{dV}{dt} \text{ rating of thyristor must be } > 0.125V/\mu s \quad (\approx \frac{2E}{T/2} = \frac{4E}{T} = 0.121V/\mu s)$$

$$4-19 \quad f = 50 \text{ Hz}$$

$$\therefore T = 20 \text{ msec}$$

Waveforms are as shown, assuming negligible lead inductances and commutation times.

i_c is seen to be a square wave with amplitude of 100 Amp.

$$\therefore V_o(t) = 500 + A e^{-t/5ms}, V, t \in [0, 10] \text{ ms.}$$

Due to symmetry:

$$\therefore V_o(0) = -V_o(T/2)$$

$$\therefore 500 + A = -[500 + A e^{-100/5ms}]$$

$$\therefore 1000 = -A(1 + e^{-2})$$

$$\therefore A = -880.80 \text{ Volts}$$

$$\therefore V_o(t) = 500 - 880.80 e^{-200t}, V, t \in [0, 10] \text{ ms.}$$

$$\therefore V_o(0) = -380.80 \text{ Volts}$$

$$V_o = 0 \text{ at } t = 2.83 \text{ ms}$$

$$i_R^{(0)} = \frac{V_o}{R} = 100 - 176.16 e^{-200t}, A, t \in [0, 10] \text{ ms.}$$

$$\therefore i_R(0) = -176.16 \text{ Amp.}$$

$$\therefore i_c(t) = 100 - i_R(t) = 176.16 e^{-200t}, A, t \in [0, 10] \text{ ms.}$$

$$\therefore i_c(0) = 176.16 A, i_c(2.83) = 100 A, i_c(10) = 23.84 A.$$

Note that V_s is running at double frequency, i.e. 100 Hz.



From waveforms, the time available for thyristors recovery is 2.83 ms.

To find α of load:

$$\therefore i_{\text{load}} = I = 100 \text{ Amp}$$

$$\therefore i_{\text{load, fundamental}} = \frac{2}{20\sqrt{2}} \int_0^{\infty} i_o \sin \omega t dt = \frac{4}{20\sqrt{2}} \int_0^{\infty} 100 \sin \frac{\pi}{T} t dt = \frac{400}{20\sqrt{2}} \left[-\cos \left(\frac{\pi}{T} t \right) \right]_0^{\infty} / \left(\frac{\pi}{T} \right) = \frac{400}{20\sqrt{2}} \cdot \frac{2\pi}{\pi} \cdot \left[-\cos \pi + \cos 0 \right] = \frac{400}{\pi \sqrt{2}}$$
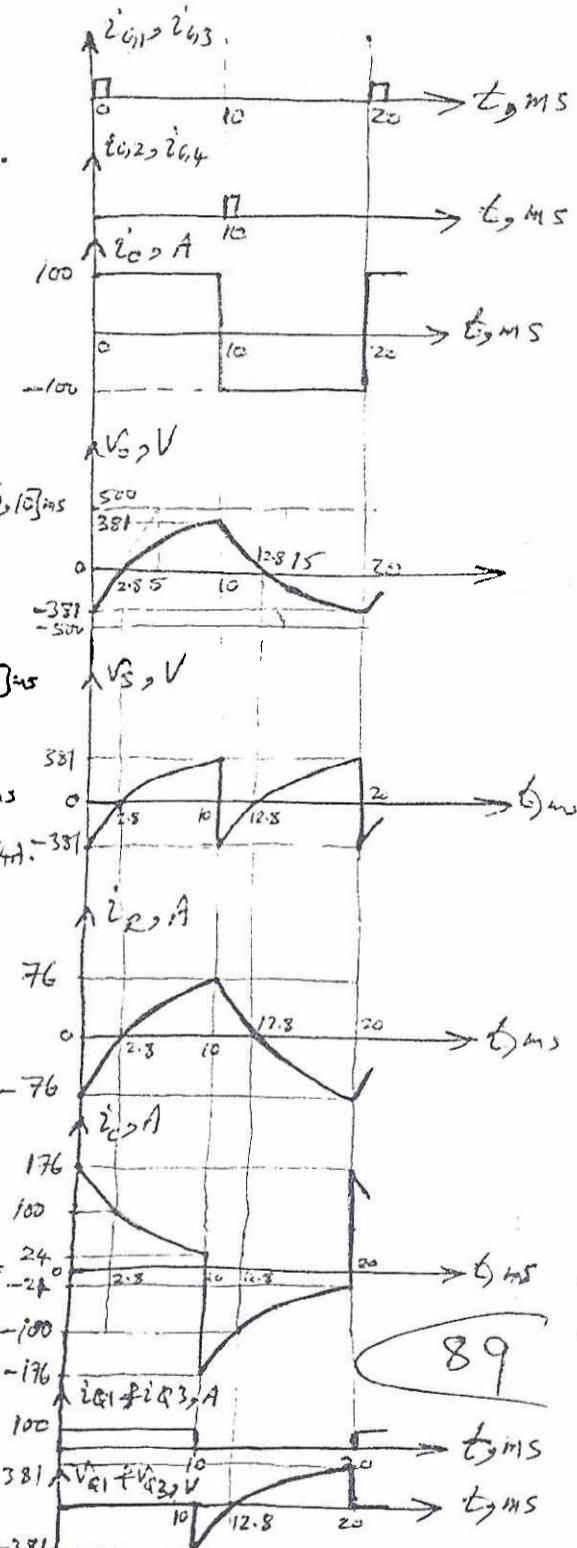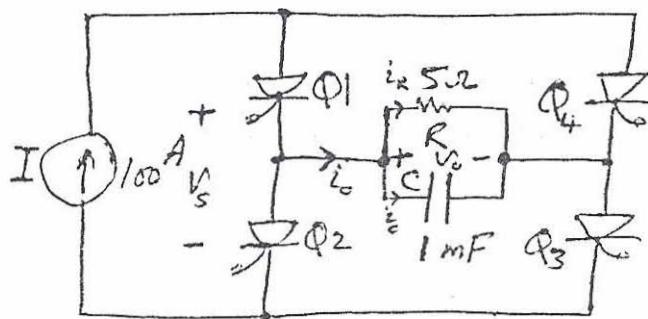
$$\therefore \left(\frac{i_o}{I} \right)^2 = \frac{i_{\text{load, fundamental}}^2}{I^2} = \sqrt{1 - \left(\frac{i_{\text{load, fundamental}}}{I} \right)^2} = \sqrt{1 - \left(\frac{4}{\pi \sqrt{2}} \right)^2} = \sqrt{1 - \frac{16}{\pi^2}} = 1.4352 = 43.52\%$$



5-1-a $V \in [0, \sqrt{2}E]$

∴ Current mode is always discontinuous, and the control range of α is given by:

$$V_Q(\alpha) = \sqrt{2}E \sin \alpha - V \geq 0$$

$$\therefore \alpha \in \left[\sin^{-1}\left(\frac{V}{\sqrt{2}E}\right), \pi - \sin^{-1}\left(\frac{V}{\sqrt{2}E}\right) \right]$$

If α is outside the above range, the thyristor will not fire since V_Q is negative.

The output current is of pulsating nature and is given by:

$$i_o(wt) = \frac{\sqrt{2}E}{Z} \sin(wt - \phi) - \frac{V}{R} + A e^{-(wt-\alpha)/taf}, \quad t \in [\alpha, \beta]$$

with $Z = \sqrt{R^2 + \omega^2 L^2}$ $\Rightarrow \tan \phi = \omega L / R$


$$\therefore i_o(\alpha) = 0 = \frac{\sqrt{2}E}{Z} \sin(\alpha - \phi) - \frac{V}{R} + A \quad \therefore A = \frac{V}{R} - \frac{\sqrt{2}E}{Z} \sin(\alpha - \phi)$$

$\therefore i_o(wt) = \frac{\sqrt{2}E}{Z} \left\{ \sin(wt - \phi) - \sin(\alpha - \phi) \cdot e^{-(wt-\alpha)/taf} \right\} + \frac{V}{R} \left\{ e^{-(wt-\alpha)/taf} - 1 \right\} \quad (1)$


$\therefore i_o(\beta) = 0 \quad \therefore \beta$ could be obtained from the following expression:

$\frac{\sqrt{2}E}{Z} \left\{ \sin(\beta - \phi) - \sin(\alpha - \phi) e^{-(\beta - \alpha)/taf} \right\} = \frac{V}{R} \cdot \left\{ 1 - e^{-(\beta - \alpha)/taf} \right\}. \quad (2)$

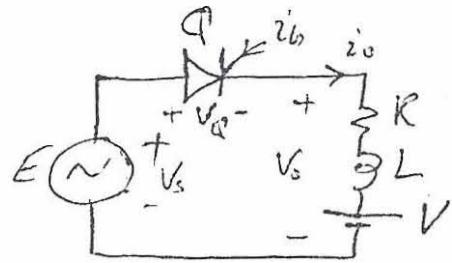f. $v_o(wt) = \begin{cases} \sqrt{2}E \sin wt & w t \in [\alpha, \beta] \\ V & \text{otherwise} \end{cases}$ during one cycle $[\alpha, 2\pi] \quad (3)(90)$



HWCR for R-L-V load

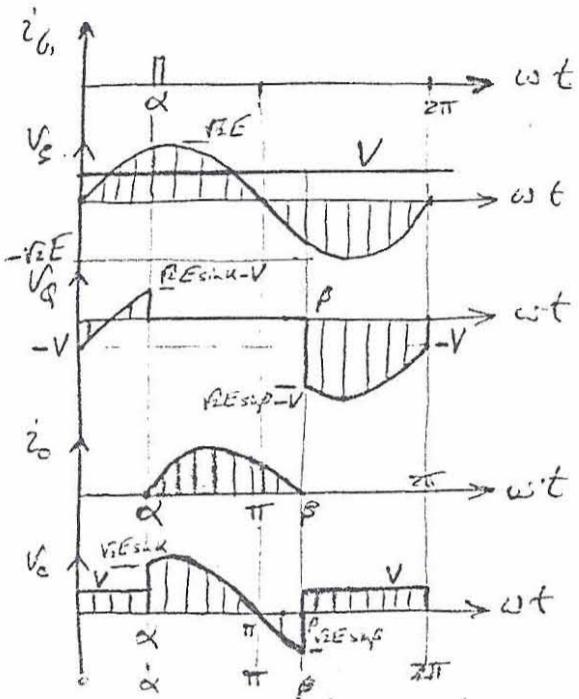

$$\therefore V_{\text{av}} = \frac{1}{2\pi} \cdot \int_0^{2\pi} v_0(\omega t) dt = \frac{1}{2\pi} \left[V(2\pi - (\beta - \alpha)) + \int_{\alpha}^{\beta} v_0 \sin \omega t dt \right] =$$

$$= \frac{1}{2\pi} \left[V(2\pi + \alpha - \beta) - \frac{V_2 E}{\omega} \cos \omega t \Big|_{\alpha}^{\beta} \right] = \frac{1}{2\pi} \left[V(2\pi + \alpha - \beta) + V_2 E (\cos \alpha - \cos \beta) \right]$$

$$\# \therefore V_{\text{av}} = V \cdot \left(1 - \frac{\beta - \alpha}{2\pi} \right) + \frac{E}{\pi R^2} (\cos \alpha - \cos \beta). \quad (4)$$

$$\# \neq i_{\text{av}} = \frac{V_{\text{av}} - V}{R} = \left[\frac{E}{\pi R^2} (\cos \alpha - \cos \beta) - V \left(\frac{\beta - \alpha}{2\pi} \right) \right] / R \quad (5)$$

$$\text{As for } i_{\text{rms}}: \quad 2\pi i_{\text{rms}}^2 = \int_0^{2\pi} i_e^2(\omega) dt$$

$$\therefore 2\pi i_{\text{rms}}^2 = \int_{\alpha}^{\beta} \left[\frac{2E^2}{Z^2} \left\{ \sin^2(\omega t - \phi) - 2 \sin(\alpha - \phi) \sin(\omega t - \phi) \cdot e^{-\omega(t-\alpha)/L_f} + \right. \right.$$

$$+ \sin^2(\alpha - \phi) \cdot e^{-2(\omega t - \alpha)/L_f} \left. \right\} + \frac{V^2}{R^2} \left\{ e^{-2(\omega t - \alpha)/L_f} - 2e^{-\omega(t-\alpha)/L_f} + 1 \right\} +$$

$$+ \frac{V_2 E V}{Z R} \left\{ \sin(\omega t - \phi) e^{-\omega(t-\alpha)/L_f} - \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{-2(\omega t - \alpha)/L_f} + \sin(\alpha - \phi) e^{-\omega(t-\alpha)/L_f} \right\} dt$$

$$= \frac{2E^2}{Z^2} \left\{ \frac{\omega t}{2} - \frac{\sin 2(\omega t - \phi)}{4} + 2 \sin(\alpha - \phi) \cdot e^{-\omega(t-\alpha)/L_f} \frac{-\omega(t-\alpha)/L_f + \cot \phi \cdot \sin(\omega t - \phi)}{1 + \cot^2 \phi} \right. \\ + \sin^2(\alpha - \phi) \cdot \frac{e^{-2(\omega t - \alpha)/L_f}}{-2 \cot \phi} \Big|_{\alpha}^{\beta} + \frac{V^2}{R^2} \left\{ \frac{e^{-2(\omega t - \alpha)/L_f}}{-2 \omega t \phi} - 2 \cdot \frac{e^{-\omega(t-\alpha)/L_f}}{-\omega t \phi} + \omega t \right\}_{\alpha}^{\beta}$$

$$+ \frac{V_2 E V}{Z R} \left\{ -e^{-\omega(t-\alpha)/L_f} \frac{-\cos(\omega t - \phi) + \cot \phi \sin(\omega t - \phi)}{1 + \cot^2 \phi} + \cos(\omega t - \phi) \cdot \frac{\sin(\alpha - \phi) \cdot e^{-\omega(t-\alpha)/L_f}}{-2 \omega t \phi} + \frac{\sin(\alpha - \phi) \cdot e^{-\omega(t-\alpha)/L_f}}{-\omega t \phi} \right\}_{\alpha}^{\beta}$$

$$= \frac{2E^2}{Z^2} \left\{ \frac{\beta - \alpha}{2} - \frac{\sin 2(\beta - \phi) - \sin 2(\alpha - \phi)}{4} + 2 \sin^2 \phi \sin(\alpha - \phi) \left[e^{-\omega(\beta - \alpha)/L_f} \frac{-\cos(\beta - \phi) + \cot \phi \sin(\beta - \phi) - \cos(\alpha - \phi)}{-\cot \phi \sin(\alpha - \phi)} \right] \right. \\ + \sin^2(\alpha - \phi) \tan \phi \cdot \frac{1 - e^{-\omega(\beta - \alpha)/L_f}}{2} \Big| + \frac{V^2}{R^2} \left\{ \tan \phi \cdot \left(\frac{1 - e^{-\omega(\beta - \alpha)/L_f}}{2} \right) + 2 \tan \phi \left(e^{-\omega(\beta - \alpha)/L_f} - 1 \right) \right. \\ + \left. \beta - \alpha \right\} + \frac{V_2 E V}{Z R} \left\{ \sin^2 \phi \left[\cos(\alpha - \phi) + \cot \phi \sin(\alpha - \phi) - e^{-\omega(\beta - \alpha)/L_f} \left(\cos(\beta - \phi) + \cot \phi \sin(\beta - \phi) \right) \right] \right. \\ + \left. \cos(\beta - \phi) - \cos(\alpha - \phi) + \tan \phi \cdot \left(\frac{e^{-\omega(\beta - \alpha)/L_f}}{2} - 1 \right) \cdot \sin(\alpha - \phi) + \tan \phi \sin(\alpha - \phi) \left(1 - e^{-\omega(\beta - \alpha)/L_f} \right) \right\} -$$

$$= \frac{2E^2}{Z^2} \left\{ \frac{\beta - \alpha}{2} + \frac{\sin 2(\beta - \phi) - \sin 2(\alpha - \phi)}{4} + 2 \sin^2 \phi \sin(\alpha - \phi) \left[e^{-\omega(\beta - \alpha)/L_f} \sin \beta - \sin \alpha \right] \right. \\ + \left. + 5 \sin^2(\alpha - \phi) \tan \phi \cdot \left(1 - e^{-\omega(\beta - \alpha)/L_f} \right) \right\} + \frac{V^2}{R^2} \left\{ \beta - \alpha + 5 \tan \phi \left(4e^{-\omega(\beta - \alpha)/L_f} - 3 - e^{-\omega(\beta - \alpha)/L_f} \right) \right\} +$$

$$+ \frac{\sqrt{2}EV}{ZR} \cdot \left\{ \sin\phi \left(\sin\alpha - e^{-j(\beta-\alpha)/tan\phi} \right) + \cos(\beta-\phi) - \cos(\alpha-\phi) + \right. \\ \left. + 0.5 \tan\phi \sin(\alpha-\phi) \cdot \left(e^{-j(\beta-\alpha)/tan\phi} + 1 - 2e^{-j(\beta-\alpha)/tan\phi} \right) \right\} \quad (6)$$

Hence:

$$\# i_{o_{rms}} = \sqrt{(RHS \text{ of } (6)) / 2\pi} \quad (7)$$

As for $V_{o_{rms}}$, it is much simpler:

$$\therefore V_{o_{rms}}^2 / 2\pi = \int_0^{2\pi} V_o^2(\omega t) dt = V^2(2\pi + \alpha - \beta) + \int_0^P (V_2 \sin \omega t)^2 dt = \\ = V^2(2\pi + \alpha - \beta) + 2E^2 \left(\frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right)_0^P = \\ = V^2(2\pi + \alpha - \beta) + 2E^2 \left(\frac{\beta - \alpha}{2} - \frac{\sin 2\beta - \sin 2\alpha}{4} \right)$$

$$\# \therefore V_{o_{rms}} = \sqrt{V^2 \left(1 - \frac{\beta - \alpha}{2\pi} \right) + E^2 \left(\frac{\beta - \alpha}{2\pi} - \frac{\sin 2\beta - \sin 2\alpha}{4\pi} \right)} \quad (8)$$

$$\# \neq K_i = \frac{i_{o_{ac}}}{i_{o_{av}}} = \sqrt{\frac{i_{o_{rms}}^2 - i_{o_{av}}^2}{i_{o_{av}}^2}} = \sqrt{\left(\frac{i_{o_{rms}}}{i_{o_{av}}} \right)^2 - 1} \quad (9)$$

$$\# \neq K_o = \frac{V_{o_{ac}}}{V_{o_{av}}} = \sqrt{\left(\frac{V_{o_{rms}}}{V_{o_{av}}} \right)^2 - 1} \quad (10)$$

$$\# \neq P_{o_{av}} = R * i_{o_{rms}}^2 + V * i_{o_{av}} \quad (11)$$

5-1-b This case is easily obtained by letting $V=0$ in all the expressions of **5-1-a**.

\therefore Control range of α is between $[0, \pi]$

$$\# \neq i_o(\omega t) = \frac{\sqrt{2}E}{Z} \left\{ \sin(\omega t - \phi) - \sin(\alpha - \phi) \cdot e^{-j(\omega t - \alpha) / \tan\phi} \right\} \quad (1)$$

$$\# \neq \text{Condition for } \beta \text{ is: } \sin(\beta - \phi) = \sin(\alpha - \phi) \cdot e^{-j(\beta - \alpha) / \tan\phi} \quad (2)$$

$$\# \neq V_o(\omega t) = \sqrt{2}E \sin \omega t, \omega t \in [\alpha, \bar{\alpha}] \quad (\text{zero otherwise}) \quad (3)$$

$$\# \neq V_{o_{av}} = \frac{E}{\pi\sqrt{2}} \cdot (\cos \alpha - \cos \beta) \quad (4)$$

$$\# \neq i_{o_{av}} = \frac{E}{\pi\sqrt{2}R} \cdot (\cos \alpha - \cos \beta) \quad (5)$$

$$\# \neq i_{o_{rms}} = \frac{E}{\pi Z} \cdot \sqrt{\frac{\beta-\alpha}{2\pi} + \frac{\sin 2(\alpha-\beta) - \sin 2(\beta-\alpha)}{4\pi} + \frac{2}{\pi} \cdot \sin \phi \cdot \sin(\alpha-\beta) \cdot \left[e^{-\frac{(\beta-\alpha)\tan \phi}{2}} \sin \phi - \sin \alpha \right] + \frac{1}{2\pi} \cdot \sin^2(\alpha-\beta) \cdot \tan \phi \left(1 - e^{-\frac{2\beta \tan \phi}{\pi}} \right)}. \quad (6)$$



$$\# \neq V_{o_{rms}} = E \cdot \sqrt{\frac{\beta-\alpha}{2\pi} - \frac{\sin 2\beta - \sin 2\alpha}{4\pi}} \quad (7)$$

$$\# \neq k_i = \sqrt{\left(\frac{i_{o_{rms}}}{i_{o_{av}}}\right)^2 - 1} \quad (8)$$

$$\# \neq k_a = \sqrt{\left(\frac{V_{o_{rms}}}{V_{o_{av}}}\right)^2 - 1} \quad (9)$$

$$\# \neq P_{o_{av}} = R \cdot i_{o_{rms}}^2 \quad (10)$$

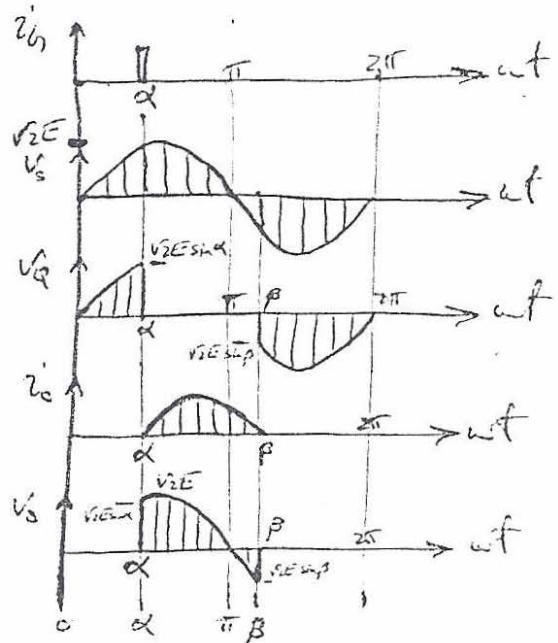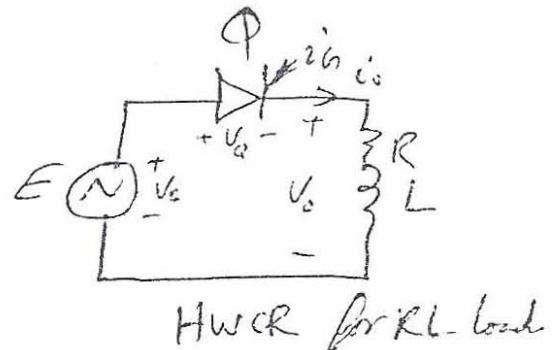The circuit & waveforms
are as shown here.



5-1-C This case is further obtained from

the expressions of 5-1-b by

Letting $L=0$; whereby, all load

voltages are proportional to load

currents, as follows:

$$\# \quad \beta = \pi \text{ always} \quad (1)$$

$$\# : V_o(\omega t) = R i_o(\omega t) = \sqrt{2} E \sin \omega t \quad (2)$$

$\omega t \in [\alpha, \pi]$

$$\# \quad V_{o_{av}} = R * i_{o_{av}} = \frac{E}{\pi\sqrt{2}} (1 + \cos \alpha) \quad (3)$$


$$\# \quad V_{o_{rms}} = R * i_{o_{rms}} = E * \sqrt{\frac{\pi - \alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}} \quad (4)$$

$$\# \quad K_i = K_v = \sqrt{\frac{(i_{o_{rms}})^2}{(i_{o_{av}})^2} - 1} \quad (5)$$


$$\# \quad P_{o_{av}} = R * i_{o_{av}}^2 = \frac{E^2}{R} \left(\frac{\pi - \alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi} \right) \quad (6)$$

The circuit & waveforms

are as shown.

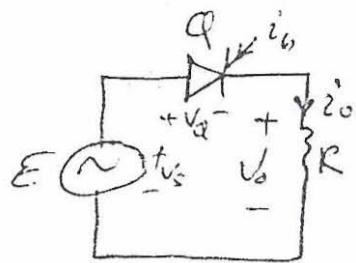

HWSCR for R load

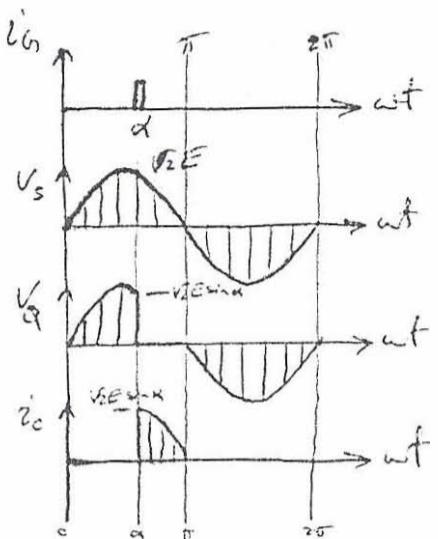

S-2-a

The HSCR when forced commutation is used will be modified by placing a free-wheeling diode across the load circuit as shown.

Again, for circuit to perform, then the range of V is:

$$V \in [0, \sqrt{2}E],$$

and the control range of α is:

$$\alpha \in \left[\sin^{-1}\left(\frac{V}{\sqrt{2}E}\right), \pi - \sin^{-1}\left(\frac{V}{\sqrt{2}E}\right) \right],$$

where \sin^{-1} is defined over first quadrant. Current Mode could be continuous, discontinuous or critical depending upon circuit parameters. Each mode will be considered separately.

S-2-a-I

First, the discontinuous mode, where waveforms are as shown. Here:

α is the firing angle,
 β is the commutation angle,
 γ is the extinction angle.



The control range of β is:

$\beta \in (\alpha, \pi]$, because after $wt = \pi$, v_s reverses and gets Q through D.

The value of I is given using Eq.1 of S-1-a by $\circlearrowright 95$

$$I = i_o(\beta) = \frac{\sqrt{2}E}{Z} \left\{ \sin(\beta - \phi) - \sin(\alpha - \phi) e^{(\alpha - \beta)/t_{0, \phi}} \right\} - \frac{V}{R} \left\{ 1 - e^{(\alpha - \beta)/t_{0, \phi}} \right\}, \quad (1)$$

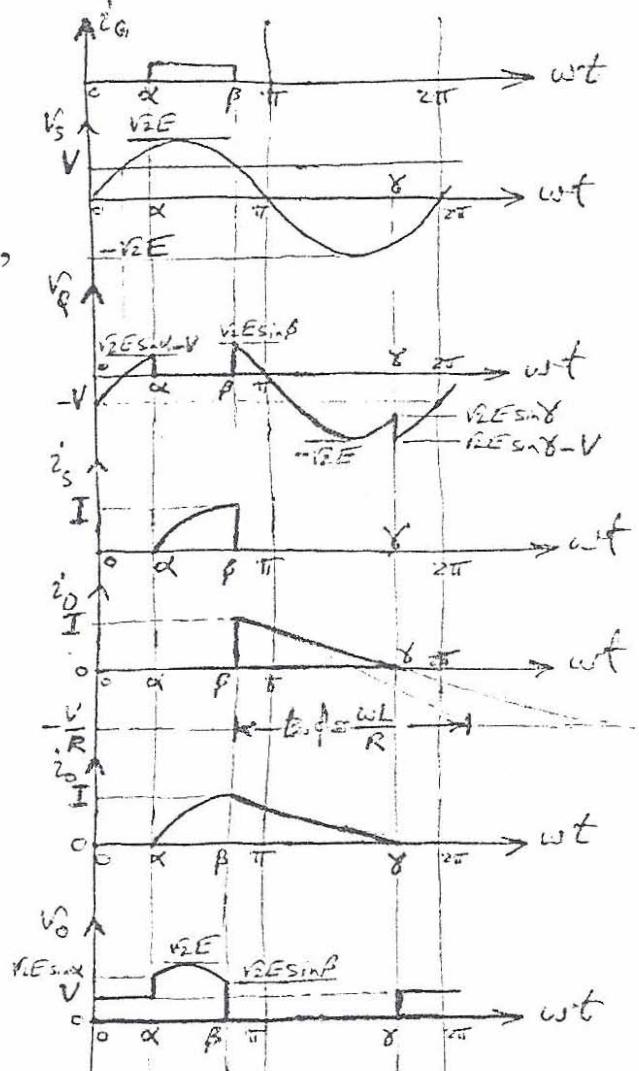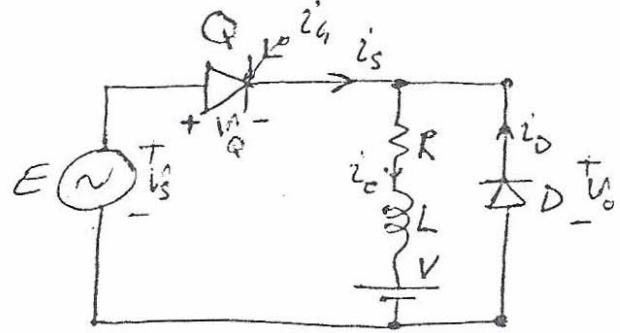where the above equation describes the current during $wt \in [\alpha, \beta]$.



For $\omega t \in [\beta, \gamma]$, $i_o(\omega t)$ is given by:

$$i_o(\omega t) = -\frac{V}{R} + \left(I + \frac{V}{R}\right) e^{-(\omega t - \beta) / \tan \phi} \quad (2)$$

Hence, $i_o(\gamma) = 0$ gives γ as:

$$\# \quad \gamma = \beta + \tan \phi \cdot \ln \left(1 + \frac{IR}{V}\right) \quad (3)$$

$i_o(\omega t)$ then keeps at zero till $2\pi + \alpha$ comes for a new cycle.

$$\# \quad i_o(\omega t) = \begin{cases} \text{as in Eq. 1 of } [S-1-a] & \text{for } \omega t \in [\alpha, \beta] \\ \text{as in Eq. 2 above} & \text{for } \omega t \in [\beta, \gamma] \\ \text{Zero} & \text{for } \omega t \in [\gamma, 2\pi + \alpha] \end{cases} \quad (4)$$

The output voltage, on the other hand, is given by:

$$\# \quad V_o(\omega t) = \begin{cases} \sqrt{2} E \sin \omega t & \text{for } \omega t \in (\alpha, \beta) \\ \text{Zero} & \text{for } \omega t \in (\beta, \gamma) \\ V & \text{for } \omega t \in (\gamma, 2\pi + \alpha) \end{cases} \quad (5)$$

Hence,

$$V_{o_{av}} = \frac{1}{2\pi} \left[\int_{\alpha}^{\beta} \sqrt{2} E \sin \omega t dt + 0 + \int_{\gamma}^{2\pi + \alpha} V dt \right] = \frac{1}{2\pi} \left[\sqrt{2} E \cos \omega t \Big|_{\alpha}^{\beta} + V \cdot \omega t \Big|_{\gamma}^{2\pi + \alpha} \right]$$

$$\# \quad \therefore V_{o_{av}} = \frac{1}{2\pi} \left[\sqrt{2} E (\cos \alpha - \cos \beta) + V \cdot (2\pi + \alpha - \gamma) \right] \quad (6)$$

$$\# \quad \therefore i_{car} = \frac{V_{o_{av}} - V}{R} = \frac{\sqrt{2} E (\cos \alpha - \cos \beta) - V (\gamma - \alpha)}{2\pi R} \quad (7)$$

$$\# \quad V_{o_{rms}}^2 = \frac{1}{2\pi} \left[\int_{\alpha}^{\beta} 2E^2 \sin^2 \omega t dt + 0 + \int_{\gamma}^{2\pi + \alpha} V^2 dt \right] = \frac{1}{2\pi} \left[E^2 \int_{\alpha}^{\beta} (1 - \cos 2\omega t) dt + V^2 \cdot \omega t \Big|_{\gamma}^{2\pi + \alpha} \right]$$

$$= \frac{1}{2\pi} \cdot \left[\frac{E^2}{2} \cdot (2\beta - 2\alpha - \sin 2\beta + \sin 2\alpha) + V^2 (2\pi + \alpha - \gamma) \right]$$

$$\# \quad \therefore V_{o_{rms}} = \sqrt{V^2 \left(1 - \frac{\gamma - \alpha}{2\pi}\right) + E^2 \left(\frac{\beta - \alpha}{2\pi} - \frac{\sin 2\beta - \sin 2\alpha}{4\pi}\right)} \quad (8)$$

As for i_{rms} it is three components and is given as:

$$i_{rms}^2 = \frac{1}{2\pi} \left[2\pi i_{rms}^2 \text{ of (6) in } [5-1-\alpha] + \int_0^\infty \left[-\frac{V}{R} + (I + \frac{V}{R}) e^{-(\omega t - \phi)/tan\beta} \right]^2 dt + 0 \right] =$$

$$= i_{rms}^2 \text{ of } [5-1-\alpha] + \frac{1}{2\pi} \left[\frac{V^2}{R^2} \omega t + (I + \frac{V}{R})^2 \cdot \frac{e^{-2(\omega t - \phi)/tan\beta}}{-2/tan\beta} - \frac{2V(I + \frac{V}{R}) e^{-\alpha/\tan\beta}}{R} \right]$$

$$\therefore i_{rms}^2 = \sqrt{i_{rms}^2 \text{ of } [5-1-\alpha] + \frac{V^2}{R^2} \cdot \frac{\alpha - \phi}{2\pi} + \left(\frac{V+IR}{R} \right)^2 \cdot \tan\beta \cdot \left(\frac{1-e^{-2(\alpha-\phi)/tan\beta}}{4\pi} \right) - \frac{V(V+IR)}{\pi R^2} \cdot \tan\beta \cdot (1-e^{-\alpha/\tan\beta})}$$

$$\therefore K_i = \sqrt{\left(\frac{i_{rms}}{i_{car}} \right)^2 - 1} \quad (10) \quad \xrightarrow{(9)}$$

$$\therefore K_v = \sqrt{\left(\frac{v_{rms}}{v_{car}} \right)^2 - 1} \quad (11)$$

$$\therefore P_{car} = i_{rms}^2 \cdot R + i_{car} \cdot V \quad (12)$$

5-2-a-II Second, the critical mode, whereby γ in the above waveforms extends till it is just equal to $2\pi + \alpha$. Hence, this mode occurs, using Eq. 3, when:

$$2\pi + \alpha = \beta + \tan\phi \cdot \ln\left(\frac{V+IR}{V}\right), \text{ i.e. when:}$$

$I = \frac{V}{R} \cdot \left[e^{(2\pi + \alpha - \beta)/\tan\phi} - 1 \right]$. Using this in (1), then the critical mode occurs when β satisfies the equation:

$$\frac{\sqrt{2}E}{2} \left\{ \sin(\beta - \phi) - \sin(\alpha - \phi) \cdot e^{(\alpha - \beta)\cot\phi} \right\} - \frac{V}{R} \cdot \left\{ e^{2\pi\cot\phi} - 1 \right\} \cdot e^{(\alpha - \beta)\cot\phi} = 0$$

OR:

$$\sqrt{2}E \cos\phi \cdot \left\{ e^{(\alpha - \beta)\cot\phi} \cdot \sin(\beta - \phi) - \sin(\alpha - \phi) \right\} - V \left(e^{2\pi\cot\phi} - 1 \right) = 0. \quad (13)$$

As for the expressions, they are just as for discontinuous mode with $\beta = \phi$.

97

5-5-b-I

Since current mode is continuous, then v_o is a switched version of v_s as shown in the figure. The gating signals are symmetrical so that the output voltage and current is at twice the frequency.

$$\begin{aligned} \bar{v}_o &= \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} \sqrt{2} E \sin \omega t dt = \\ &= \frac{1}{\pi} \cdot \sqrt{2} E \cdot \frac{-\cos \omega t}{\omega} \Big|_{\alpha}^{\pi+\alpha} = \\ &= \frac{\sqrt{2} E}{\pi} (\cos \alpha - \cos(\pi + \alpha)) = \\ &= \frac{\sqrt{2} E}{\pi} (\cos \alpha + \cos \alpha) = \frac{2\sqrt{2} E}{\pi} \cos \alpha \end{aligned}$$


$$\therefore i_{av} = \frac{v_{oav} - v}{R} = \frac{2\sqrt{2} E \cos \alpha - \pi V}{\pi R}$$

$$\therefore V_{rms}^2 = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} 2E^2 \sin^2 \omega t dt =$$


$$= \frac{2E^2}{2\pi} \left(\omega t - \frac{\sin 2\omega t}{2} \right)_{\alpha}^{\pi+\alpha} =$$

$$= \frac{E^2}{\pi} \left(\pi + \alpha - \alpha - \frac{\sin(2\pi + 2\alpha) - \sin 2\alpha}{2} \right)$$
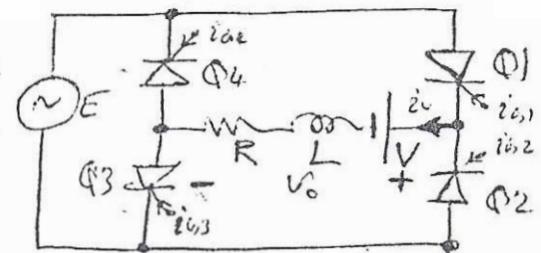
$$= \frac{E^2}{\pi} \left(\pi - \frac{\sin 2\alpha - \sin 2\alpha}{2} \right) = E^2$$



FWCR for KLV load.

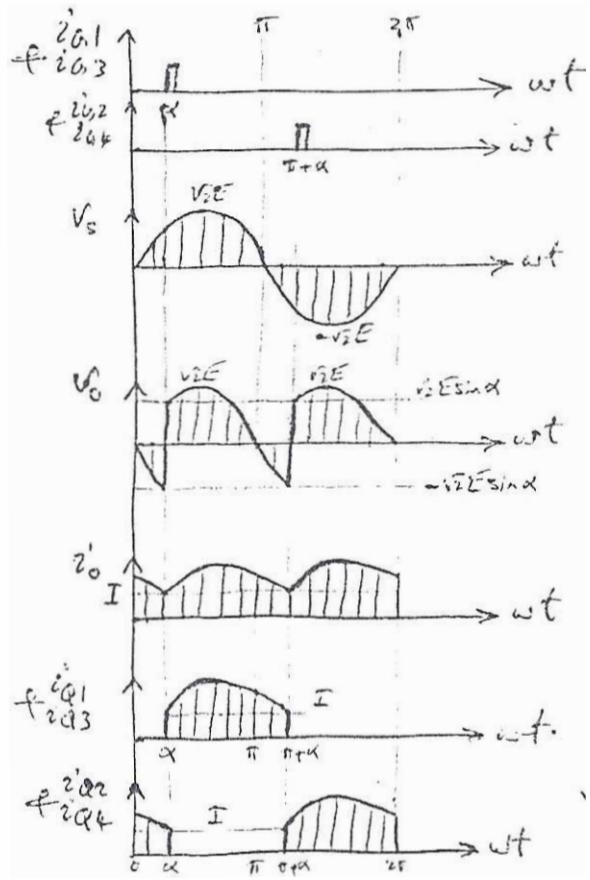

$$\therefore V_{rms} = E$$

(This is expected, since squaring v_o is equal to squaring v_s) (98)

$$\therefore K_v = \frac{V_{oav}}{V_{av}} = \sqrt{\frac{V_{oav}^2 - V_{av}^2}{V_{av}^2}} = \sqrt{\left(\frac{V_{oav}}{V_{av}}\right)^2 - 1} = \sqrt{\frac{\pi^2}{8 \cos^2 \alpha} - 1}$$


S-10 a) Circuit is as shown (assuming symmetrical 3 ϕ supply).

b) $V_{AN} = \sqrt{2}E \sin(\omega t)$

$V_{BN} = \sqrt{2}E \sin(\omega t - 120^\circ)$

$V_{CN} = \sqrt{2}E \sin(\omega t + 120^\circ)$

$$\begin{aligned}\therefore V_{AB} &= V_A - V_B = \\ &= \sqrt{2}E (\sin \omega t - \sin(\omega t - 120^\circ)) = \\ &= \sqrt{2}E [\sin \omega t (1 - \cos 120^\circ) \\ &\quad + \cos \omega t \sin 120^\circ] = \\ &= \sqrt{2}E [\sin \omega t (1 + \frac{1}{2}) + \\ &\quad + \cos \omega t \cdot \frac{\sqrt{3}}{2}] = \\ &= \sqrt{2}E \left[\frac{\sqrt{3}}{2} \sin \omega t + \frac{1}{2} \cos \omega t \right] =\end{aligned}$$

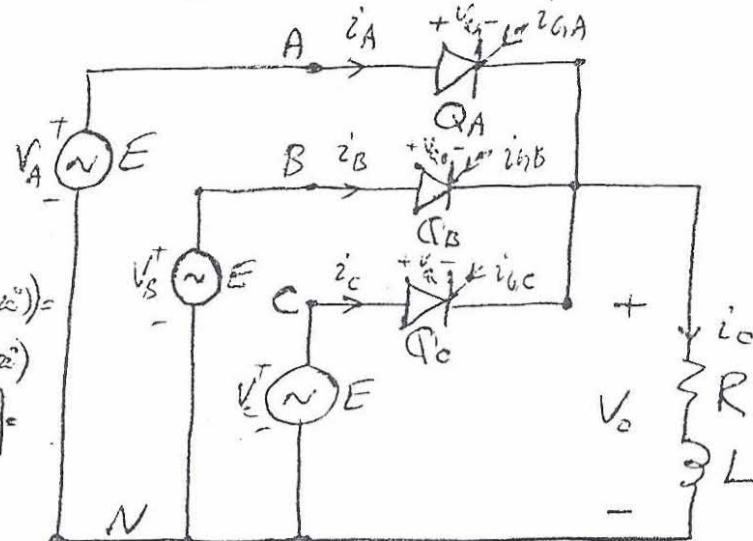

3 ϕ HCR for RL Load.

$$\begin{aligned}&= \sqrt{2}E \left[\sin \omega t \cos 30^\circ + \cos \omega t \sin 30^\circ \right] \\ &= \sqrt{2}E \sin(\omega t + 30^\circ)\end{aligned}$$

Similarly:

$\therefore V_{BC} = \sqrt{2}E \sin(\omega t - 90^\circ)$

$\therefore V_{CA} = \sqrt{2}E \sin(\omega t + 150^\circ)$

$\therefore V_{AC} = -\sqrt{2}E \sin(\omega t + 150^\circ) = \sqrt{2}E \sin(\omega t - 30^\circ)$

\therefore Supply is AC \therefore Three current modes for i.

\therefore Current i₁, i₂, i₃ is assumed continuous, first.

\therefore Circuit is symmetrical.

\therefore Every thyristor conducts for $\frac{2\pi}{3}$ ($\frac{1}{3}$ cycle).

\therefore Q_A conducts after Q_C & before Q_B.

\therefore Before firing Q_A, $V_{QA} = V_{AC} \therefore \alpha > 30^\circ$

$\therefore \alpha \in (30^\circ, 30^\circ + 120^\circ) = (30^\circ, 150^\circ)$, and $V_{QA} = 0$ for $\frac{1}{3}$ cycle after α .

Then when Q_B is fired at $\frac{2\pi}{3} + \alpha$,


$\therefore V_{QA} = V_{AB}$ for $\frac{1}{3}$ cycle after $\frac{2\pi}{3} + \alpha$.

Then Q_C is fired at $\frac{4\pi}{3} + \alpha$ and

$V_{QA} = V_{AC}$ for $\frac{1}{3}$ cycle after $\frac{4\pi}{3} + \alpha$.

This completes one cycle, giving the waveforms shown above. The other phase waveforms are obtained by 120° shift for B & 240° shift for C.

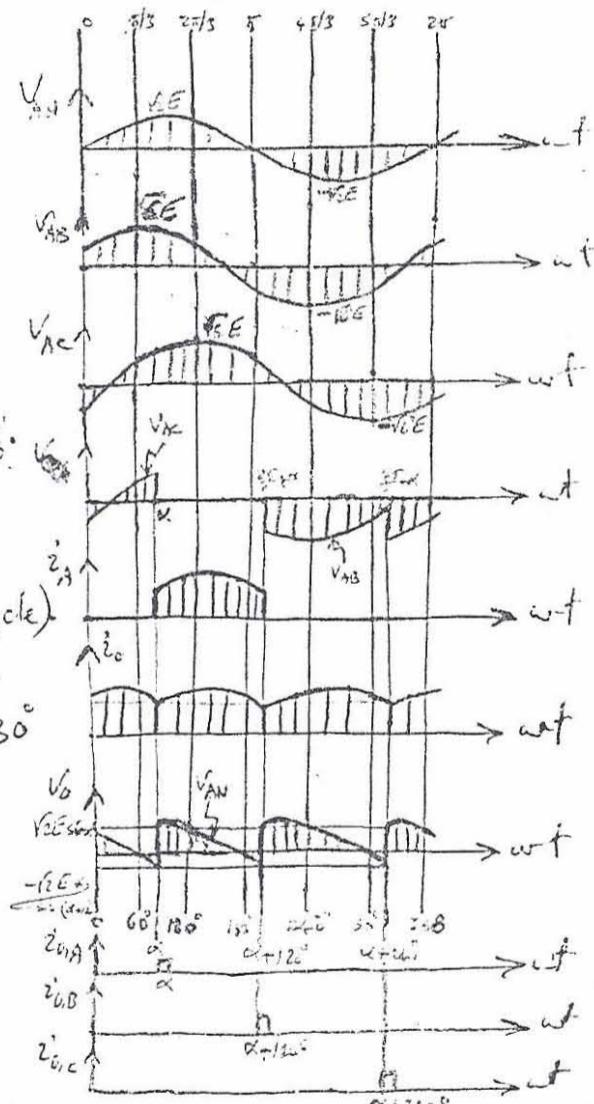During the conduction of Q_A $\therefore V_o = V_{AN}$ for $\omega t \in (\alpha, \alpha + \frac{2\pi}{3})$



And for $\alpha \in [\alpha + \frac{2\pi}{3}, \alpha + \frac{4\pi}{3}] \Rightarrow V_o = V_{BN}$ since Q_B is on.
 Finally for $\alpha \in [\alpha + \frac{4\pi}{3}, \alpha + 2\pi]$ Q_C is on $\Rightarrow V_o = V_{CN}$.

As for the output current, i_o:

$$\therefore i_o = i_A + i_B + i_C \text{ as shown above.}$$

(Note that i_o & V_o are of period = $\frac{2\pi}{3}$).

c): Range of α is between 30° & 150° relative to each phase,
 [i.e. within $\pm 60^\circ$ off phase peak], for controlled operation.

$$\text{d) } V_{o_{av}} = \frac{1}{\frac{2\pi}{3}} \int_{\alpha}^{\alpha + \frac{2\pi}{3}} \sqrt{2}E \sin(\alpha + t) dt = \frac{3\sqrt{2}E}{2\pi} \left[-\cos(t) \right]_{\alpha}^{\alpha + \frac{2\pi}{3}} = \\ = \frac{3\sqrt{2}E}{2\pi} \left[\cos(\alpha) - \cos(\alpha + 2\pi) \right] = \frac{3\sqrt{2}E}{2\pi} \left[\cos(\alpha + 60^\circ - 60^\circ) - \cos(\alpha + 60^\circ + 60^\circ) \right] = \\ = \frac{3\sqrt{2}E}{2\pi} \cdot 2 \sin(\alpha + 60^\circ) \sin 60^\circ = \frac{3\sqrt{2}E}{2\pi} \cdot 2 \cdot \frac{\sqrt{3}}{2} \sin(\alpha + 60^\circ) =$$

$$\therefore V_{o_{av}} = \frac{3}{\pi} \cdot \frac{\sqrt{3}}{2} \cdot E \sin(\alpha + 60^\circ) \quad \Rightarrow \alpha \in \text{Continuous range.}$$

Note: $V_{o_{av}} \in \left[\frac{-3}{2\pi} \sqrt{\frac{3}{2}} E, \frac{3}{\pi} \sqrt{\frac{3}{2}} E \right]$ for $\alpha \in [30^\circ, 150^\circ]$, i.e. the output controlled voltage varies between -0.585 ± 1.170 of E.

Hence, $i_{o_{av}} \in [-0.585, 1.170]$ of E/R , and since i_o can't be negative, then α must not reach 150° for continuous mode operation. In fact i_o must be strictly > 0 for continuous current to flow. i.e. $\sin(\alpha + 60^\circ) > 0 \Rightarrow \alpha < 120^\circ$.

The smaller L/R the lower α_{max} is, and at $L=0, \alpha_{max} = 60^\circ$.

To get the exact value of α_{max} for any RL, then

Consider the condition for β in the 1st HWCR of [5-1-b],

which is just the same as for this case.

$$\therefore \sin(\beta - \phi) = \sin(\alpha - \phi) e^{(x-\beta)/t_a \phi}$$

Now put $\beta = \alpha_{\max} + 2\pi/3$ (just critical mode)

$$\therefore \sin(\alpha_{\max} + 2\pi/3 - \phi) = \sin(\alpha_{\max} - \phi) e^{-\frac{2\pi}{3t_a \phi}}$$

$$\therefore \sin(\alpha_{\max} - \phi) \cos \frac{2\pi}{3} + \cos(\alpha_{\max} - \phi) \sin \frac{2\pi}{3} = \sin(\alpha_{\max} - \phi) e^{-\frac{2\pi}{3t_a \phi}} = 0$$

$$\therefore -\sin(\alpha_{\max} - \phi) \left[\frac{1}{2} + e^{-\frac{2\pi}{3t_a \phi}} \right] + \cos(\alpha_{\max} - \phi) \cdot \frac{\sqrt{3}}{2} = 0$$

$$\therefore \tan(\alpha_{\max} - \phi) = \frac{\sqrt{3}}{1 + 2e^{-\frac{2\pi}{3t_a \phi}}}$$

$$\therefore \alpha_{\max} = \phi + \tan^{-1} \left[\frac{\sqrt{3}}{1 + 2e^{-\frac{2\pi}{3t_a \phi}}} \right]$$

Indeed, for resistive load, $L=0$ & $\phi=0 \therefore \alpha_{\max} = 60^\circ$

& for inductive load, $R=0$ & $\phi=\pi/2 \therefore \alpha_{\max} = 120^\circ$

Hence:

For continuous mode $\therefore \alpha \in [30^\circ, \alpha_{\max}]$

& for discontinuous mode $\therefore \alpha \in [\alpha_{\max}, 150^\circ]$.

Thus giving an overall control range of $\alpha \in [30^\circ, 150^\circ]$.

\therefore for continuous mode, $V_{o_{av}} = \frac{3}{\pi} \cdot \sqrt{\frac{3}{2}} \cdot E \sin(\alpha + 60^\circ)$

e) & for continuous mode, $i_{o_{av}} = \underline{\frac{3}{\pi} \cdot \sqrt{\frac{3}{2}} \cdot \frac{E}{R} \cdot \sin(\alpha + 60^\circ)}$.

(1)

- S-12 1. The circuit is HW HCR with RLV Load, with control range of: $\alpha \in [\sin^{-1} \frac{121}{341}, \pi - \sin^{-1} \frac{121}{341}] \rightarrow 0^\circ \text{ to } 90^\circ$
 $\alpha \in [20.8^\circ, 159.2^\circ]$

2. Waveforms are as shown for $\alpha = 90^\circ$

Current mode is expected to be discontinuous, since, the charging angle is $\pi/2$ & the angle available for discharge is $3\pi/2$ with $-121V$ force.

Let's find β to be absolutely sure.

For $wt \in [\pi, \pi]$:

$$\therefore i_o(wt) = \frac{341 \sin(wt - \pi + 20\pi + 52m/2.5)}{\sqrt{2.5^2 + (20\pi + 52m)^2}} - \frac{121}{2.5}$$

$$= A e^{-2.5wt/\omega_{n,52m}}$$

$$= 17.255 \sin(wt - 82.73^\circ) - 48.4$$

$$+ A e^{-12753(wt - \pi/2)}, \text{ Amp}$$

$$\therefore i_o(\pi) = 0 \quad \therefore A = 46.22 \text{ Amp}$$

$$\therefore I_\pi = i_o(\pi) = 6.546 \text{ Amp}$$

ii. For $wt \in [\pi, \beta]$:

$$\therefore i_o = (48.4 + 6.546) e^{-12753(wt - \pi)} - 48.4, \text{ A}$$

$$\therefore 0 = i_o(\beta) \Rightarrow \beta = 4.136 \text{ rad} = 237^\circ$$

$$\therefore \beta = 237^\circ < 2\pi + \alpha = 360 + 90 = 450^\circ$$

Mode is actually discontinuous.


3. Q conducts in each cycle for 90° i.e. $\frac{\pi}{2\pi} = \frac{\pi}{240\pi} = \frac{1}{240} \text{ s} = 4.17 \text{ ms}$

when D conducts for $237^\circ - 180^\circ = 57^\circ$ i.e. $\frac{57}{180} \cdot \frac{\pi}{2\pi} = 2.64 \text{ ms}$

Q is commutated by the line voltage through D.

$$4. V_{o,av} = \frac{121 * \pi/2 + 341 * \pi/2 * \frac{2}{\pi} + 0 + 121 * (2\pi - \alpha, 136)}{2\pi} = 125.87 \text{ Volts}$$
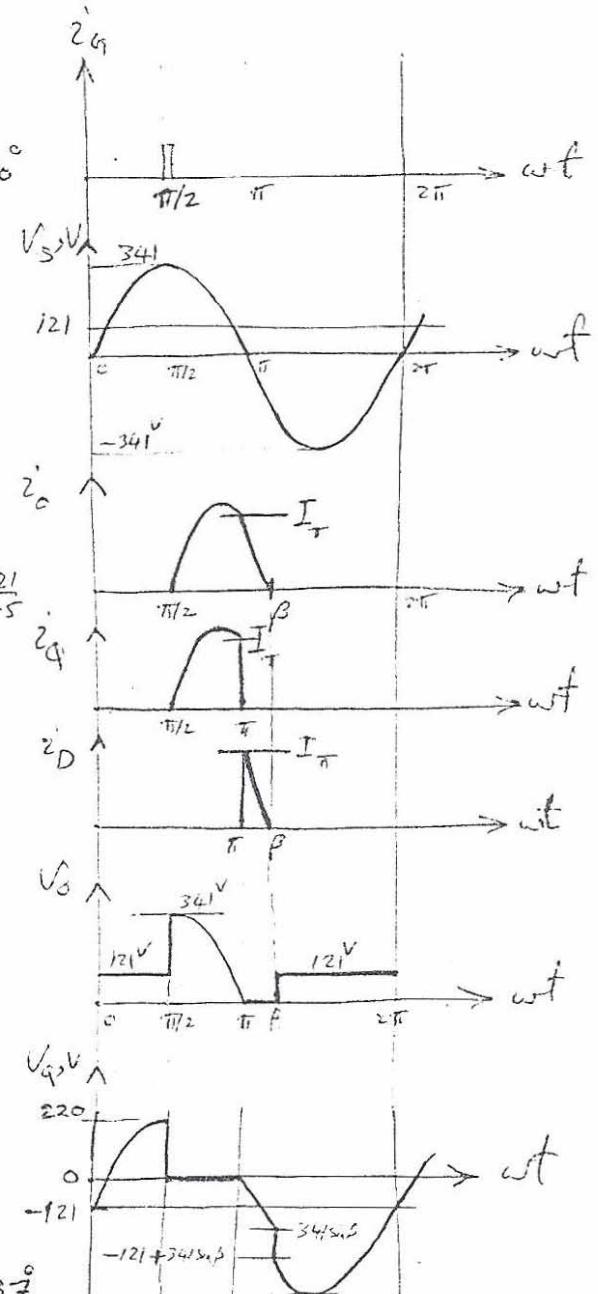
$$\therefore i_{car} = \frac{V_{o,av} - 121}{2.5} = \frac{125.87 - 121}{2.5} = 1.949 \text{ Amp}$$



$$f. V_{o_{rms}}^2 = \frac{1}{2\pi} \left[|121|^2 * \frac{\pi}{2} + 341^2 * \frac{\pi}{2} * \frac{1}{2} + 0 + |121|^2 (2\pi - 4.136) \right] = 23199 V^2$$

$$\therefore V_{o_{rms}} = 152.3 \text{ Volts}$$

$$P_v = i_{o_{av}} \cdot V = 1.949 * 121 = 235.83 \text{ Watts.}$$

5. For Q :

$$t_p = \left[180 + \sin\left(\frac{i_{21}}{341}\right) \right] / 180 * \pi / 120\pi = 9.296 \text{ msec}$$

$$V_{FB} = 220 \text{ Volts}$$

$$V_{RB} = 462 \text{ Volts}$$

For D :

P_j can be found assuming $V_F = 1 \text{ Volt}$ & straight line current segment (as $\frac{L}{R} = \frac{52 \text{ m}}{2.5} = 20.8 \text{ ms} \gg \frac{P-T}{V_F} = \frac{52^2}{120} \frac{\pi}{120} = 2.64 \text{ msec}$)
 $P_j = I\pi * 1 * (\beta - \pi) / 2 / 2\pi = 6.546 * (4.136 - 3.142) / 4\pi = 0.518 \text{ W}$

$$T_j = 25 + .5 * .518 = 25.26^\circ \text{C}$$

6-1 The two back-to-back thyristors could be well replaced by a triac. The current mode for large ($\alpha \approx \pi$) α values is discontinuous and is given by:

(see 6.1-b)

$$i_c(t) = \frac{\sqrt{2}E}{Z} \left\{ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{\alpha-\omega t}{L/R}} \right\} \quad (1)$$

for $\omega t \in [\alpha, \beta]$

$$\text{and } i_c(t) = 0 \text{ for } \omega t \in [\beta, \pi + \alpha]$$

The other half of $i_c(t)$ is just symmetrical.

The condition for β is given by:

(see 6.1-b)

$$\sin(\beta - \phi) - \sin(\alpha - \phi) e^{\frac{\alpha-\beta}{L/R}} = 0 \quad (2)$$

As α decreases, the discontinuity gap will narrow till at $\beta - \pi = \alpha$ it is zero

\therefore Controllability of α is such that $\beta = \pi + \alpha$. Putting this into (2):

$$\therefore \sin(\pi + \alpha - \phi) - \sin(\alpha - \phi) e^{\frac{\alpha-\pi-\phi}{L/R}} = 0$$

$$\therefore -\sin(\alpha - \phi) \cdot [1 + e^{-\pi/L/R}] = 0$$



$$\therefore 1 + e^{-\pi/L/R} > 0$$

$$\therefore \sin(\alpha - \phi) = 0 \quad \therefore \alpha \leq \phi$$

\therefore Control range of α is

$$\alpha \in [\phi, \pi]$$

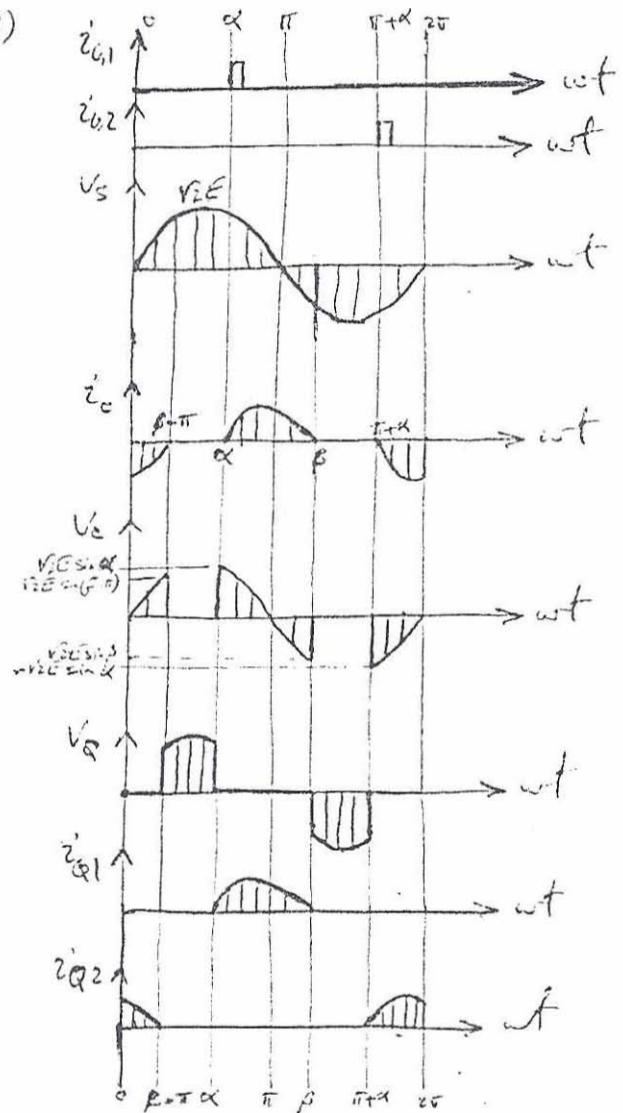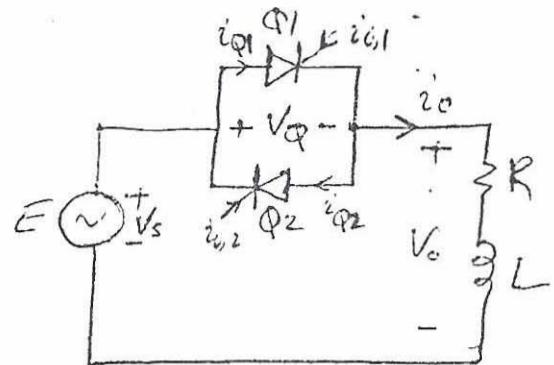(Note: This is obvious since at critical case $i_c(t) = \frac{\sqrt{2}E}{Z} \sin(\omega t - \phi)$ and has no exponential term in $i_c(t)$, hence α must be ϕ). 104



Hence; within α range, this problem is typical to [6.1-b] with the difference that it has one more pulse of both current and voltage at the negative half, i.e. averages are zero.

$$\therefore V_{o_{rms}}^2 = 2 \left[V_{o_{rms}} \text{ of } [6.1-b] \right]^2$$

$$\therefore V_{o_{rms}} = \sqrt{2} \cdot E \cdot \sqrt{\frac{\beta - \alpha}{2\pi} - \frac{\sin 2\beta - \sin 2\alpha}{4\pi}} \quad (3)$$

$$\therefore i_{o_{rms}} = \sqrt{2} \left[i_{o_{rms}} \text{ of } [6.1-b] \right] \Rightarrow$$

$$\therefore i_{o_{rms}} = \frac{\sqrt{2} E}{Z} \sqrt{\frac{\beta - \alpha}{2\pi} + \frac{\sin 2(\alpha - \phi) - \sin 2(\beta - \phi)}{4\pi} + \frac{2}{\pi} \sin \phi \sin(\alpha - \phi) \left[e^{\frac{i\omega t}{2\pi}} - \frac{\sin \phi}{\sin \beta} \right] + \frac{\sin^2(\beta - \phi) \tan^2(1 - e^{-\frac{\alpha}{2\pi}})}{2\pi}} \quad (4)$$

$$\therefore P_o = i_{o_{rms}}^2 * R \quad (5)$$

$$\therefore Pf = \frac{P}{i_{o_{rms}} \cdot V_{o_{rms}}} = \frac{i_{o_{rms}}^2 * R}{i_{o_{rms}} \cdot V_{o_{rms}}} = \frac{i_{o_{rms}} * R}{V_{o_{rms}}} \quad (6)$$

When $\alpha = \phi$ the above parameters comes simply to:

$$i_o(t) = \frac{\sqrt{2} E}{Z} \sin(\omega t - \phi) \quad (7)$$

$$\therefore \beta - \phi = \pi \Rightarrow \beta = \pi + \phi \quad (8)$$

$$\therefore V_{o_{rms}} = E \quad (9)$$


$$\therefore i_{o_{rms}} = \frac{E}{Z} \quad (10)$$

$$\therefore Pf = \frac{R}{Z} = fPf \quad (11)$$

$$\therefore \text{Finally } \rho_i = \frac{\rho_{\text{thermocell}}}{i_{o_{rms}}} = 0 \quad (12)$$

(Note: this is simply because we lost control i.e. Q1-PQ2 appear as stated)

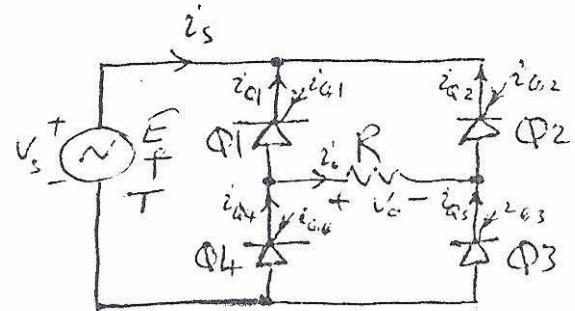7-1 a) The shown circuit is of a cyclo-converter that supplies ac to the load at half the frequency of the supply, since the period of the output is twice that of the input.



b) The waveforms are as shown.

$$c) v_o \text{ fundamental} = a \sin\left(\frac{2\pi t}{T}\right) + b \cos\left(\frac{2\pi t}{T}\right) \quad [\text{no average}]$$

$$\therefore a = \frac{2}{2T} \int v_o(t) \sin\left(\frac{\pi t}{T}\right) dt = \\ = \frac{1}{T} * 2 \int_{-\pi/2}^{\pi/2} \sqrt{2}E \sin\left(\frac{2\pi t}{T}\right) \sin\left(\frac{\pi t}{T}\right) dt \\ = -\frac{2\sqrt{2}E}{T} \int_{-\pi/2}^{\pi/2} 2 \sin\left(\frac{\pi t}{T}\right) \cos\left(\frac{\pi t}{T}\right) dt \\ = -\frac{4\sqrt{2}E}{T} \cdot \frac{\sin^3\left(\frac{\pi t}{T}\right)}{3\pi/2} \Big|_0^{\pi/2} = -\frac{4\sqrt{2}E}{3\pi} [1-0] = \frac{4\sqrt{2}E}{3\pi}$$

$$\text{if } b = \frac{2}{2T} \int v_o(t) \cos\left(\frac{\pi t}{T}\right) dt = \frac{1}{T} * 2 \int_{-\pi/2}^{\pi/2} \sqrt{2}E \sin\left(\frac{2\pi t}{T}\right) \cos\left(\frac{\pi t}{T}\right) dt = \\ = -\frac{2\sqrt{2}E}{T} \int_{-\pi/2}^{\pi/2} 2 \sin\left(\frac{\pi t}{T}\right) \cos^2\left(\frac{\pi t}{T}\right) dt = -\frac{4\sqrt{2}E}{T} \int_{-\pi/2}^{\pi/2} \frac{\cos^3\left(\frac{\pi t}{T}\right)}{3\pi/2} dt = -\frac{4\sqrt{2}E}{3\pi} [1-0] = -\frac{4\sqrt{2}E}{3\pi}$$

$$\therefore V_o \text{ fundamental rms} = \sqrt{(a^2 + b^2)/2} = \frac{4\sqrt{2}E}{3\pi}$$

$$\therefore i_o \text{ fundamental rms} = \frac{4\sqrt{2}E}{3\pi R}$$


$$d) P_{load} = \frac{V_o^2}{R} = \frac{1}{R} \cdot \frac{1}{2T} [E \cdot I + E^2] = \frac{E^2}{2R} = i_o^2 \text{ rms}$$

$$e) \rho f = \frac{P_{load}}{i_o \cdot V_{rms}} = \frac{E^2/2R}{\frac{1}{2} \cdot \frac{V_{rms}}{E}} = \frac{E/2R}{\sqrt{E^2/2R}} = \frac{1/2}{\sqrt{1/2}} = \sqrt{1/2} = \frac{1}{\sqrt{2}} = .7071$$


$$f) \text{ Resistive load, } \therefore \angle i_o \text{ fundamental} = 0 \quad \therefore \rho f = \cos 0 = 1 \quad (0.6)$$

$$g) \frac{V_o}{V_s} (\text{resistive load}) = \frac{V_o \text{ fundamental}}{V_{rms}} = \sqrt{1 - \left(\frac{V_o \text{ fundamental}}{V_{rms}}\right)^2} = \sqrt{1 - \left(\frac{4\sqrt{2}E/3\pi}{E/2}\right)^2} = \sqrt{1 - \frac{64}{9\pi^2}} = 0.5287 \approx 53\%$$

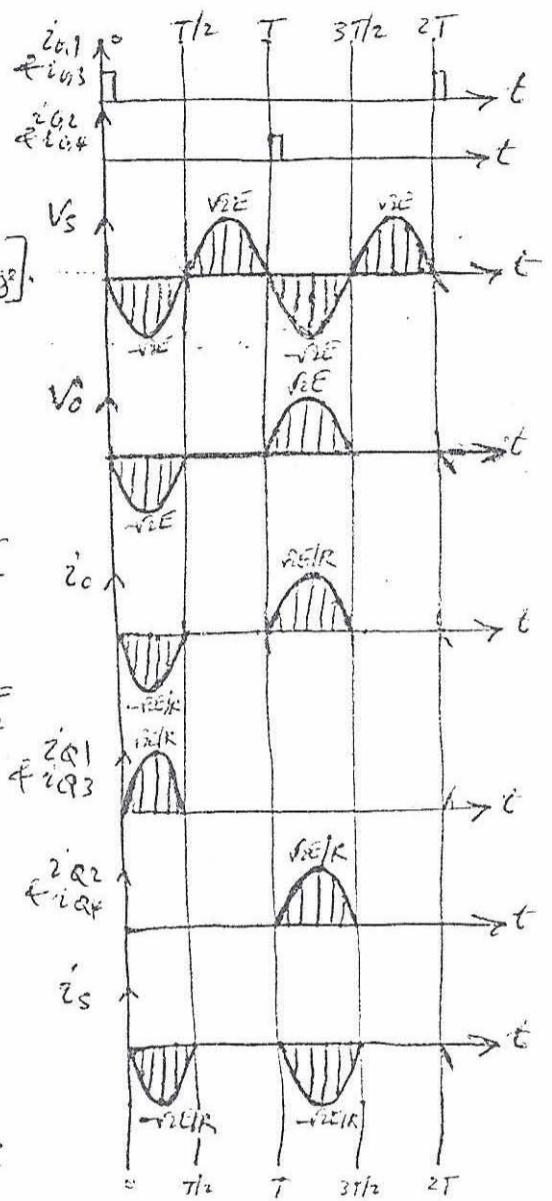
h) Disadvantage of circuit is that the supply current has a dc offset.



8-2

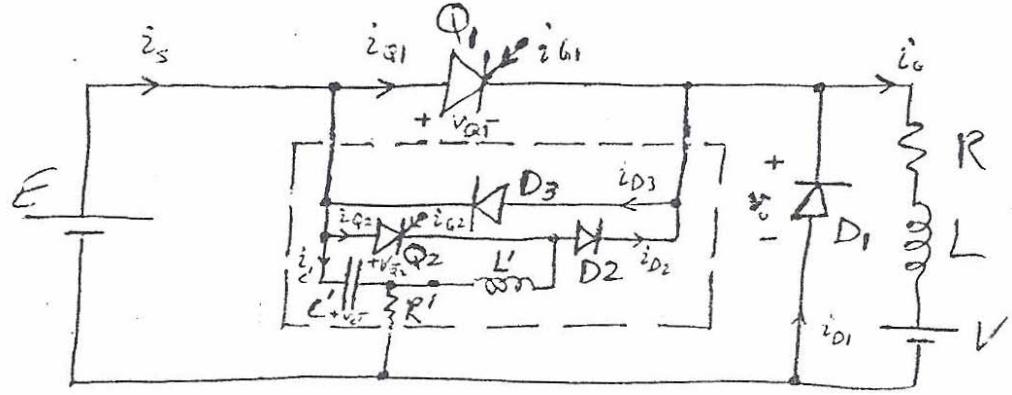

The dashed box is the circuit for forced commutation. It is so designed that $L'C'$ will ring at frequency much higher than that of chopping, and the ringing period is very small compared to $R'C'$ time constant. At the start of a chopping cycle, C' is charged to E when Q_1 is gated, hence current i_o flows from supply through Q_1 to the load. No other supply current is going to flow at this stage, since D_3 is reverse biased by drop on Q_1 & since Q_2 is not yet gated and since C' is fully charged to E . When we want to commutate Q_1 at $t = \tau$ a gate pulse is provided to Q_2 . Hence, the loop consisting of $L'C'$ & Q_2 will ring for half a cycle then Q_2 will be off. During this half cycle, current through Q_1 is almost constant, D_3 is still off, D_2 is still off, current through R' is almost zero, and D_1 is off. As Q_2 becomes off, voltage across C' is almost $-E$ and it will force its ringing current through $C'L'D_2$ & Q_1 . As the ringing current increases, the net Q_1 current decreases, till it is shut off at the instant ringing current = I_{max} .

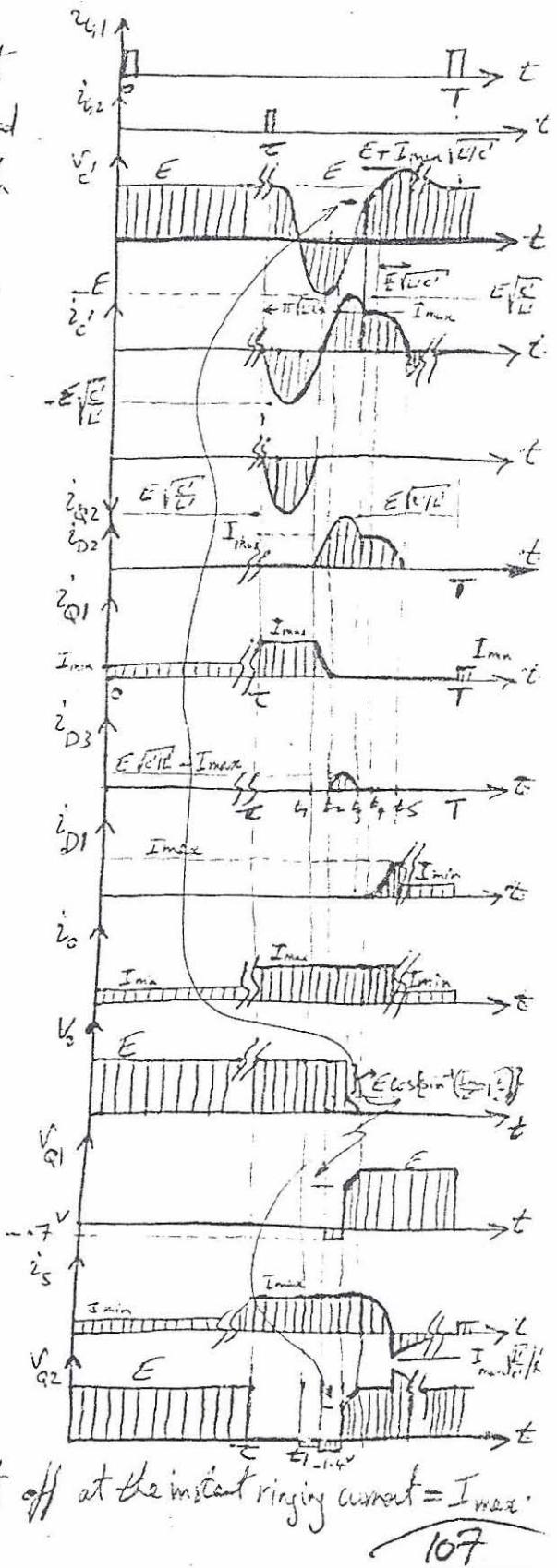

107

At this instant on, ringing current flows through $C'L'D_2$ and the parallel paths of D_3 and RLVE combination. After peaking, ringing current becomes again equal to I_{max} whereby, ringing stops, and its held there till C' charges back again to almost E . Now, D_1 is on and current through $C'L'D_2$ oscillates to a stop. During freewheeling period C' discharges to E ready for next chopping cycle. The waveforms are as shown above, and components are assumed ideal.

The circuit will look like the following, at various instants of time. All rectifiers in the illustrative figures are on and could be assumed short circuit, where:

$$t_1 = \tau + \pi \sqrt{L/C'}$$

$$\text{if } t_2 = \tau + \sqrt{L/C'} \left\{ \pi + \sin^{-1} \left(\frac{I_{max}}{E} \cdot \sqrt{\frac{L}{C'}} \right) \right\}$$

$$= t_1 + \sqrt{L/C'} \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L}{C'}} \right)$$

$$\text{if } t_3 = \tau + \sqrt{L/C'} \left\{ 2\pi - \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L}{C'}} \right) \right\}$$

$$\text{if } t_4 = t_3 + \frac{C'E}{I_{max}} \left[1 - \cos \left\{ \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L}{C'}} \right) \right\} \right]$$

$$\text{if } t_5 = t_4 + \frac{\pi}{2} \sqrt{L/C'}$$

The total commutation time is just below $\frac{5\pi}{2}\sqrt{L/C'}$ and

thyristor Q_1 is reversed biased during:

$$t_{off} = t_3 - t_2 =$$

$$= \sqrt{L/C'} \left\{ \pi - 2 \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L}{C'}} \right) \right\},$$

provided that $I_{max} < E/\sqrt{C'}$,

otherwise commutation fails.






$$t \in [\tau, t_1]$$

$$t \in [t_2, t_3]$$

$$t \in [t_3, t_4]$$

$$t \in [t_4, t_5]$$

$$t \in [t_5, T]$$

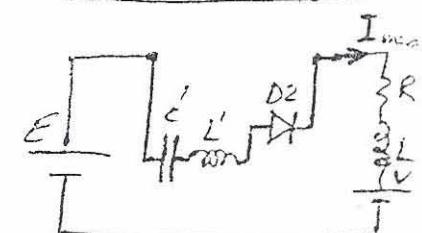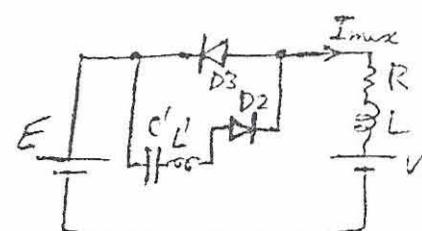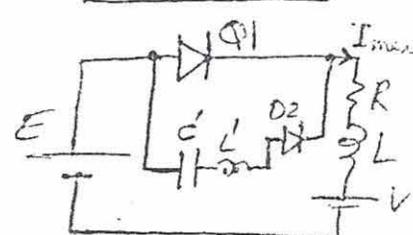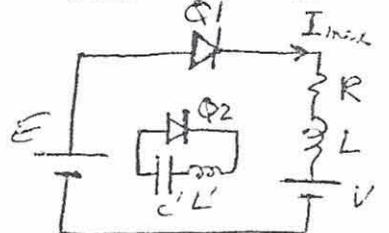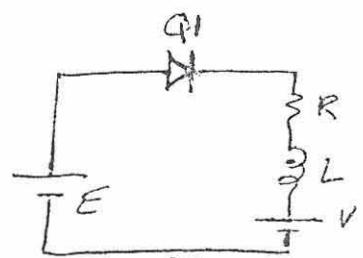

$$E = 600V, L' = 42\mu H, C' = 6\mu F, T = 2500\mu s,$$

$$I_{max} = 150A$$

a) $t_{off} = \sqrt{L'C'} \left\{ \pi - 2 \sin^{-1} \left(\frac{I_{max}}{E} \cdot \sqrt{\frac{L'}{C'}} \right) \right\} = 26.93 \mu sec$

$\therefore t_1$ must be $\leq 26.93 \mu sec$

b) $t_C \approx \frac{\pi}{2} \sqrt{L'C'} = \frac{\pi}{2} \cdot \sqrt{42 \cdot 6} = 124.68 \mu sec \ll T$ (OK)

(Note: the exact figure is slightly less $= t_5 - \tau =$

$$\begin{aligned} &= t_4 + \frac{\pi}{2} \sqrt{L'C'} - \tau = t_3 + \frac{C'E}{I_{max}} \left[1 - \cos \left\{ \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L'}{C'}} \right) \right\} \right] + \frac{\pi}{2} \sqrt{L'C'} - \tau \\ &= \tau + \sqrt{L'C'} \left\{ 2\pi - \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L'}{C'}} \right) \right\} + \frac{C'E}{I_{max}} \left[1 - \sqrt{1 - \frac{I_{max}^2 L'}{E^2 C'}} \right] + \frac{\pi}{2} \sqrt{L'C'} - \tau \\ &= \frac{\pi}{2} \sqrt{L'C'} - \left[\sqrt{L'C'} \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L'}{C'}} \right) - \frac{C'E - \sqrt{C'^2 E^2 - C'L'I_{max}^2}}{I_{max}} \right] \\ &= 124.68 - 5.47 = 119.21 \mu sec. \end{aligned}$$

d) $t_{off} = t_3 - t_1 = \sqrt{L'C'} \left\{ \pi - \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L'}{C'}} \right) \right\} = 38.40 \mu sec$

c) For sketch, consider start of commutation as reference:

$$\therefore t_1 = \pi \sqrt{L'C'} = 49.9 \mu sec,$$

$$\therefore t_2 = 61.3 \mu s, \quad t_3 = 88.3 \mu sec, \quad t_4 = 94.3 \mu sec$$

$$\therefore t_5 = 119.2 \mu sec$$

$$\therefore V_{c_{max}} = E + I_{max} \sqrt{\frac{L'}{C'}} = 996.9 \text{ volts}$$

$$\therefore i_{c_{max}} = E \sqrt{\frac{C'}{L'}} = 226.8 \text{ Amps}$$

$$\therefore V_{c_{precharge}} = E \cos \left\{ \sin^{-1} \left(\frac{I_{max}}{E} \sqrt{\frac{L'}{C'}} \right) \right\} = 450 \text{ volts}$$

$$\therefore i_{D3_{max}} = E \sqrt{\frac{C'}{L'}} - I_{max} = 76.8 \text{ Amps}$$

